

وَمَا أُوتِيتُمْ مِنَ الْعِلْمِ إِلَّا قَلِيلًا

Analog IC Design


Lecture 05 MOSFET Small Signal Model

Dr. Hesham A. Omran


Integrated Circuits Lab (ICL)
Electronics and Communications Eng. Dept.
Faculty of Engineering
Ain Shams University

N-Channel MOSFET Structure

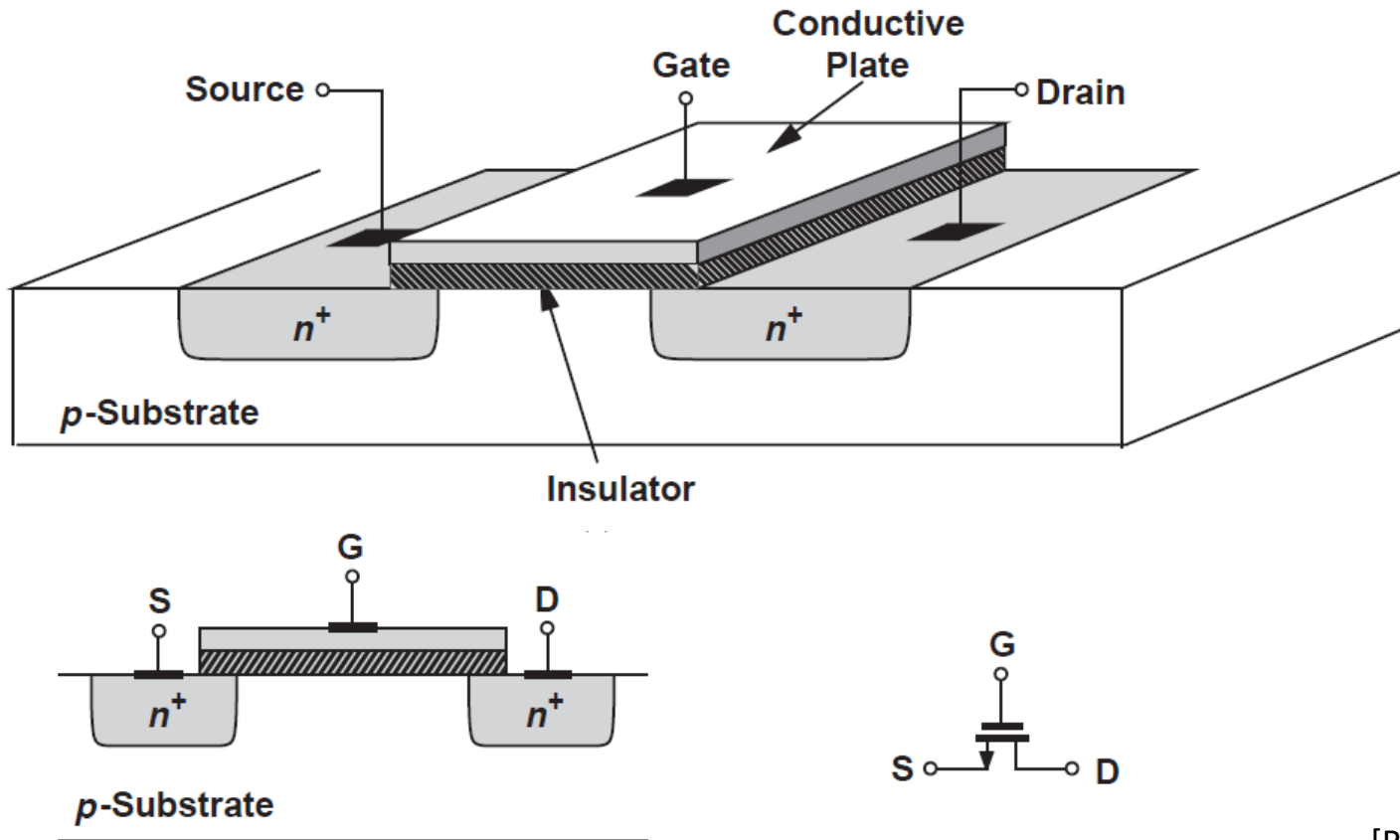- ❑ MOSFET: Metal-oxide-semiconductor field-effect transistor
- ❑ Three-terminal device: Gate (G), Source (S), and Drain (D)
- ❑ Substrate/Bulk/Body (S/B) can be treated as a fourth terminal





Regions of Operation Summary

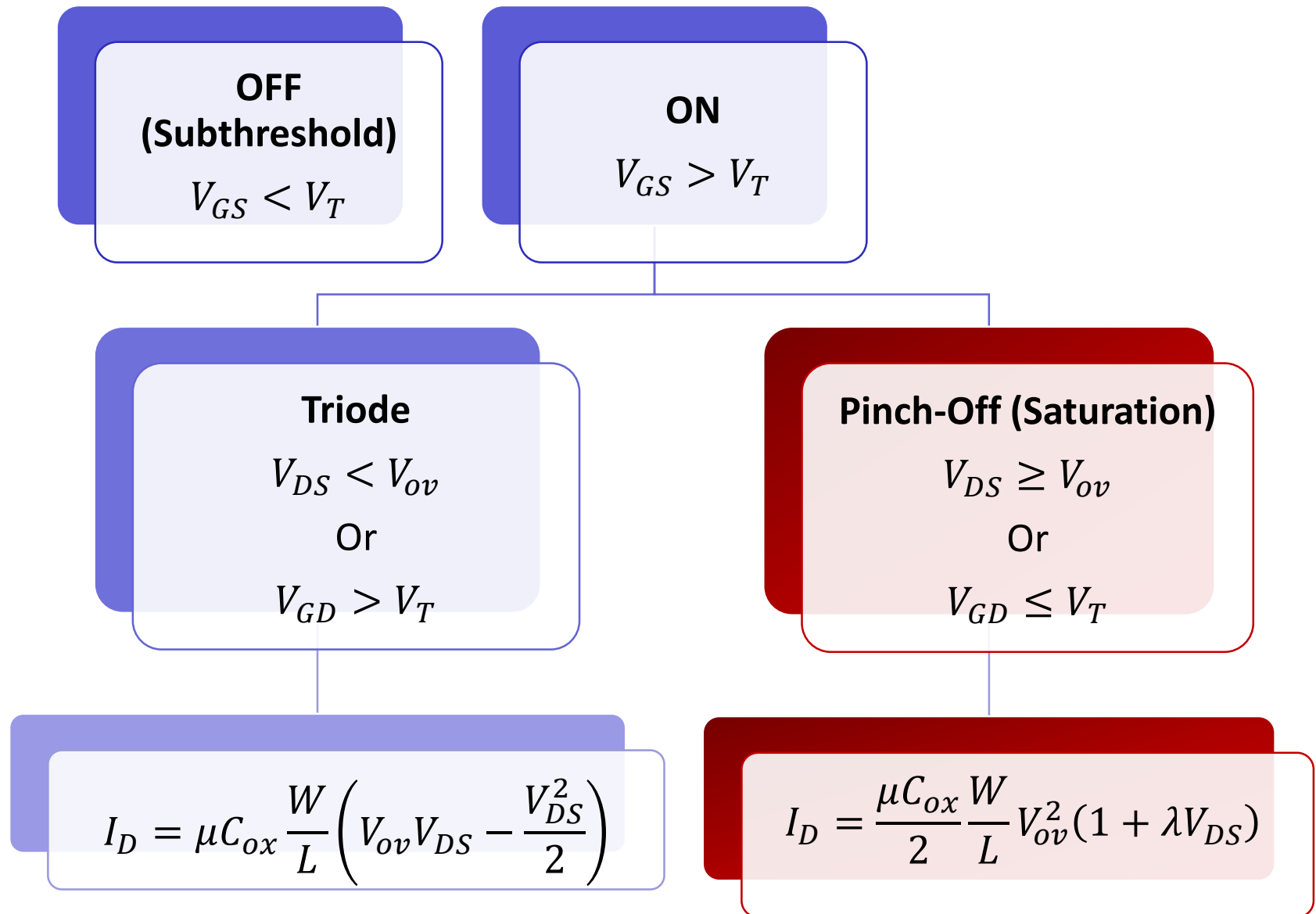

MOSFET in Saturation

- ❑ The channel is pinched off if the difference between the gate and drain voltages is not sufficient to create an inversion layer

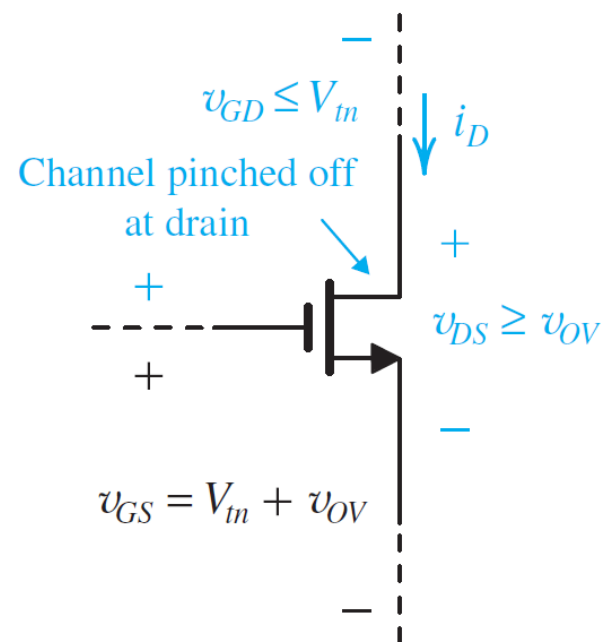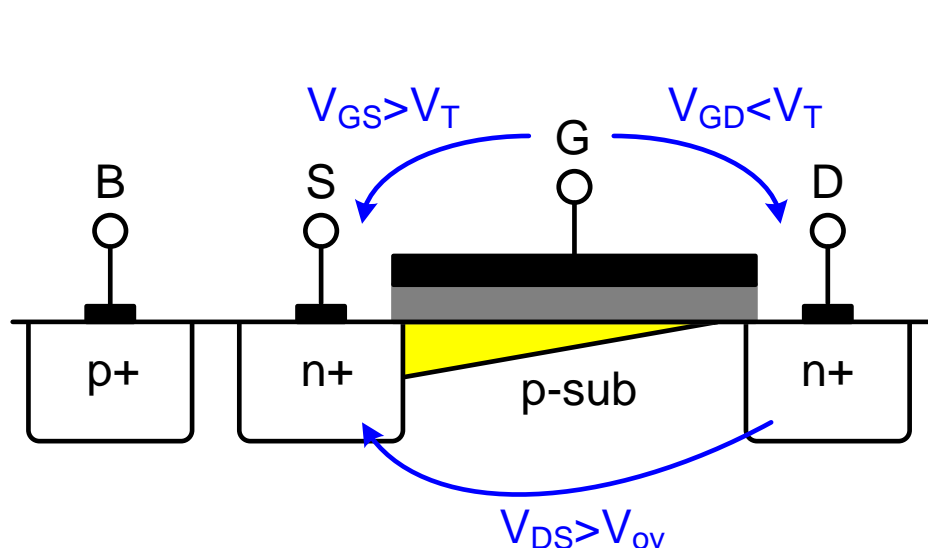
$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \cdot V_{ov}^2 (1 + \lambda V_{DS})$$



Large Signal Model

- ❑ The channel is pinched off if the difference between the gate and drain voltages is not sufficient to create an inversion layer

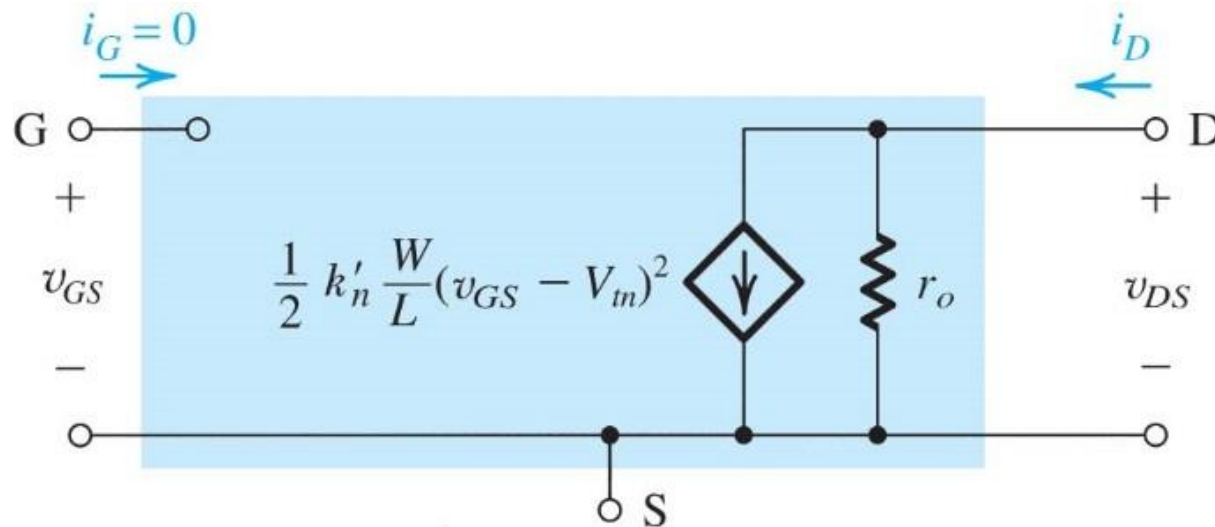
$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \cdot V_{ov}^2 (1 + \lambda V_{DS})$$



Small Signal Approximation

- ❑ The transistor is a VCCS
- ❑ Transconductance: how well it converts the voltage to a current

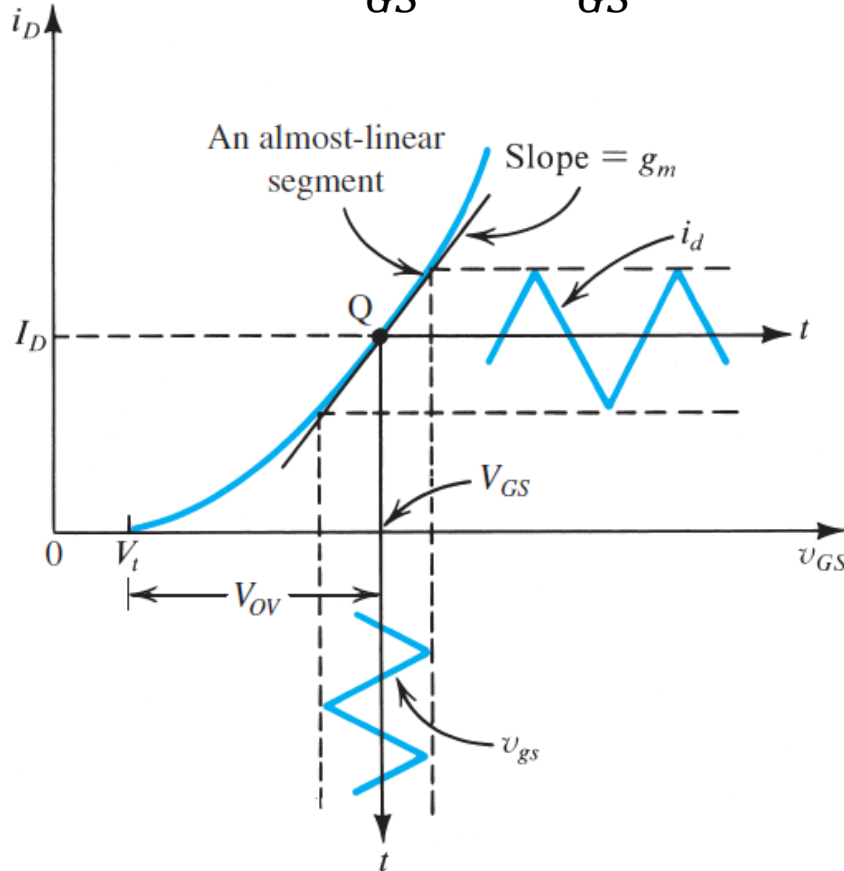
$$g_m = \frac{\Delta I_D}{\Delta V_{GS}} = \frac{\partial I_D}{\partial V_{GS}}$$





Small Signal Model

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}} = \frac{\partial I_D}{\partial V_{GS}}$$
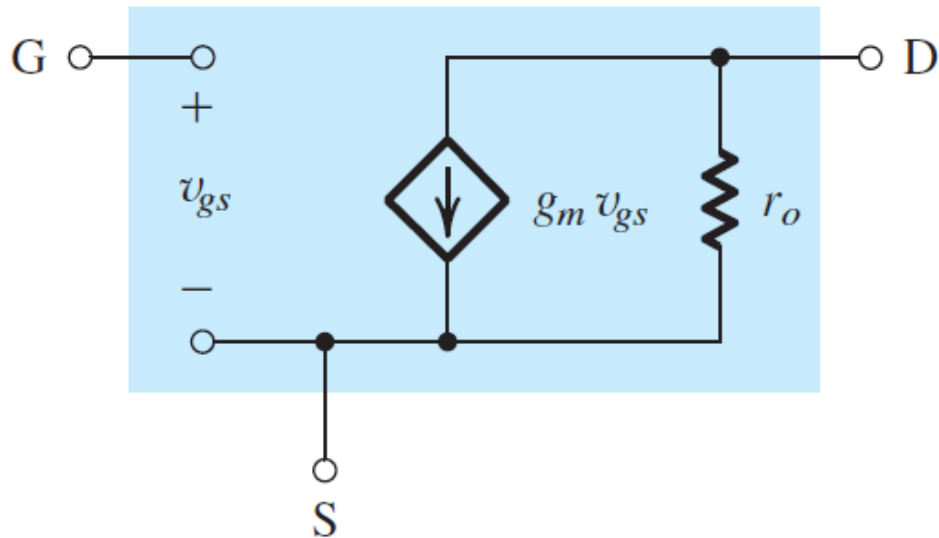
$$r_o = \frac{\Delta V_{DS}}{\Delta I_D} = \frac{1}{\frac{\partial I_D}{\partial V_{DS}}}$$




Large Signal vs Small Signal Model

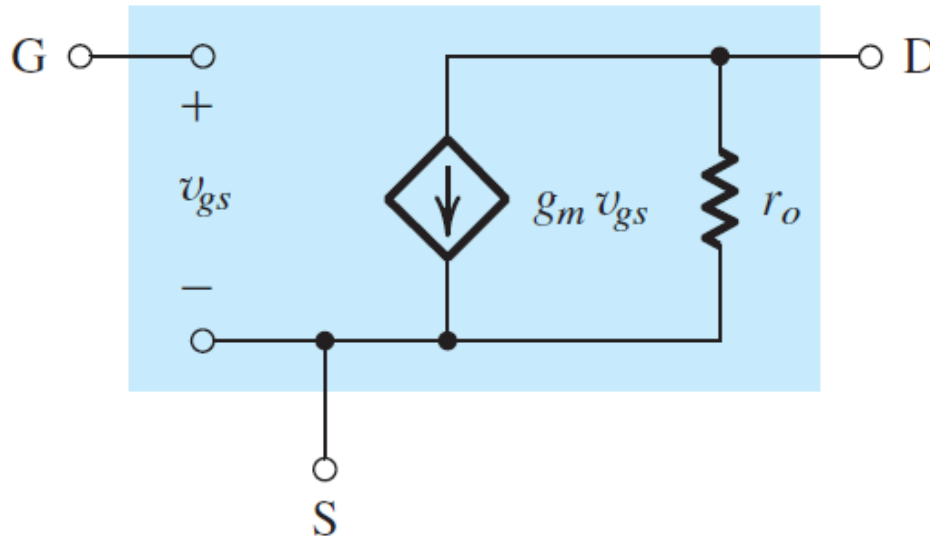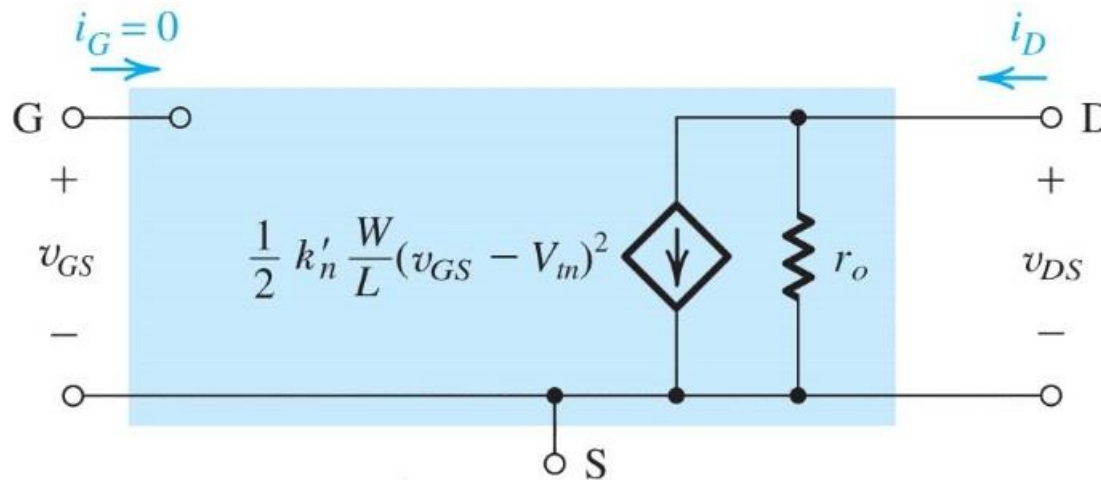

Transconductance

- ❑ The transistor is a VCCS
- ❑ Transconductance: how well it converts the voltage to a current
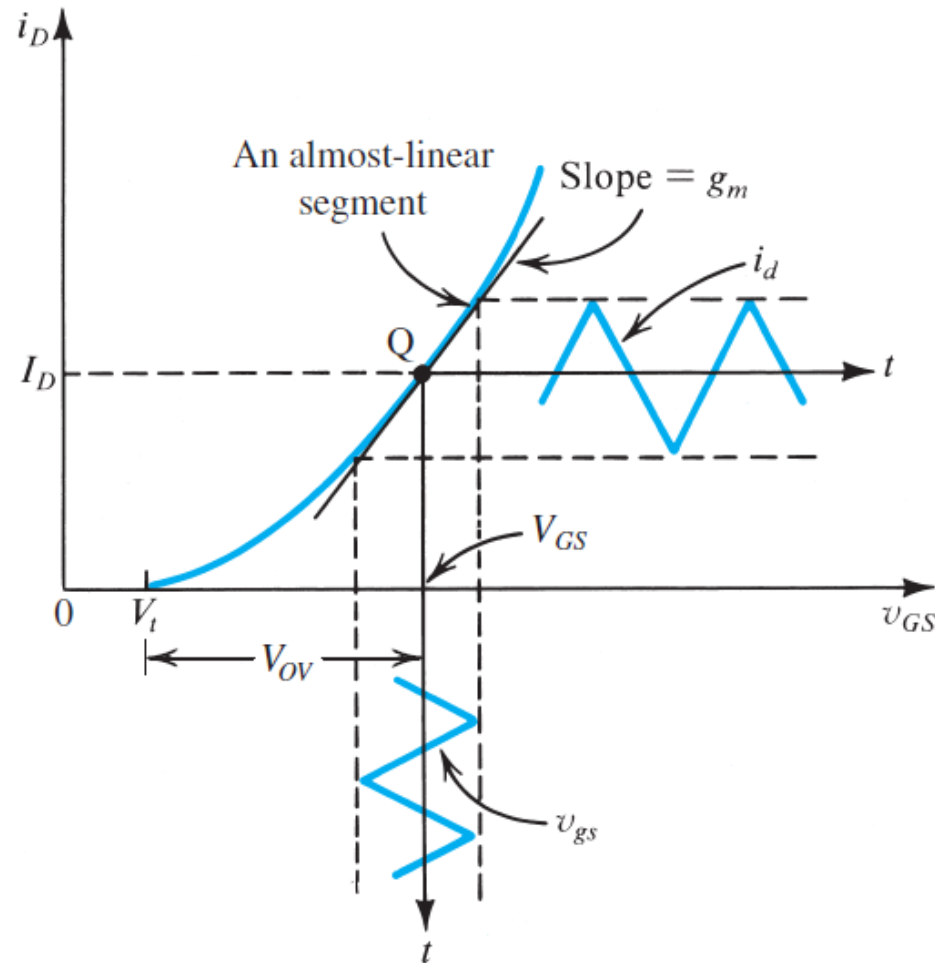
$$\begin{aligned} I_D &\approx \frac{\mu_n C_{ox}}{2} \frac{W}{L} \cdot V_{ov}^2 \\ g_m &= \frac{\Delta I_D}{\Delta V_{GS}} = \frac{\partial I_D}{\partial V_{GS}} = \frac{\partial I_D}{\partial V_{ov}} \\ &= \mu C_{ox} \frac{W}{L} V_{ov} \\ &= \sqrt{\mu C_{ox} \frac{W}{L} \cdot 2I_D} \\ &= \frac{2I_D}{V_{ov}} \end{aligned}$$



Transconductance

$$I_D \approx \frac{\mu_n C_{ox}}{2} \frac{W}{L} \cdot V_{ov}^2$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu C_{ox} \frac{W}{L} V_{ov} = \sqrt{\mu C_{ox} \frac{W}{L} \cdot 2I_D} = \frac{2I_D}{V_{ov}}$$



$\frac{W}{L}$ Constant $V_{GS} - V_{TH}$ Variable	$\frac{W}{L}$ Variable $V_{GS} - V_{TH}$ Constant	$\frac{W}{L}$ Variable $V_{GS} - V_{TH}$ Constant
$g_m \propto \sqrt{I_D}$	$g_m \propto I_D$	$g_m \propto \sqrt{\frac{W}{L}}$
$g_m \propto V_{GS} - V_{TH}$	$g_m \propto \frac{W}{L}$	$g_m \propto \frac{1}{V_{GS} - V_{TH}}$

Body Effect

- V_{SB} affects the charge required to invert the channel
 - Increasing V_S or decreasing V_B increases V_{TH}

$$V_{TH} = V_{TH0} + \gamma \left(\sqrt{2\Phi_F + V_{SB}} - \sqrt{|2\Phi_F|} \right)$$

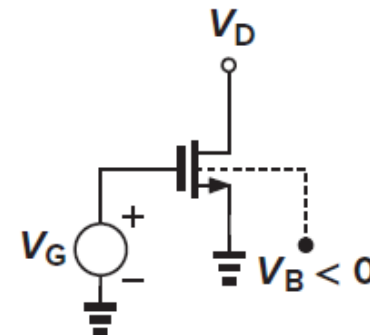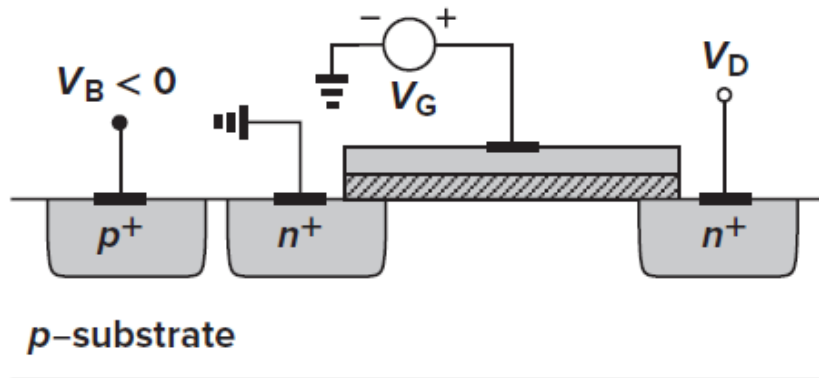- ϕ_F = surface potential at threshold
 - Depends on doping level and intrinsic carrier concentration n_i
- γ = *body effect coefficient*
 - Depends on C_{ox} and doping



Bulk Transconductance

- ❑ The bulk behaves as a second gate that changes the output current

$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}}$$

$$\begin{aligned} g_{mb} &= g_m \frac{\gamma}{2\sqrt{2\Phi_F + V_{SB}}} \\ &= \eta g_m \end{aligned}$$

- ❑ η is typically $0.1 \rightarrow 0.25$


Output Resistance

- I_D increases with V_{DS} in saturation

$$I_D = \frac{\mu_n C_{ox} W}{2 L} \cdot V_{ov}^2 (1 + \lambda V_{DS})$$

- The VCCS is not ideal → it has output resistance
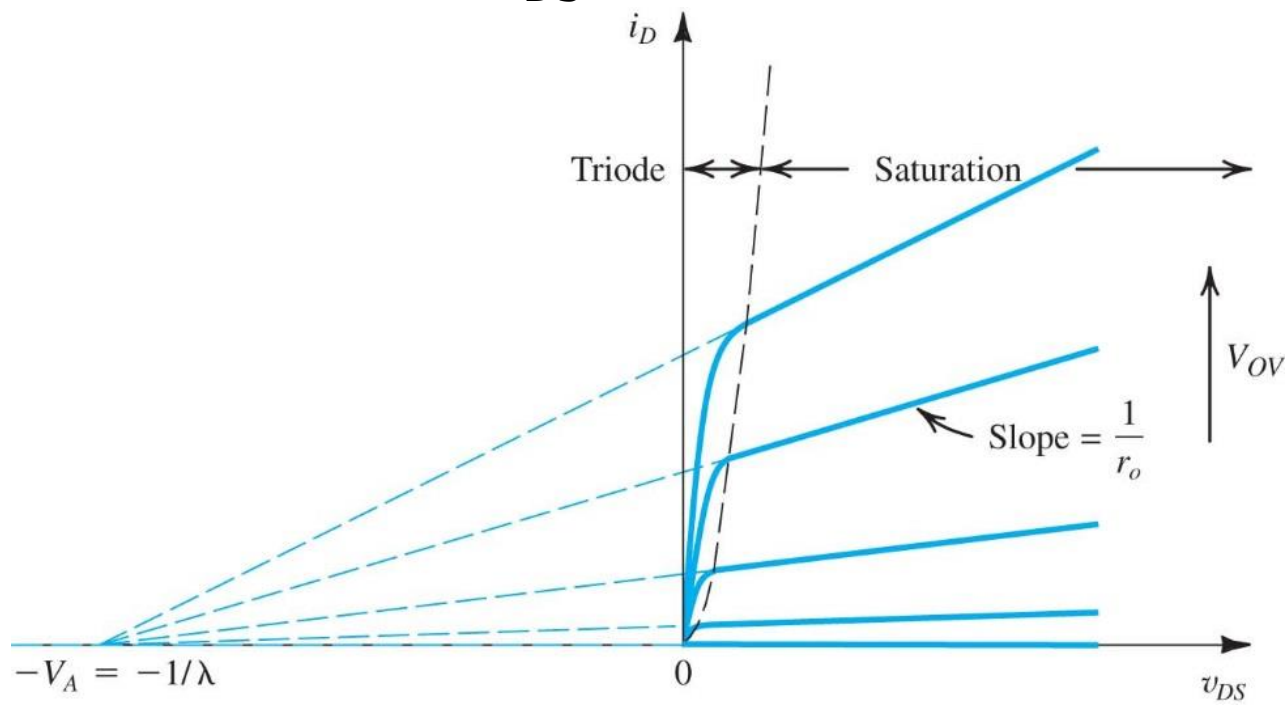
$$r_o = \frac{\Delta V_{DS}}{\Delta I_D} = \frac{1}{\frac{\partial I_D}{\partial V_{DS}}} = \frac{1}{\lambda I_D}, \quad \lambda \propto \frac{1}{L}$$




Low-Frequency Small-Signal Model

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu C_{ox} \frac{W}{L} V_{ov} = \sqrt{\mu C_{ox} \frac{W}{L} \cdot 2I_D} = \frac{2I_D}{V_{ov}}$$

$$g_{mb} = \eta g_m, \quad \eta \approx 0.1 - 0.25$$
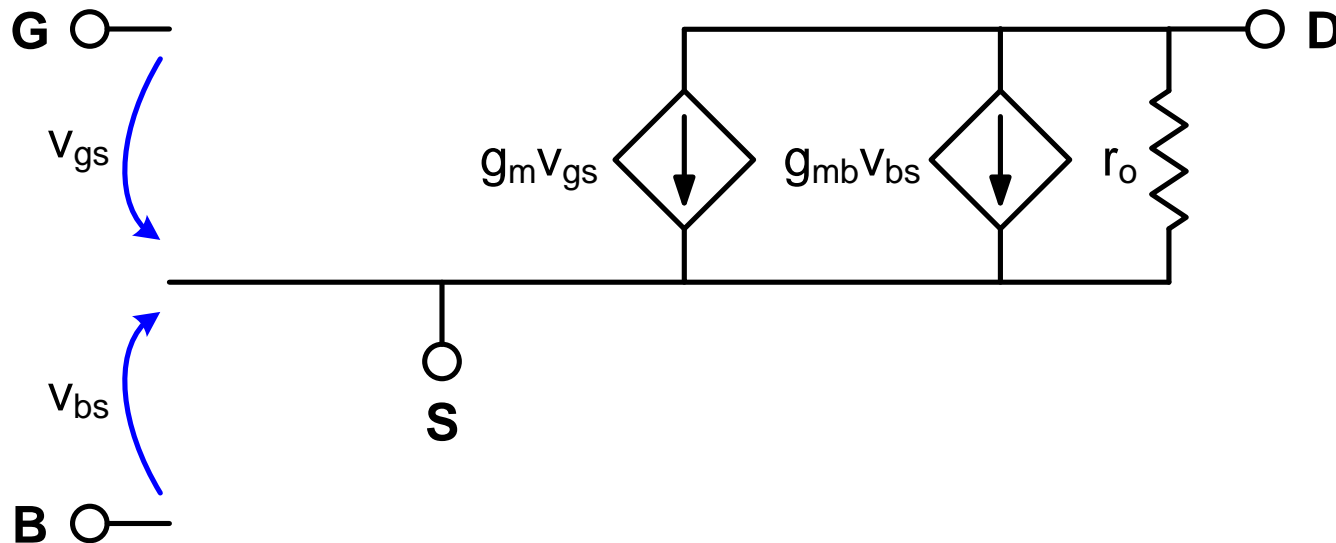
$$r_o = \frac{1}{\frac{\partial I_D}{\partial V_{DS}}} = \frac{1}{\lambda I_D}, \quad \lambda \propto \frac{1}{L}$$



Intrinsic Gain

$$v_{out} = -(g_m v_{in}) r_o$$

$$|A_v| = \left| \frac{v_{out}}{v_{in}} \right| = g_m r_o$$


- $g_m r_o$ is the max gain that can be obtained from a single transistor
- Common approximations that we usually use

$$g_m r_o \gg 1$$

$$r_o \gg \frac{1}{g_m}$$


$$g_m + \frac{1}{r_o} \approx g_m$$
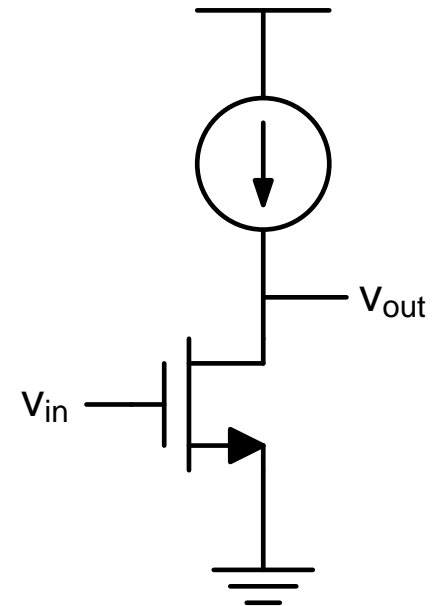
$$r_o // \frac{1}{g_m} \approx \frac{1}{g_m}$$




Short Channel Effects: Velocity Saturation

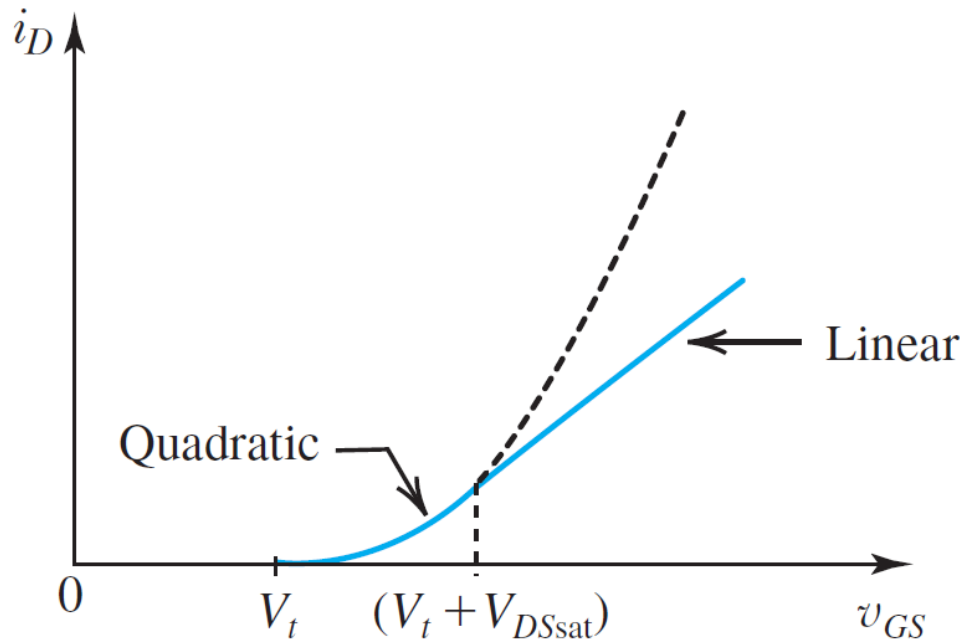- ❑ ID-VGS quadratic: $g_m = \frac{\partial I_D}{\partial V_{GS}} = \text{linear} \rightarrow g_m$ increases with V_{GS}
- ❑ ID-VGS linear: $g_m = \frac{\partial I_D}{\partial V_{GS}} = \text{constant} \rightarrow g_m$ saturates




Short Channel Effects: CLM and DIBL

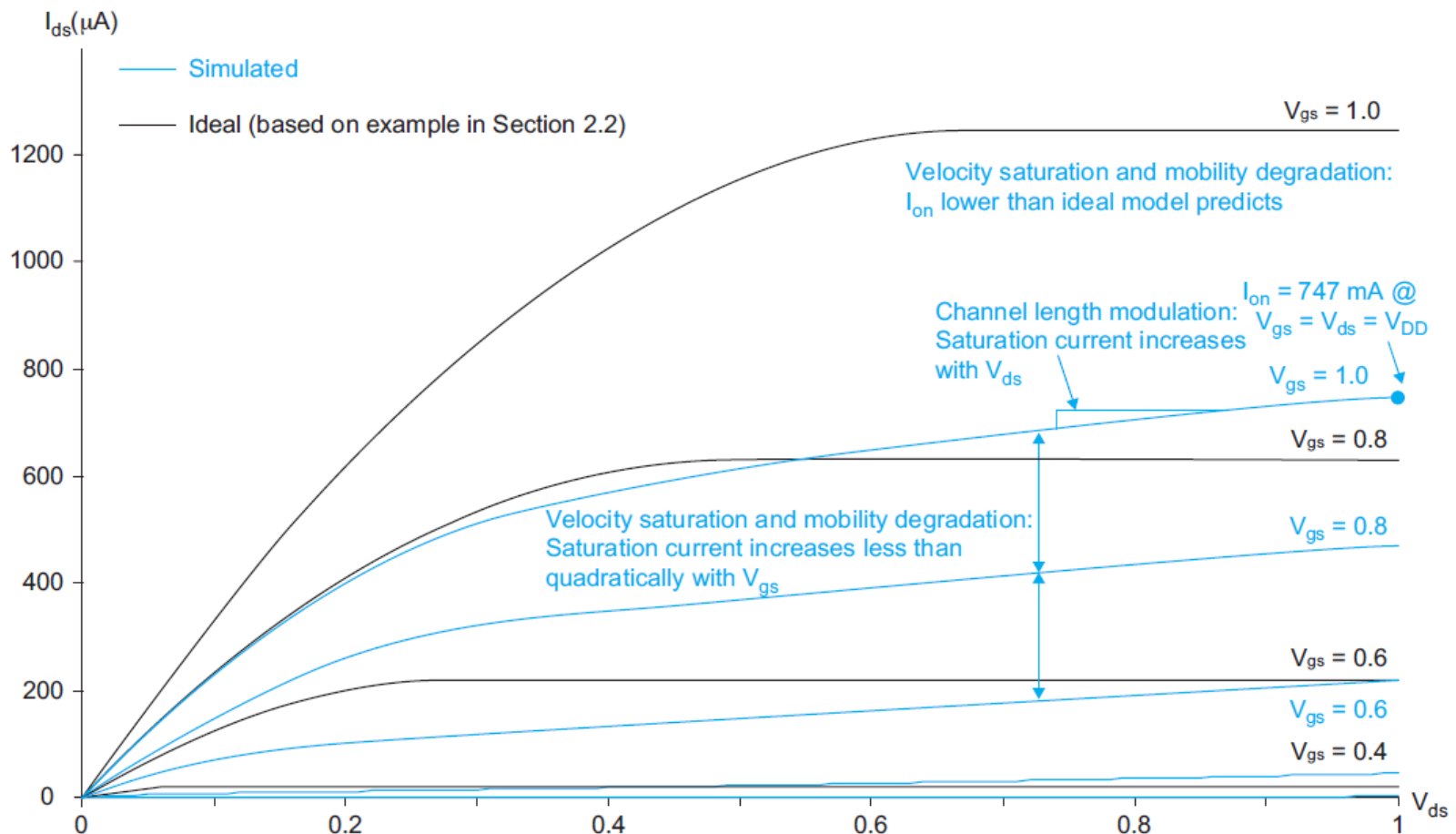
- ❑ ID-VDS horizontal: no V_{DS} dependence \rightarrow ideal current source
- ❑ More slope \rightarrow more V_{DS} dependence \rightarrow smaller r_o \rightarrow smaller gain




MOSFET Amplifier Configurations

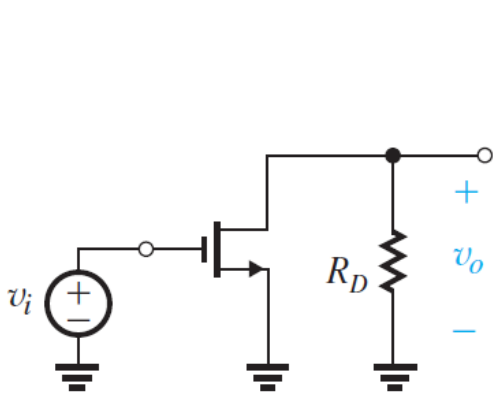

(a) Common Source (CS)

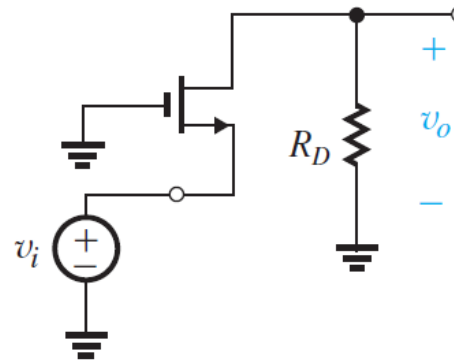

(b) Common Gate (CG)

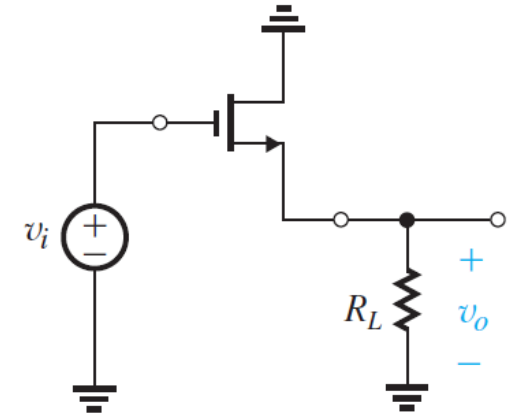

(c) Common Drain (CD)
or Source Follower

Topology	Input	Output
Common-Source	Gate	Drain
Common-Gate	Source	Drain
Common-Drain (Source-Follower)	Gate	Source

MOSFET Amplifier Analysis Steps

1. DC analysis
 - Coupling and bypass capacitors \rightarrow open-circuit (o.c)
 - Calculate Q-point and check operation in saturation ($V_{DS} > V_{ov}$)
2. Calculate small signal parameters (g_m, r_o)
3. Draw the small signal equivalent circuit
 - DC voltage source \rightarrow short-circuit (s.c.)
 - DC current source \rightarrow open-circuit (o.c.)
 - Coupling and bypass capacitors \rightarrow short-circuit (s.c)
4. Determine the amplifier parameters
 - Input resistance and output resistance
 - Voltage gain and current gain

Thank you!

Transconductance

- ❑ The transconductance drops in the triode region
 - Thus, for amplifiers, we usually employ MOSFETs in saturation

$$g_m = \frac{\partial}{\partial V_{GS}} \left\{ \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2] \right\}$$
$$= \mu_n C_{ox} \frac{W}{L} V_{DS}$$

