

وَمَا أُوتِيتُمْ مِنَ الْعِلْمِ إِلَّا قَلِيلًا

Analog IC Design

Lecture 08 Frequency Response (1)



Dr. Hesham A. Omran

Integrated Circuits Lab (ICL)
Electronics and Communications Eng. Dept.
Faculty of Engineering
Ain Shams University

MOSFET in Saturation

- ❑ The channel is pinched off if the difference between the gate and drain voltages is not sufficient to create an inversion layer
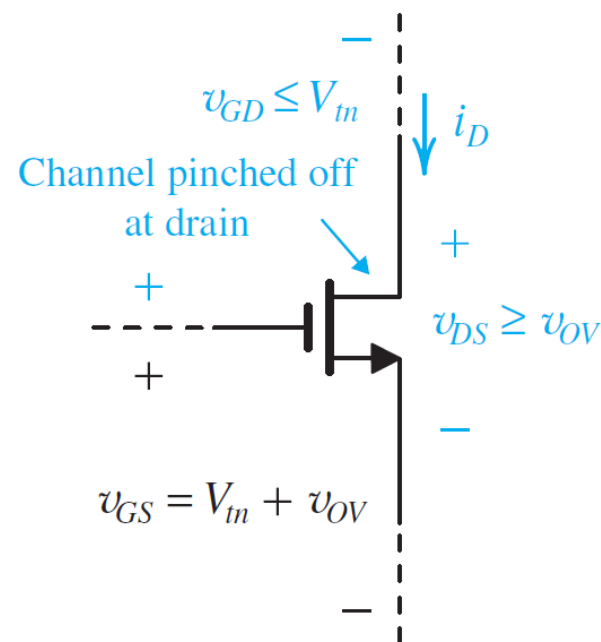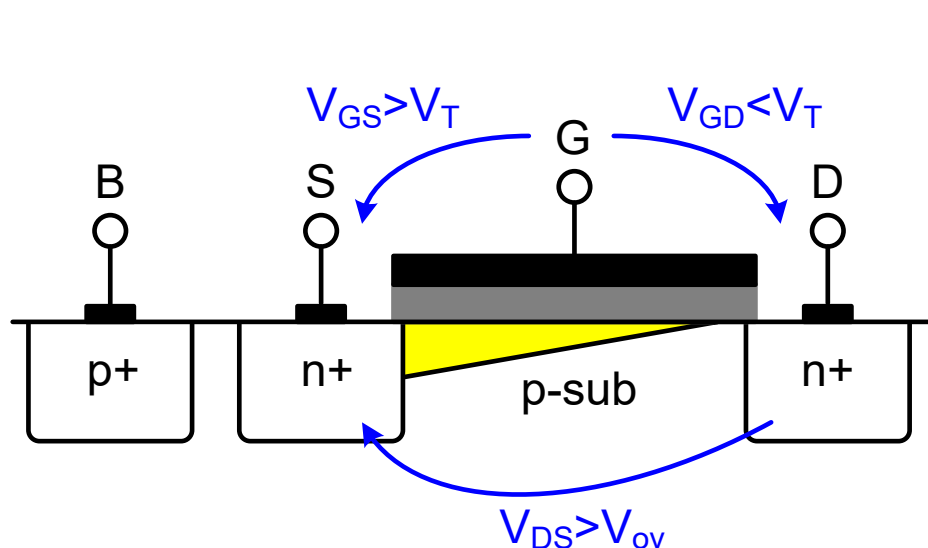
$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \cdot V_{ov}^2 (1 + \lambda V_{DS})$$



Regions of Operation Summary

OFF
(Subthreshold)

$$V_{GS} < V_T$$

ON

$$V_{GS} > V_T$$

Triode

$$V_{DS} < V_{ov}$$

Or

$$V_{GD} > V_T$$

Pinch-Off
(Saturation)

$$V_{DS} \geq V_{ov}$$

Or

$$V_{GD} \leq V_T$$

$$I_D = \mu C_{ox} \frac{W}{L} \left(V_{ov} V_{DS} - \frac{V_{DS}^2}{2} \right)$$


$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} V_{ov}^2 (1 + \lambda V_{DS})$$

Low-Frequency Small-Signal Model


$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu C_{ox} \frac{W}{L} V_{ov} = \sqrt{\mu C_{ox} \frac{W}{L} \cdot 2I_D} = \frac{2I_D}{V_{ov}}$$

$$g_{mb} = \eta g_m, \quad \eta \approx 0.1 - 0.25$$

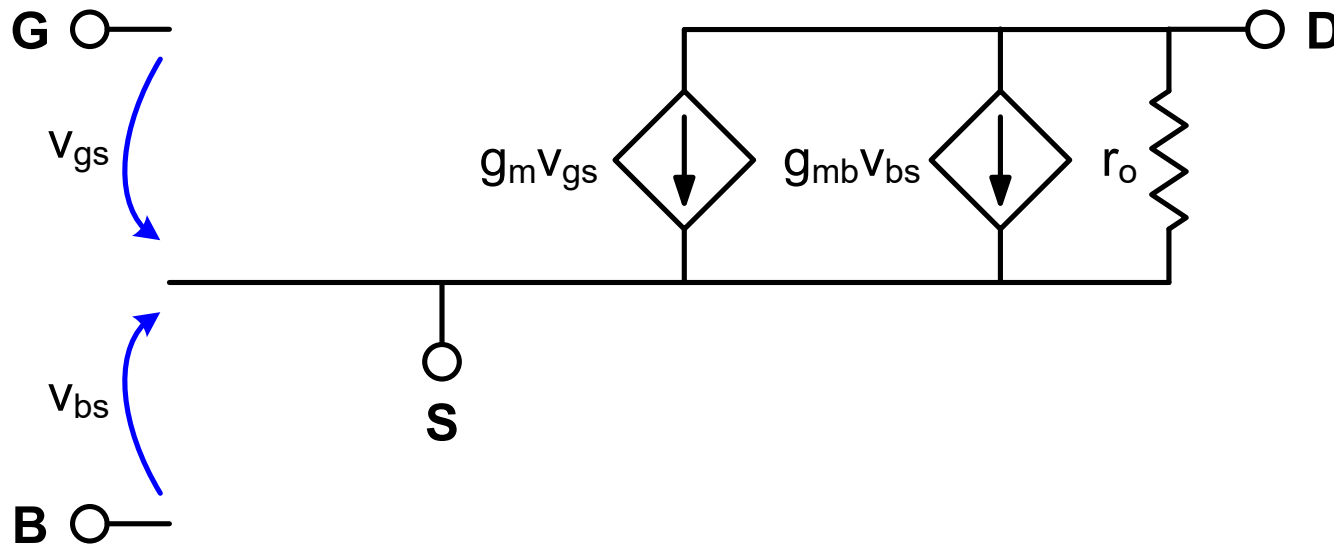
$$r_o = \frac{1}{\frac{\partial I_D}{\partial V_{DS}}} = \frac{1}{\lambda I_D}, \quad \lambda \propto \frac{1}{L}$$



Rin/out Shortcuts Summary


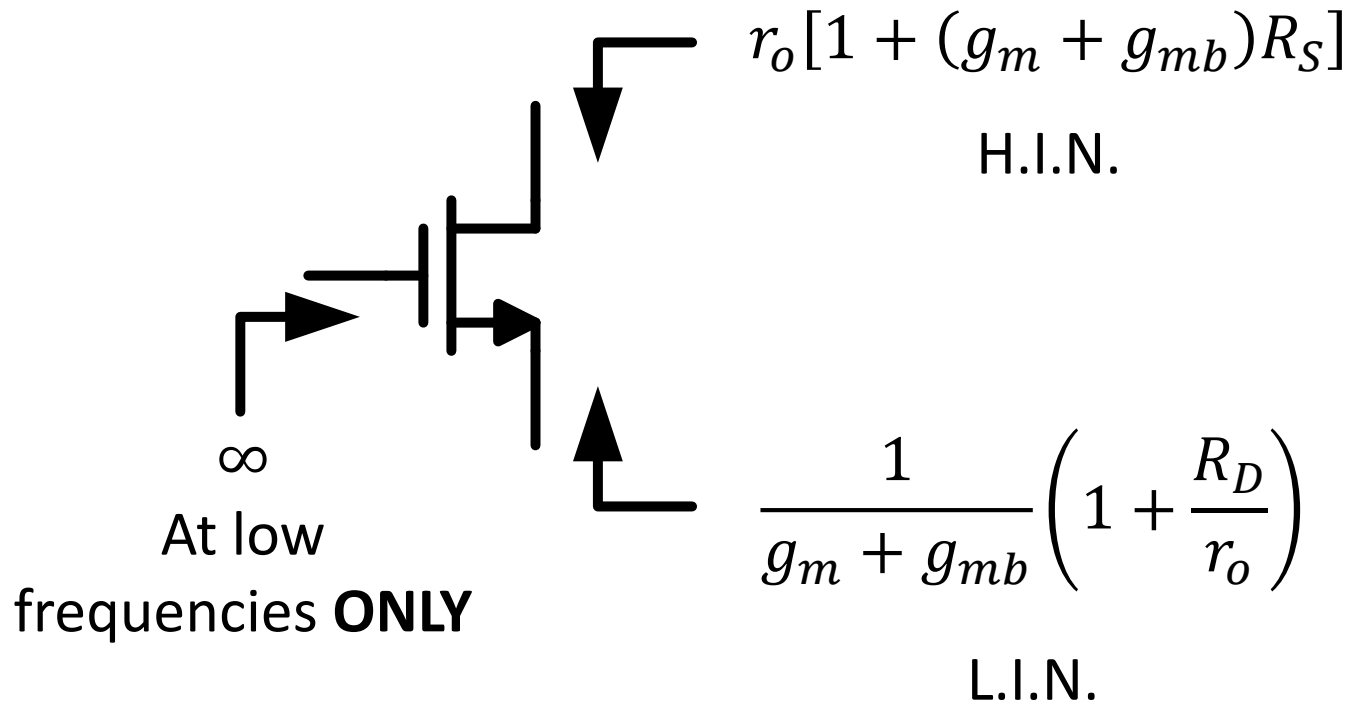


Active Load (Source OFF)

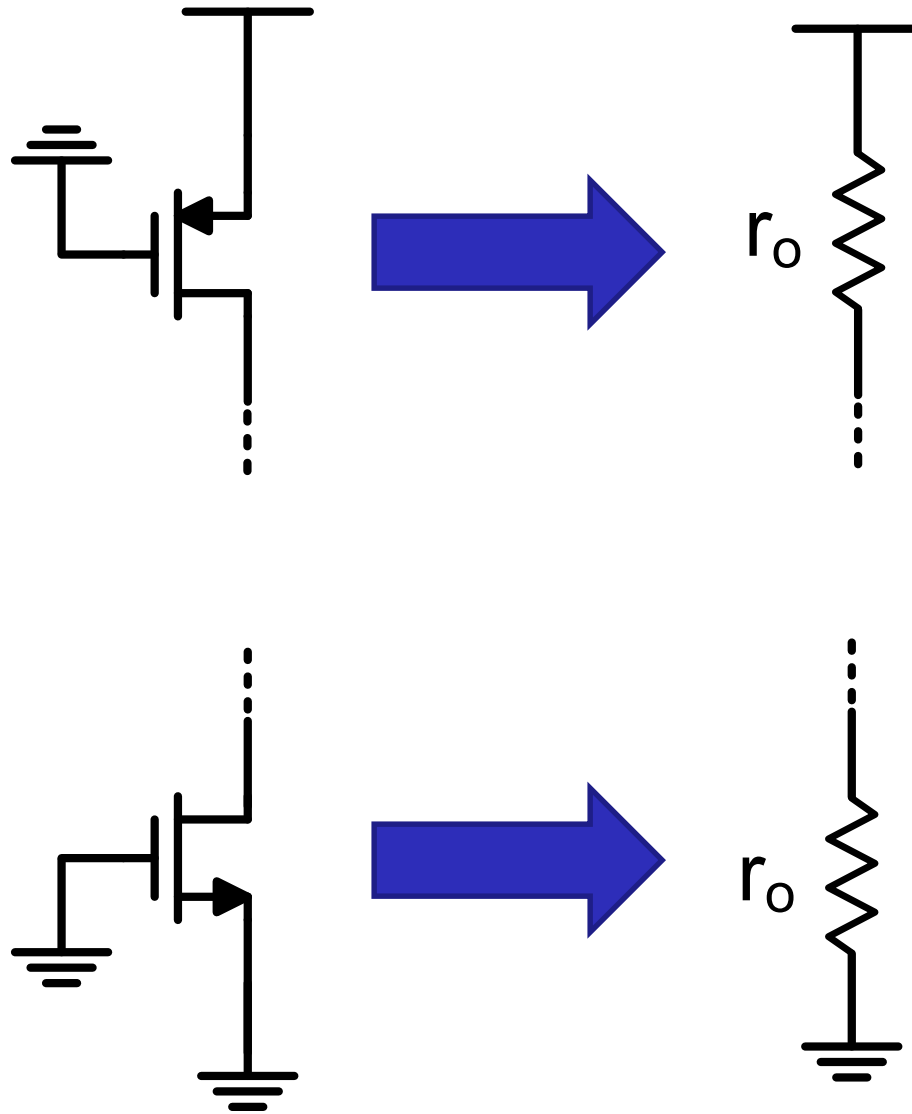

Diode Connected (Source Absorption)

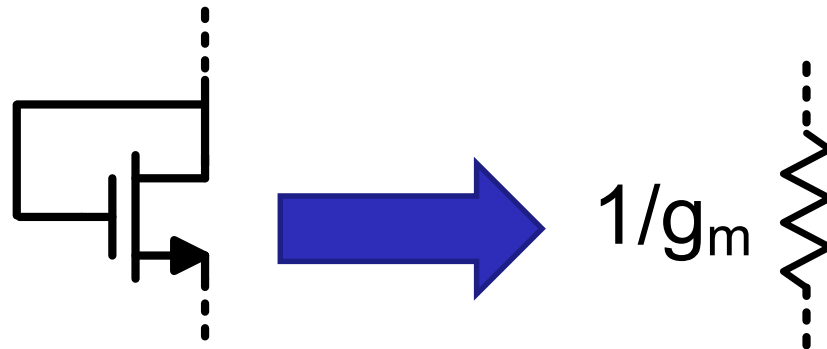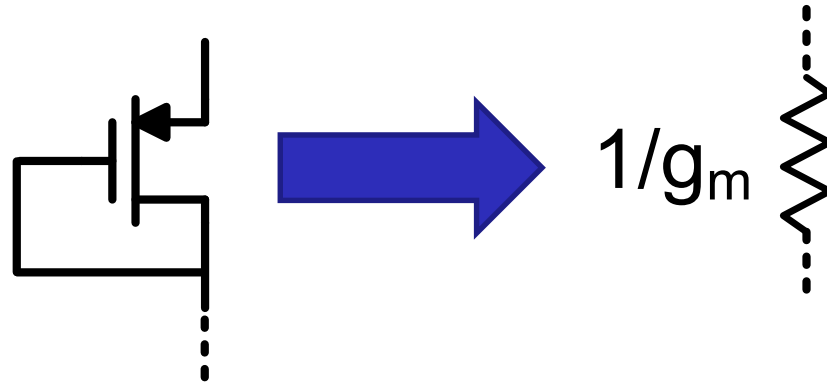- ❑ Always in saturation
- ❑ Bulk effect: $g_m \rightarrow g_m + g_{mb}$



Why GmRout?

$$R_{out} = \frac{v_x}{i_x} @ v_{in} = 0$$



$$G_m = \frac{i_{out,sc}}{v_{in}}$$

$$A_v = G_m R_{out}$$




$$A_i = G_m R_{in}$$

□ Divide and conquer

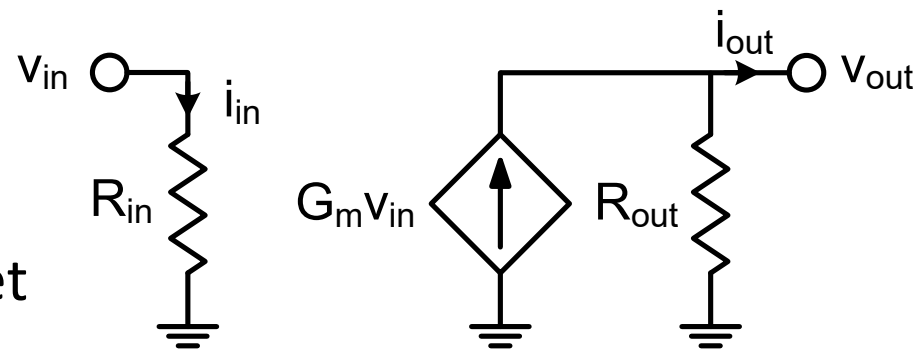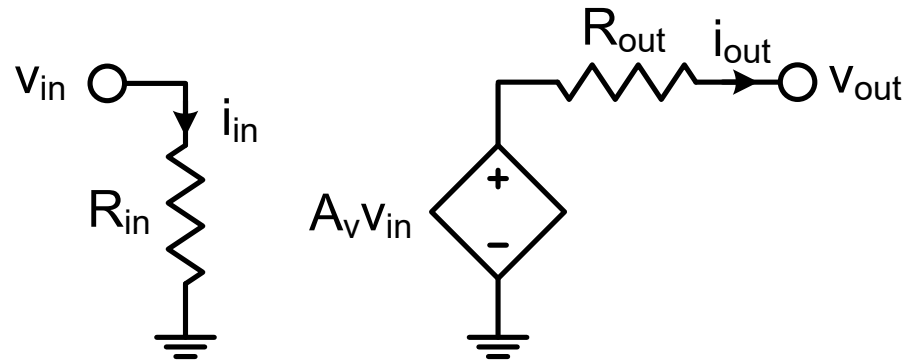- Rout simplified: $v_{in}=0$
- Gm simplified: $v_{out}=0$
- We already need $R_{in/out}$
- We can quickly and easily get $R_{in/out}$ from the shortcuts




Summary of Basic Topologies

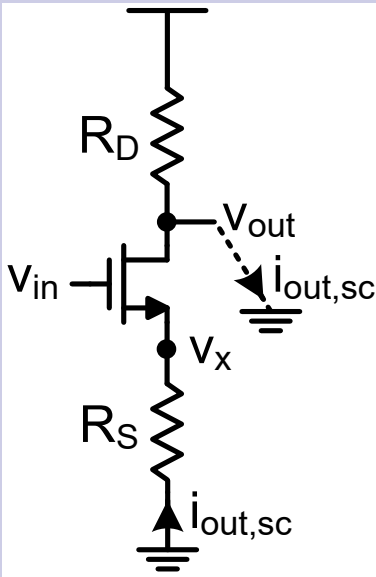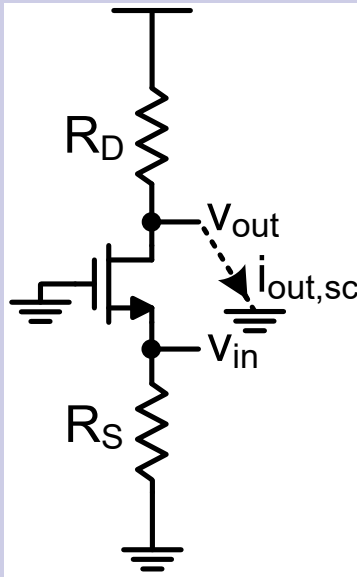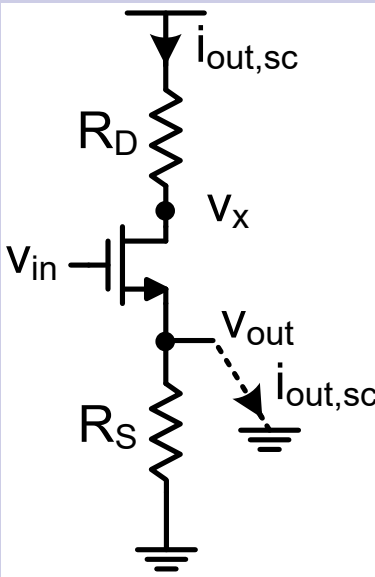
| | CS | CG | CD (SF) |
|-------------|---|--|---|
| |  |  |  |
| | Voltage & current amplifier | Current buffer | Voltage buffer |
| Rin | ∞ | $R_S // \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$ | ∞ |
| Rout | $R_D // r_o [1 + (g_m + g_{mb})R_S]$ | $R_D // r_o$ | $R_S // \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$ |
| Gm | $\frac{-g_m}{1 + (g_m + g_{mb})R_S}$ | $g_m + g_{mb}$ | $\frac{g_m}{1 + R_D/r_o}$ |

Frequency Response


LPF

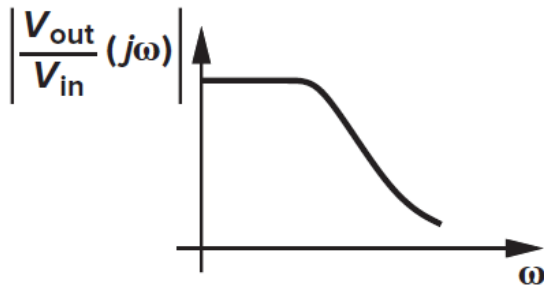

BPF

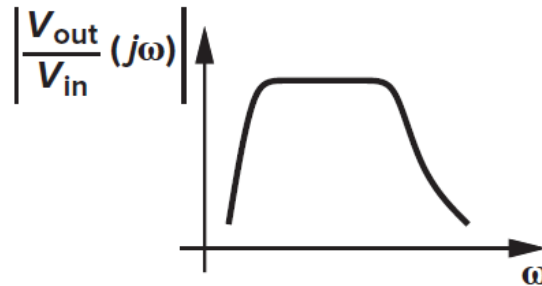

HPF

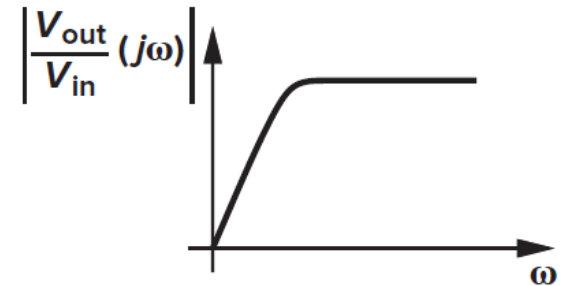

Poles and Zeros


- ❑ Transfer function

$$H(s) = \frac{N(s)}{D(s)}$$

- ❑ Zeros: roots of numerator $\Rightarrow N(s)$
- ❑ Poles: roots of denominator $\Rightarrow D(s)$
- ❑ Frequency response: $s \Rightarrow j\omega$

$$H(j\omega) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = |H(j\omega)|e^{j\phi}$$

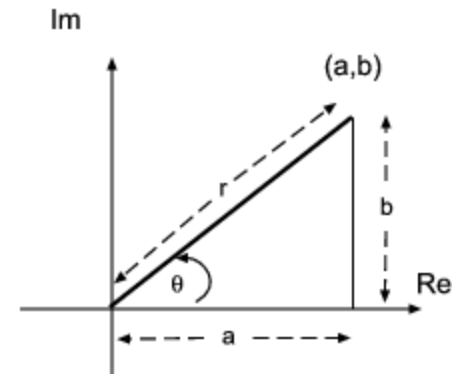- ❑ Magnitude($a + jb$) = $\sqrt{a^2 + b^2}$
- ❑ Phase($a + jb$) = $\tan^{-1} \frac{b}{a}$





1st Order LPF

$$H(s) = \frac{v_{out}}{v_{in}} = \frac{1/sC}{R + 1/sC} = \frac{1}{1 + sRC} = \frac{1}{1 + s\tau}$$


$$H(j\omega) = \frac{v_{out}}{v_{in}} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + \frac{j\omega}{\omega_c}}$$

- ❑ $\tau = RC$: time constant
- ❑ $\omega_c = \frac{1}{\tau} = \frac{1}{RC}$: cutoff/corner frequency
- ❑ Poles: $s_p = -\frac{1}{\tau} = -\omega_c$
- ❑ Zeros: ?
- ❑ $|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$
- ❑ $P(H(j\omega)) = -\tan^{-1} \frac{\omega}{\omega_c}$

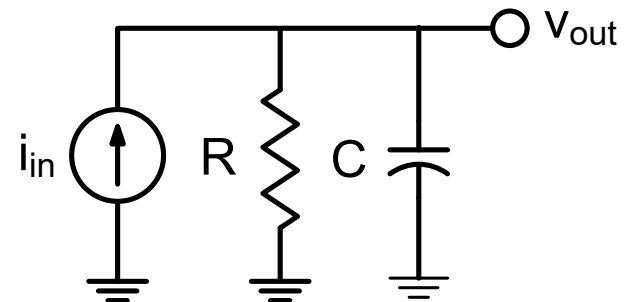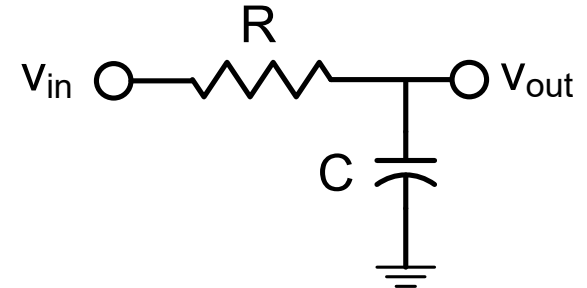


1st Order LPF

$20 \log |H(j\omega)| \text{ (dB)}$

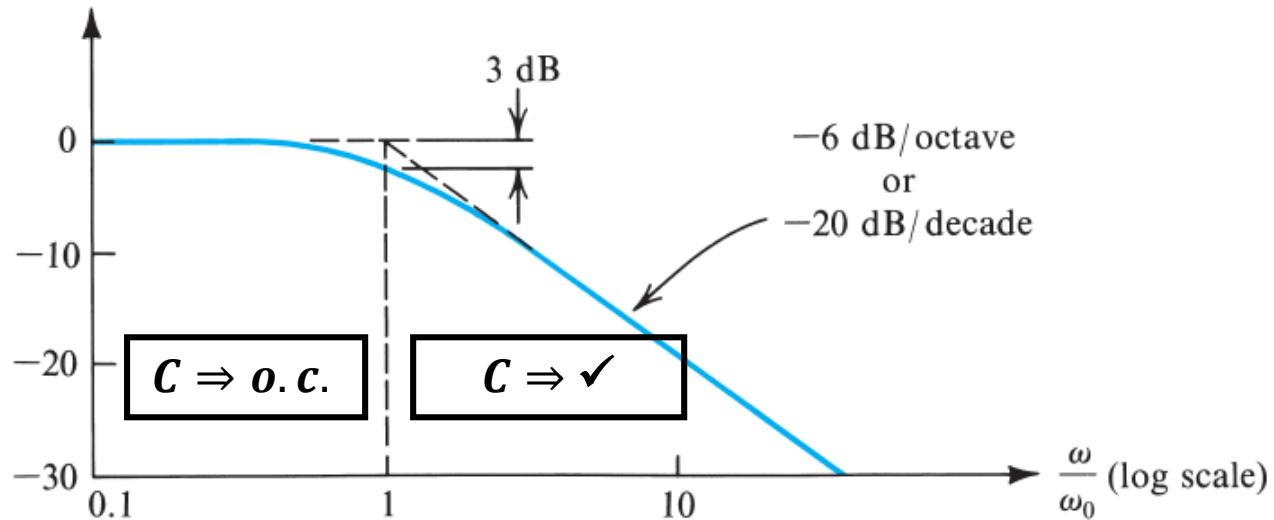

(a)

$P(H(j\omega))$

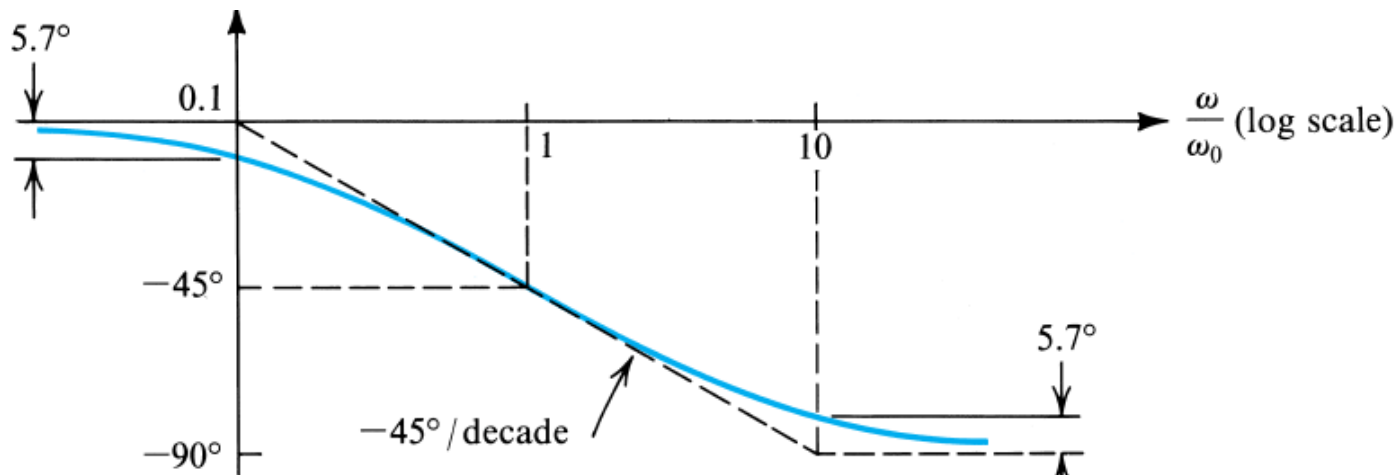

(b)

1st Order HPF

$$H(s) = \frac{v_{out}}{v_{in}} = \frac{R}{R + 1/sC} = \frac{sRC}{1 + sRC} = \frac{s\tau}{1 + s\tau}$$


$$H(j\omega) = \frac{v_{out}}{v_{in}} = \frac{R}{R + 1/j\omega C} = \frac{j\omega RC}{1 + j\omega RC} = \frac{\frac{j\omega}{\omega_c}}{1 + \frac{j\omega}{\omega_c}}$$

❑ Poles: $s_p = -\frac{1}{\tau} = -\omega_c$

❑ Zeros: $s_z = 0$


❑ $|H(j\omega)| = \frac{\frac{\omega}{\omega_c}}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$

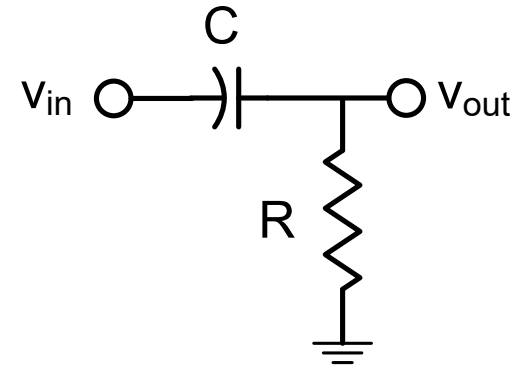❑ $P(H(j\omega)) = 90^\circ - \tan^{-1} \frac{\omega}{\omega_c}$




1st Order HPF

$20 \log|H(j\omega)|$ (dB)

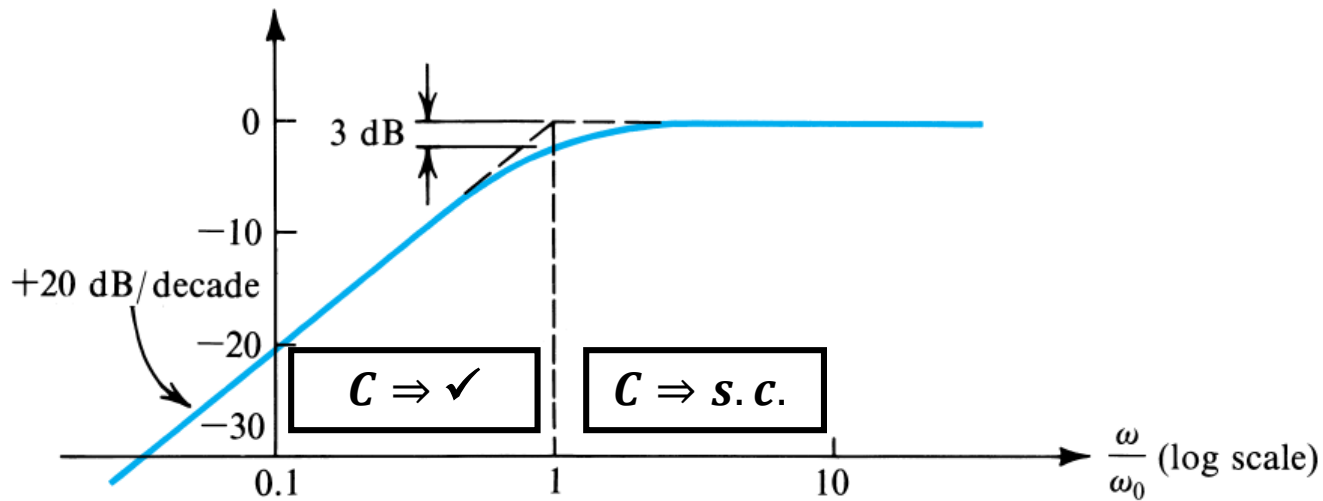

(a)


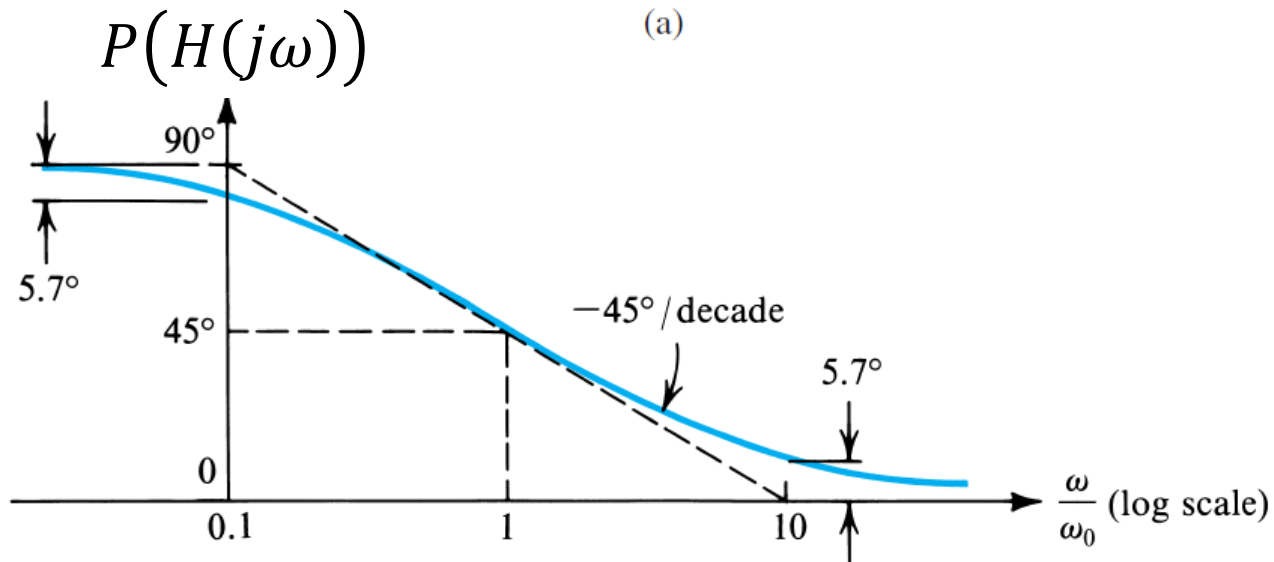


(b)


Bode Plot Rules

| | Pole | Zero |
|------------------|---|--|
| Magnitude | -20 dB/decade Actual Mag @ pole: -3 dB | +20 dB/decade Actual Mag @ zero: +3 dB |
| Phase | -90° Actual Phase @ pole: -45° | LHP zero: +90° Actual Phase @ zero: +45° RHP zero: -90° Actual Phase @ zero: -45° |

Where are the Capacitors?

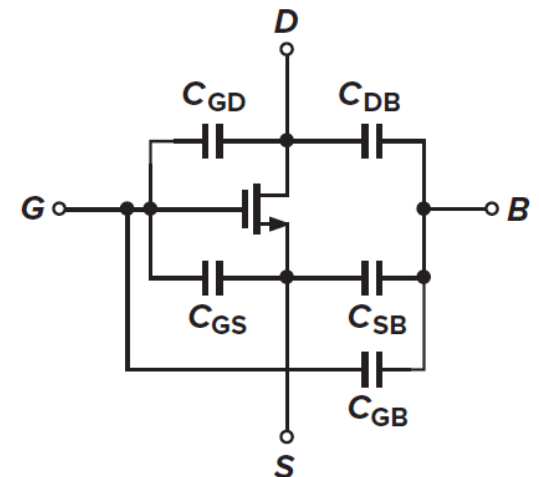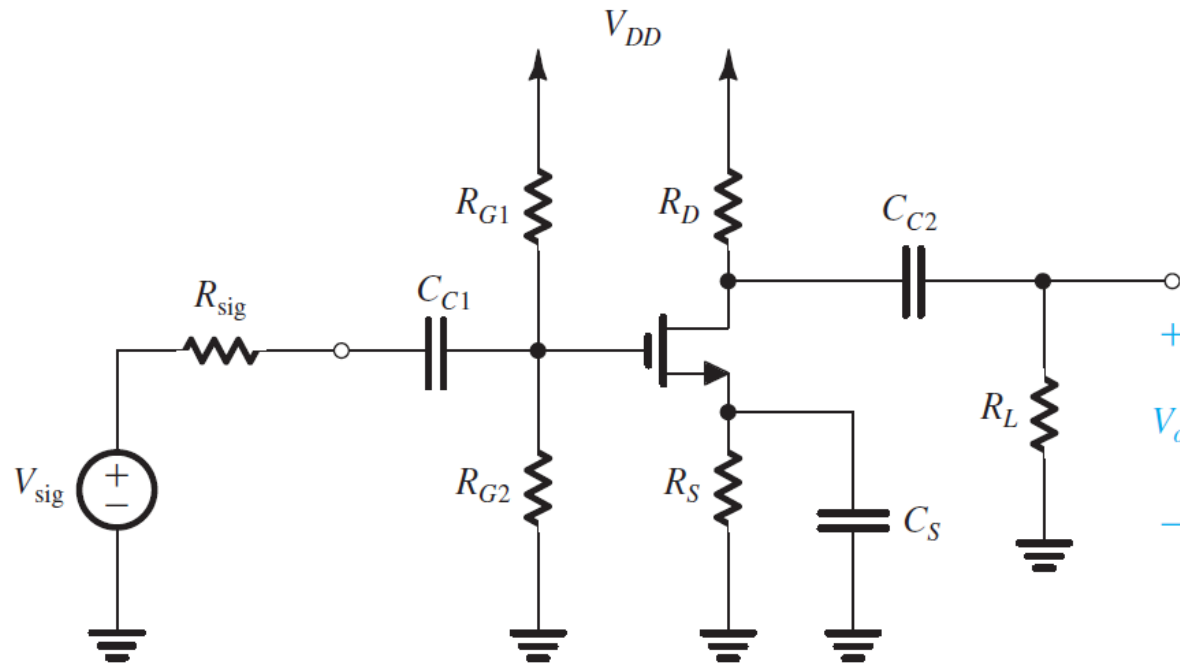

Frequency Response

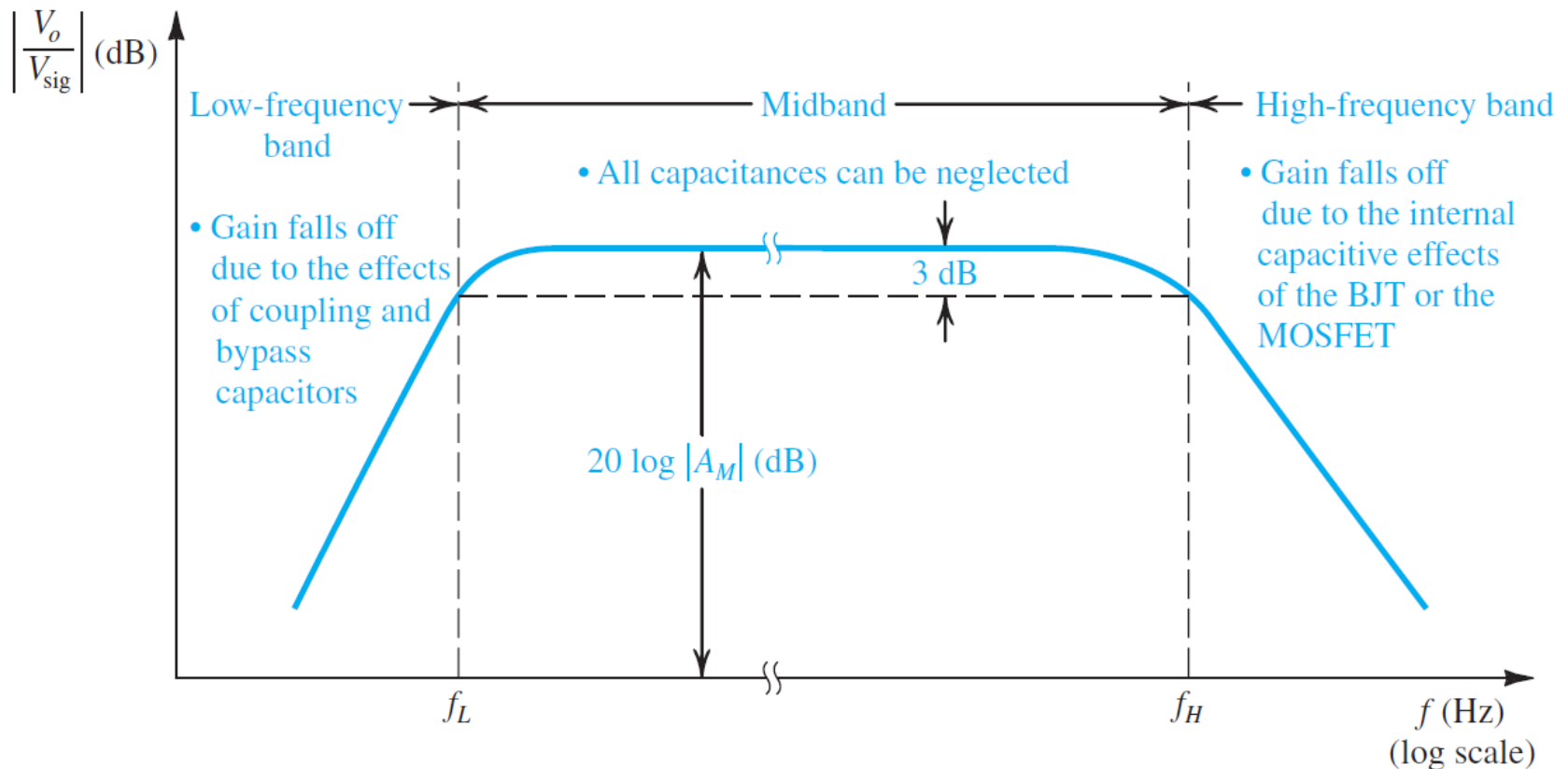


| | | | |
|---------------------|------|------|------|
| Coupling and bypass | ✓ | S.C. | S.C. |
| Intrinsic and load | O.C. | O.C. | ✓ |

SCTC and OCTC Techniques

- ❑ Low-frequency range (LFR) => Not common in IC design
 - Only consider one cap at a time
 - Assume other caps are s.c.
 - s.c. time constant (SCTC) technique
 - $\omega_L \approx \omega_{L1} + \omega_{L2} + \dots$
 - Highest pole dominates (L.I.N. dominates)
- ❑ **High-frequency range (HFR) => More important in IC design**
 - **Only consider one cap at a time**
 - **Assume other caps are o.c.**
 - **o.c. time constant (OCTC) technique**
 - $\omega_H \approx \omega_{H1} // \omega_{H2} // \dots$
 - **Lowest pole dominates (H.I.N. dominates)**
- ❑ Both provide good approx if one pole is dominant (and poles are real)

Effect of Bypass Capacitor

- Does C_S act as a LPF or a HPF?

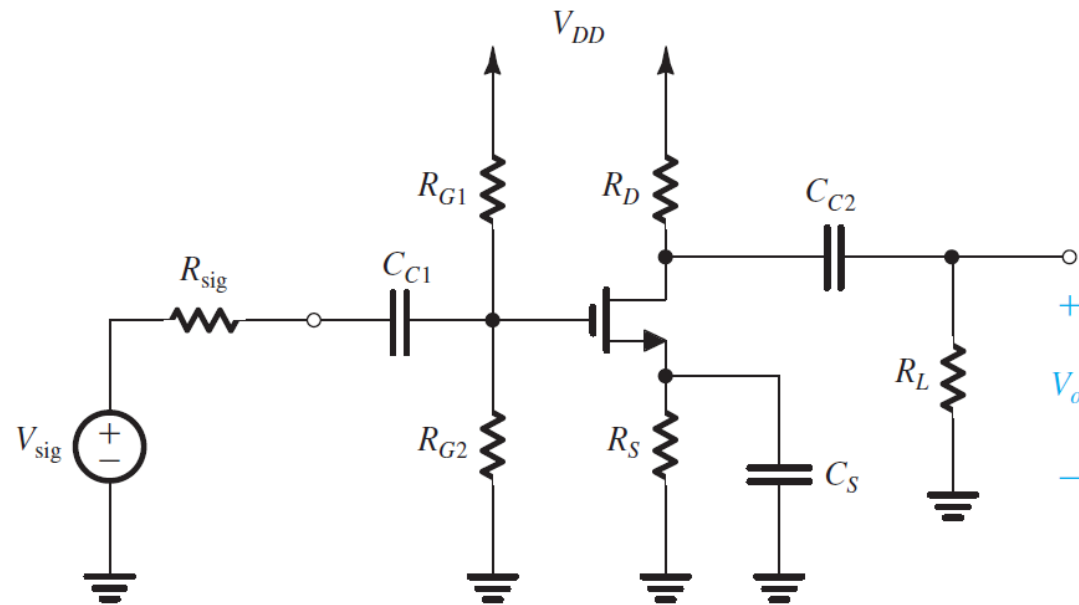


Calculating Zeros by Inspection

1. Find the value $s = s_z$ that makes $H(s) = 0 \Rightarrow v_{out} = 0$

□ Ex1: C_{c1} : $v_o = 0$ if $Z_{C_1} = \infty$

$$- Z_{C_1} = \frac{1}{sC_1}$$


$$- \Rightarrow s_{z1} = 0$$

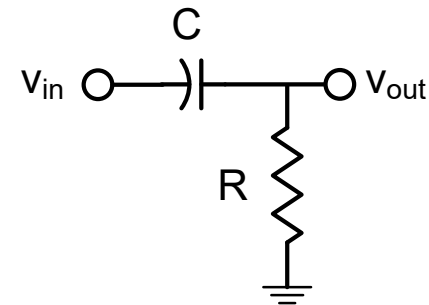

□ Ex2: C_S : $v_o = 0$ if $Z_S = \infty$

$$- Z_S = \frac{R_S}{1+sR_SC_S}$$
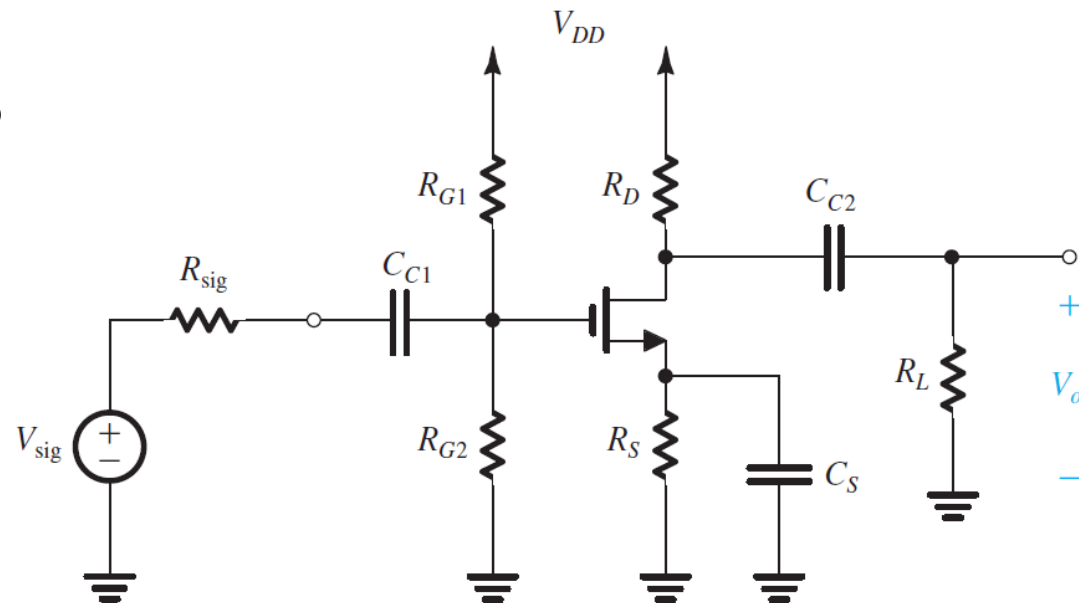
$$- \Rightarrow s_{z2} = -\frac{1}{R_SC_S}$$



Calculating Poles by Inspection

1. Set $v_{in} = 0$
2. Calculate thevenin resistance ($R_{th,i}$) seen by each cap (C_i)


$$3. s_{p,i} = -\frac{1}{R_{th,i}C_i}$$

□ Ex1: $C_{c1}: R_{th} = R_{sig} + R_G$

$$\Rightarrow s_{p1} = -\frac{1}{(R_{sig} + R_G)C_{c1}}$$

□ Ex2: $C_S: R_{th} \approx R_S // \frac{1}{g_m}$

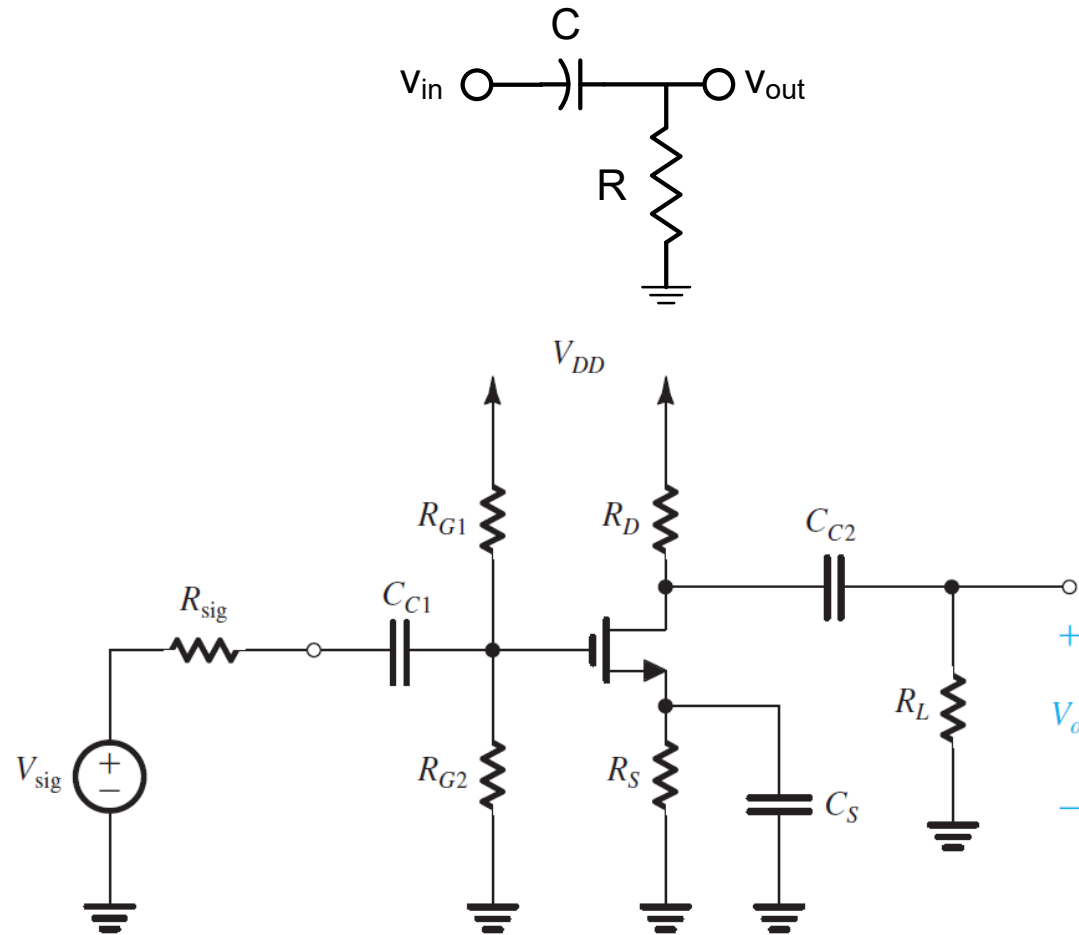
$$\Rightarrow s_{p2} = -\frac{1}{(R_S // \frac{1}{g_m})C_S}$$



Calculating Poles by Inspection

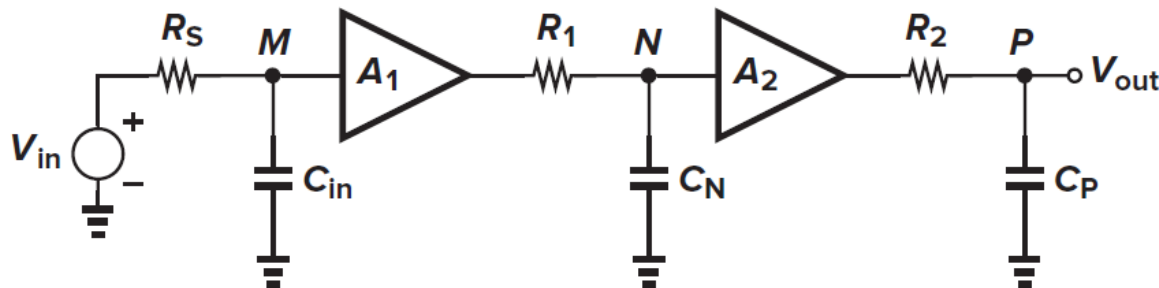1. Set $v_{in} = 0$
 2. Calculate thevenin resistance ($R_{th,i}$) seen by each cap (C_i)
 3. $s_{p,i} = -\frac{1}{R_{th,i}C_i}$
- Examples:
- Each node is associated with a pole
 - H.I.N. dominates

$$\frac{V_{out}}{V_{in}}(s) = \frac{A_1}{1 + R_S C_{in}s} \cdot \frac{A_2}{1 + R_1 C_N s} \cdot \frac{1}{1 + R_2 C_P s}$$



Thank you!