

وَمَا أُوتِيتُمْ مِنَ الْعِلْمِ إِلَّا قَلِيلًا

Analog IC Design

Lecture 15

OTA / Op-Amp Topologies



Dr. Hesham A. Omran

Integrated Circuits Lab (ICL)
Electronics and Communications Eng. Dept.
Faculty of Engineering
Ain Shams University

MOSFET in Saturation

- ❑ The channel is pinched off if the difference between the gate and drain voltages is not sufficient to create an inversion layer
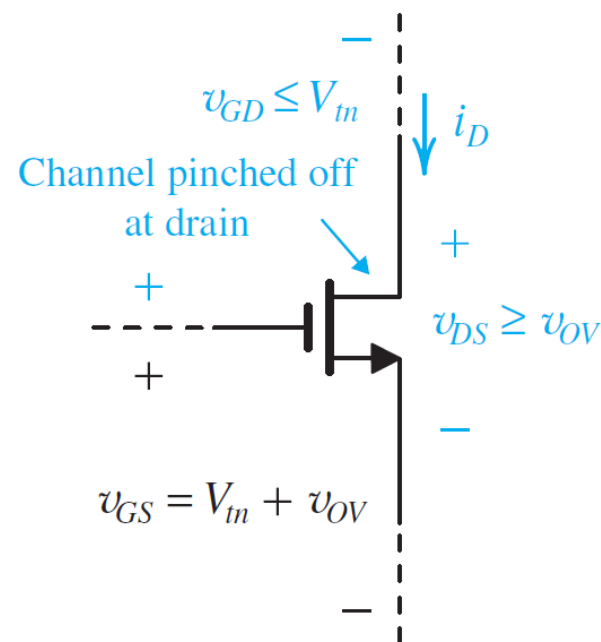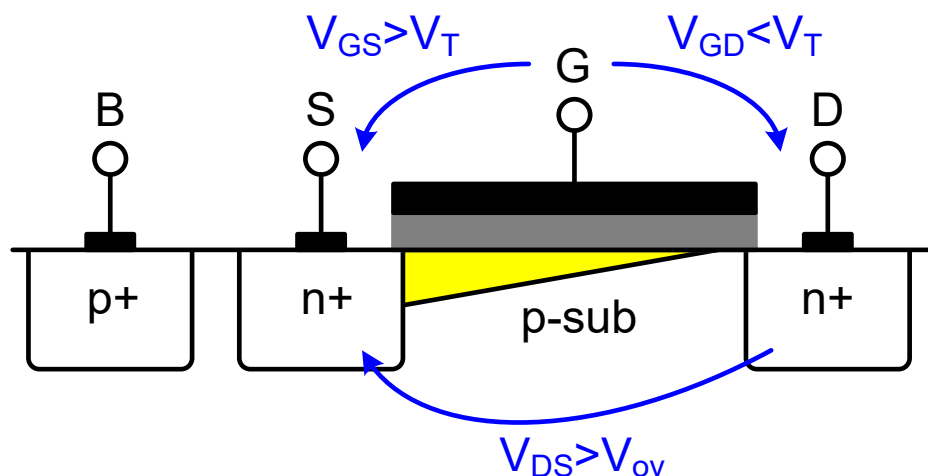
$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \cdot V_{ov}^2 (1 + \lambda V_{DS})$$



Regions of Operation Summary

OFF
(Subthreshold)

$$V_{GS} < V_T$$

ON

$$V_{GS} > V_T$$

Triode

$$V_{DS} < V_{ov}$$

Or

$$V_{GD} > V_T$$

Pinch-Off
(Saturation)

$$V_{DS} \geq V_{ov}$$

Or

$$V_{GD} \leq V_T$$

$$I_D = \mu C_{ox} \frac{W}{L} \left(V_{ov} V_{DS} - \frac{V_{DS}^2}{2} \right)$$


$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} V_{ov}^2 (1 + \lambda V_{DS})$$

Low-Frequency Small-Signal Model


$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu C_{ox} \frac{W}{L} V_{ov} = \sqrt{\mu C_{ox} \frac{W}{L} \cdot 2I_D} = \frac{2I_D}{V_{ov}}$$

$$g_{mb} = \eta g_m, \quad \eta \approx 0.1 - 0.25$$

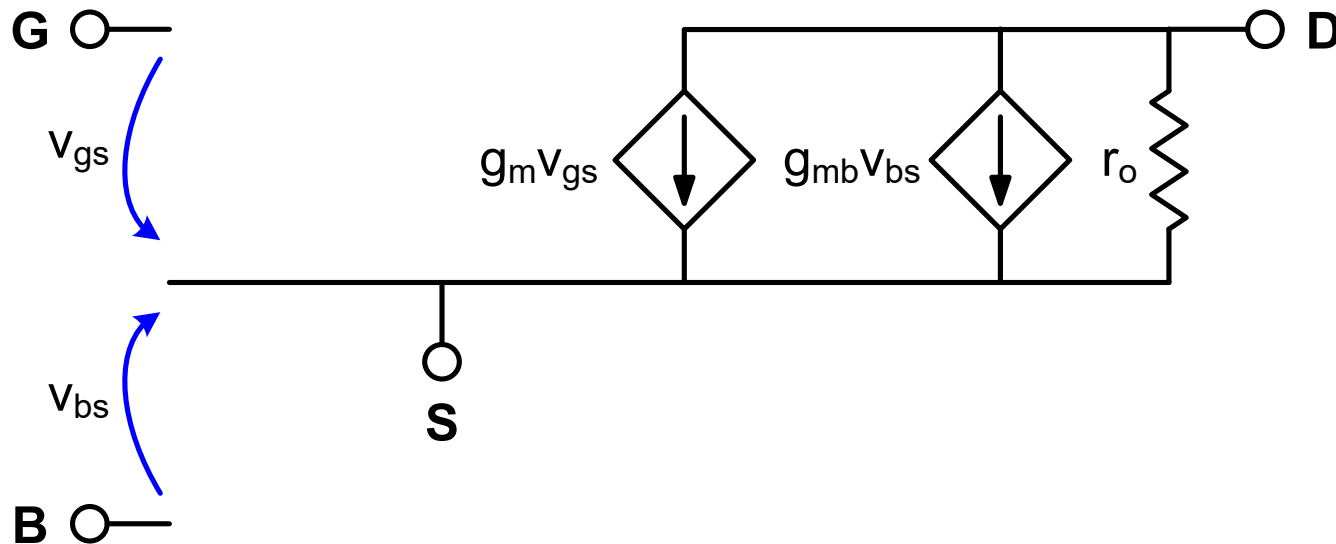
$$r_o = \frac{1}{\frac{\partial I_D}{\partial V_{DS}}} = \frac{1}{\lambda I_D}, \quad \lambda \propto \frac{1}{L}$$



Rin/out Shortcuts Summary


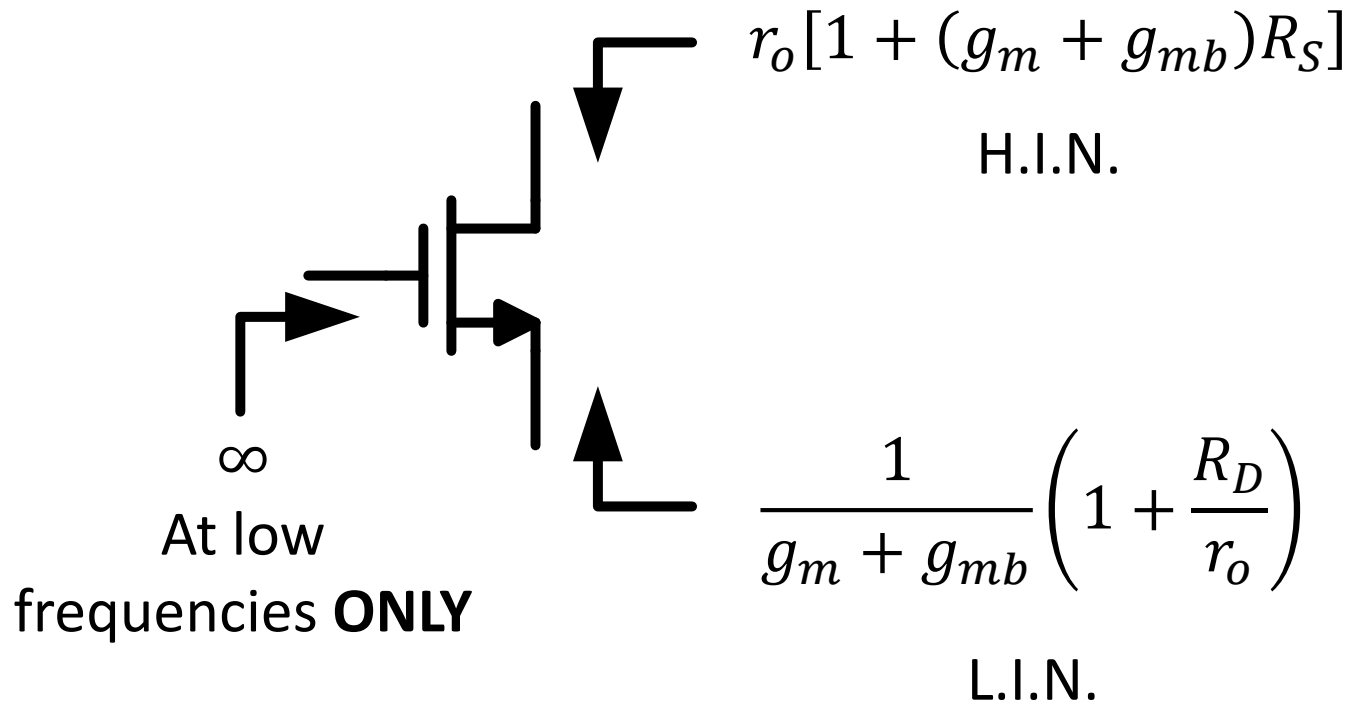


Active Load (Source OFF)

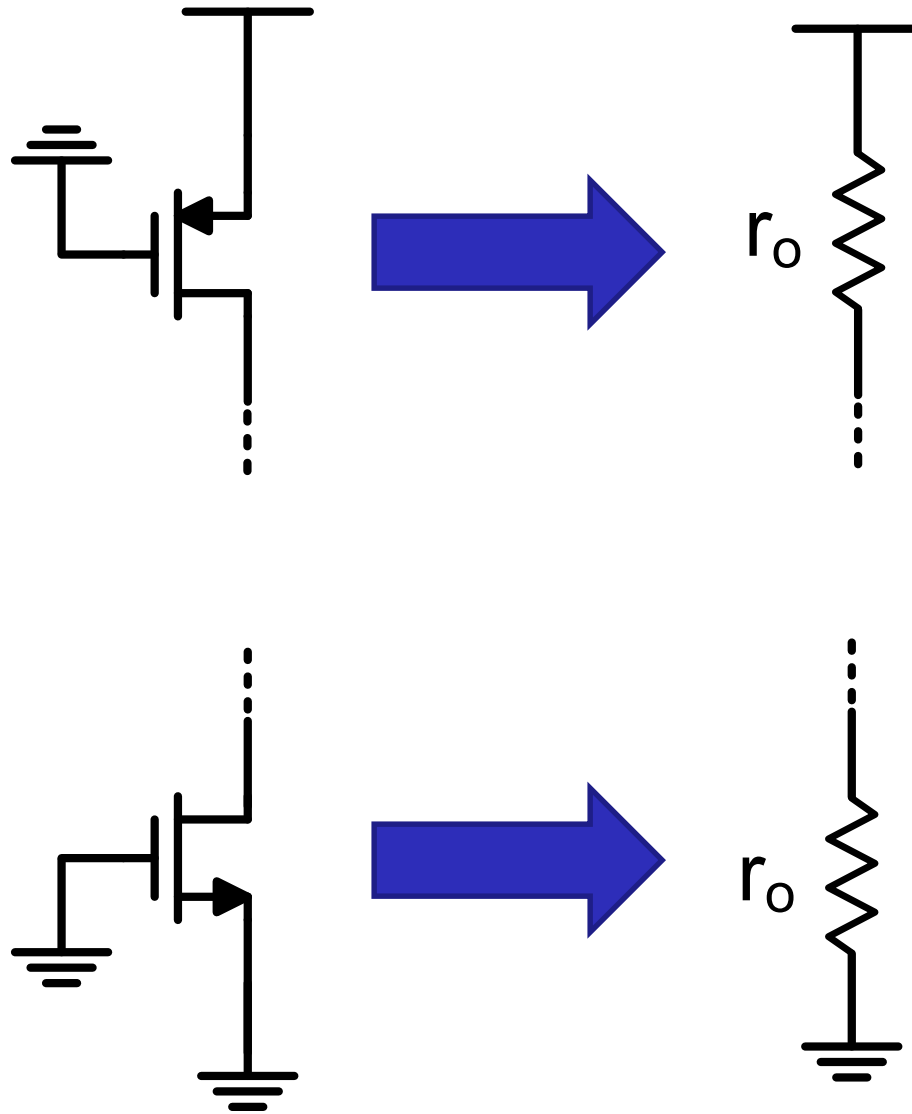

Diode Connected (Source Absorption)

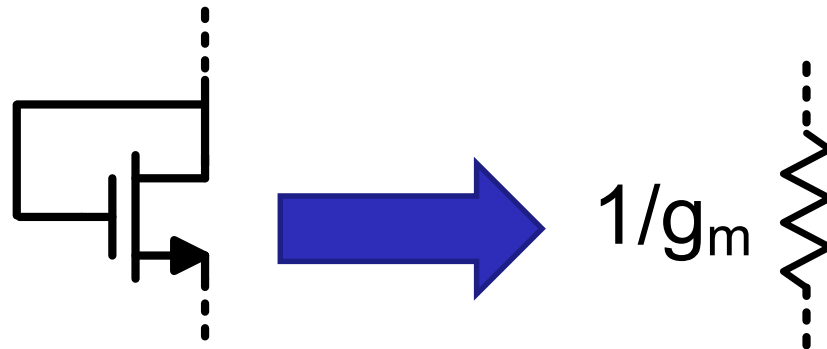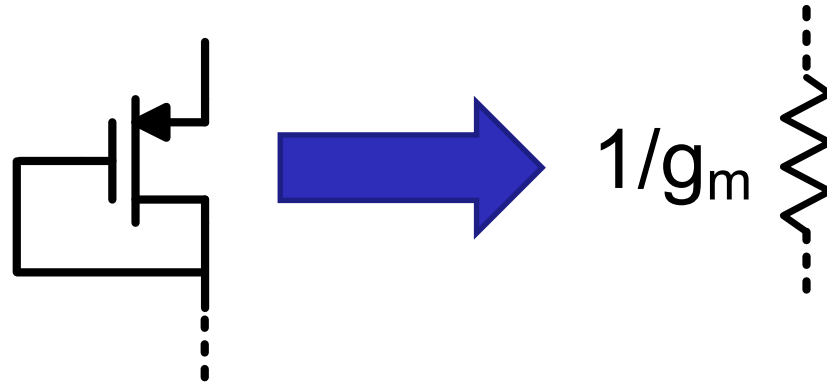- ❑ Always in saturation
- ❑ Bulk effect: $g_m \rightarrow g_m + g_{mb}$



Why GmRout?

$$R_{out} = \frac{v_x}{i_x} @ v_{in} = 0$$



$$G_m = \frac{i_{out,sc}}{v_{in}}$$

$$A_v = G_m R_{out}$$

$$A_i = G_m R_{in}$$

□ Divide and conquer

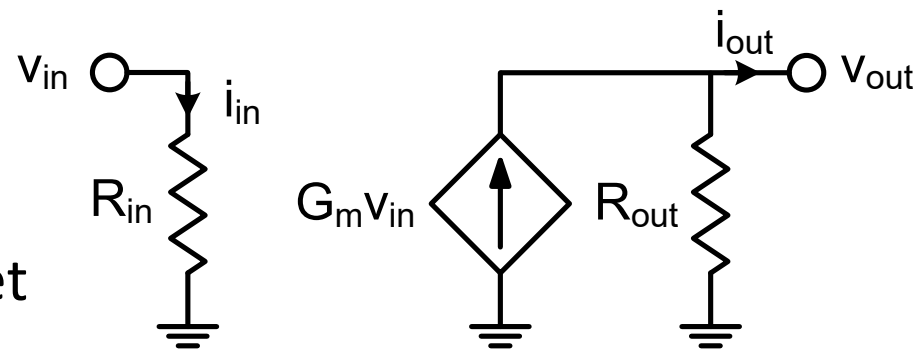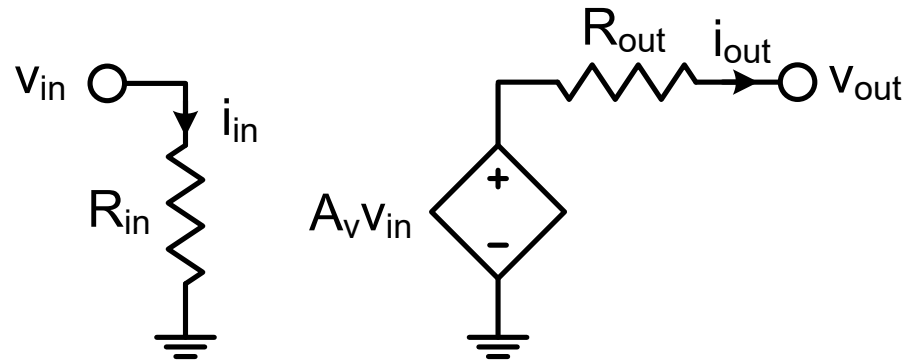- Rout simplified: $v_{in}=0$
- Gm simplified: $v_{out}=0$
- We already need Rin/out
- We can quickly and easily get Rin/out from the shortcuts



Summary of Basic Topologies



	CS	CG	CD (SF)
	Voltage & current amplifier	Current buffer	Voltage buffer
Rin	∞	$R_S // \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$	∞
Rout	$R_D // r_o [1 + (g_m + g_{mb})R_S]$	$R_D // r_o$	$R_S // \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$
Gm	$\frac{-g_m}{1 + (g_m + g_{mb})R_S}$	$g_m + g_{mb}$	$\frac{g_m}{1 + R_D/r_o}$

Differential Amplifier

	Pseudo Diff Amp	Diff Pair (w/ ideal CS)	Diff Pair (w/ R_{SS})
A_{vd}	$-g_m R_D$	$-g_m R_D$	$-g_m R_D$
A_{vCM}	$-g_m R_D$	0	$\frac{-g_m R_D}{1 + 2(g_m + g_{mb})R_{SS}}$
A_{vd}/A_{vCM}	1	∞	$2(g_m + g_{mb})R_{SS} \gg 1$

What is an OTA / Op-Amp?

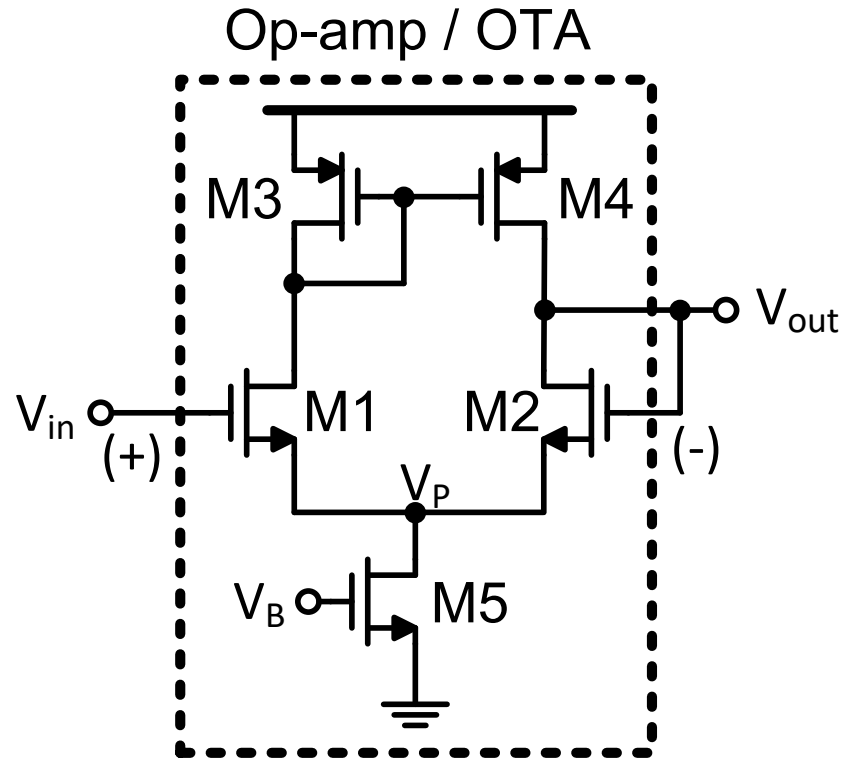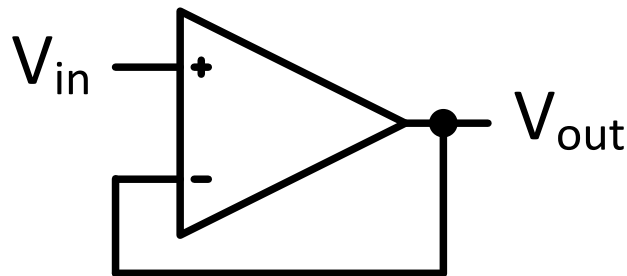- ❑ An op-amp is simply a high gain differential amplifier
- ❑ The gain can be increased by using cascodes and multi-stage amplifiers



Op-Amp vs OTA

- ❑ An OTA is an op-amp without an output stage (buffer)
- ❑ Some designers just use op-amp name and symbol for both


	Op-amp	OTA
Rout	LOW	HIGH
Model		
Diff input, SE output		
Fully diff		

OTA / Op-Amp

- ❑ Integral part of many analog and mixed-signal systems
 - DC bias generation
 - Amplification
 - Filtering
- ❑ Challenges
 - Supply voltage and channel length scaling
 - Energy efficiency


Finite Gain

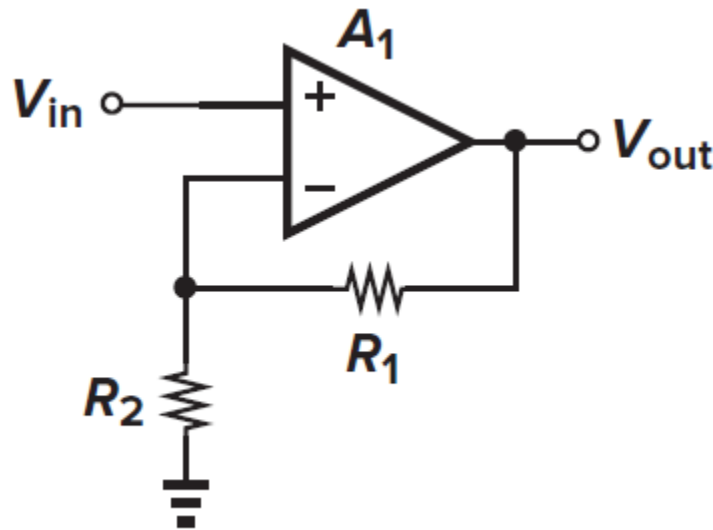- ❑ Gain determined by ratio of matched components
 - Very low sensitivity to PVT variations
- ❑ Example: $A_1 > 60$ dB for error $< 1\%$





$$\frac{V_{out}}{V_{in}} \approx \left(1 + \frac{R_1}{R_2}\right) \left(1 - \frac{R_1 + R_2}{R_2} \frac{1}{A_1}\right)$$

Finite Small-Signal Bandwidth

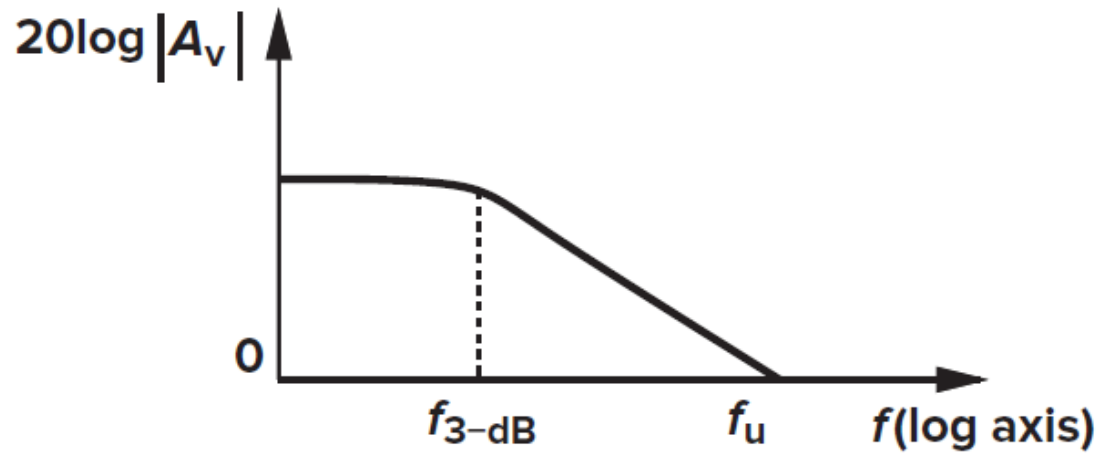
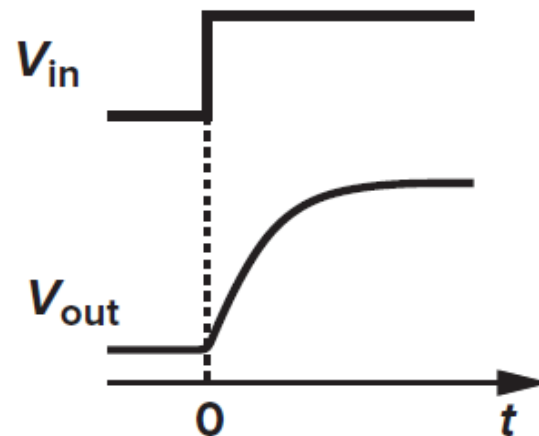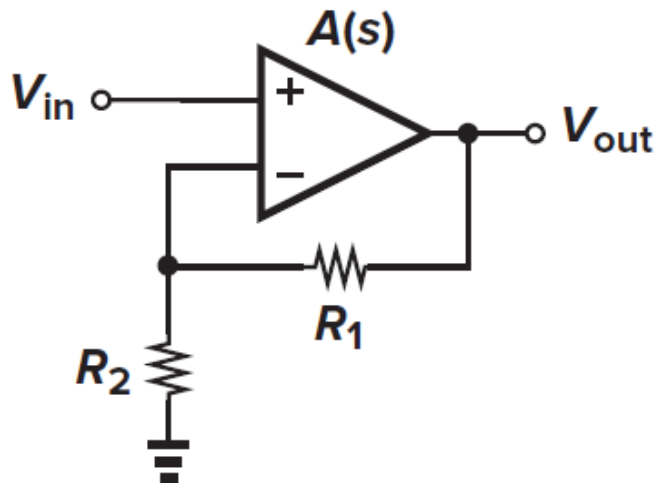
$$\tau \approx \left(1 + \frac{R_1}{R_2} \right) \frac{1}{A_0 \omega_0}$$





OTA Topologies

1. Simple single-stage OTA
2. Telescopic cascode OTA
3. Folded cascode OTA
4. Two-stage OTA
5. Gain boosted OTA

Simple Single-Stage OTAs

- Simple, but limited gain

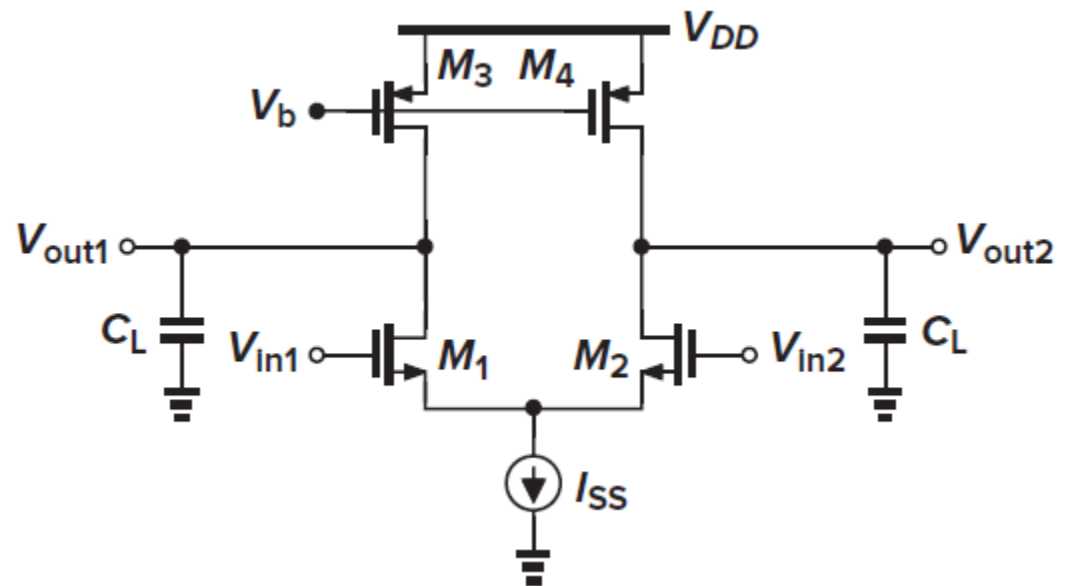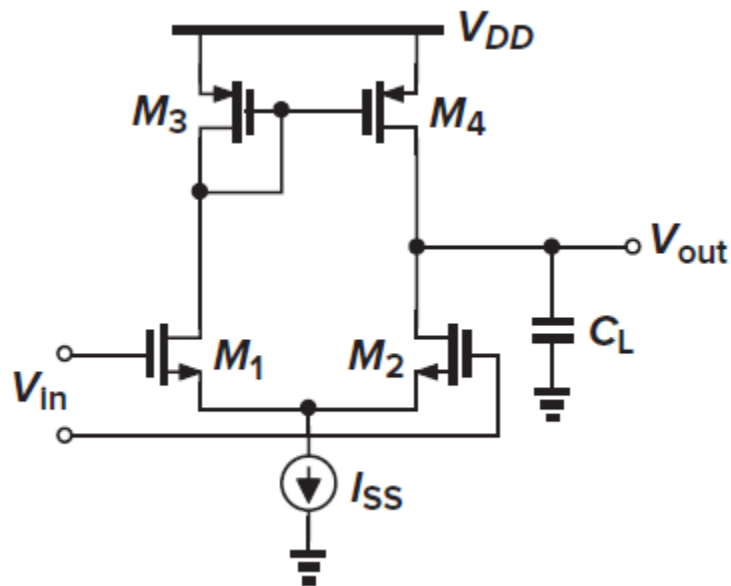

Simple Single-Stage OTA CMIR (OL)

□ $V_{in,CM}$ Range




□ V_{out} Range



□ $V_{in,CM,max}$ and $V_{out,min}$ are coupled


□ If max output swing is desired

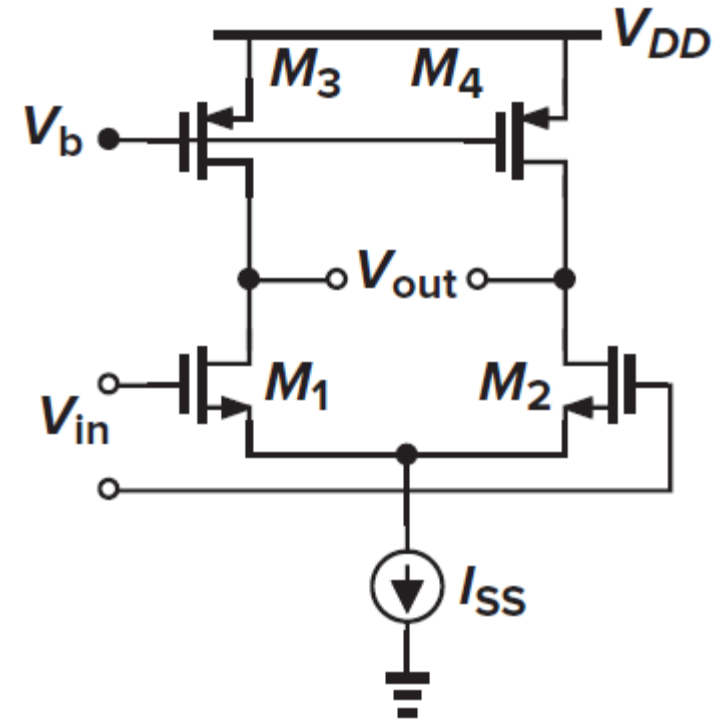- M1 at edge of sat
- No range for $V_{in,CM}$



Simple Single-Stage OTA Output Swing

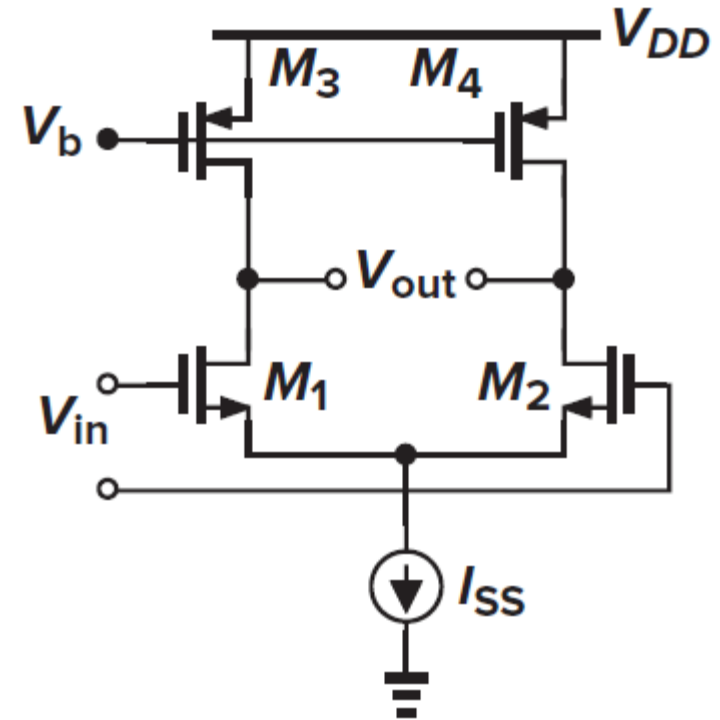□ *Max Diff Swing* $\approx 2(V_{DD} - 3V_{ov})$



5T OTA as a Buffer

- V_{in} Range (OL, without FB)




- V_{out} Range (OL, without FB)




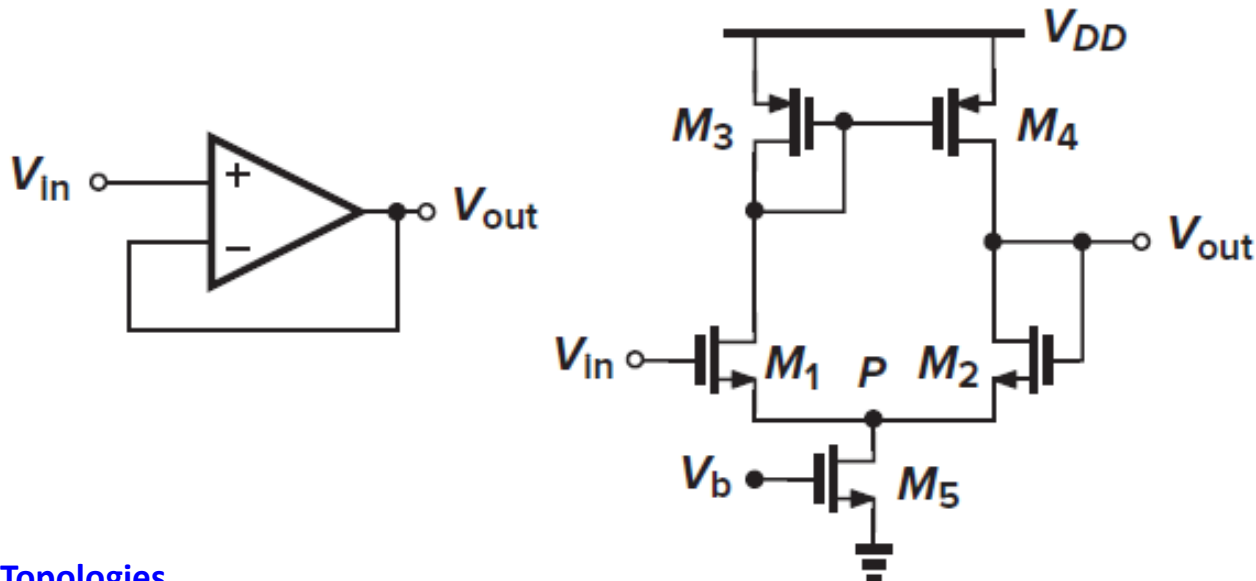
- Example: $V_{DD} = 1.2\text{ V}$, $V_{TH} = 0.3\text{ V}$, and $V_{ov} = 0.1\text{ V}$

- $V_{in} (V_{out}) = 0.5 - 1.1\text{ V} \rightarrow \text{Max swing} = 0.6\text{ V}$



Telescopic Cascode

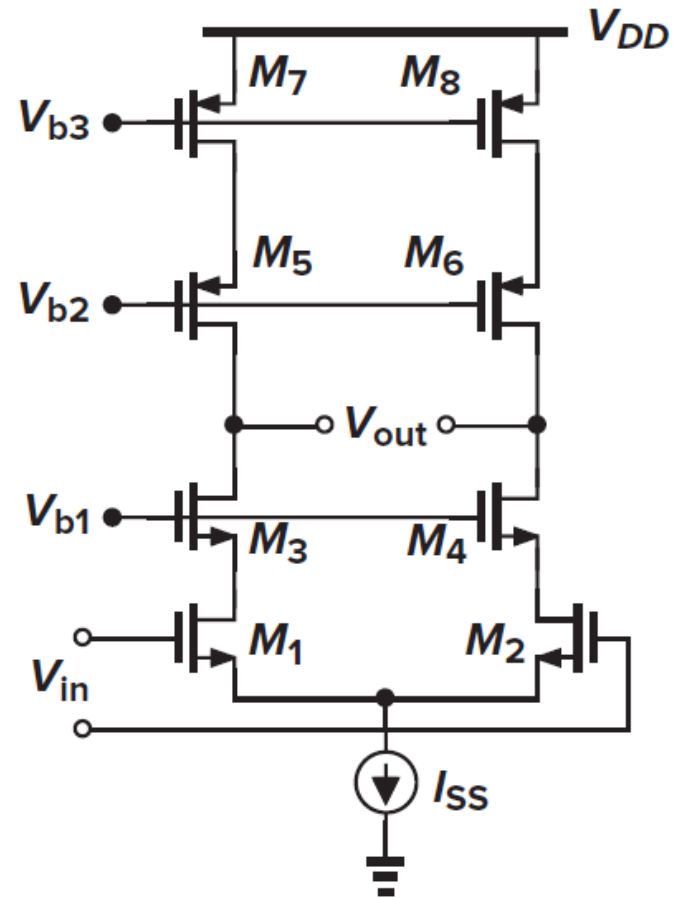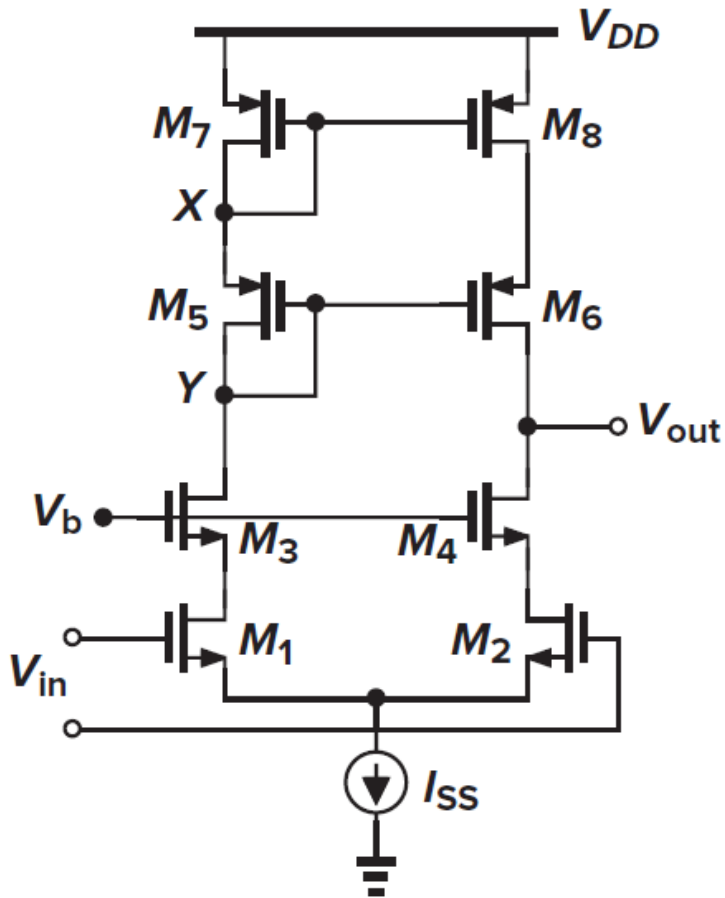- Higher DC gain, but limited swing and additional poles



Telescopic Cascode CMIR (OL)

□ $V_{in,CM}$ Range




□ V_{out} Range



□ $V_{in,CM,max}$ and $V_{out,min}$ are coupled


□ If max output swing is desired

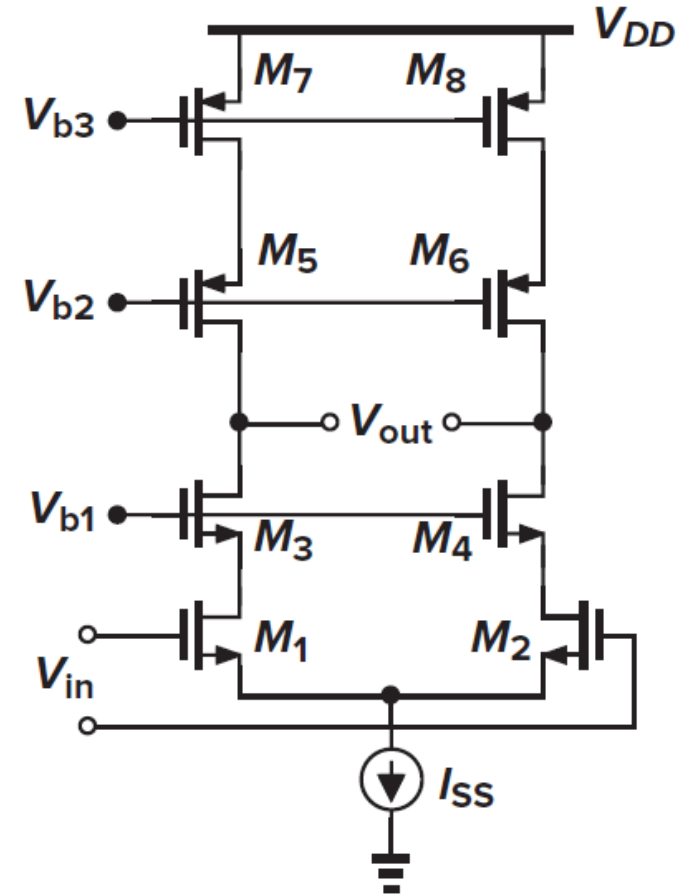- M1 at edge of sat
- No range for $V_{in,CM}$



Telescopic Cascode Output Swing (OL)

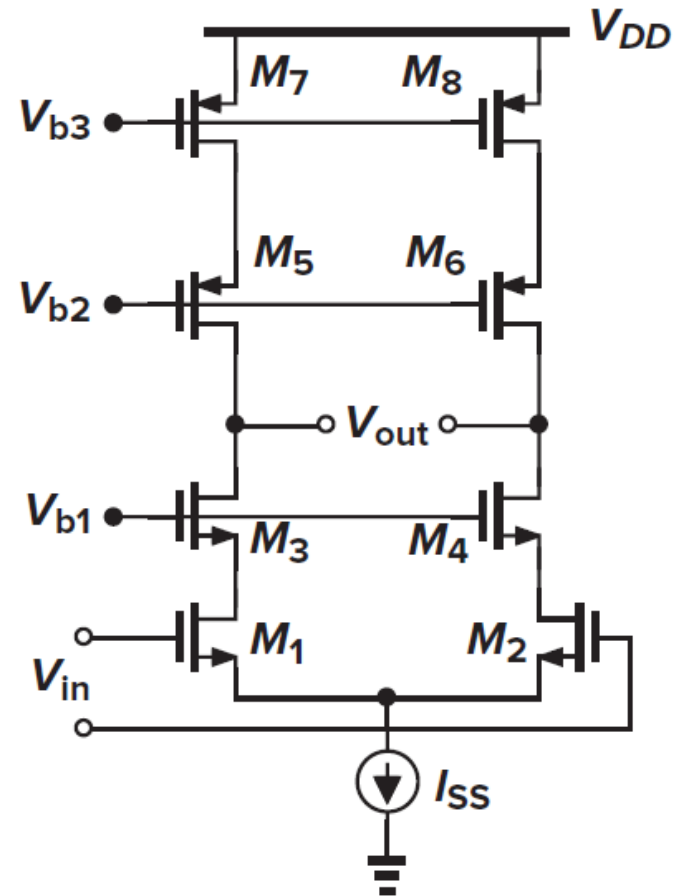- ❑ $Max\ Diff\ Swing \approx 2(V_{DD} - 5V_{ov})$
- ❑ The choice of bias voltages is critical to maintain output swing
- ❑ $V_{b1} \geq V_{THN} + V_{ov3} + V_{ov1} + V_{ISS}$
- ❑ $V_{b2} \leq V_{DD} - V_{THP} - V_{ov5} - V_{ov7}$
- ❑ Place M1 and M7 just at the edge of sat for max output swing



Telescopic Cascode as a Buffer

□ V_{in} Range (OL, without FB)




□ V_{out} Range (OL, without FB)





□ $Max\ Swing = V_{THN} - V_{ov3}$



□ Example: $V_{DD} = 1.2\text{ V}$, $V_{TH} = 0.3\text{ V}$,
and $V_{ov} = 0.1\text{ V}$

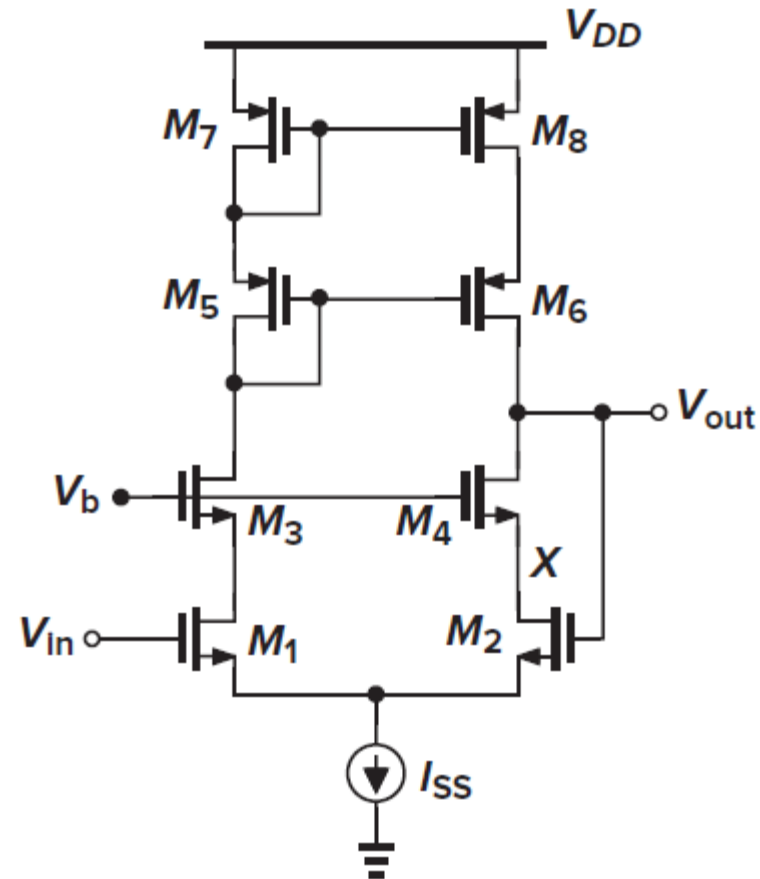- $V_{in} (V_{out}) = (V_b - 0.3) - (V_b - 0.1)\text{ V}$
- Max swing = 0.2 V
- **Independent of V_{DD} !**





Telescopic Cascode CM Range (CL)

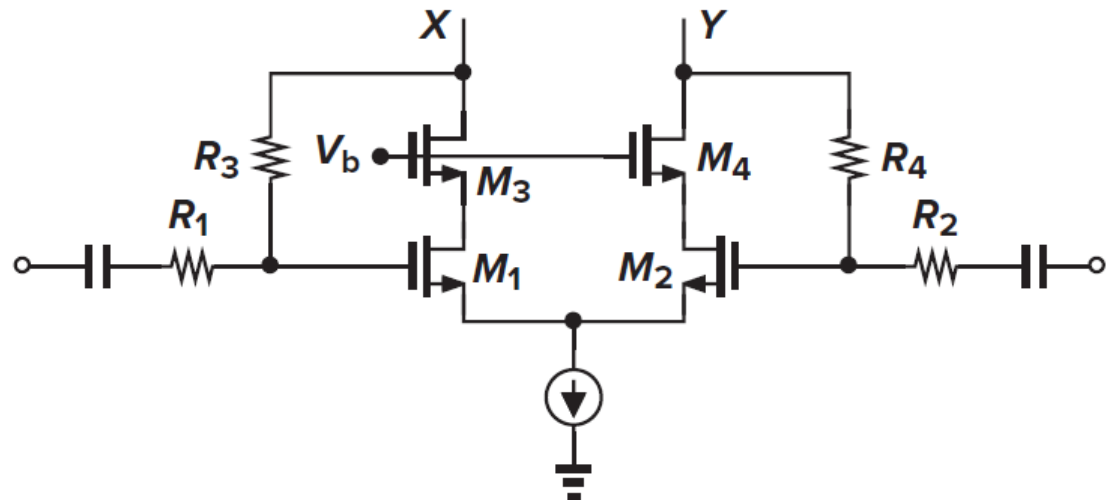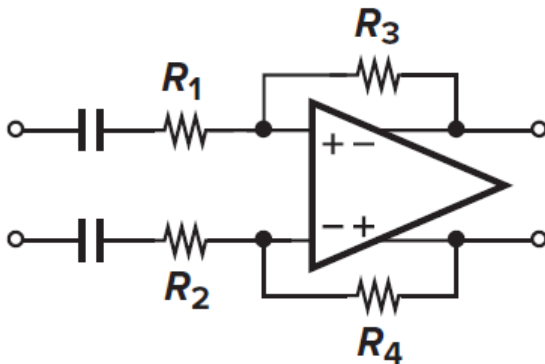- ❑ Input and output CM levels are equal (why?) → similar to buffer
- ❑ $V_{in,CM}$ Range 
- ❑ $V_{out,CM}$ Range 
- ❑ $Max\ CM\ Range = V_{THN} - V_{ov3}$
- ❑ Example: $VDD = 1.2\ V$, $V_{TH} = 0.3\ V$, and $V_{ov} = 0.1\ V$
 - $V_{CM} = (V_b - 0.3) - (V_b - 0.1)\ V \rightarrow$ Max CM range = $0.2\ V$




Telescopic Cascode Output Swing (CL)

- ❑ Assume swing at input is negligible (high open-loop gain)
 - We care more about keeping M3 and M4 in sat
 - $V_{out,min} \geq V_b - V_{THN}$
 - We can place M1 and M2 at the edge
 - Set CM level at its max value: $V_{CM} = V_b - V_{ov3}$
- ❑ $Max\ Diff\ Swing = 2 \times 2 \times (V_{THN} - V_{ov3})$
- ❑ Ex: $V_{TH} = 0.3\text{ V}$ and $V_{ov} = 0.1\text{ V}$ → Max swing = $2 \times 2 \times 0.2\text{ V} = 0.8\text{ V}$

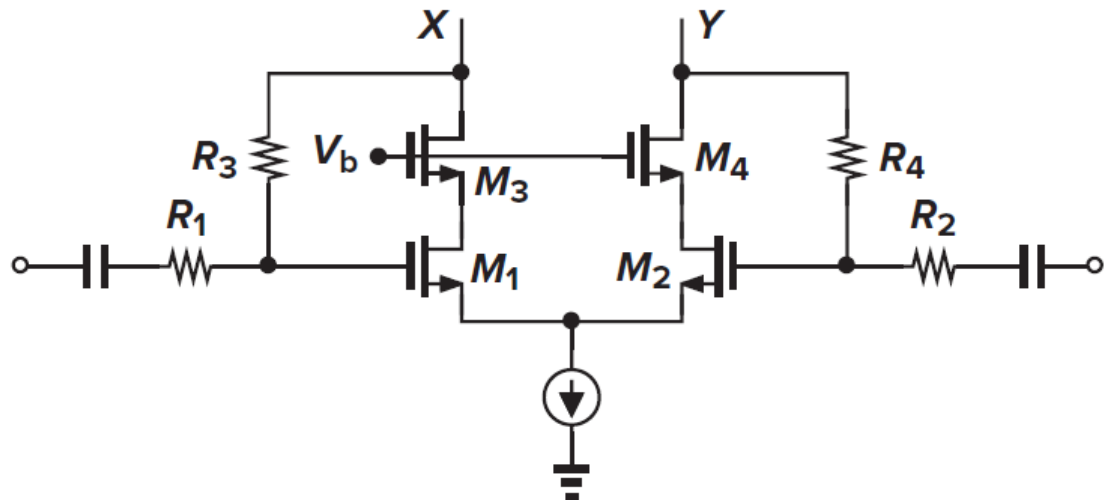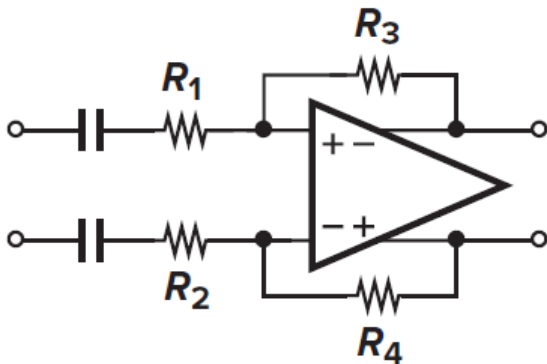


Telescopic Cascode with SE Output

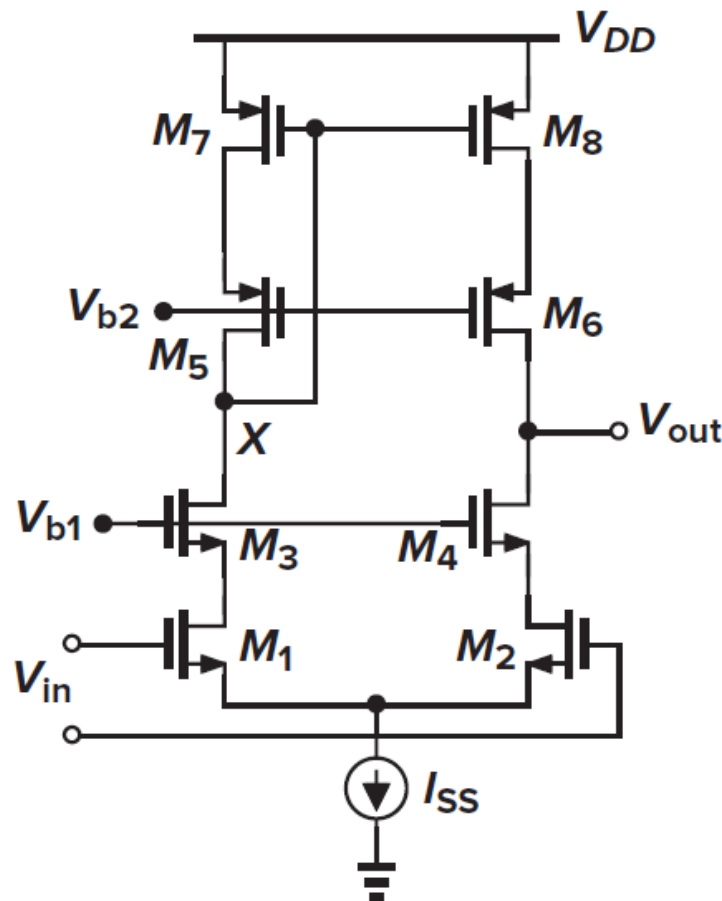- ❑ Low compliance (wide swing) current mirror load
- ❑ Note that for buffer connection, the swing is limited by M_2 and M_4





Folded Cascode

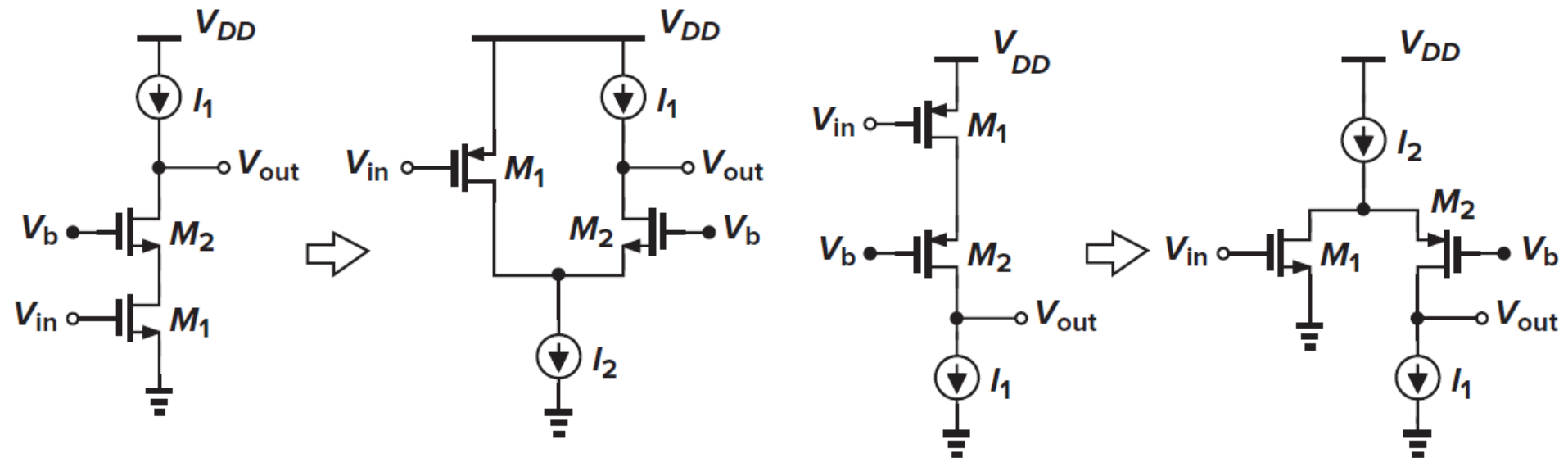


Telescopic vs Folded Cascode

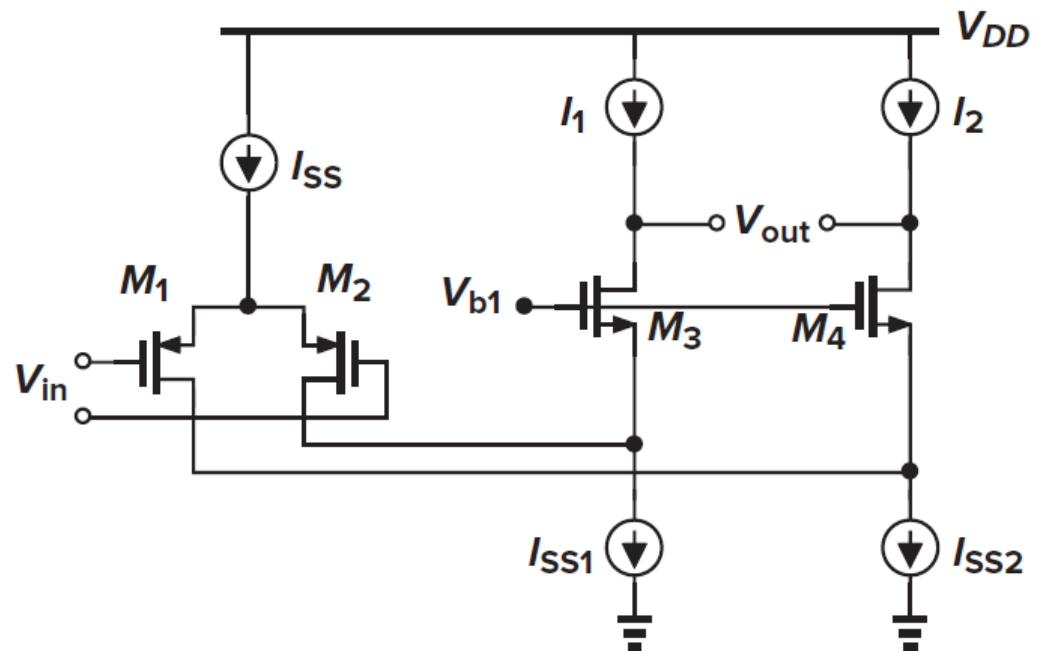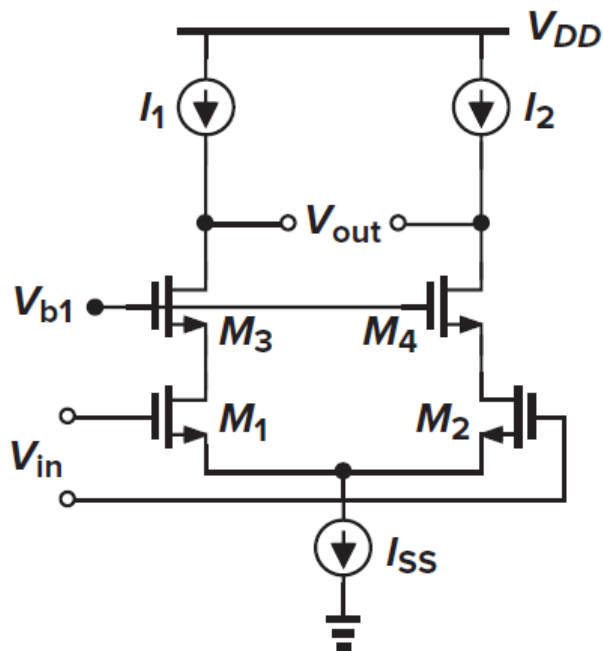- ❑ Higher power consumption: $I_{SS1,2} = \frac{I_{SS}}{2} + I_{1,2}$
 - M3,4 must remain ON when I_{SS} is fully steered on one side
 - $I_{SS1,2} > I_{SS} \rightarrow I_{1,2} > \frac{I_{SS}}{2}$
 - Ex: $I_{SS1,2} = 1.2I_{SS} \rightarrow I_{1,2} = 0.7I_{SS} \rightarrow \text{Total current} = 2.4I_{SS}$





Telescopic vs Folded Cascode

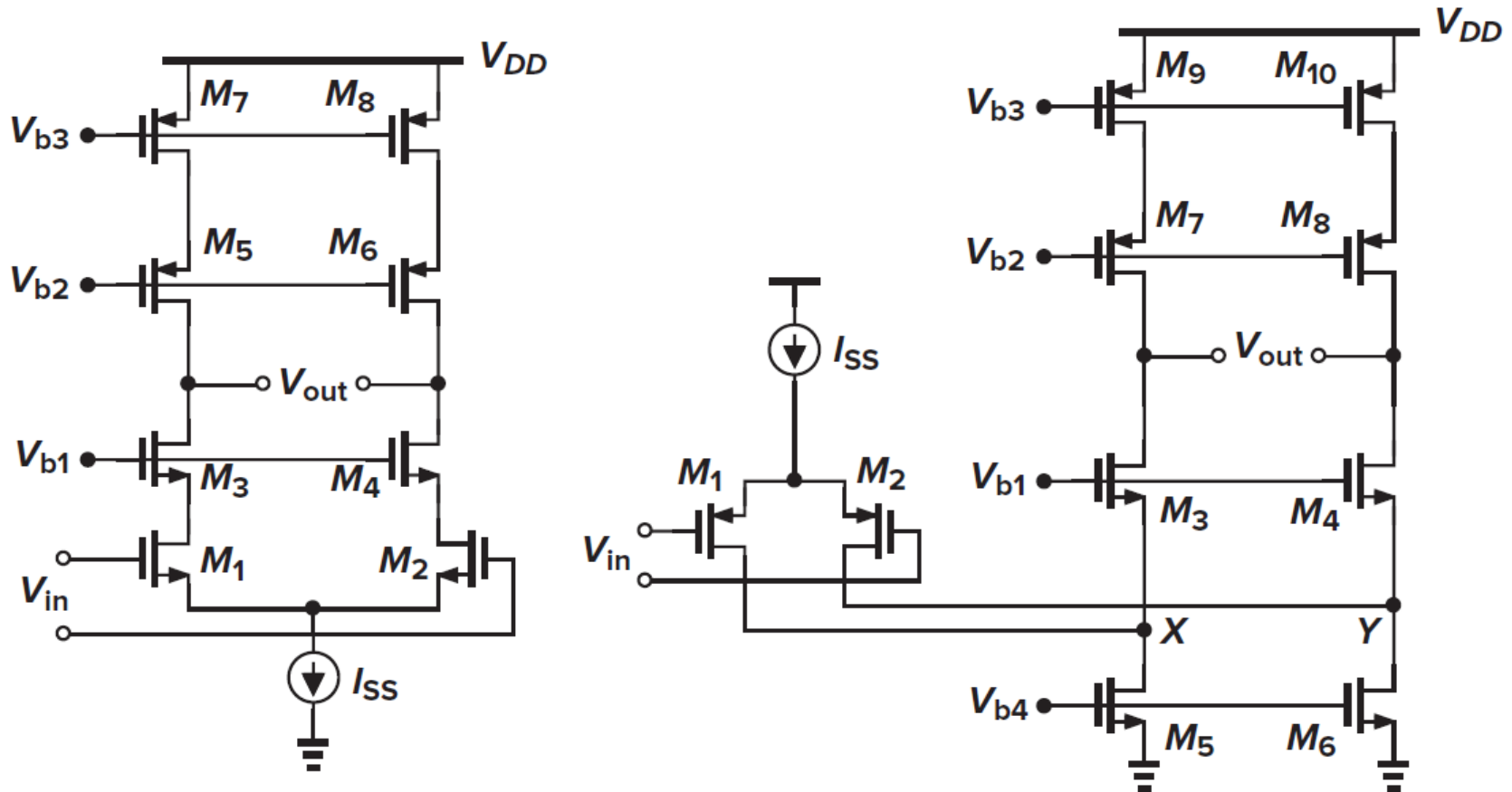- Gain lower than telescopic cascode ($r_{o1} // r_{o5}$)
 - Around two times less



Telescopic vs Folded Cascode

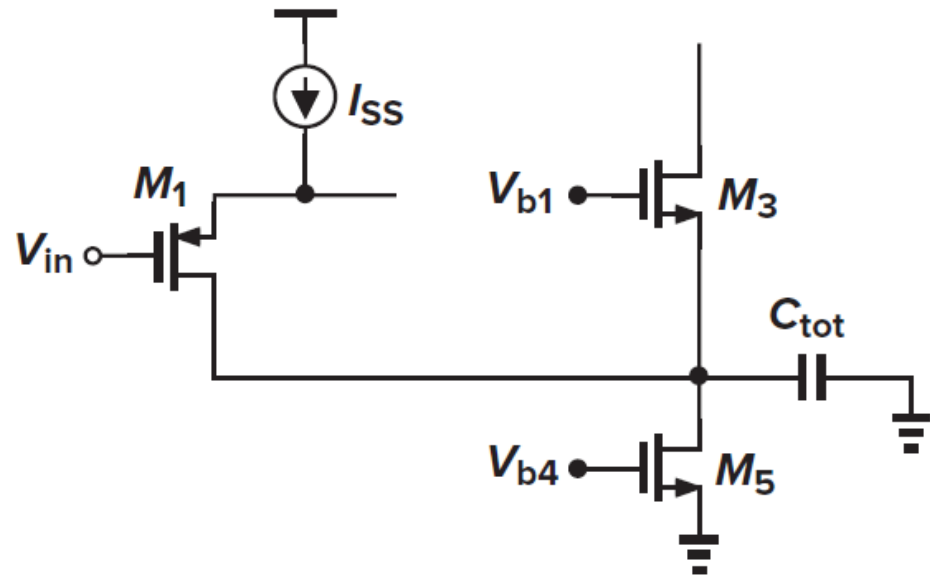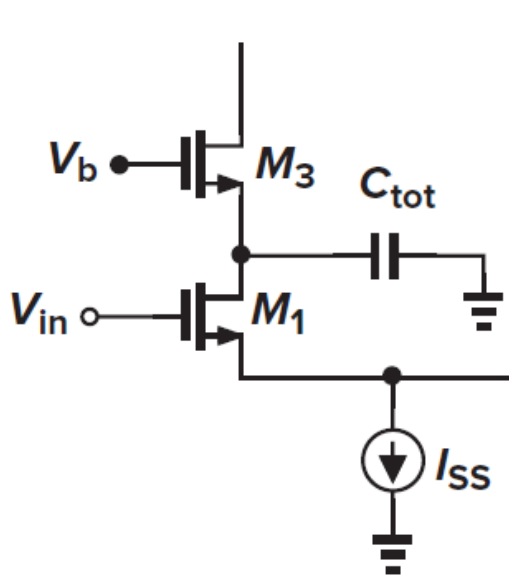- ❑ Non-dominant pole (at folding point) has higher capacitance
- ❑ Telescopic: $C_{tot} = C_{db1} + f(C_{gd1}) + C_{gs3} + C_{sb3}$
- ❑ Folded: $C_{tot} = C_{db1} + f(C_{gd1}) + C_{gs3} + C_{sb3} + C_{db5} + C_{gd5}$
- ❑ Note that M5 is large as it carries large current (large parasitics)



Folded Cascode CMIR (OL)

- $V_{in,CM}$ Range




- ### □ V_{out} Range





- ❑ $V_{in,CM}$ and V_{out} are NOT coupled

- Main advantage over telescopic**

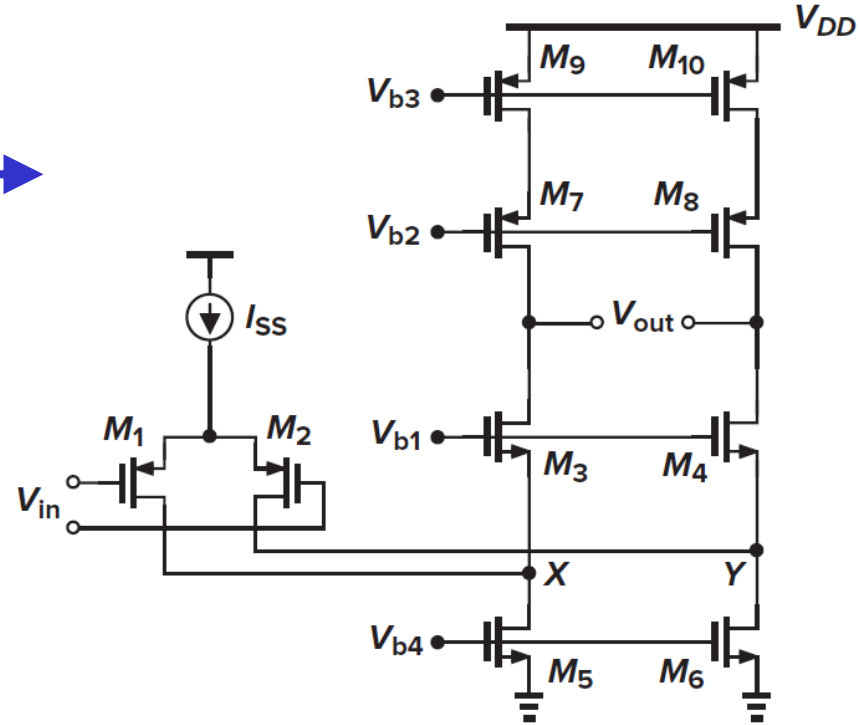- ❑ Example: $V_{DD} = 1.2 \text{ V}$,
 $V_{TH} = 0.3 \text{ V}$, and $V_{ov} = 0.1 \text{ V}$
 - $V_{CM} = -0.2 \text{ V} - 0.7 \text{ V}$
 - Max CM range = 0.9 V




Folded Cascode with Rail-to-Rail CMIR

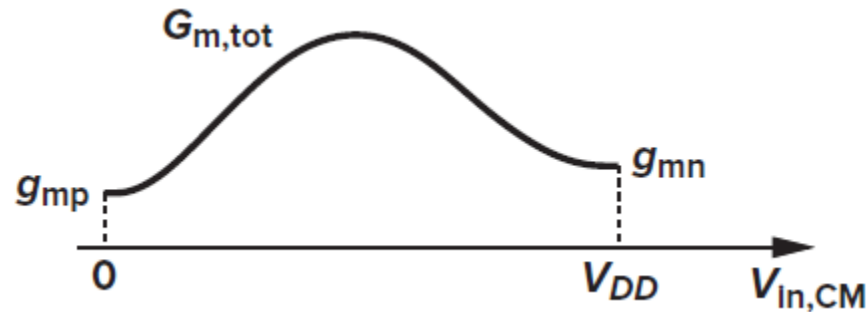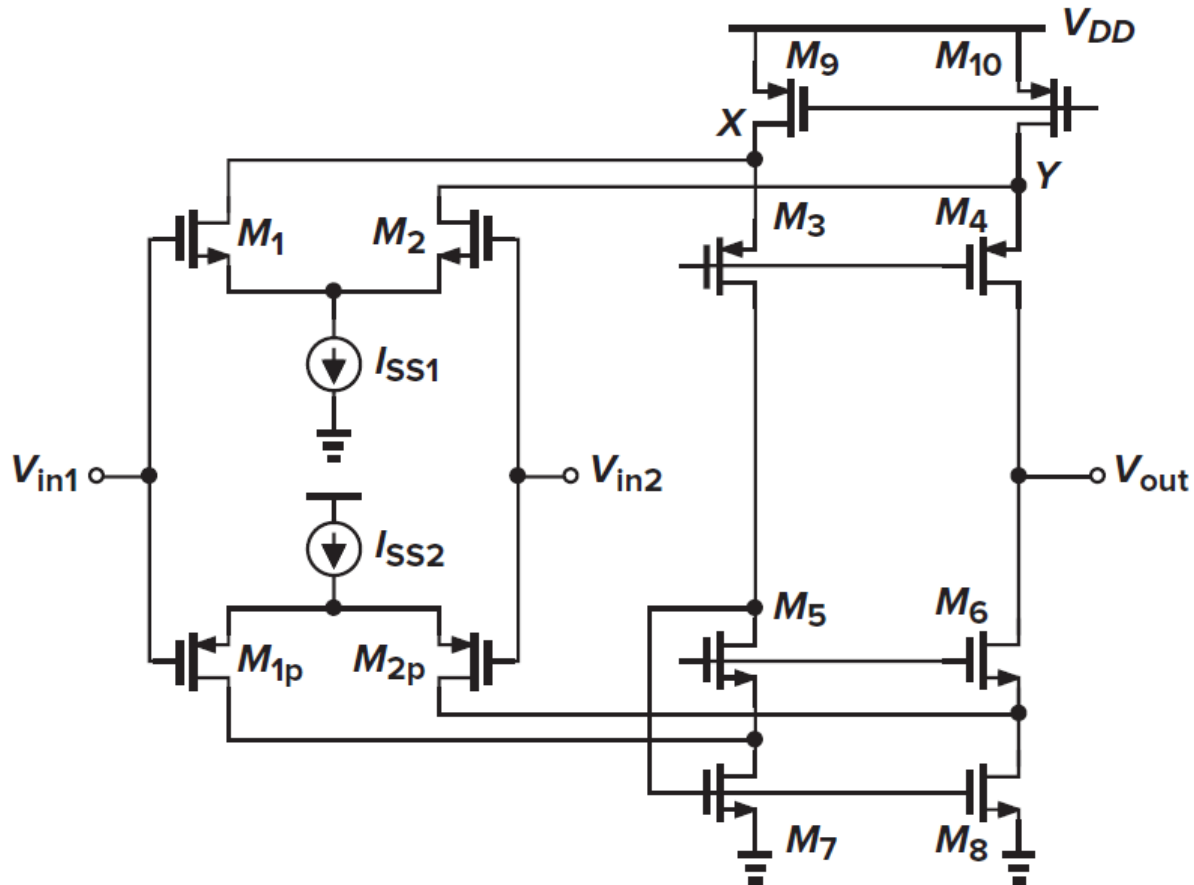


Folded Cascode Output Swing (OL)

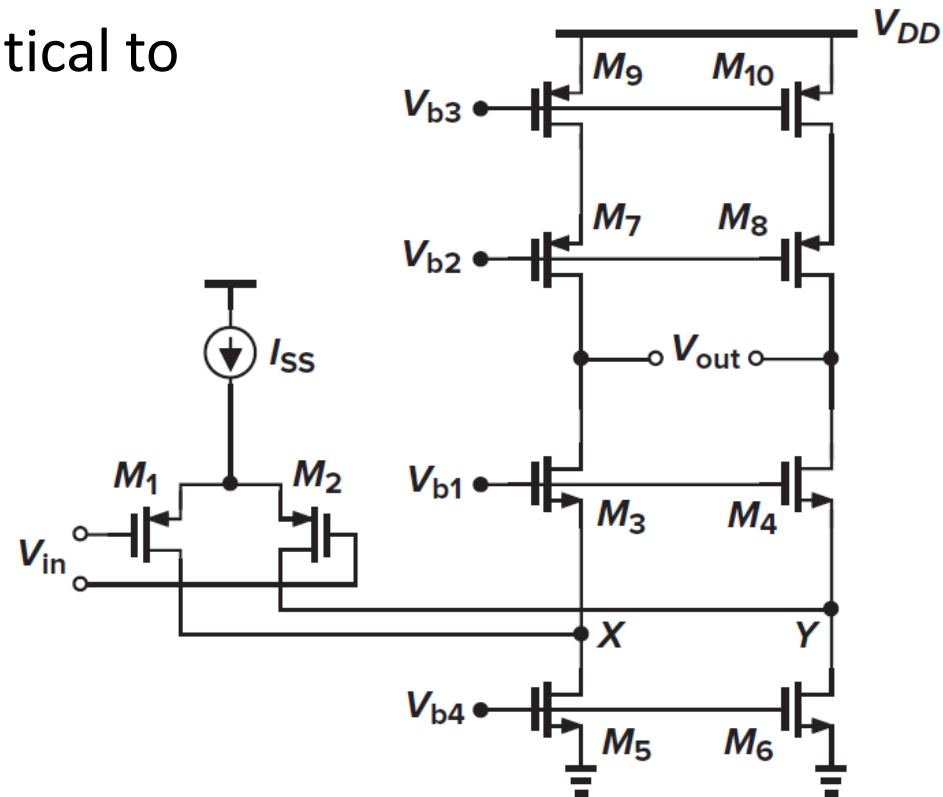- ❑ *Max Diff Swing* $\approx 2(V_{DD} - 4V_{ov})$
- ❑ Slightly better than telescopic cascode
- ❑ The choice of bias voltages is critical to maintain output swing



Folded Cascode

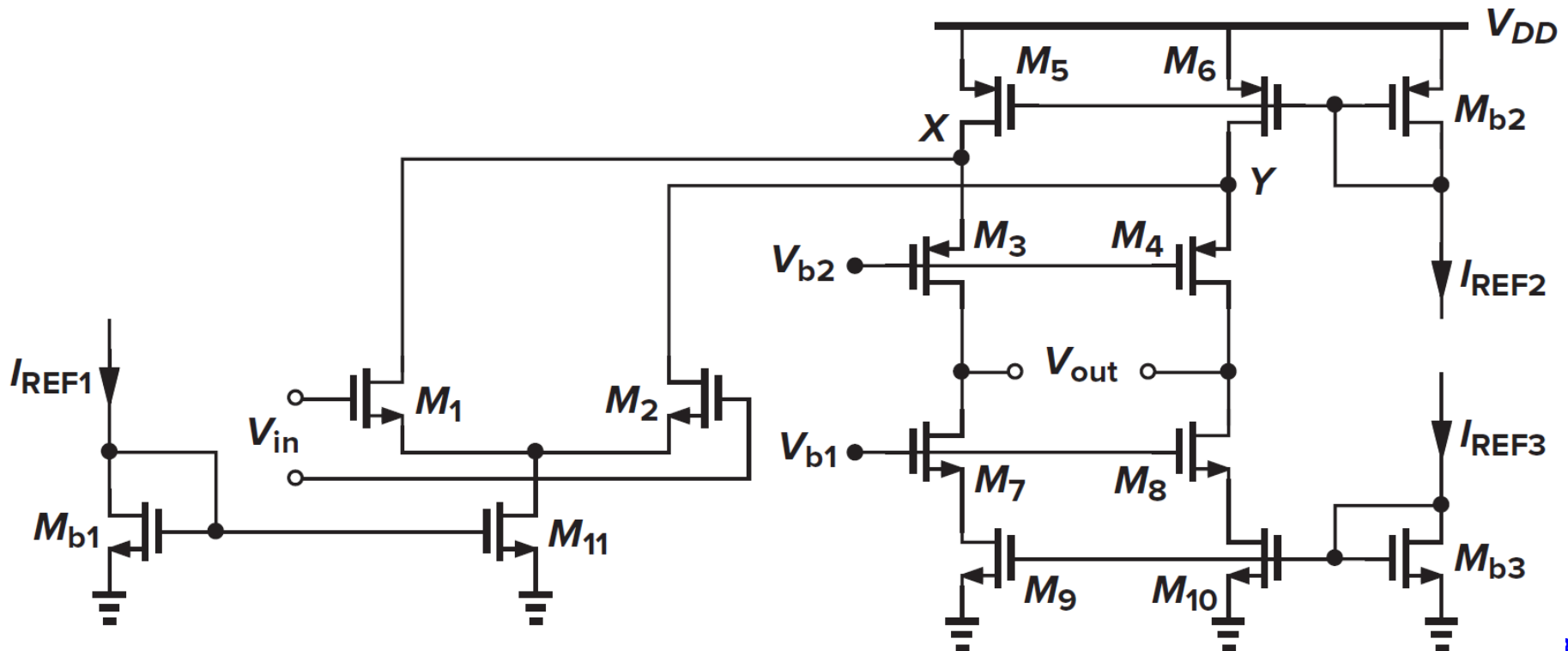- ❑ NMOS i/p stage has higher g_m for same dimensions
 - Or lower parasitics for same g_m
- ❑ But the non-dominant pole at folding point is worse
- ❑ Also body effect and flicker noise may favor PMOS i/p pair



Folded Cascode as a Buffer

□ V_{in} Range (OL, without FB)




□ V_{out} Range (OL, without FB)



□ $Max\ Swing = V_{DD} - V_{THN} - 4V_{ov}$

□ Example: $V_{DD} = 1.2\text{ V}$, $V_{TH} = 0.3\text{ V}$, and $V_{ov} = 0.1\text{ V}$

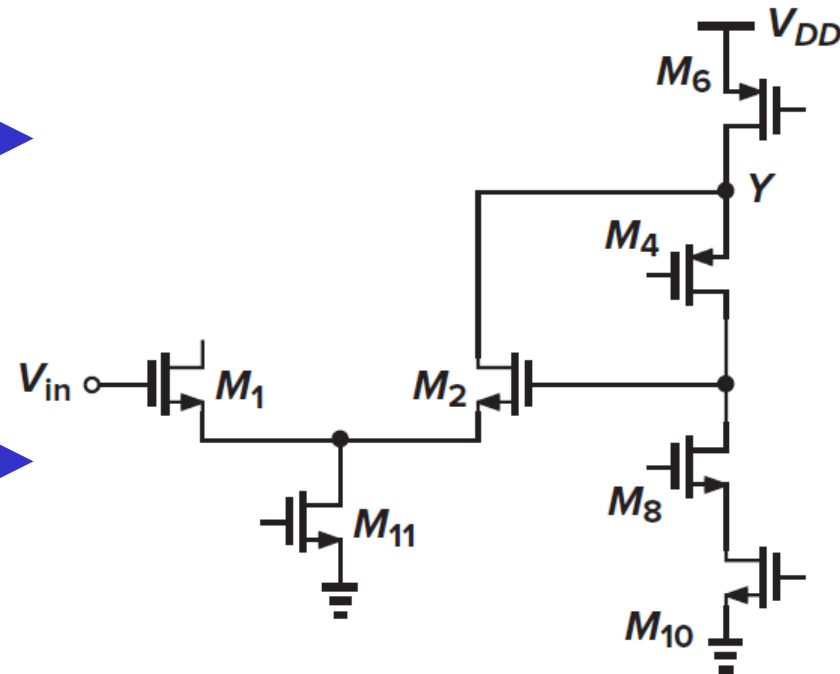
- Max swing = 0.5 V
- **Function of VDD**



Folded Cascode CM Range (CL)

❑ Input and output CM levels are equal (why?) → similar to buffer



❑ $V_{in,CM}$ Range 

❑ $V_{out,CM}$ Range 

❑ $Max\ CM\ Range = V_{DD} - V_{THN} - 4V_{ov}$



❑ Example: $V_{DD} = 1.2\ V$, $V_{TH} = 0.3\ V$, and $V_{ov} = 0.1\ V$

- Max CM range = 0.5 V

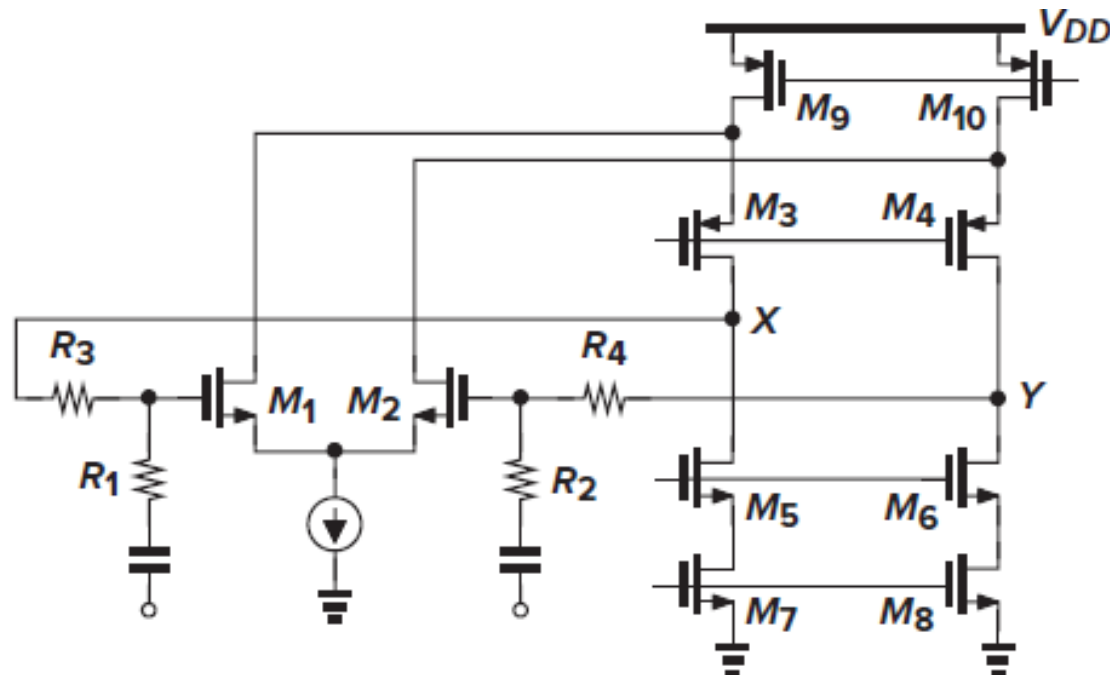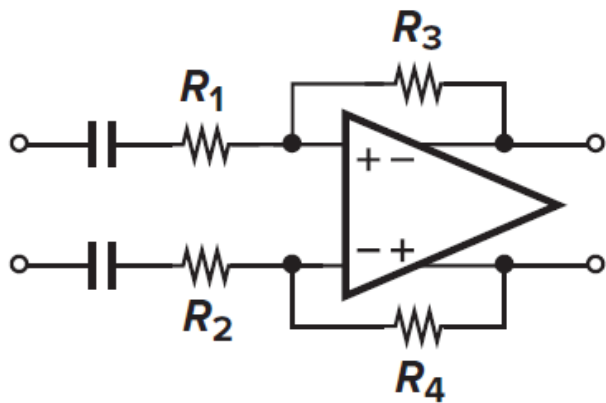


Folded Cascode Output Swing (CL)

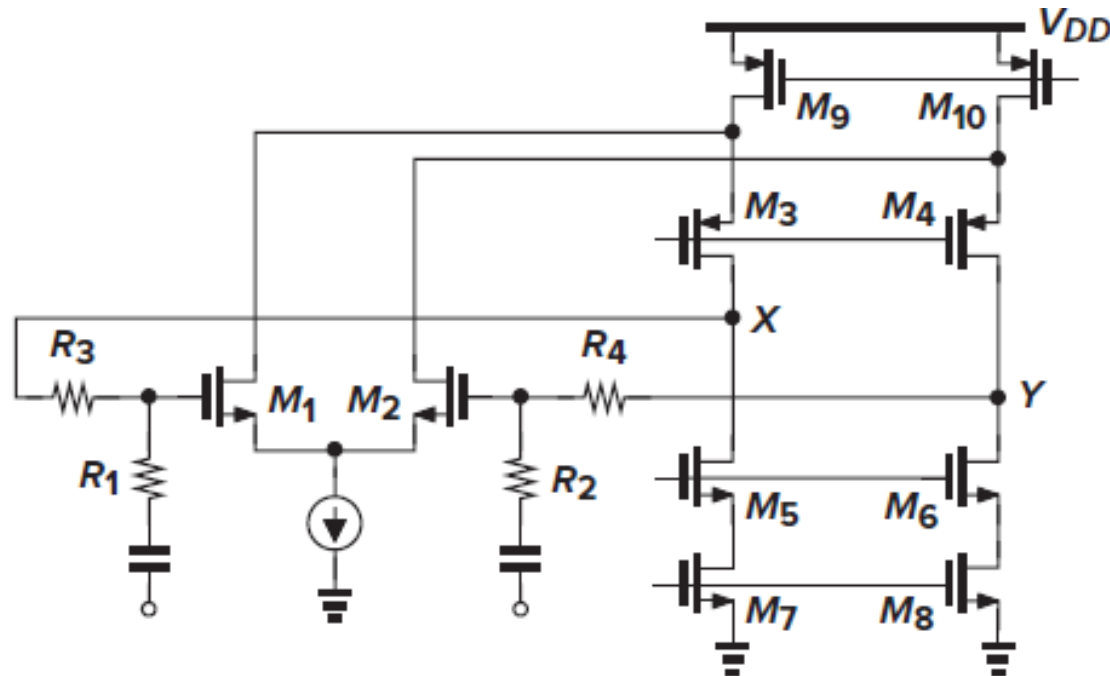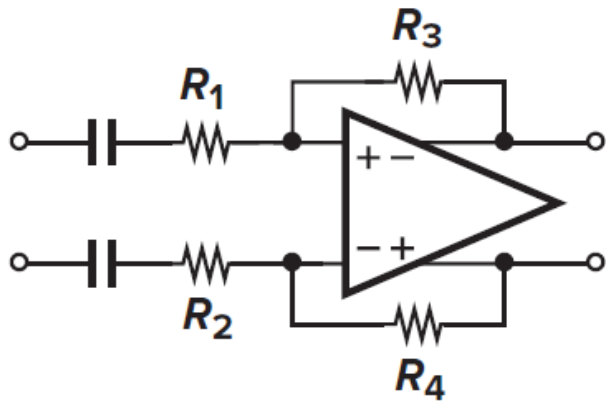- ❑ Assume swing at input is negligible (high open-loop gain)
- ❑ $V_{in,CM}$ and V_{out} are NOT coupled
- ❑ $Max\ Diff\ Swing \approx 2(V_{DD} - 4V_{ov})$
- ❑ Example: $V_{DD} = 1.2\text{ V}$, $V_{TH} = 0.3\text{ V}$, and $V_{ov} = 0.1\text{ V}$
 - Max diff swing = 1.6 V




Two-Stage OTA

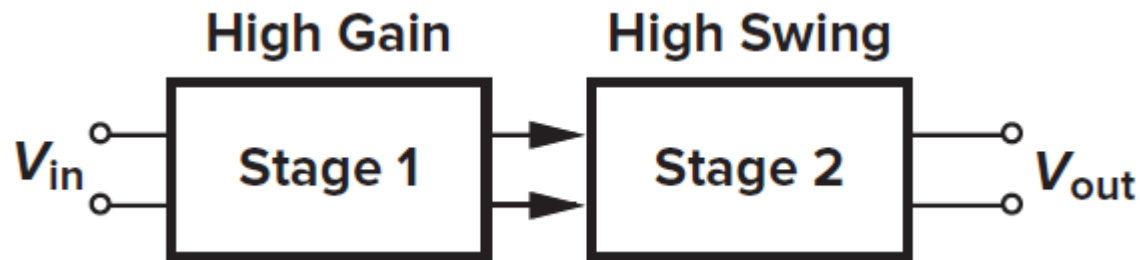- ❑ Isolates the gain and swing requirements
- ❑ But more power consumption
- ❑ And complicates stability requirements
 - More than two stages exist, but quite difficult to stabilize
- ❑ Second stage is typically configured as a simple common-source stage so as to allow maximum output swings




Two-Stage OTA

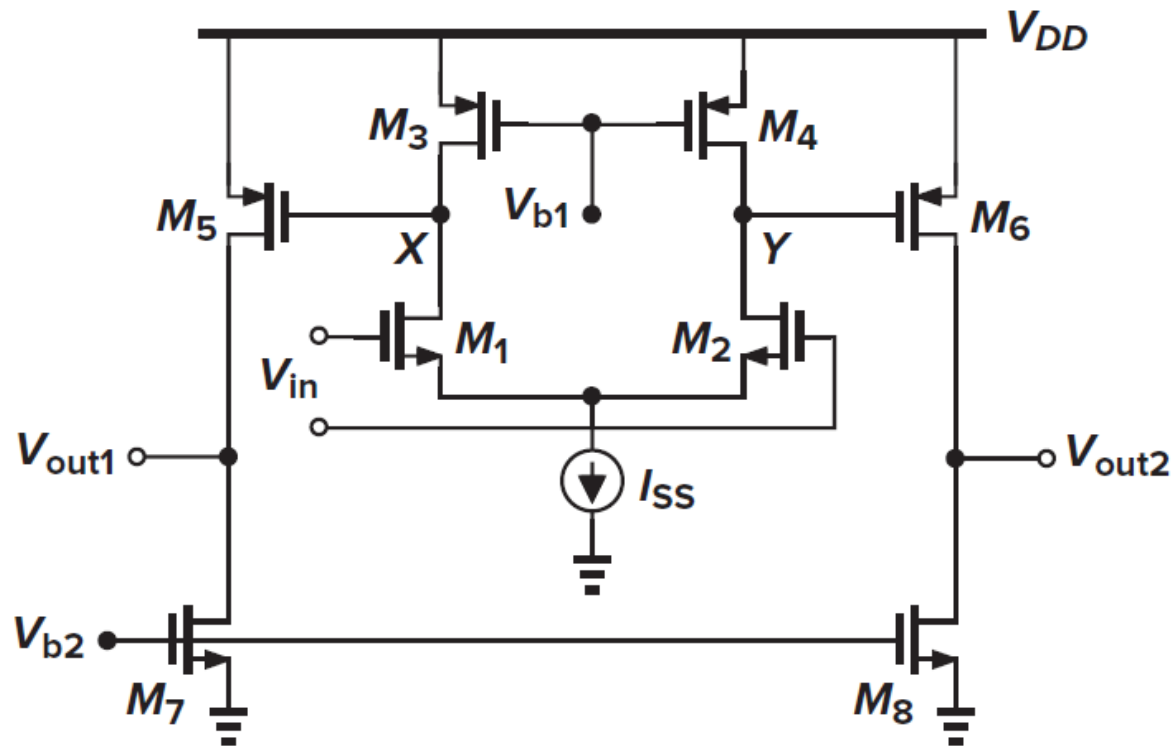□ *Max Diff Swing* $\approx 2(V_{DD} - 2V_{ov})$




Two-Stage OTA

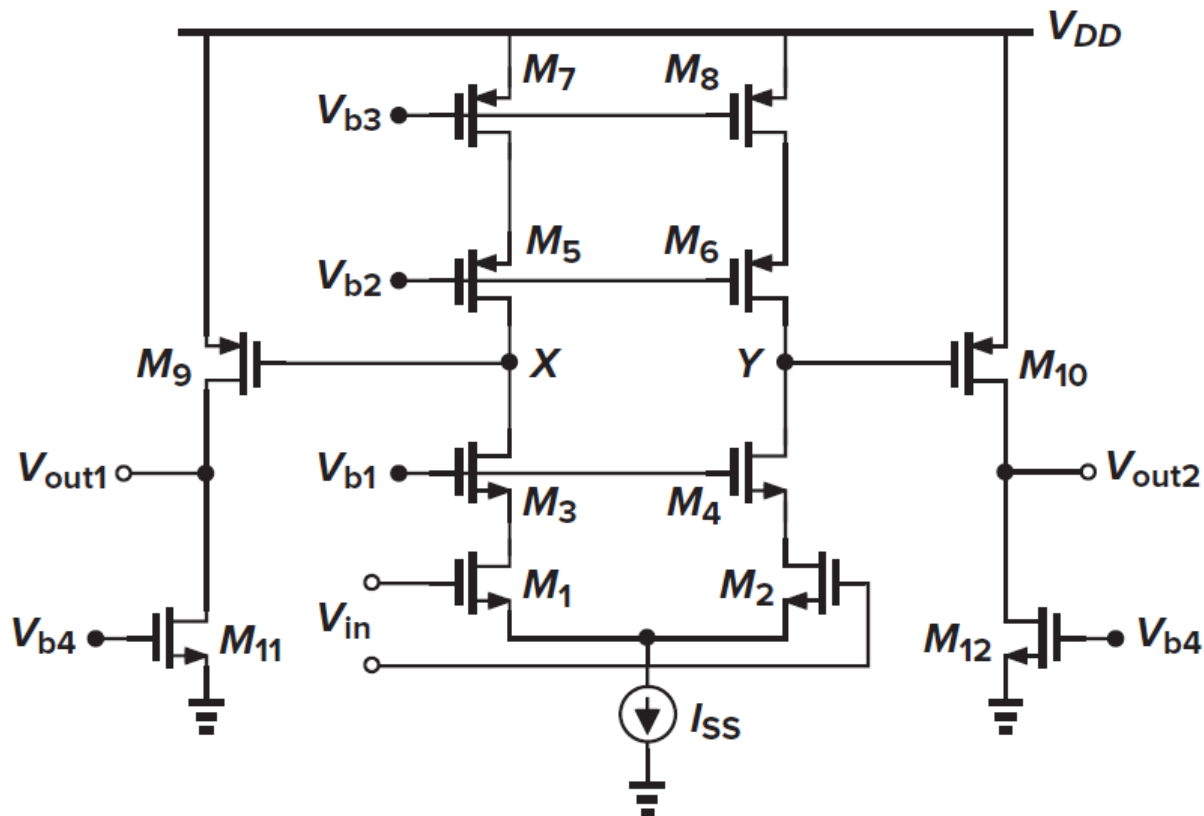
- ❑ *Max Diff Swing* $\approx 2(V_{DD} - 2V_{ov})$
- ❑ Voltage swing at X and Y is negligible



Two-Stage OTA with SE Output

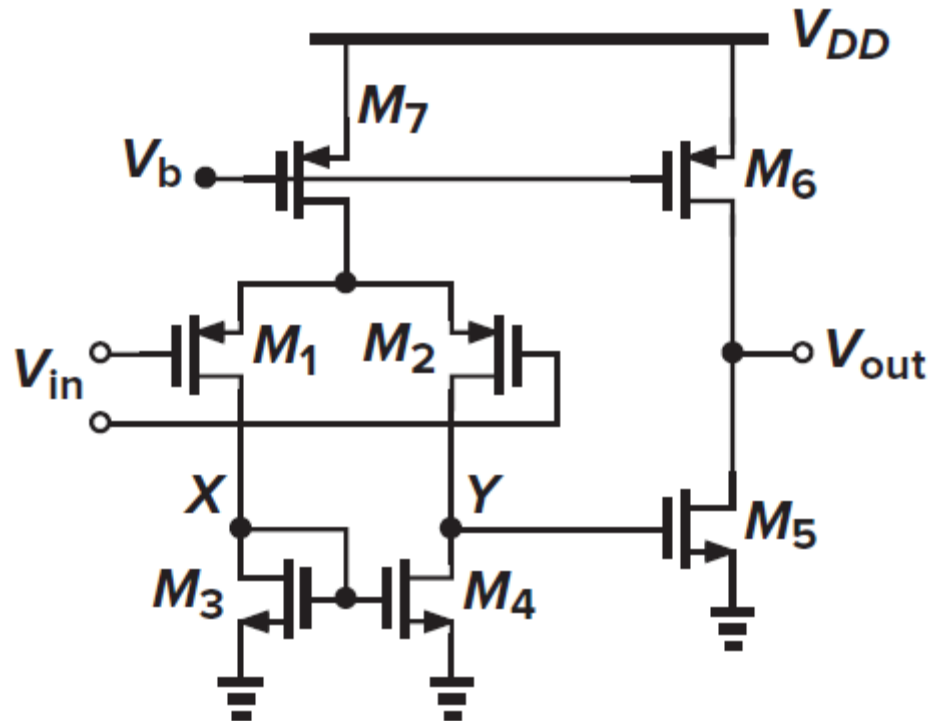


Two-Stage OTA with SE Output

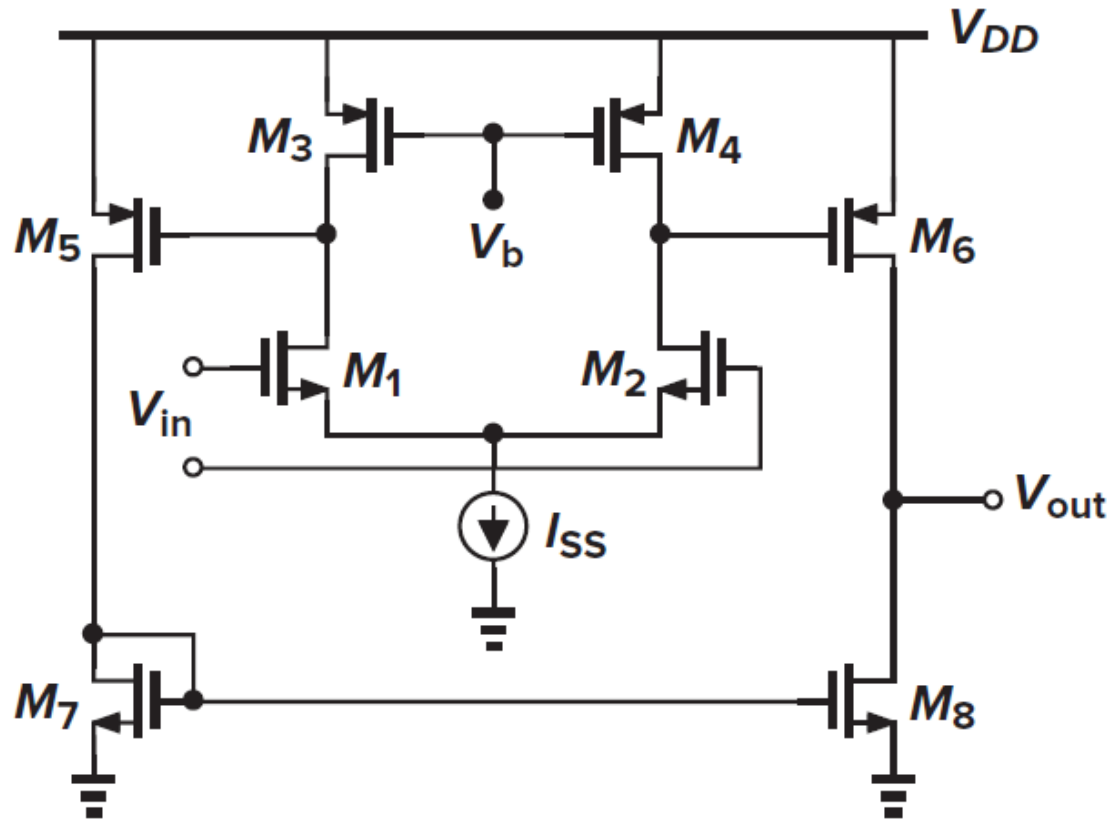

Gain Boosting: Super Transistor Perspective


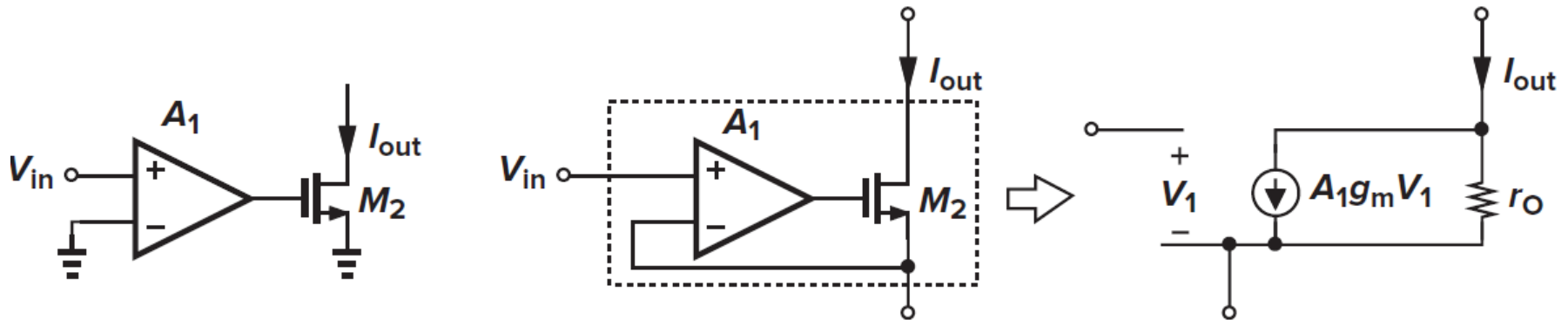
- ❑ Assume $A_1 \gg 1$
- ❑ $g_{m,super} = A_1 g_m$
- ❑ $r_{o,super} = r_o$



Gain Boosting: Super Transistor Perspective



$$\square \quad G_m \approx \frac{g_{m,\text{super}}}{1 + g_{m,\text{super}}R_S} \approx \frac{A_1 g_m}{1 + A_1 g_m R_S} \approx \frac{1}{R_S}$$
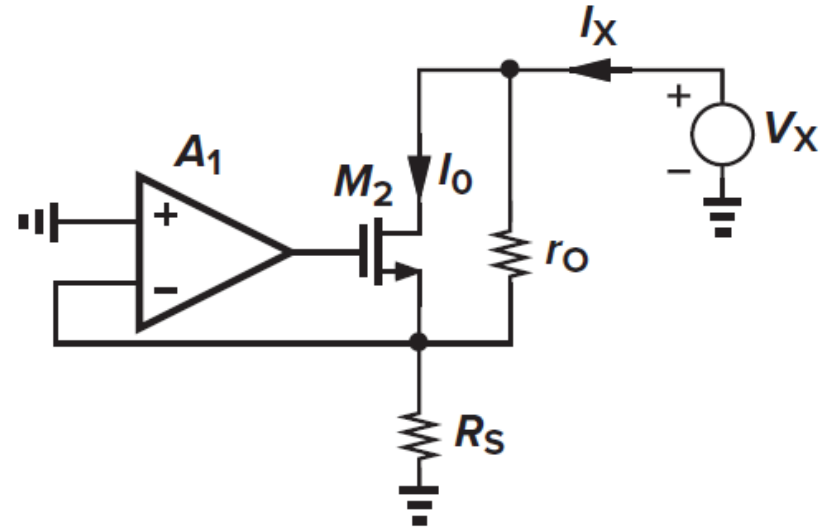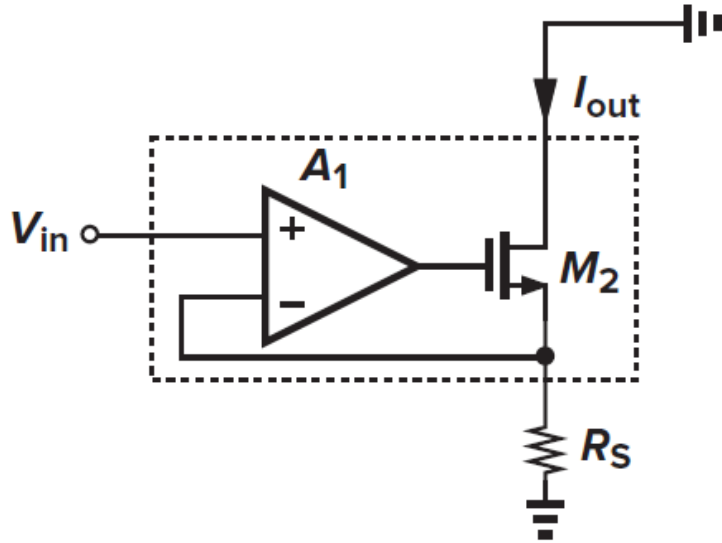
$$\square \quad R_{\text{out}} = r_o(1 + g_{m,\text{super}}R_S) = r_o(1 + A_1 g_m R_S)$$




Gain Boosting: Super Transistor Perspective
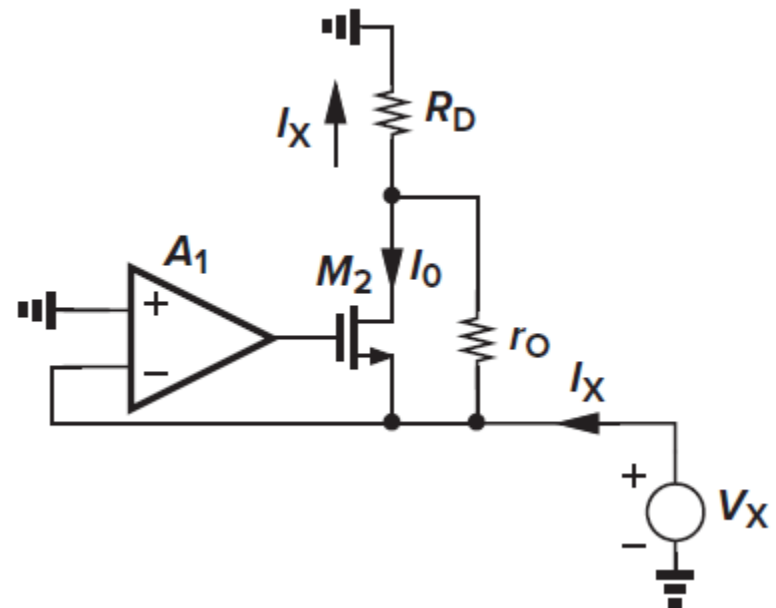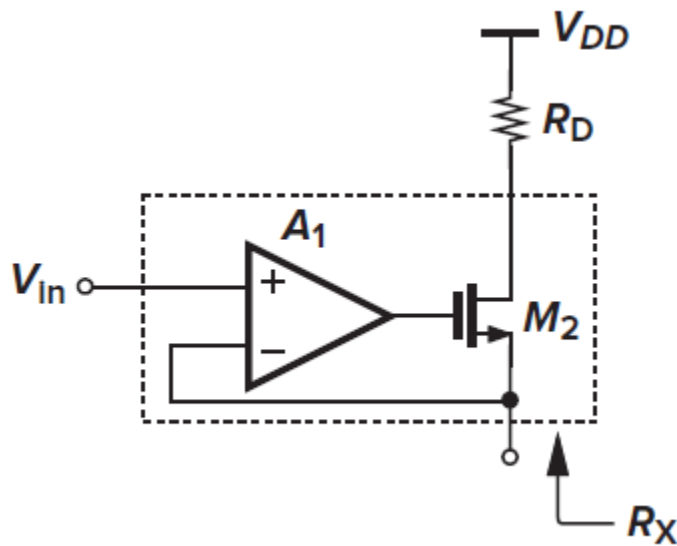
$$\square R_X \approx \frac{1}{g_{m,super}} \left(1 + \frac{R_D}{r_o} \right) \approx \frac{1}{A_1 g_m} \left(1 + \frac{R_D}{r_o} \right)$$




Gain Boosted (Regulated) Cascode

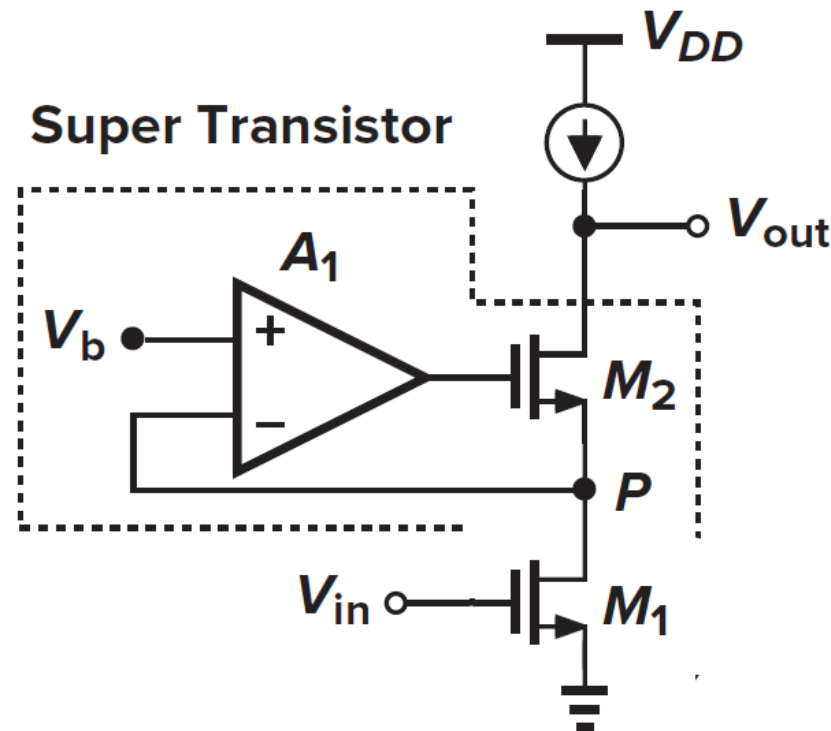- ❑ $G_m \approx g_{m1}$
- ❑ $R_{out} = r_{o2}(1 + g_{m2,super}r_{o1}) = r_{o2}(1 + A_1 g_{m2}r_{o1})$
- ❑ $A_v \approx A_1(g_{m1}r_{o1})(g_{m2}r_{o2})$
- ❑ Gain is boosted while preserving headroom




Gain Boosting Implementation

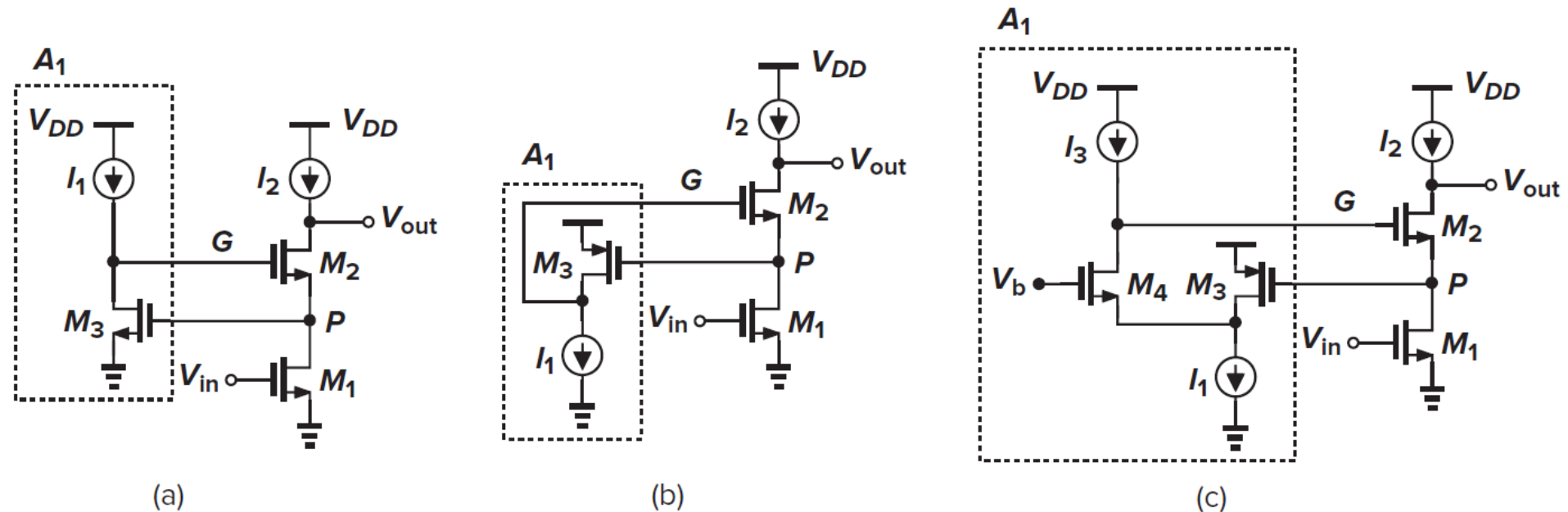- ❑ NMOS CS (a): headroom limitation
 - $V_P = V_{TH} + V_{ov3}$ instead of V_{ov1}
- ❑ PMOS CS (b): M3 will be in triode
 - $V_G - V_P > V_{TH}$
- ❑ Folded cascode (c): M4 provide level shift




Gain Boosted OTA

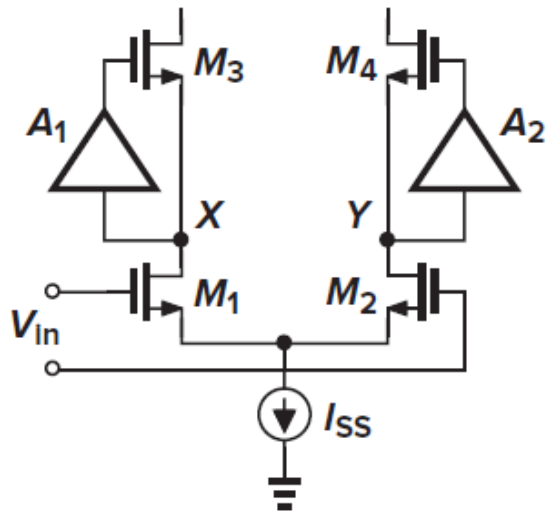
- ❑ NMOS CS implementation replaced by a diff pair
- ❑ Headroom limitation
 - $V_{X,Y} = V_{TH} + V_{ov5,6} + V_{ISS2}$ instead of $V_{ov1} + V_{ISS1}$



(a)

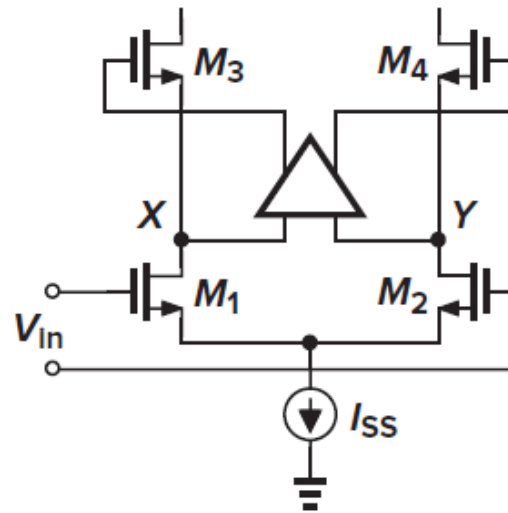


(b)

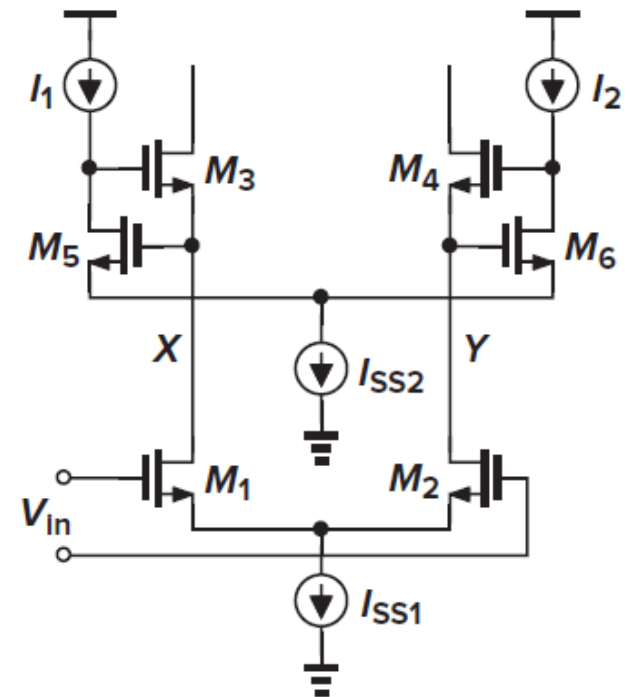

(c)



Gain Boosted OTA

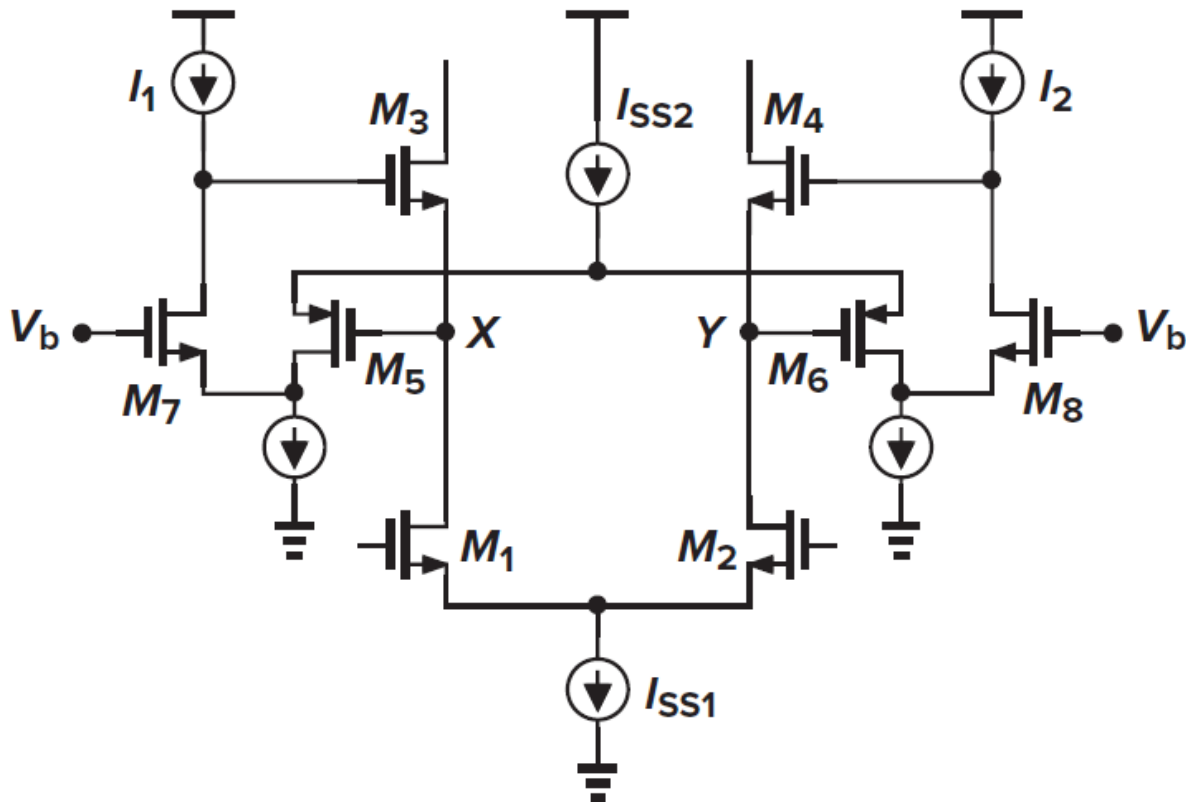- ❑ Folded-cascode used as auxiliary amplifier
- ❑ No headroom limitation
 - $V_{X,Y} = V_{ov1} + V_{ISS1}$



Bonus Question

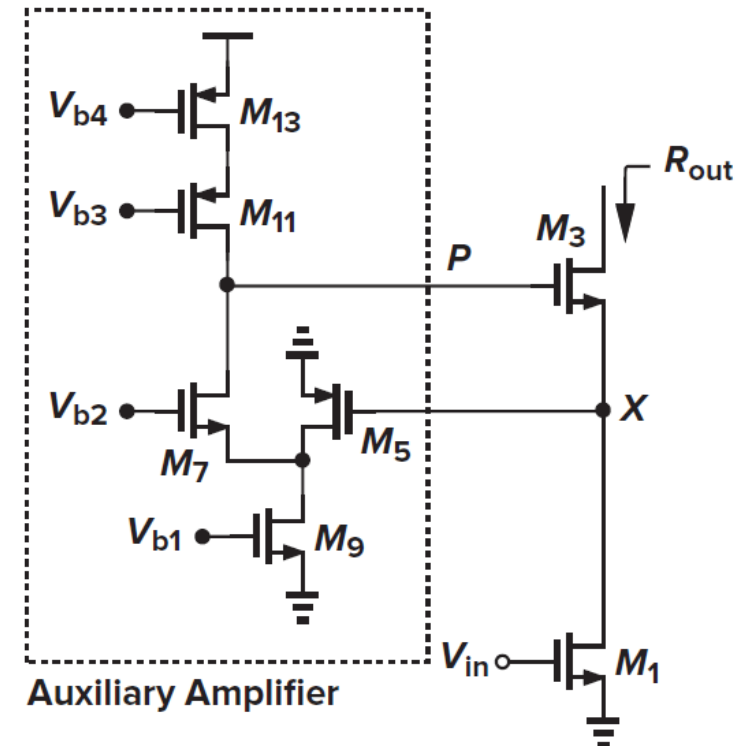
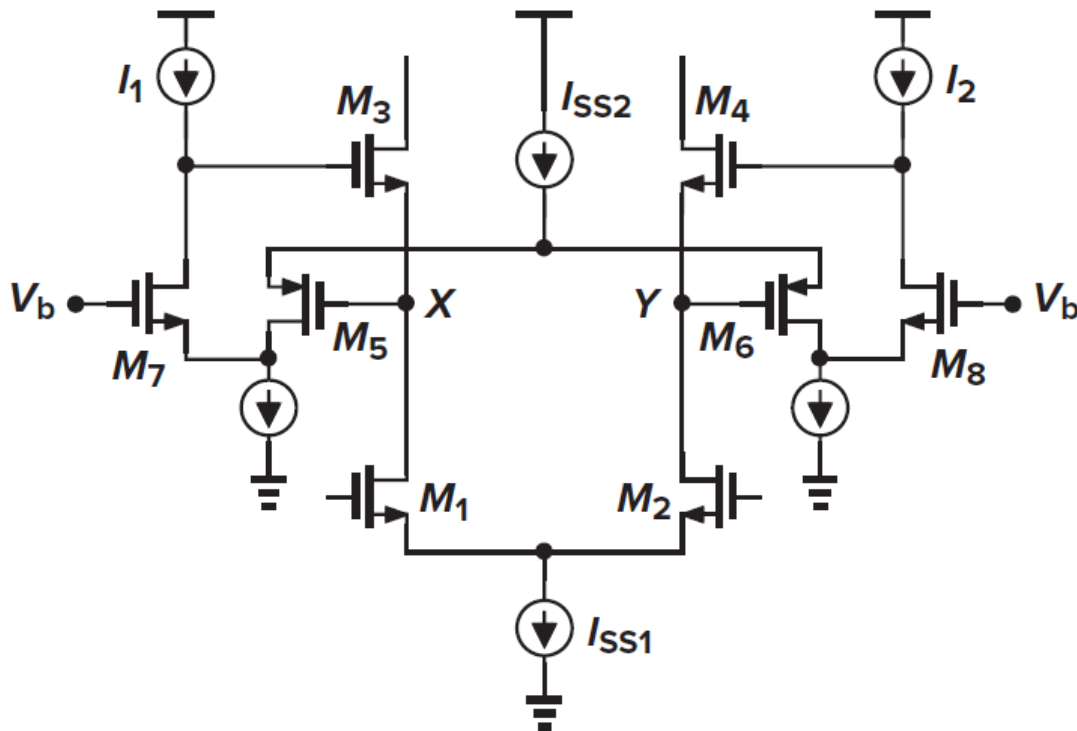
- Calculate the voltage gain. Assume all transistors have the same g_m and r_o . Assume the load is ideal CS (not drawn).



15: OTA / Op-Amp Topologies


-
- The diagram shows a Wilson current mirror circuit with an auxiliary amplifier. The main mirror consists of three NMOS transistors: M_1 at the bottom with gate voltage V_{in} , M_3 at the top with gate voltage P , and M_5 in the middle with gate voltage X . The source of M_1 is grounded, and the source of M_3 is connected to a load resistor R_{out} and ground. The source of M_5 is connected to the gates of M_1 and M_3 . The drain of M_1 is connected to the gate of M_5 . The drain of M_3 is connected to the gate of M_1 . The drain of M_5 is connected to the gates of M_3 and M_1 . The auxiliary amplifier, enclosed in a dashed box, contains four NMOS transistors: M_7 , M_9 , M_{11} , and M_{13} . The gates of M_7 and M_9 are connected to V_{b2} and V_{b1} respectively. The gates of M_{11} and M_{13} are connected to V_{b3} and V_{b4} respectively. The sources of M_7 and M_9 are connected to ground. The sources of M_{11} and M_{13} are connected to the gates of M_7 and M_9 respectively. The drains of M_7 and M_9 are connected to the gates of M_{11} and M_{13} respectively. The drains of M_{11} and M_{13} are connected to the gates of M_7 and M_9 respectively. The output of the auxiliary amplifier is connected to the gate of M_5 .

Gain Boosted OTA

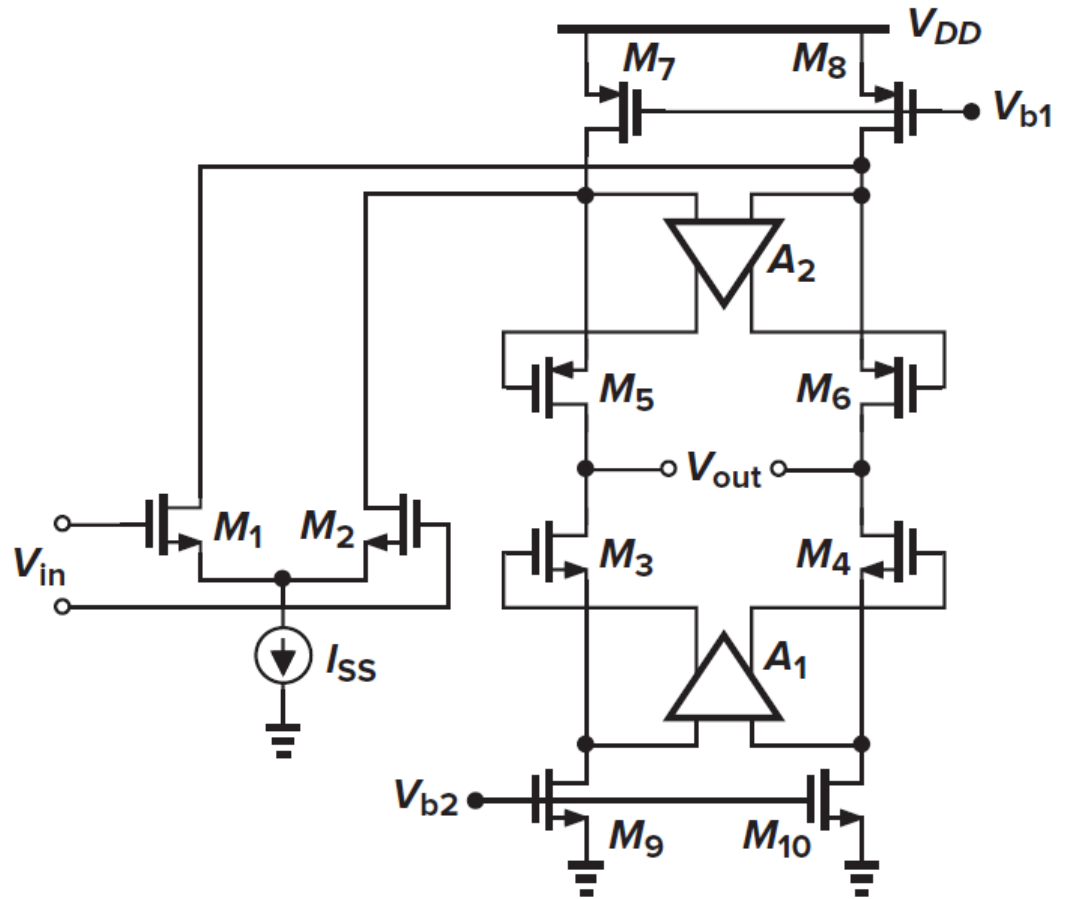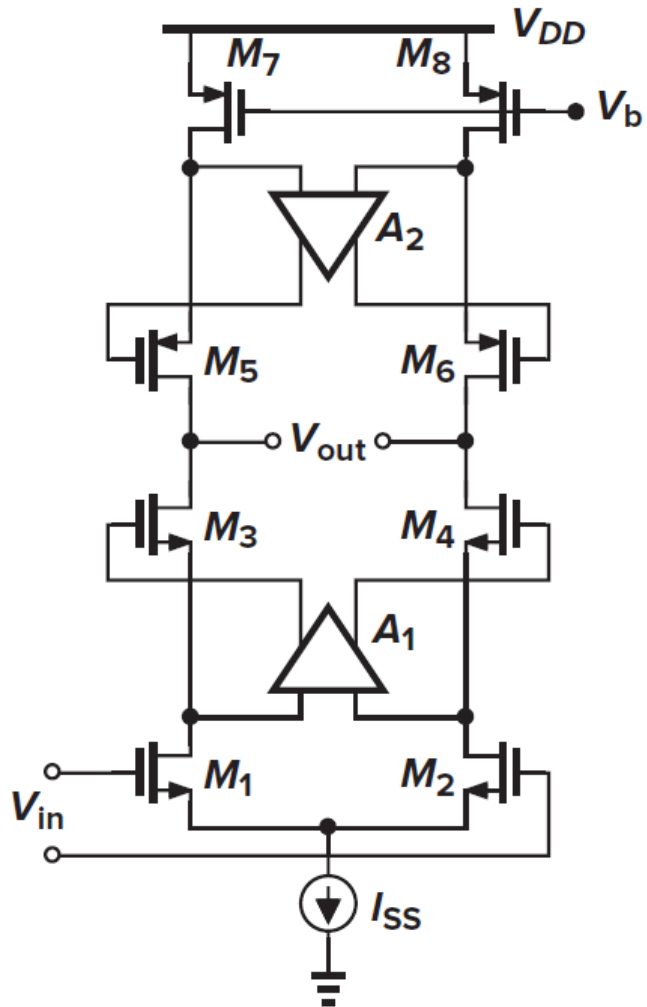

Gain Boosted OTA Frequency Response

□ See [Razavi, 2017] Section 9.4.3

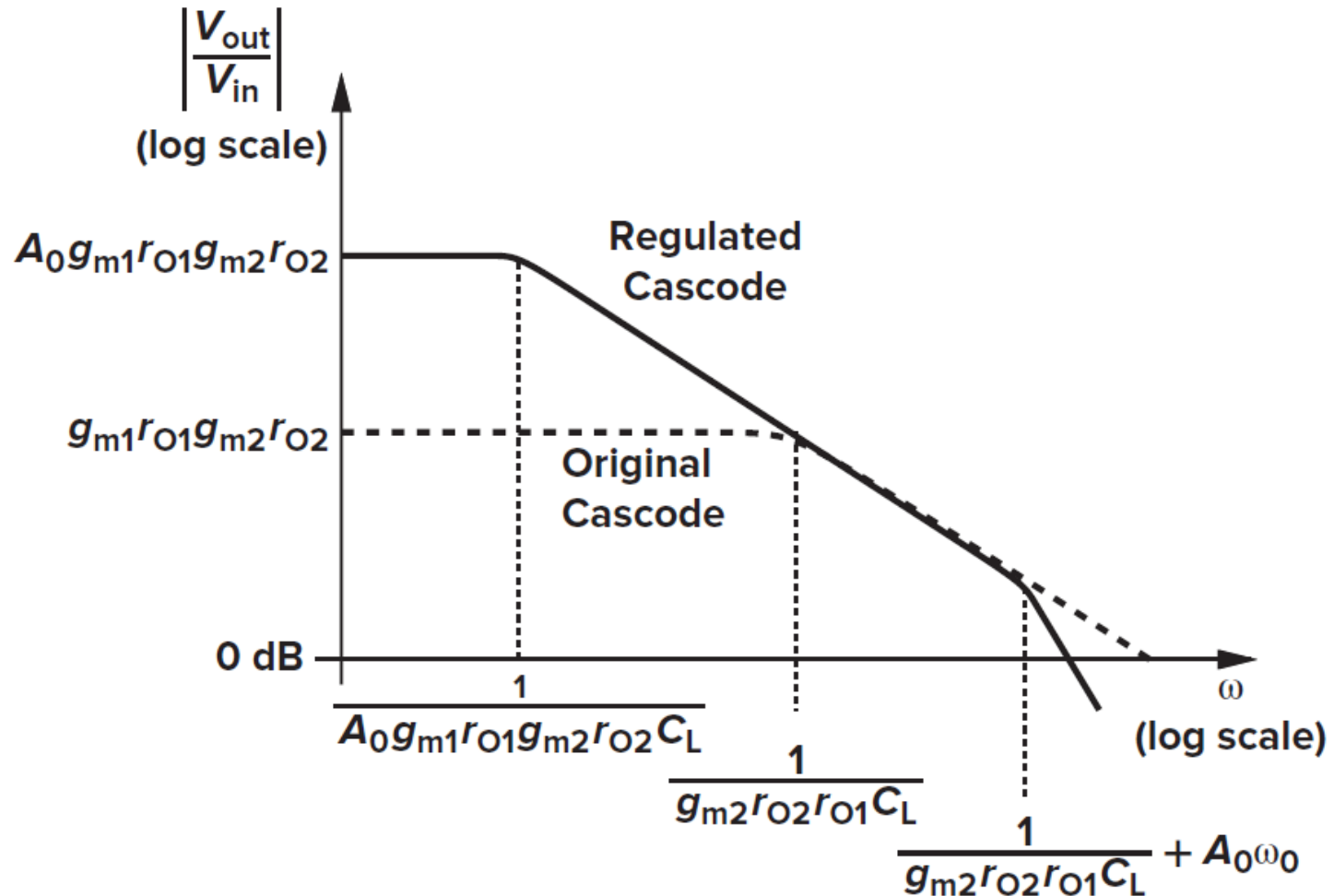

Comparison

	Gain	Output Swing	Speed	Power Dissipation	Noise
Telescopic	Medium	Medium	Highest	Low	Low
Folded-Cascode	Medium	Medium	High	Medium	Medium
Two-Stage	High	Highest	Low	Medium	Low
Gain-Boosted	High	Medium	Medium	High	Medium

Thank you!