

وَمَا أُوتِيتُمْ مِنَ الْعِلْمِ إِلَّا قَلِيلًا

Analog IC Design

Lecture 19

Common-Mode Feedback (CMFB)



Dr. Hesham A. Omran

Integrated Circuits Lab (ICL)
Electronics and Communications Eng. Dept.
Faculty of Engineering
Ain Shams University

MOSFET in Saturation

- ❑ The channel is pinched off if the difference between the gate and drain voltages is not sufficient to create an inversion layer
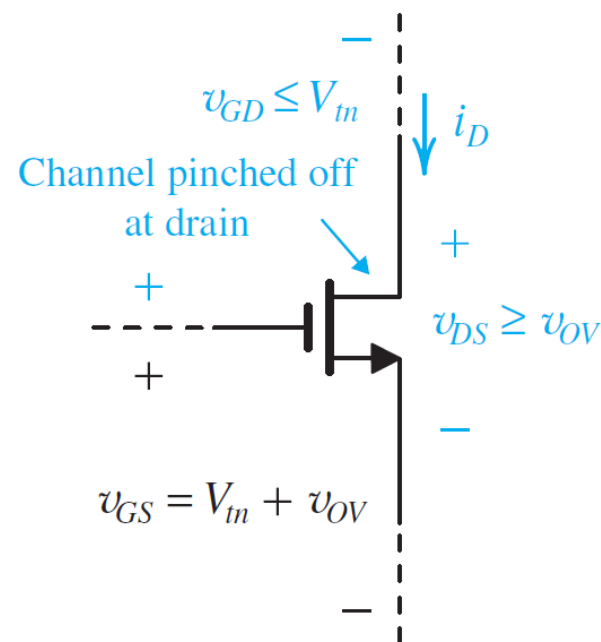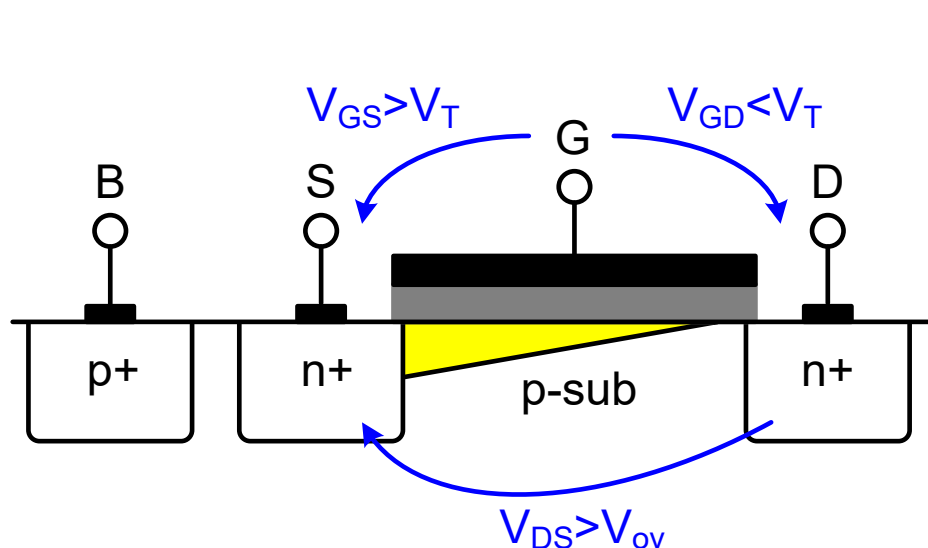
$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \cdot V_{ov}^2 (1 + \lambda V_{DS})$$



Regions of Operation Summary

OFF
(Subthreshold)

$$V_{GS} < V_T$$

ON

$$V_{GS} > V_T$$

Triode

$$V_{DS} < V_{ov}$$

Or

$$V_{GD} > V_T$$

Pinch-Off
(Saturation)

$$V_{DS} \geq V_{ov}$$

Or

$$V_{GD} \leq V_T$$

$$I_D = \mu C_{ox} \frac{W}{L} \left(V_{ov} V_{DS} - \frac{V_{DS}^2}{2} \right)$$


$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} V_{ov}^2 (1 + \lambda V_{DS})$$

Low-Frequency Small-Signal Model


$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu C_{ox} \frac{W}{L} V_{ov} = \sqrt{\mu C_{ox} \frac{W}{L} \cdot 2I_D} = \frac{2I_D}{V_{ov}}$$

$$g_{mb} = \eta g_m, \quad \eta \approx 0.1 - 0.25$$

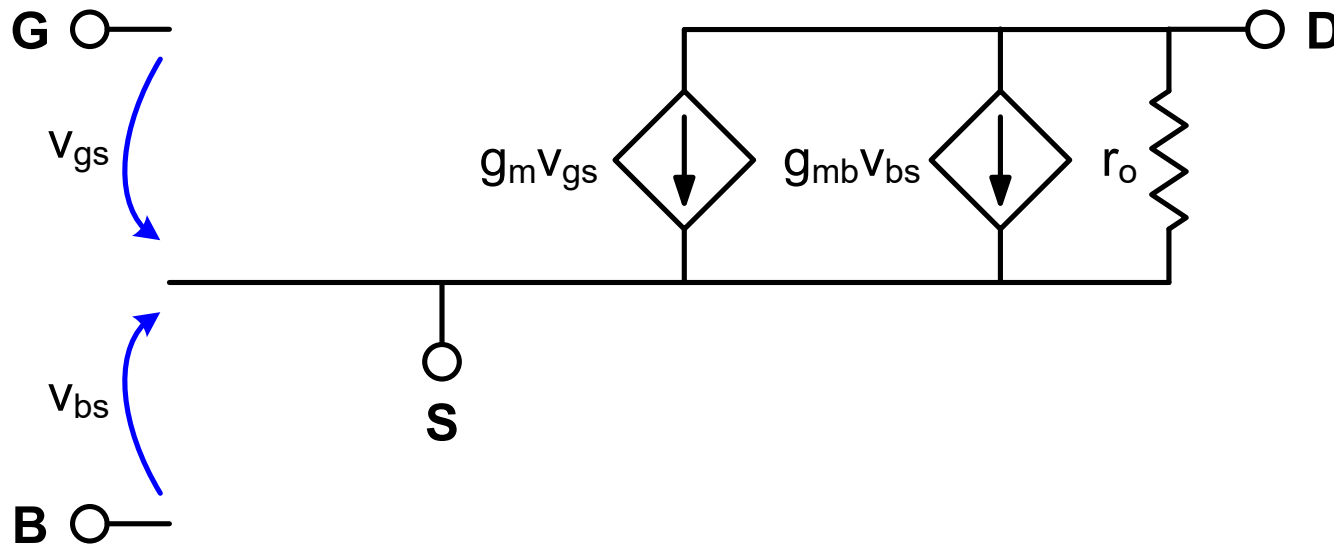
$$r_o = \frac{1}{\frac{\partial I_D}{\partial V_{DS}}} = \frac{1}{\lambda I_D}, \quad \lambda \propto \frac{1}{L}$$



Rin/out Shortcuts Summary


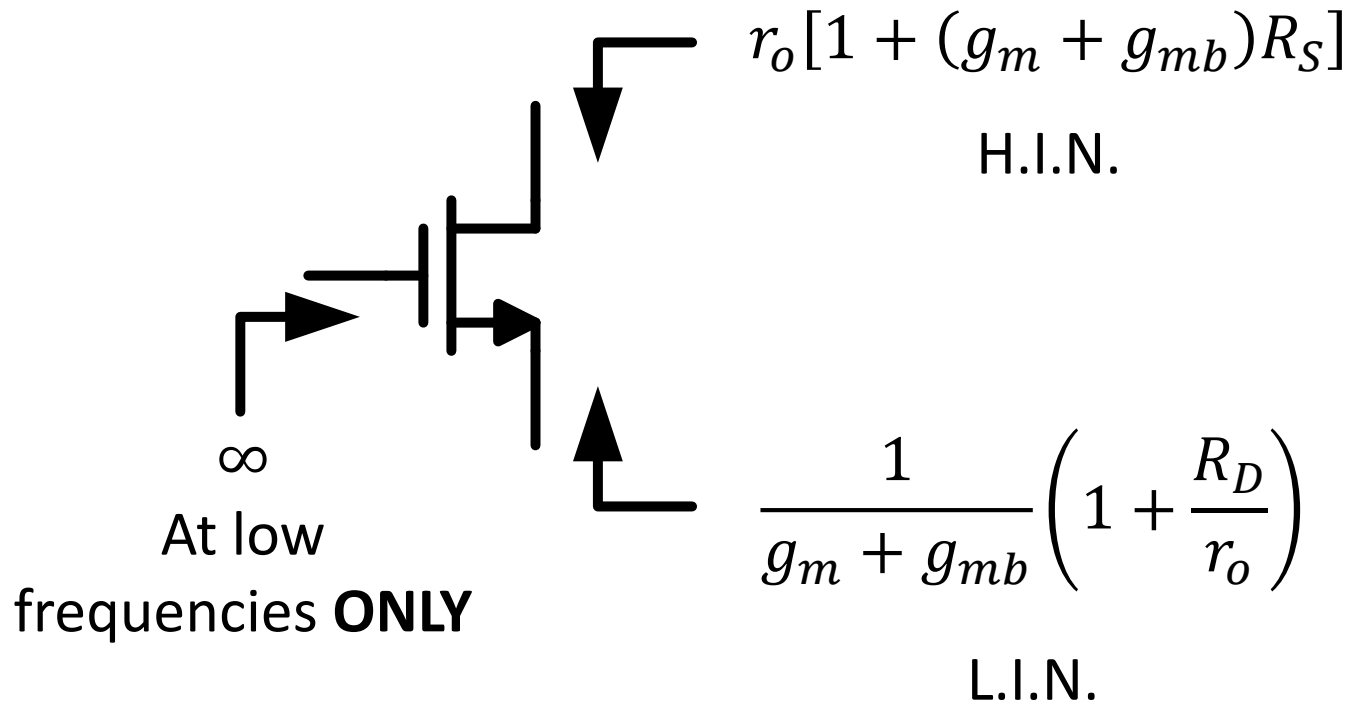


Active Load (Source OFF)

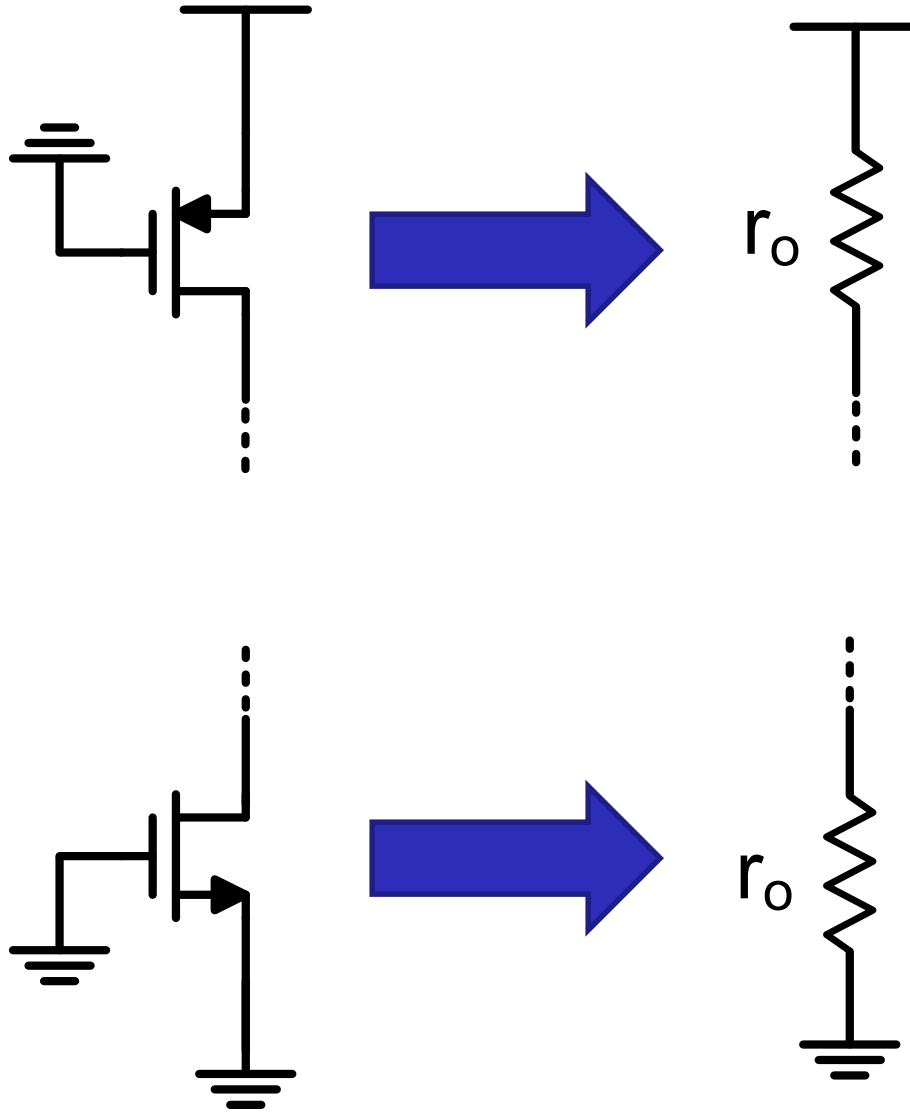

Diode Connected (Source Absorption)

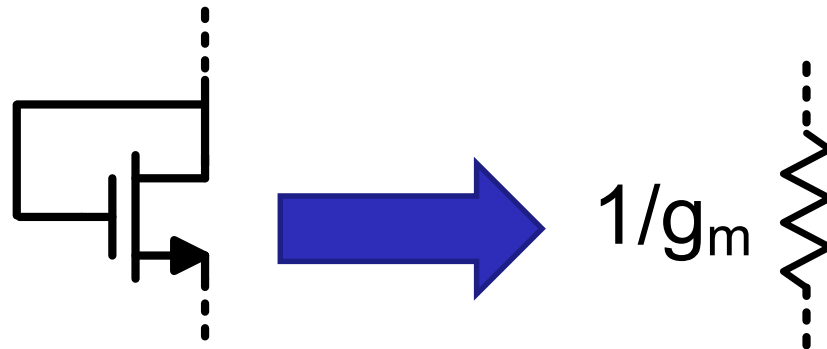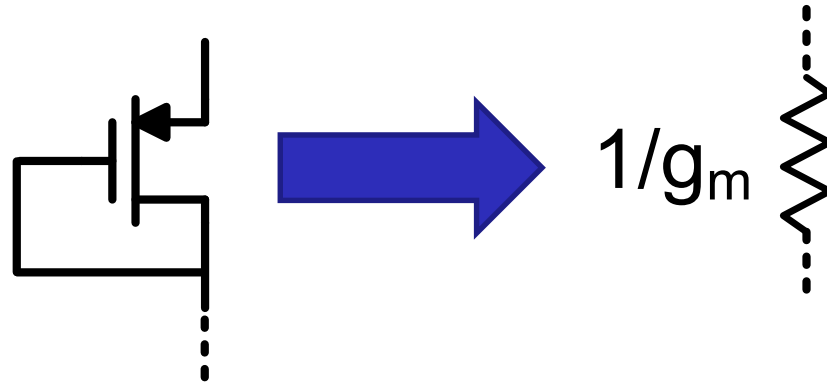- ❑ Always in saturation
- ❑ Bulk effect: $g_m \rightarrow g_m + g_{mb}$



Why GmRout?

$$R_{out} = \frac{v_x}{i_x} @ v_{in} = 0$$



$$G_m = \frac{i_{out,sc}}{v_{in}}$$

$$A_v = G_m R_{out}$$




$$A_i = G_m R_{in}$$

□ Divide and conquer

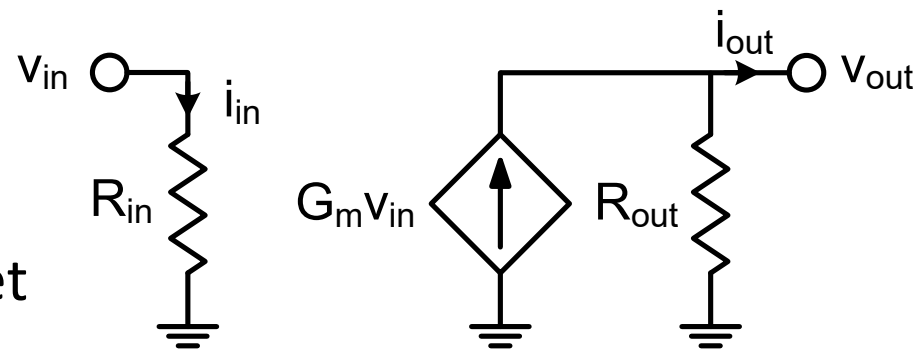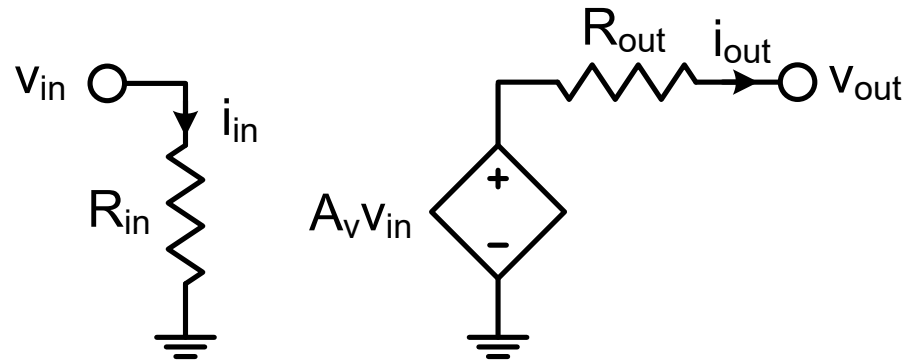- Rout simplified: $v_{in}=0$
- Gm simplified: $v_{out}=0$
- We already need $R_{in/out}$
- We can quickly and easily get $R_{in/out}$ from the shortcuts



Summary of Basic Topologies

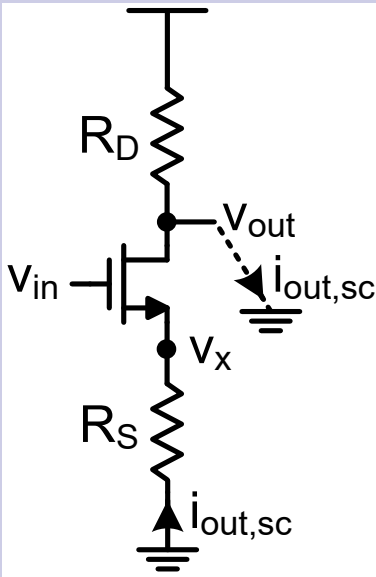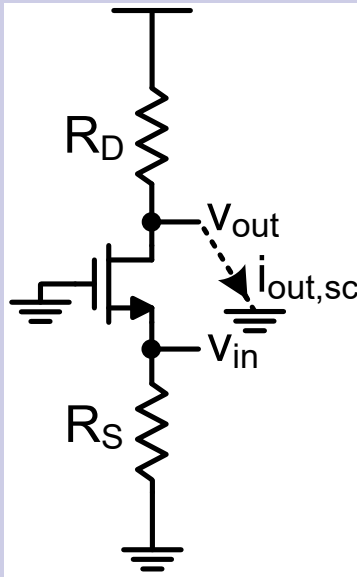
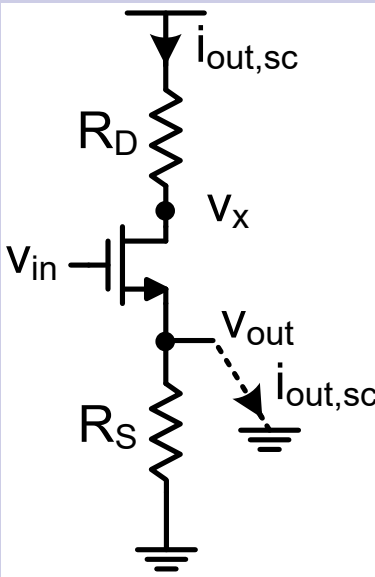
	CS	CG	CD (SF)
			
	Voltage & current amplifier	Current buffer	Voltage buffer
Rin	∞	$R_S // \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$	∞
Rout	$R_D // r_o [1 + (g_m + g_{mb})R_S]$	$R_D // r_o$	$R_S // \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$
Gm	$\frac{-g_m}{1 + (g_m + g_{mb})R_S}$	$g_m + g_{mb}$	$\frac{g_m}{1 + R_D/r_o}$

Differential Amplifier

	Pseudo Diff Amp	Diff Pair (w/ ideal CS)	Diff Pair (w/ R_{SS})
A_{vd}	$-g_m R_D$	$-g_m R_D$	$-g_m R_D$
A_{vCM}	$-g_m R_D$	0	$\frac{-g_m R_D}{1 + 2(g_m + g_{mb})R_{SS}}$
A_{vd}/A_{vCM}	1	∞	$2(g_m + g_{mb})R_{SS} \gg 1$

What is an OTA / Op-Amp?

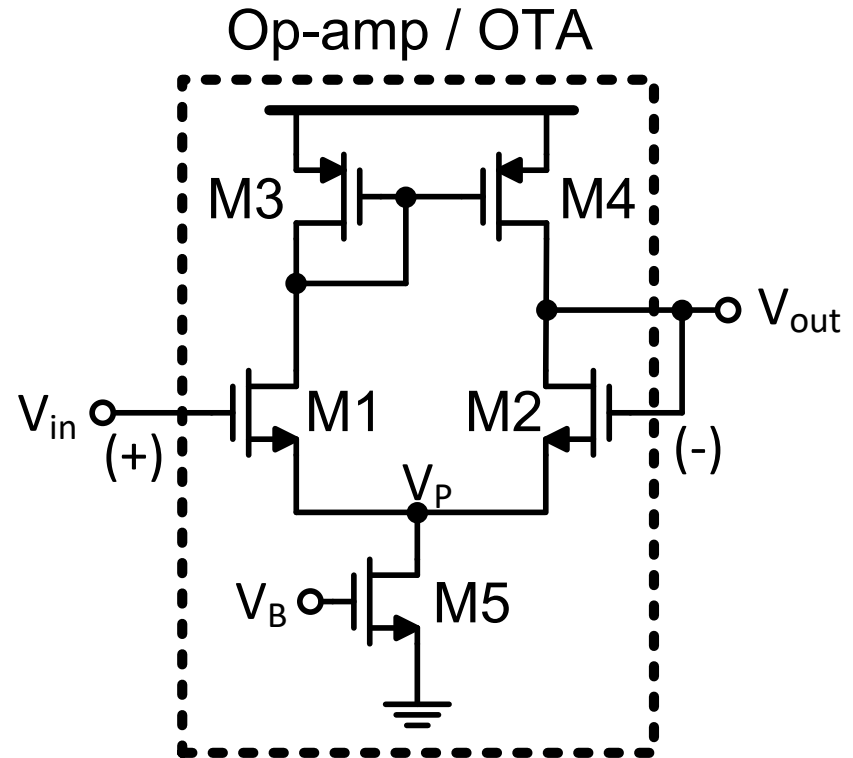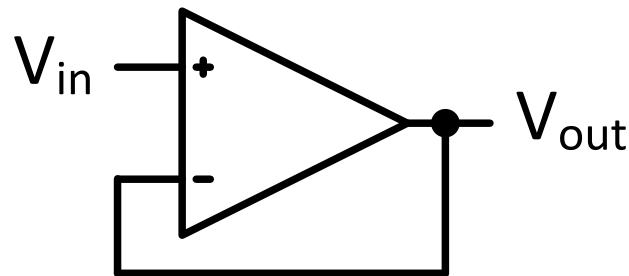- ❑ An op-amp is simply a high gain differential amplifier
- ❑ The gain can be increased by using cascodes and multi-stage amplifiers



Op-Amp vs OTA



- ❑ An OTA is an op-amp without an output stage (buffer)
- ❑ Some designers just use op-amp name and symbol for both

	Op-amp	OTA
Rout	LOW	HIGH
Model		
Diff input, SE output		
Fully diff		

Negative Feedback



- ❑ A_{OL} = Open loop (OL) gain $\gg 1$
- ❑ $A_{CL} = \frac{Y}{X}$ = Closed loop (CL) gain
- ❑ Error signal = $X - X_F$
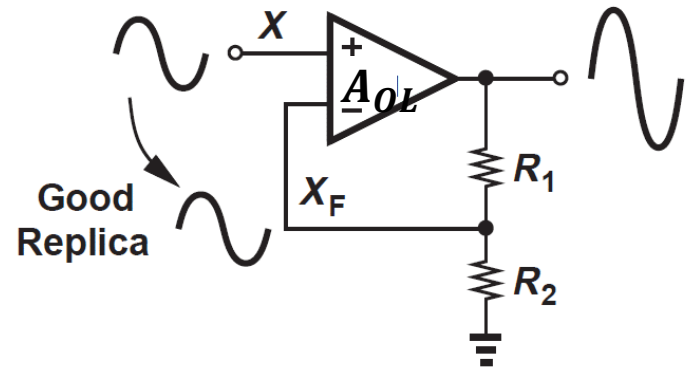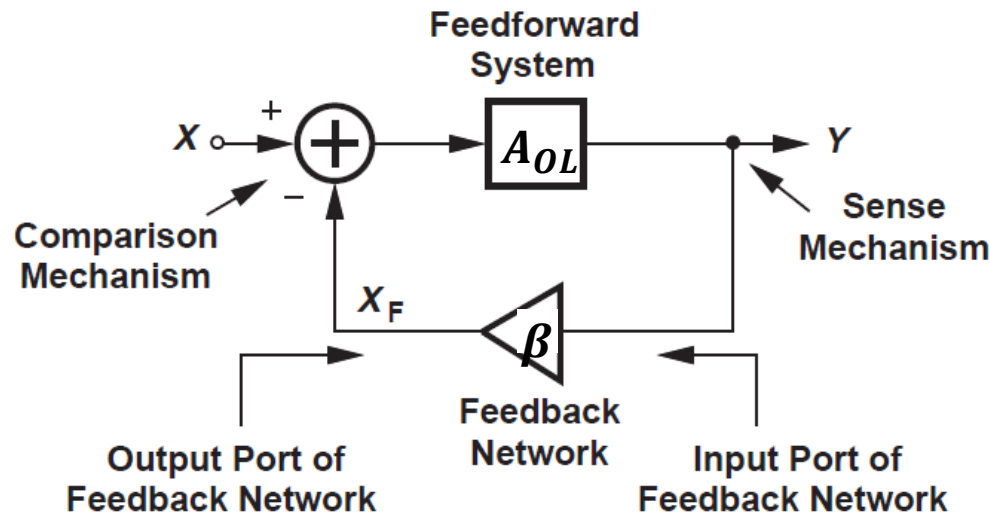
$$Y = A_{OL}(X - X_F) = A_{OL}(X - \beta Y)$$
$$A_{CL} = \frac{Y}{X} = \frac{A_{OL}}{1 + \beta \cdot A_{OL}} \approx \frac{1}{\beta}$$



Stability: Phase Margin

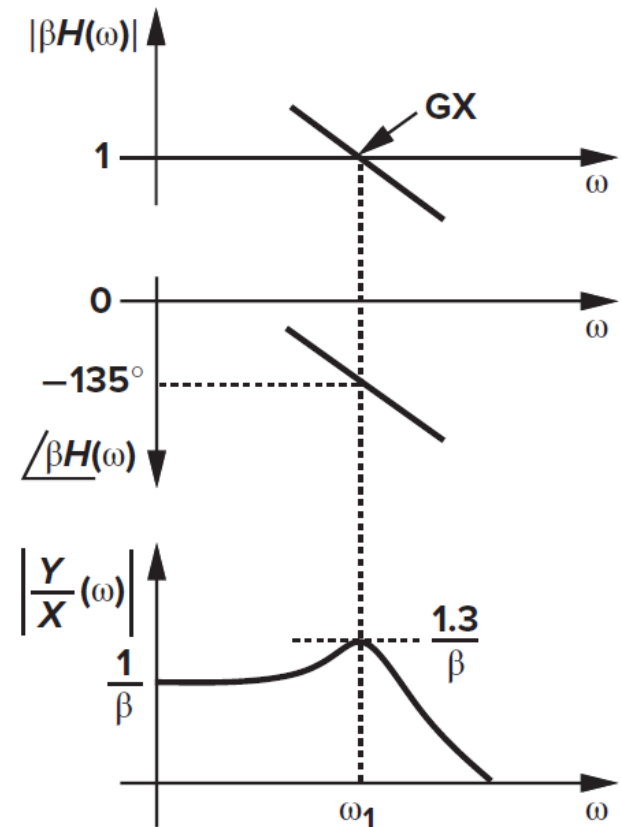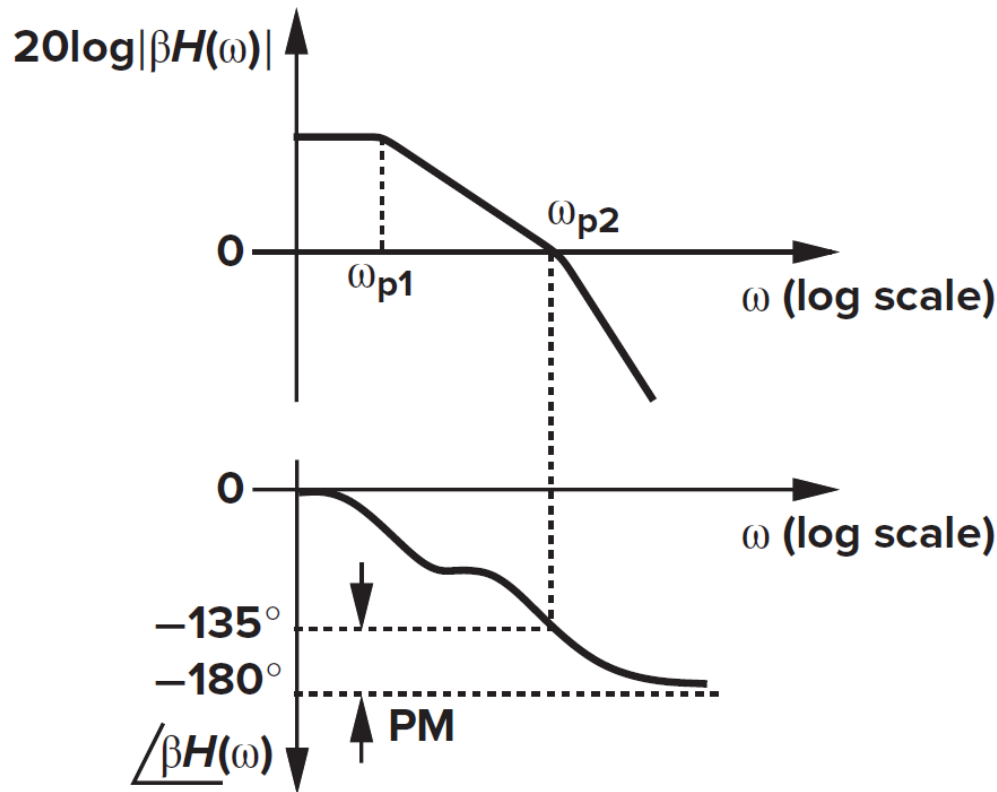- ❑ If $\omega_{p2} = \omega_u$: PM = $45^\circ \rightarrow$ typically inadequate (peaking/ringing)
- ❑ The ultimate ω_u cannot exceed $\omega_{p2} \rightarrow \omega_{p1} < \omega_u < \omega_{p2}$
 - For $\omega < \omega_u$ the Bode plot is similar to a 1st order system




Why Fully Differential Circuits

- ❑ Fully differential vs diff input SE output
 - Larger output swing
 - No mirror poles (higher speed)
 - Better CMRR
 - Better linearity (lower distortion)
- ❑ But common-mode feedback (CMFB) circuit is required...



Well Defined Input/Output CM Level

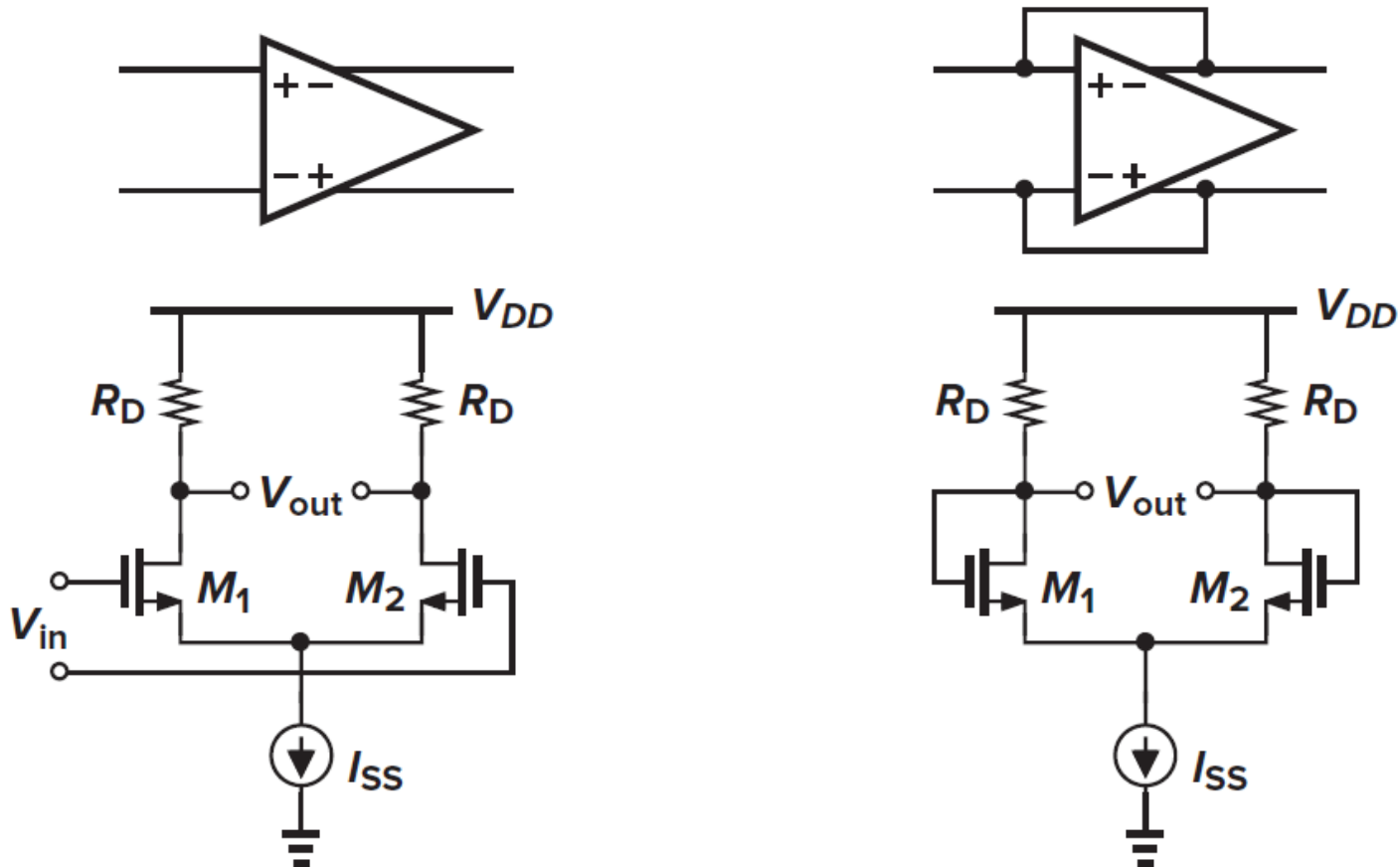- ❑ The input and output common-mode levels are fairly well defined
- ❑ $V_{CM} = V_{DD} - I_{SS} \cdot R_D / 2$





ILL-Defined Input/Output CM Level

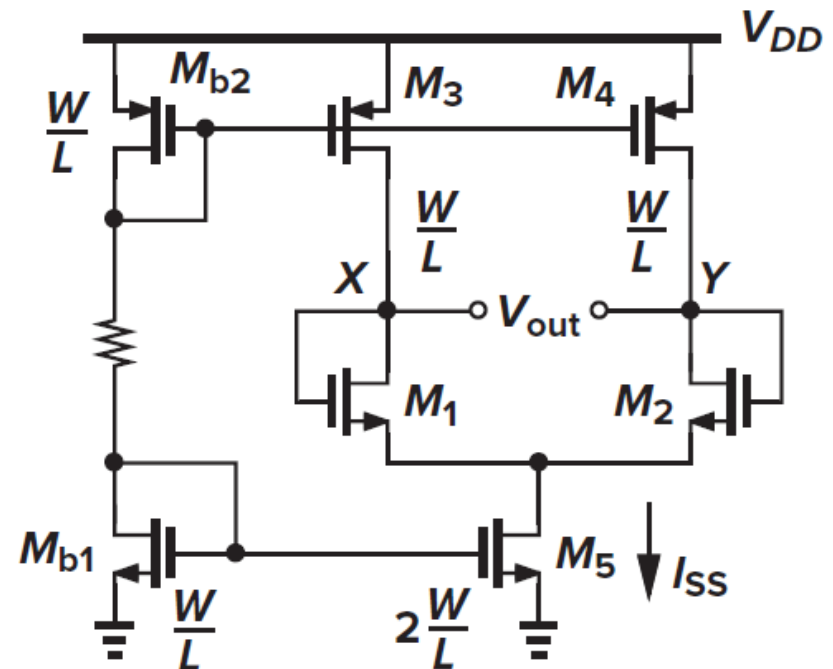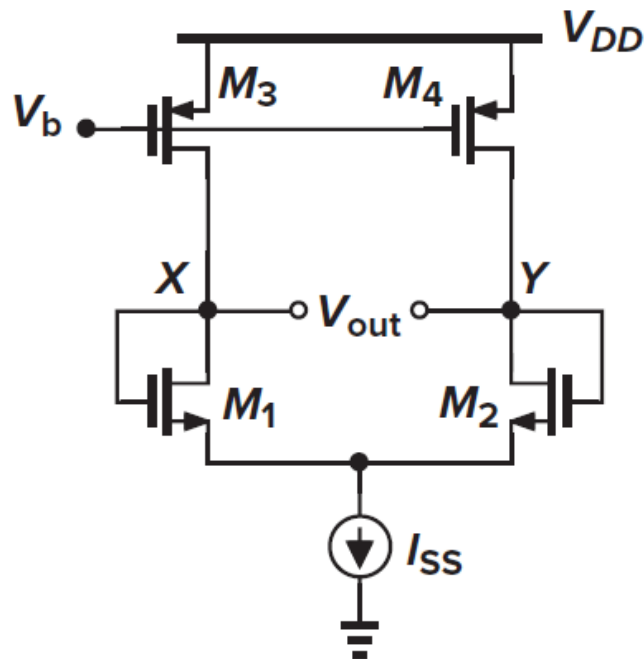- ❑ Mismatches ALWAYS create a finite error between $ID_{3,4}$ and $I_{SS}/2$
- ❑ If $ID_{3,4} > I_{SS}/2$: V_X and V_Y must rise (M_3 and M_4 enter triode) so that $ID_{3,4}$ fall to $I_{SS}/2$
- ❑ If $ID_{3,4} < I_{SS}/2$: V_X and V_Y must drop (M_1 and M_2 enter triode) region so that I_{SS} falls to $2 \cdot ID_{3,4}$




ILL-Defined Input/Output CM Level

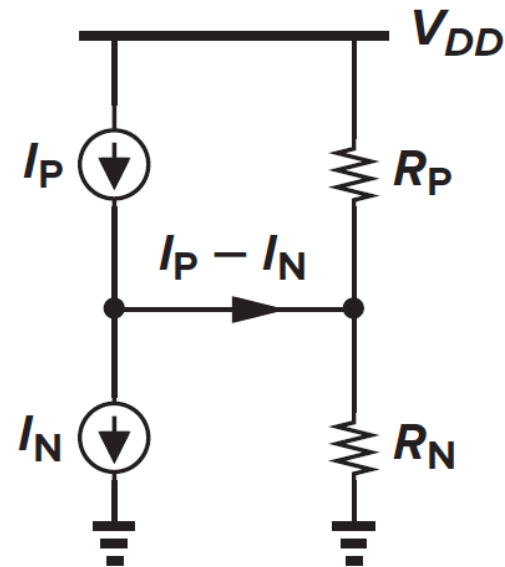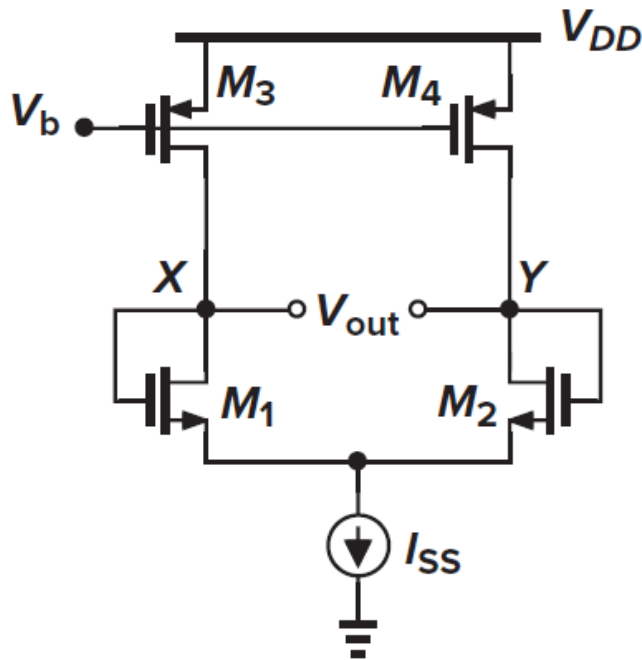- ❑ This is a fundamental problem in high-gain amplifiers
- ❑ V_b can be adjusted in simulations but not in a real circuit
- ❑ Why don't we suffer from this problem in SE output OTA?




Common-Mode Feedback (CMFB)

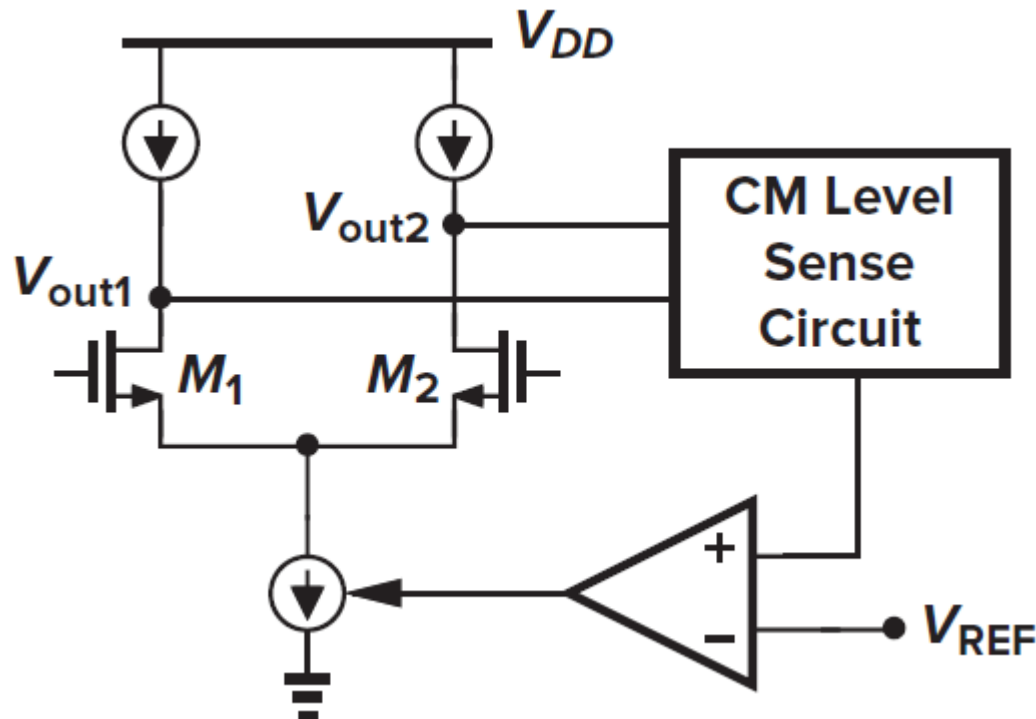- ❑ Negative FB system
 1. Sense CM level
 2. Compare it to a reference
 3. Return the error to the bias circuit




CMFB

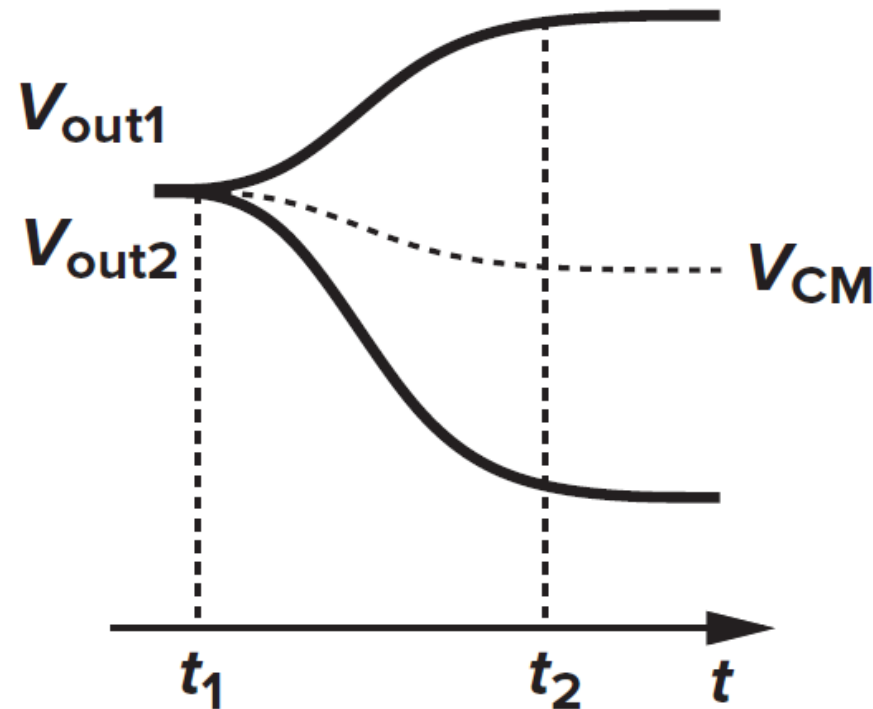- CM level must be independent of the differential signal
 - CM sensing must not depend on the differential signal




CM Sensing: Resistive Sensing

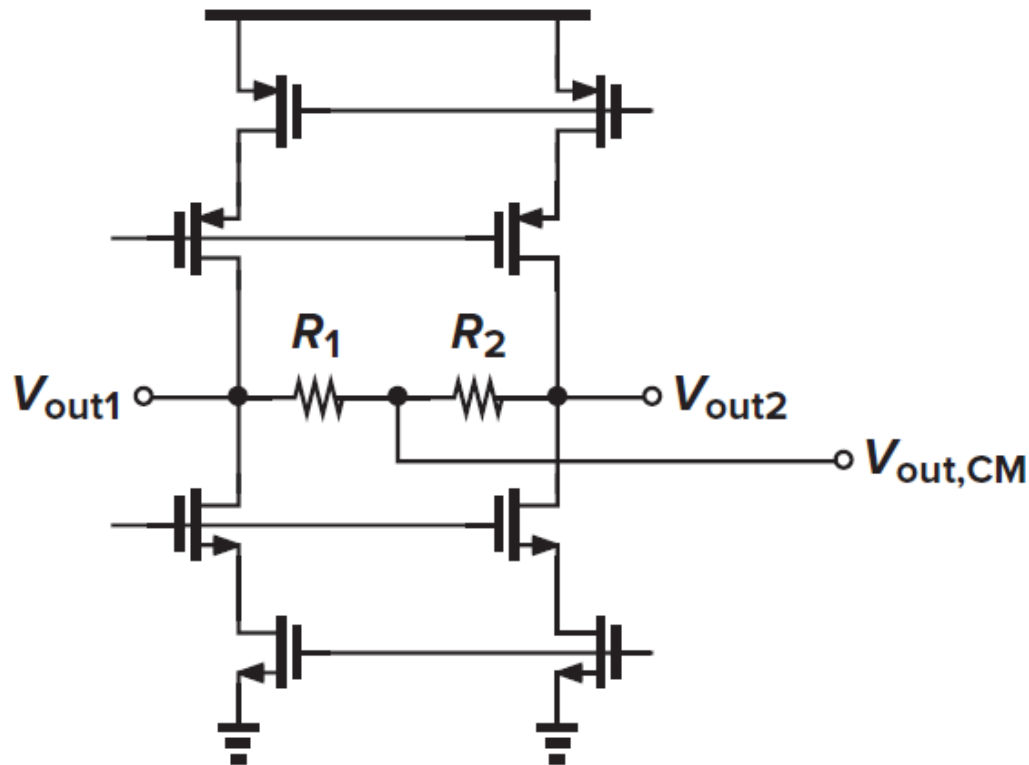- ❑ Small R will degrade the gain
- ❑ Large R occupies large area and has large parasitic capacitors
 - May degrade the CMFB loop stability!




CMFB Techniques

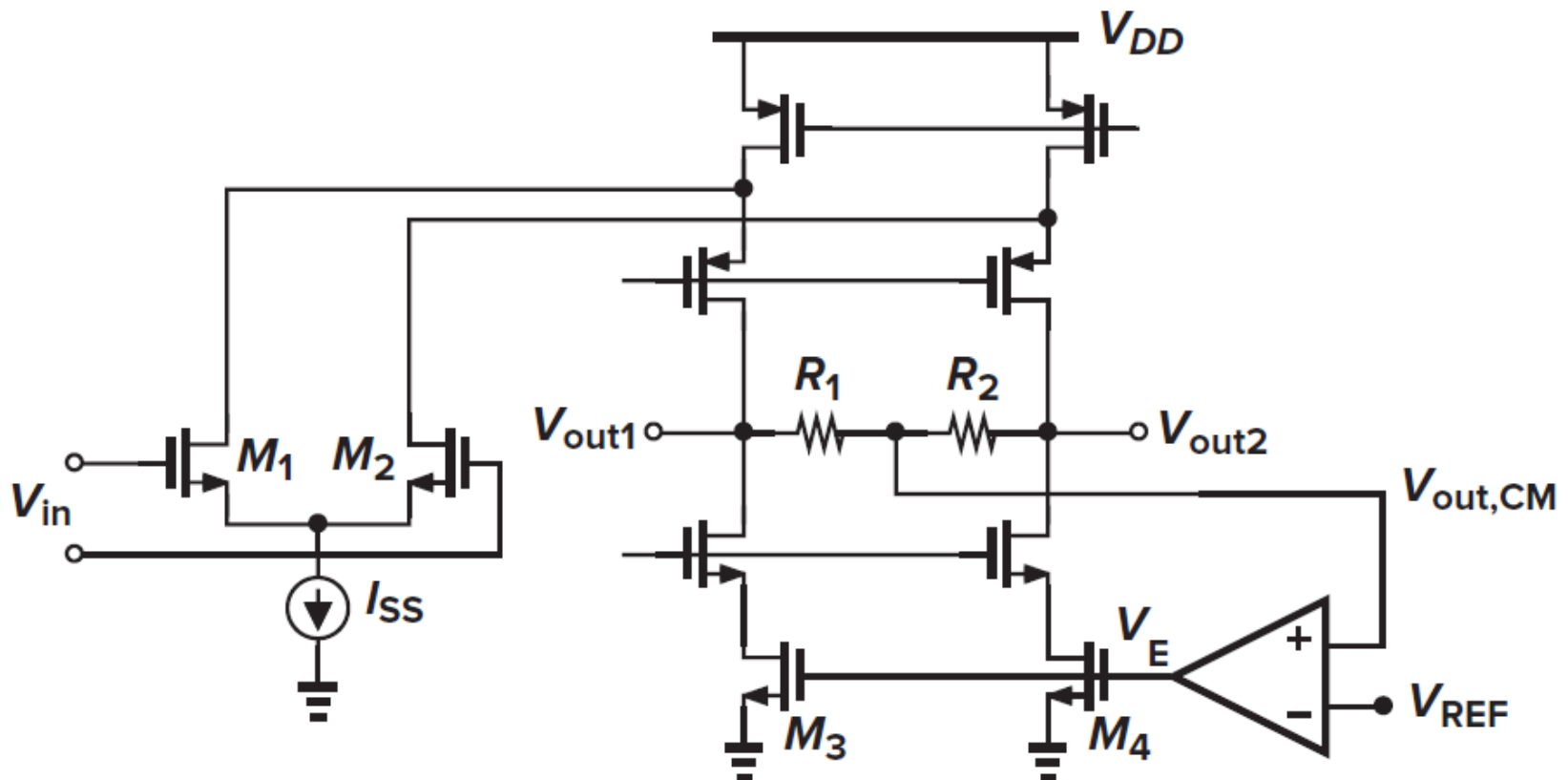- ❑ Resistive sensing
- ❑ The feedback network forces the CM level of V_{out1} and V_{out2} to approach V_{REF}
- ❑ The feedback can also be applied to the PMOS current sources




CMFB Techniques

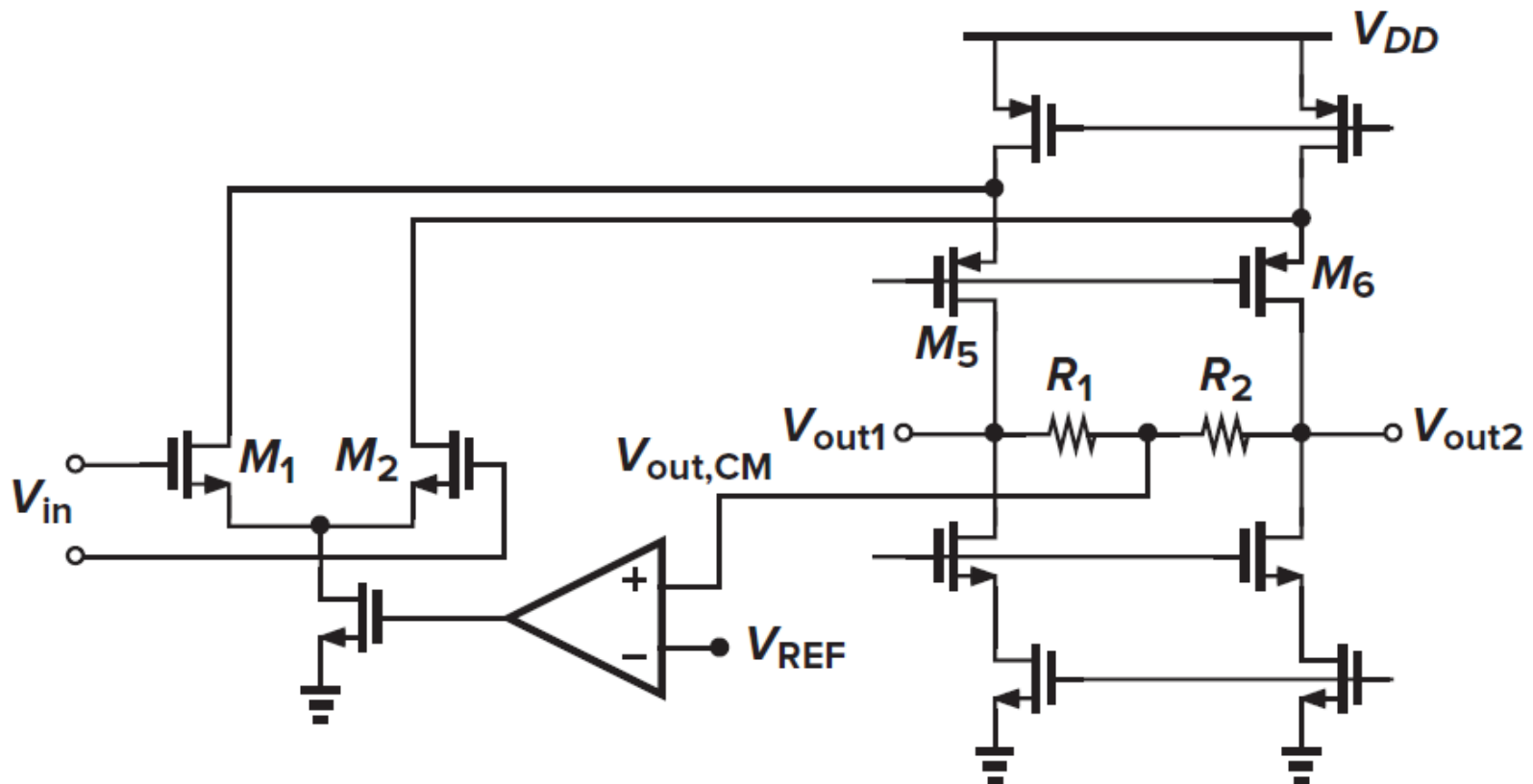- ❑ Resistive sensing
- ❑ The feedback network forces the CM level of V_{out1} and V_{out2} to approach V_{REF}




CMFB Techniques

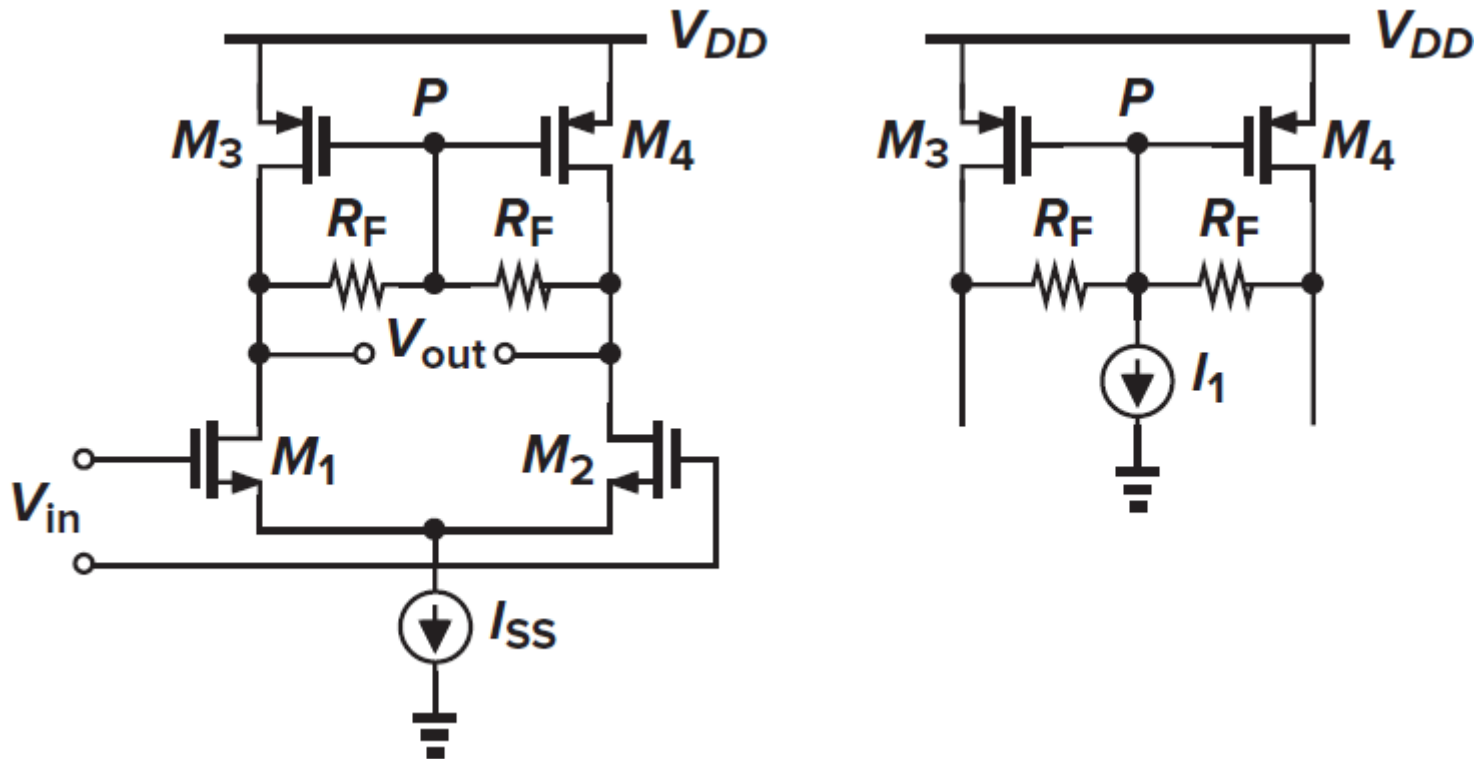- ❑ For CM level M3 and M4 behave as diode connected devices
- ❑ Maximum swing obtained by setting $\frac{I_1}{2} R_F = V_{TH}$



CMFB Techniques

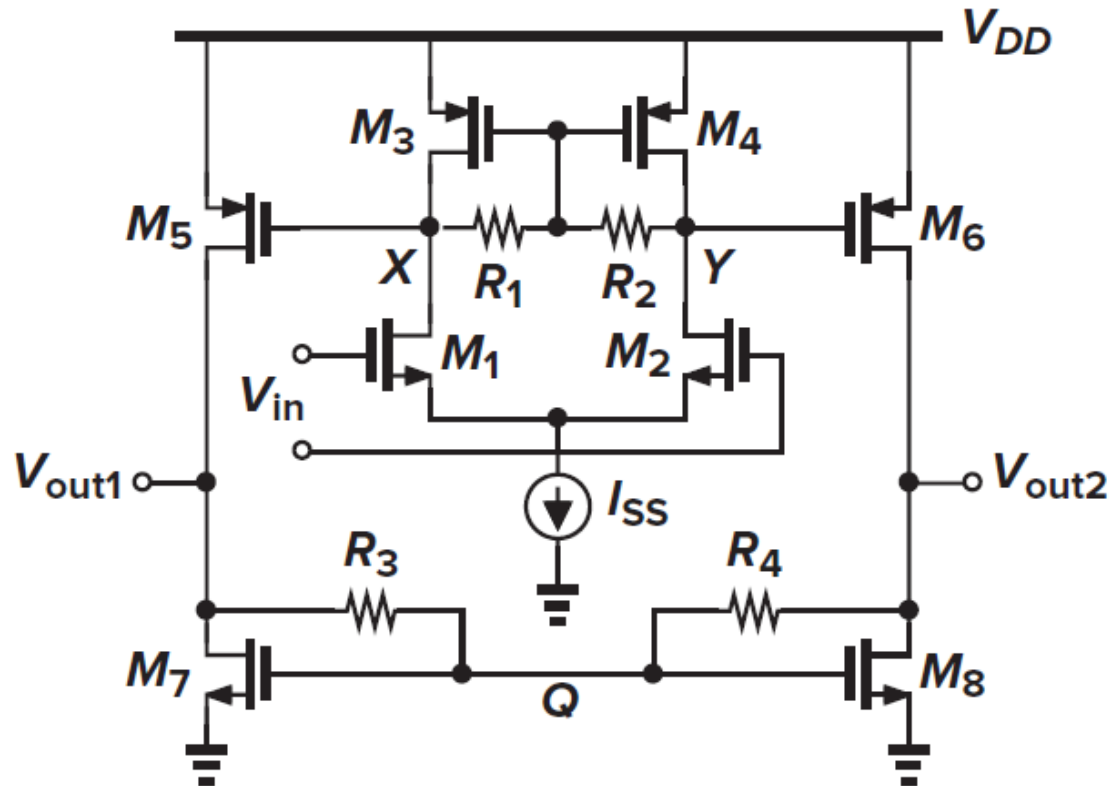
- ❑ Two stage OTA: Two separate CMFB loops for the first and second stages



CMFB Loop Stability


- ❑ Simulating CMFB loop stability

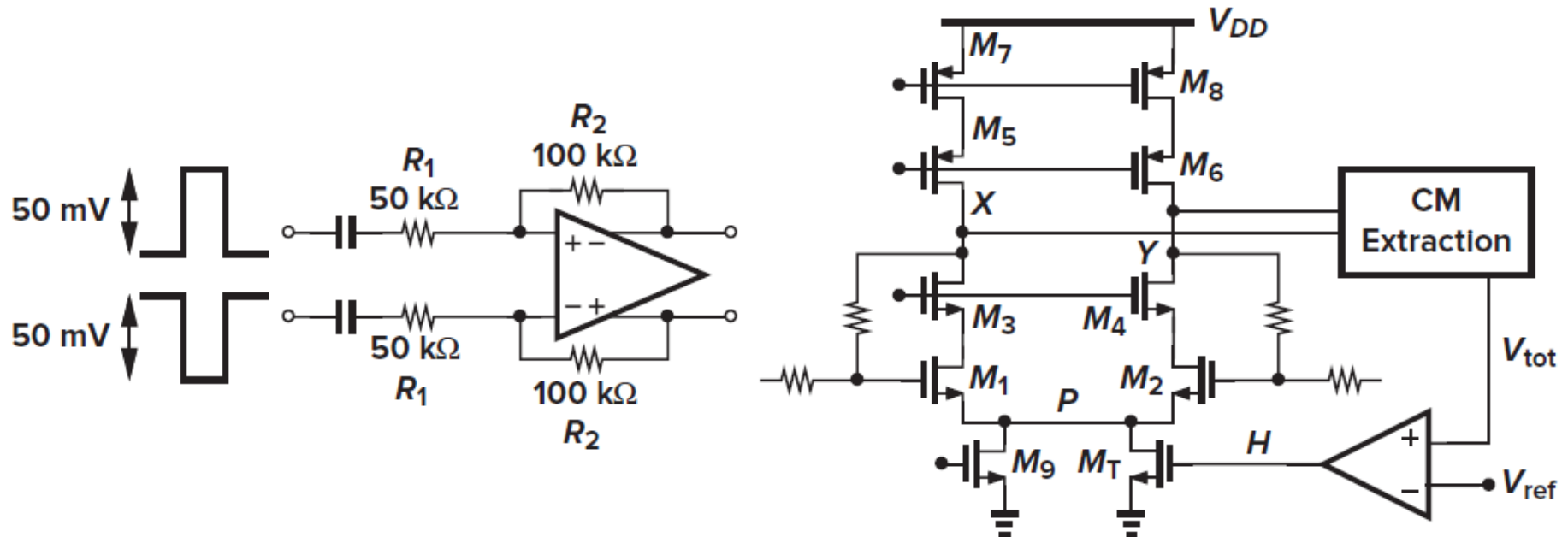- Place the OTA in a closed-loop feedback system
- Apply differential pulses (transient analysis)
 - Large signal effects are captured




CMFB Loop Stability

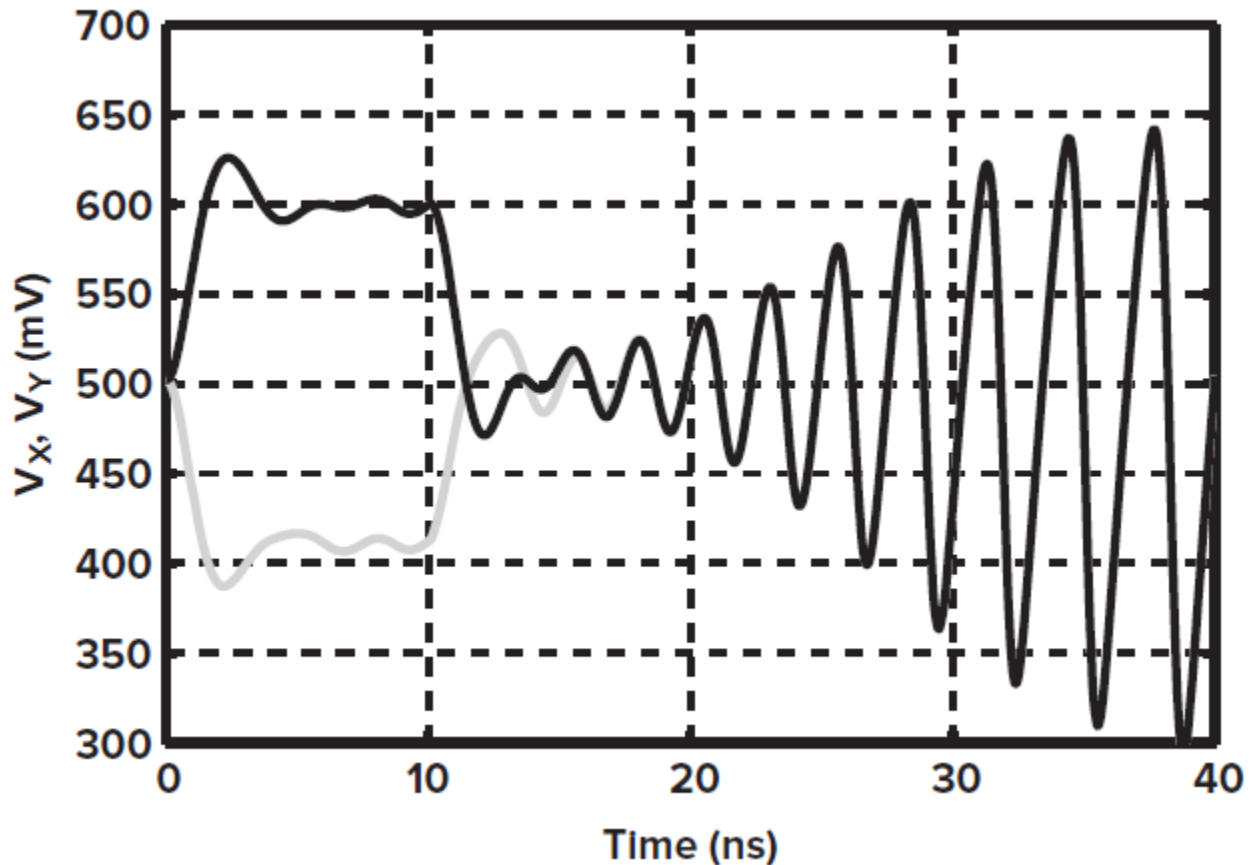- ❑ The CMFB loop is unstable!
 - Requires compensation




CMFB Loop Stability

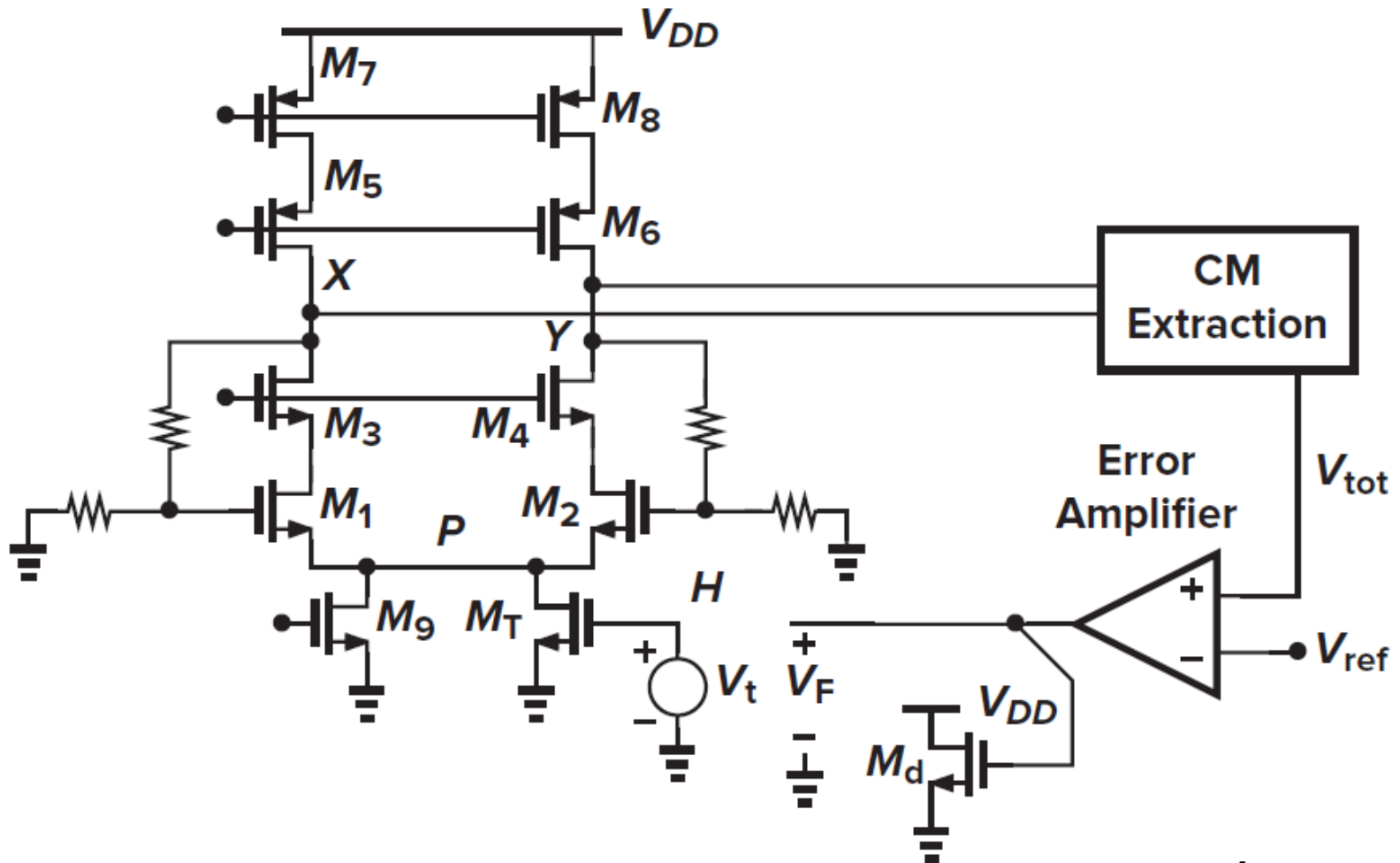- ❑ Hand analysis: Break the loop to analyze the CMFB loop gain
- ❑ Simulation: Use STB analysis (loading and bilateral effects)




CMFB Loop Stability

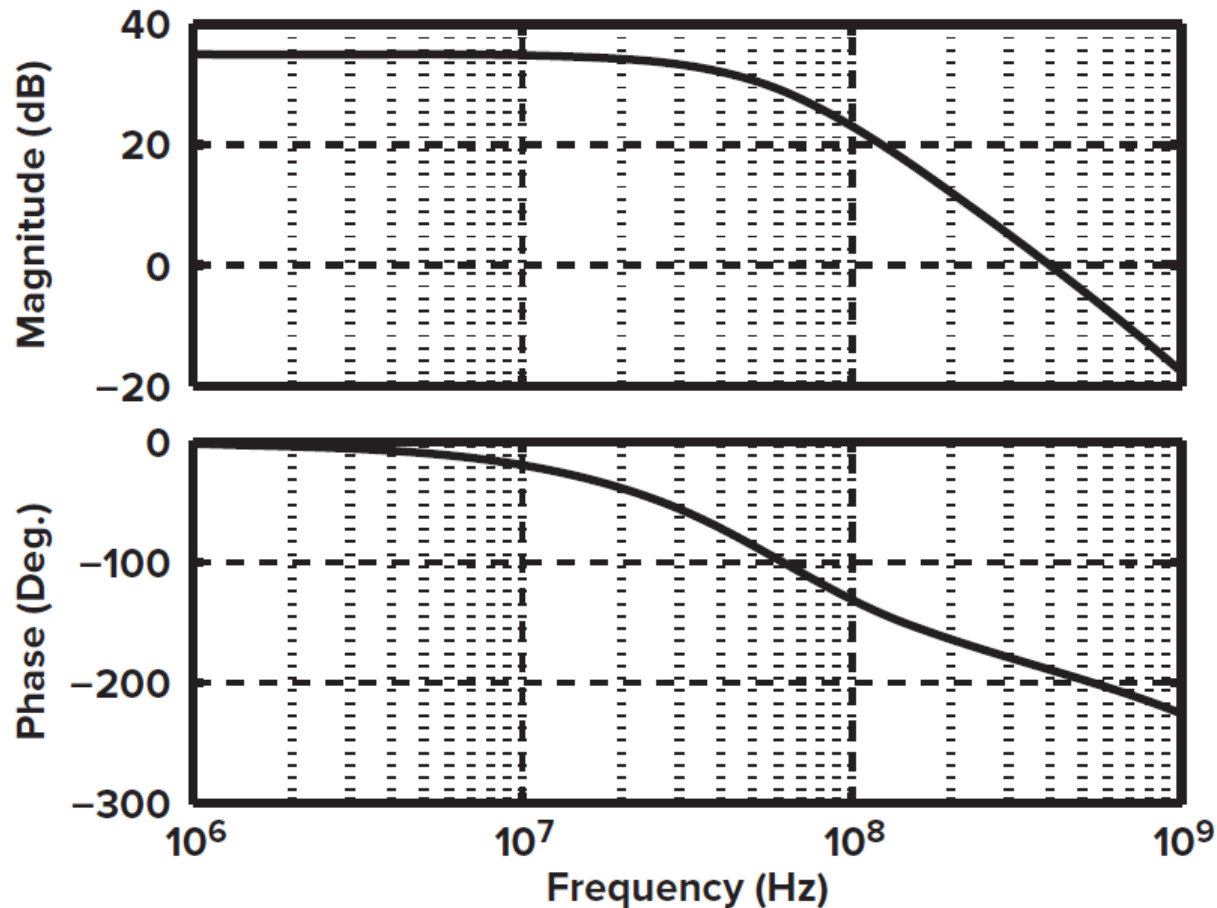- PM = -10°
- Note the CMFB loop does not require very high gain




CMFB Loop Stability

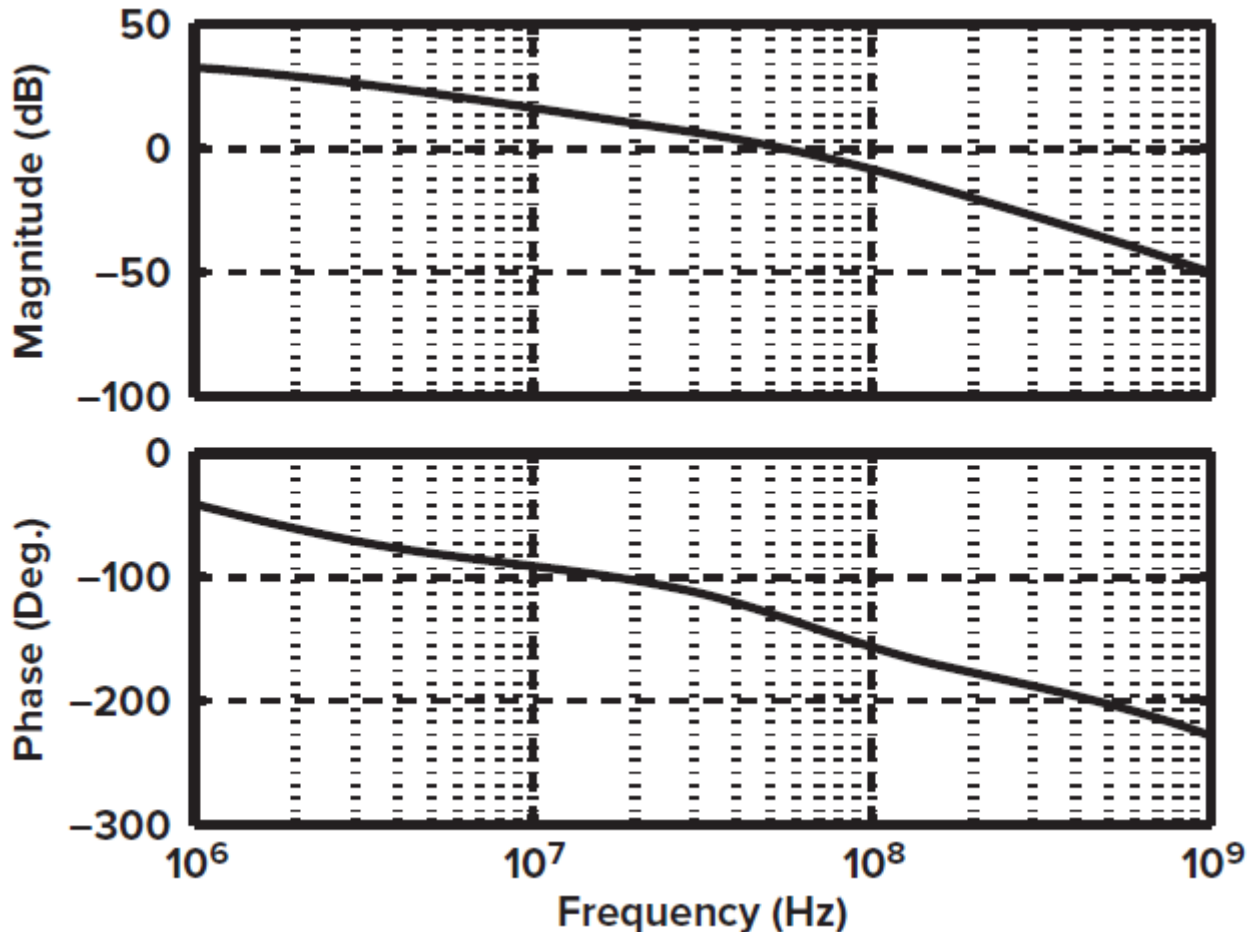- Add 3pF to the error amplifier output \rightarrow PM = 50°




CMFB Loop Stability

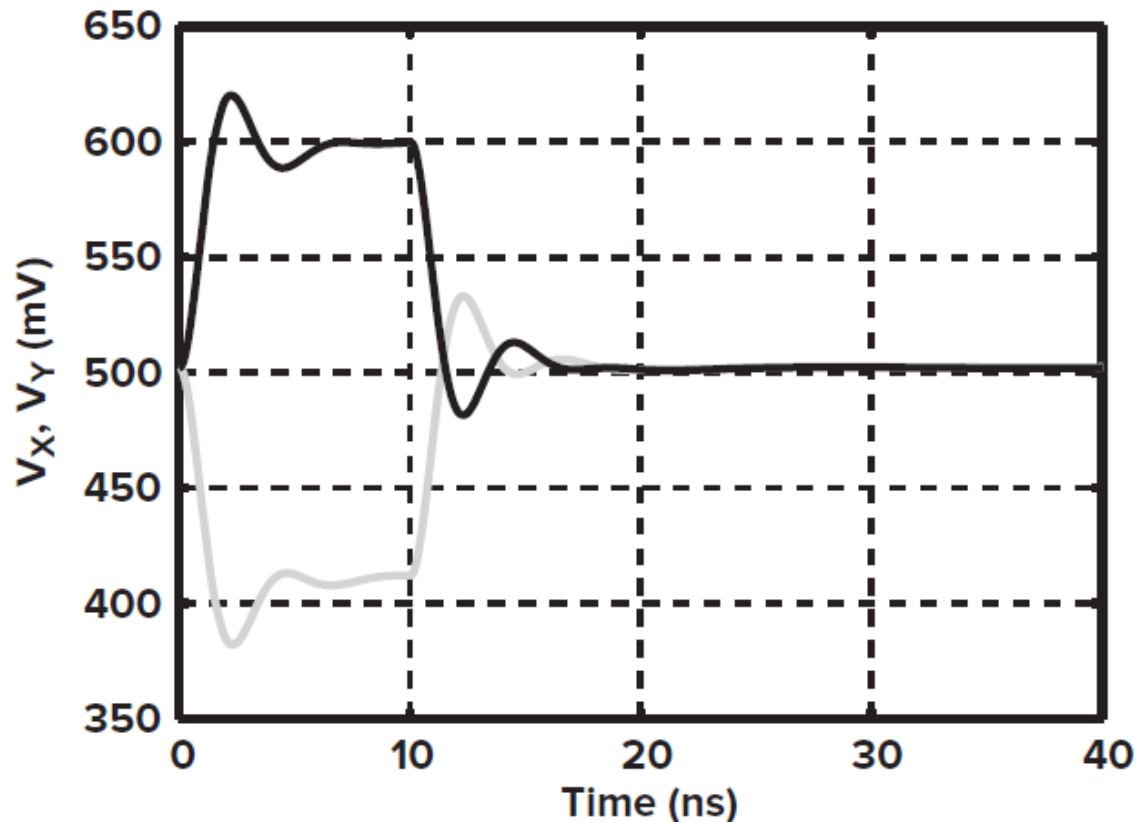- ❑ Transient analysis repeated → CMFB loop is stable
- ❑ But there is differential ringing?



CMFB Loop Stability

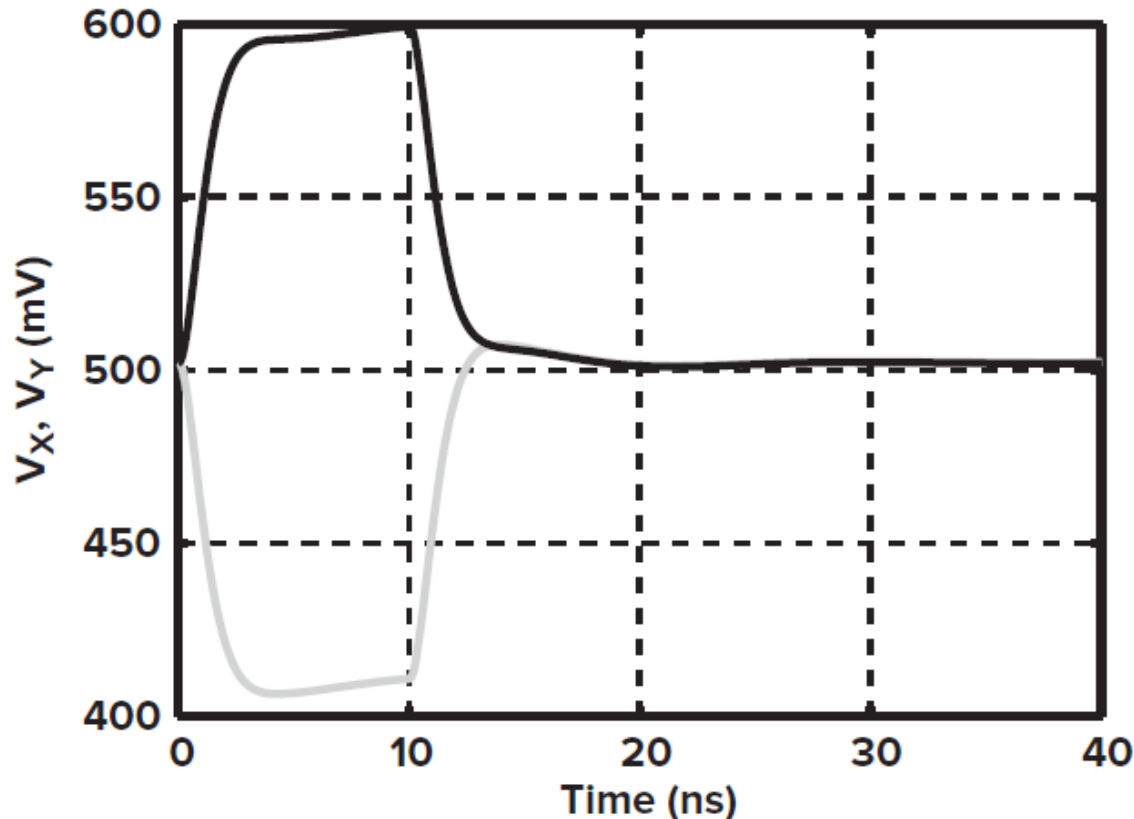
- ❑ The feedback resistance and the OTA input cap add a pole
- ❑ Fixed by adding small cap parallel with the large feedback resistance (usually required when using large feedback res)



Thank you!


CM Sensing: Source Followers

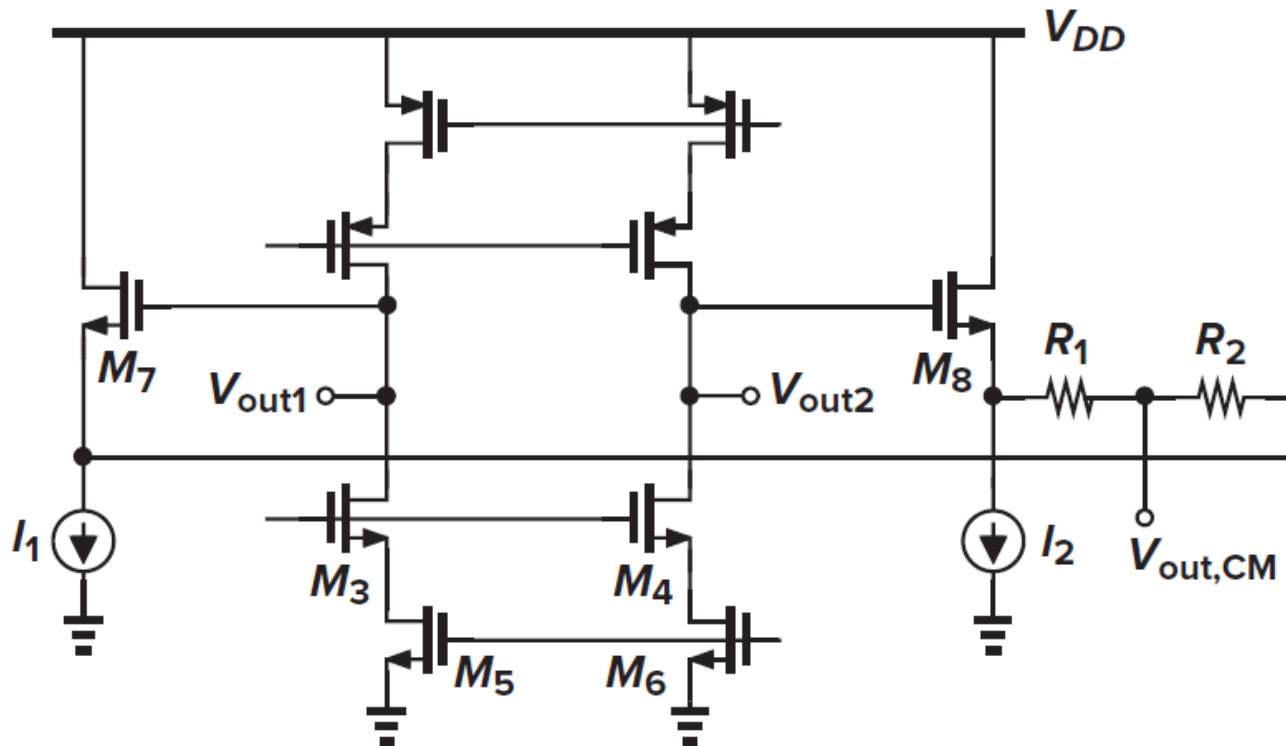- Voltage shift can be taken into account in the comparison step




CM Sensing: Source Followers

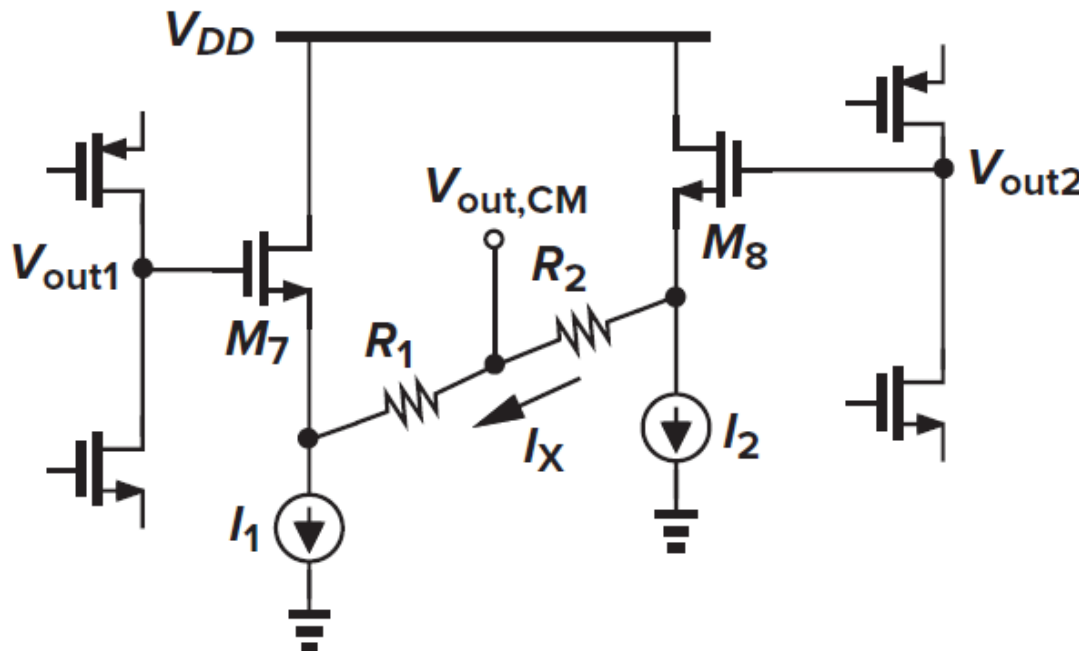- ❑ R_1 and R_2 or I_1 and I_2 must be large enough to ensure that M_7 or M_8 is not “starved” when a large differential swing appears at the output
- ❑ If $V_{out2} \gg V_{out1}$
 - I_1 must sink both $I_X \approx (V_{out2} - V_{out1})/(R_1 + R_2)$ and I_{D7} .
 - If $R_1 + R_2$ or I_1 is not sufficiently large: I_{D7} drops to zero




CM Sensing: Source Followers

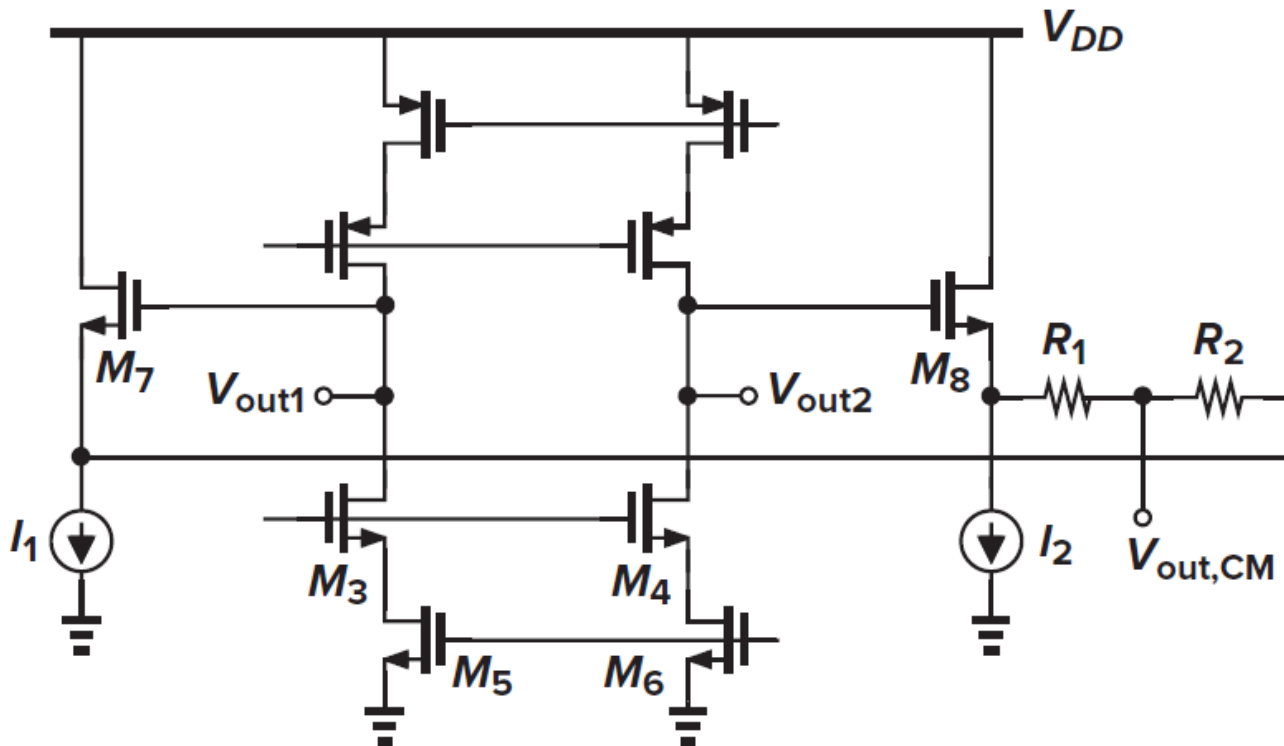- ❑ Output swing is reduced
 - Without CMFB: $V_{out,min} = V_{ov3} + V_{ov5}$
 - With CMFB: $V_{out,min} = V_{TH} + V_{ov7} + V_{I1}$




CM Sensing: Deep Triode
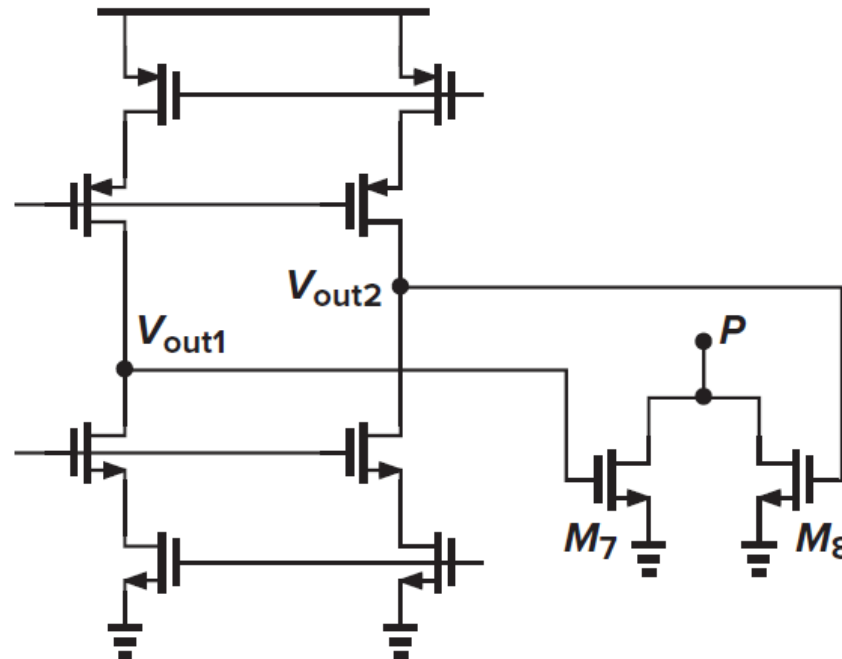
$$\begin{aligned}
 R_{tot} &= R_{on7} \parallel R_{on8} \\
 &= \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{out1} - V_{TH})} \parallel \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{out2} - V_{TH})} \\
 &= \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{out2} + V_{out1} - 2V_{TH})}
 \end{aligned}$$




CM Sensing: Deep Triode

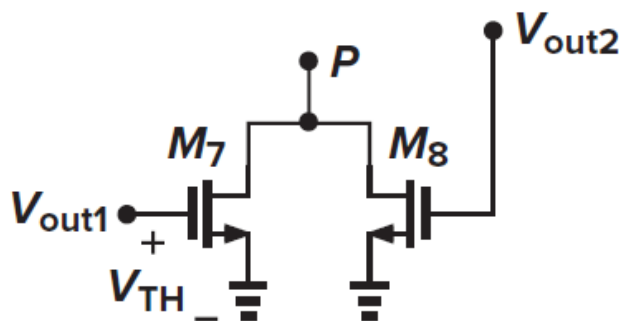- ❑ If the assumption of deep triode is invalid, R_{tot} will be function of the individual values of V_{out1} and V_{out2}
 - If V_{out1} approaches V_{TH} (V_{ov} is very small) M_7 will enter sat
 - CM sensing becomes nonlinear and dependent on the individual values of V_{out1} and V_{out2}



CMFB Techniques

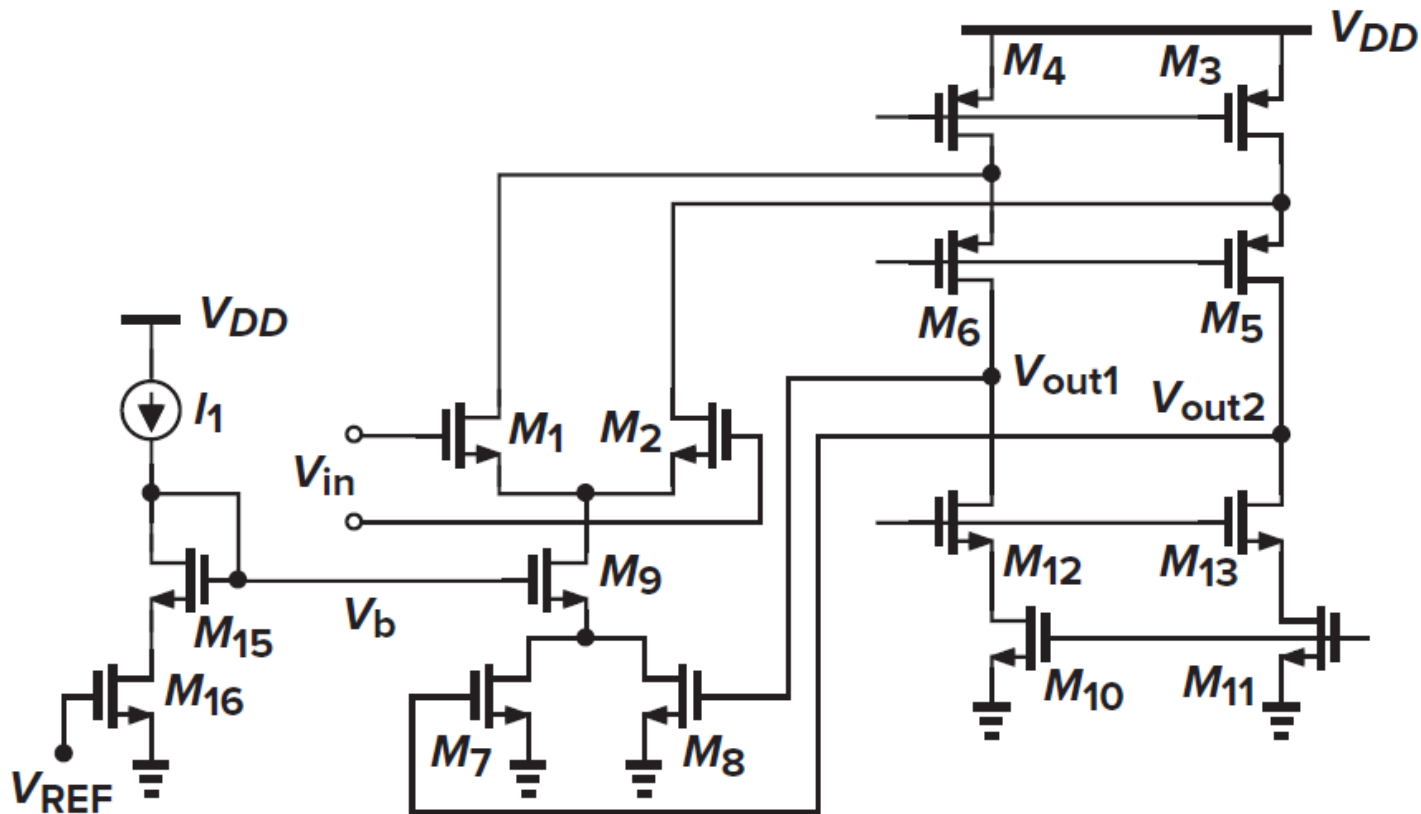- Sensing by deep triode devices
- $(W/L)_{15} = (W/L)_9$ and $(W/L)_{16} = (W/L)_7 + (W/L)_8$
- $I_{D9} = I_{D15}$ if $V_{out,CM} = V_{REF}$



Continuous Time vs Discrete Time CMFB

- ❑ Resistive sensing → Low voltage gain
- ❑ Source followers or deep triode → Limited linear range
- ❑ All the previous techniques are continuous-time CMFB circuits
- ❑ Designing continuous-time (CT) CMFB circuits that are both linear and operate with low power-supply voltages is not an easy task
 - Actually it is an area of continuing research!
- ❑ Another technique that is currently very popular is using switched-capacitor circuits
 - But the circuit must be refreshed periodically
 - Suitable for discrete time switched-capacitor circuits
 - Discrete time (DT) CMFB

Switched Capacitor CMFB

- ❑ Reset phase: S_1 , S_4 , and S_5 close
 - Capacitor charged to $V_{CM} - V_{GS6}$
- ❑ Amplification phase: S_2 and S_3 close
 - $V_{outCM} = V_C + V_{GS5} = V_{CM} - V_{GS6} + V_{GS5} \approx V_{CM}$

