

## Analog IC Design

### Lab 01

#### LPF Simulation and MOSFET Characteristics

## Part 1: Low Pass Filter Simulation (LPF)

### 1. Transient Analysis

- Design a first order low pass filter that has  $R = 1k\Omega$  and 1ns time constant.
- Apply a square wave input with  $T_{high} = T_{low} = 5ns$  and  $T_{rise} = T_{fall} = 100ps$ .
- Report transient analysis results for two periods (use max time step =  $T_{clk}/100$ ).
- Calculate rise and fall time (10% to 90%) using waveforms calculator.
- Compare simulation with analytical results in a table.
- Do parametric sweep for  $R = 1: 1: 5k\Omega$ . Report overlaid results. Comment on the results.

### 2. AC Analysis

- Report Bode Plot (magnitude and phase) for the previous LPF.
- Calculate DC gain and 3dB bandwidth using calculator expressions.
- Compare simulation with analytical results in a table.
- Do parametric sweep for  $R = 1, 10, 100, 1000k\Omega$ . Report overlaid results. Comment on the results.

### 3. Pole Zero Analysis

- Report pole zero analysis results from the AMS results browser.
- Find the pole frequency and compare it with the bandwidth calculated from AC analysis.

## Part 2: MOSFET Characteristics

### 1. ID vs VGS

- Plot  $I_D - V_{GS}$  characteristics for NMOS device. Set  $V_{DS} = V_{DD}$ , and  $V_{GS} = 0: 10m: V_{DD}$ . Plot the results overlaid for the following:
  - Short channel device:  $W = 1\mu m$  and  $L = 200nm$
  - Long channel device:  $W = 10\mu m$  and  $L = 2\mu m$ .
- Comment on the differences between short channel and long channel results.
  - Which one has higher current? Why?
  - Is the relation linear or quadratic? Why?
- Repeat for PMOS device. Comment on the differences between NMOS and PMOS.
  - Which one has higher current? Why?
  - What is the ratio between NMOS and PMOS currents?

## 2. $g_m$ vs $V_{GS}$

- a. Plot  $g_m$  vs  $V_{GS}$  for NMOS device. Set  $V_{DS} = V_{DD}$ , and  $V_{GS} = 0:10m:V_{DD}$ . Plot the results overlaid for the following:
  - Short channel device:  $W = 1\mu m$  and  $L = 200nm$
  - Long channel device:  $W = 10\mu m$  and  $L = 2\mu m$ .
- b. Comment on the differences between short channel and long channel results.
  - Does  $g_m$  increase linearly? Why?
  - Does  $g_m$  saturate? Why?

## 3. $I_D$ vs $V_{DS}$

- a. Plot  $I_D - V_{DS}$  characteristics for NMOS device. Set  $V_{DS} = 0:10m:V_{DD}$ , and  $V_{GS} = 0:0.2:V_{DD}$  (nested sweep). Plot the results overlaid for the following:
  - Short channel device:  $W = 1\mu m$  and  $L = 200nm$
  - Long channel device:  $W = 10\mu m$  and  $L = 2\mu m$ .
- b. Comment on the differences between short channel and long channel results.
  - Which one has higher current? Why?
  - Which one has higher slope in the saturation region? Why?
- c. Repeat for PMOS device. Comment on the differences between NMOS and PMOS.
  - Which one has higher current? Why?
  - What is the ratio between NMOS and PMOS currents?

## 4. $g_m$ and $r_o$ in Triode and Saturation

- a. Plot  $g_m$  and  $r_o$  vs  $V_{DS}$  for NMOS device. Use  $W = 10\mu m$  and  $L = 2\mu m$ ,  $V_{DS} = 0:10m:V_{DD}$ , and  $V_{GS} = V_{DD}$ .
- b. Comment on the variation of  $g_m$  vs  $V_{DS}$ .
  - In the first part of the curve, is the relation linear? Why?
  - Does  $g_m$  saturate? Why?
  - Where do you want to operate the transistor for analog amplifier applications?
- c. Comment on the variation of  $r_o$  vs  $V_{DS}$ .
  - Does  $r_o$  saturate? Why?
  - Where do you want to operate the transistor for analog amplifier applications?