

وَمَا أُوتِيتُمْ مِنَ الْعِلْمِ إِلَّا قَلِيلًا

Analog IC Design

Lecture 14


Negative Feedback

Dr. Hesham A. Omran

Integrated Circuits Lab (ICL)
Electronics and Communications Eng. Dept.
Faculty of Engineering
Ain Shams University

General Feedback System

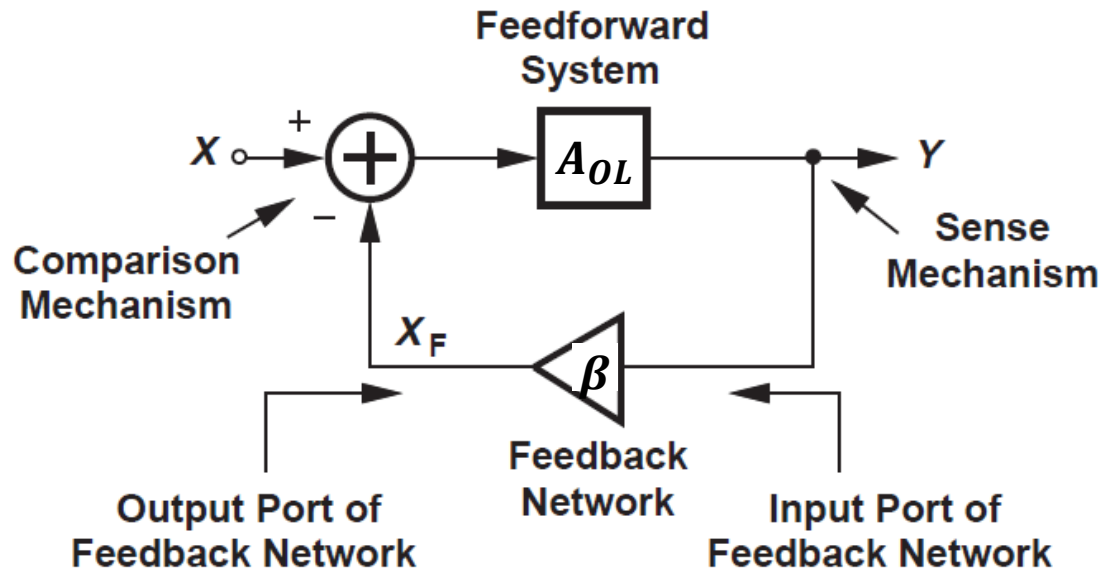
- ❑ A_{OL} = Open loop (OL) gain $\gg 1$
- ❑ $A_{CL} = \frac{Y}{X} =$ Closed loop (CL) gain
- ❑ Error signal = $X - X_F$



General Feedback System

- ❑ A_{OL} = Open loop (OL) gain $\gg 1$
- ❑ $A_{CL} = \frac{Y}{X} =$ Closed loop (CL) gain
- ❑ Error signal = $X - X_F$

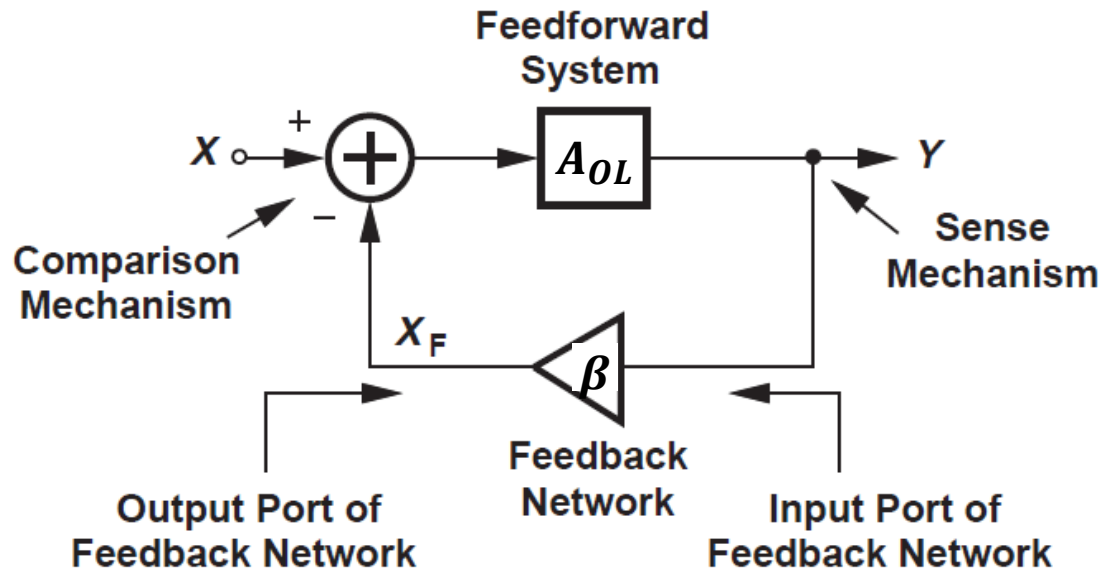
$$Y = A_{OL}(X - X_F) = A_{OL}(X - \beta Y)$$
$$A_{CL} = \frac{Y}{X} = \frac{A_{OL}}{1 + \beta \cdot A_{OL}} \approx \frac{1}{\beta}$$



Feedback Example

- ❑ Op-amp A_{OL} performs two functions: (1) subtraction of X and X_F and (2) amplification
- ❑ The network R_1 and R_2 performs two functions: (1) sensing the output voltage and (2) providing a feedback factor $\beta = \frac{R_2}{(R_1 + R_2)}$
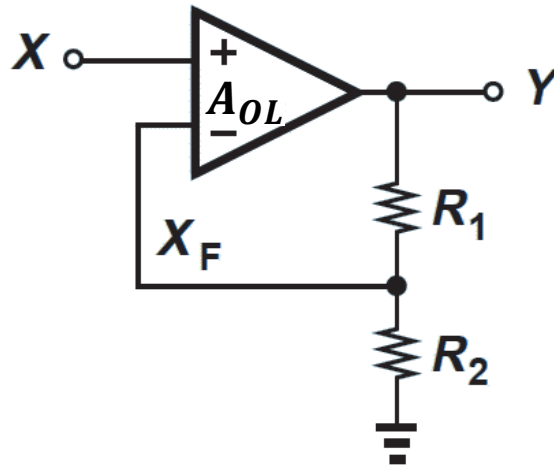
$$A_{CL} = \frac{Y}{X} = \frac{A_{OL}}{1 + \beta \cdot A_{OL}} = \frac{A_{OL}}{1 + \frac{R_2}{(R_1 + R_2)} \cdot A_{OL}} \approx \frac{R_1 + R_2}{R_2} = 1 + \frac{R_1}{R_2}$$





Feedback Example

- ❑ Negative feedback loop works to minimize the error signal



$$\text{Error} = E = X - X_F = X - \beta Y = X - \beta A_{OL} E$$
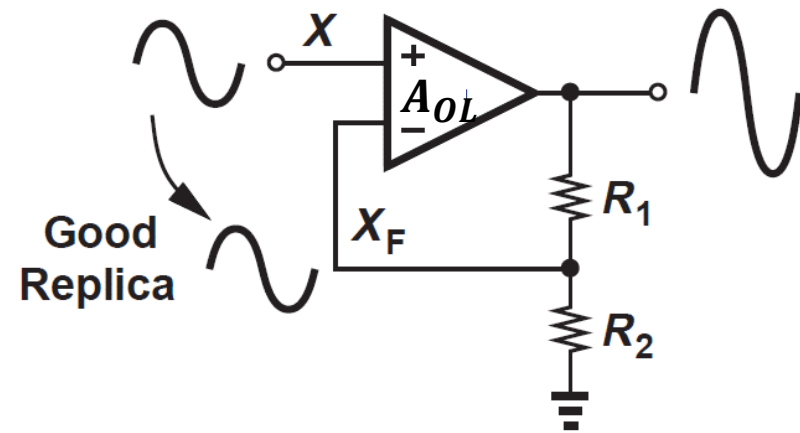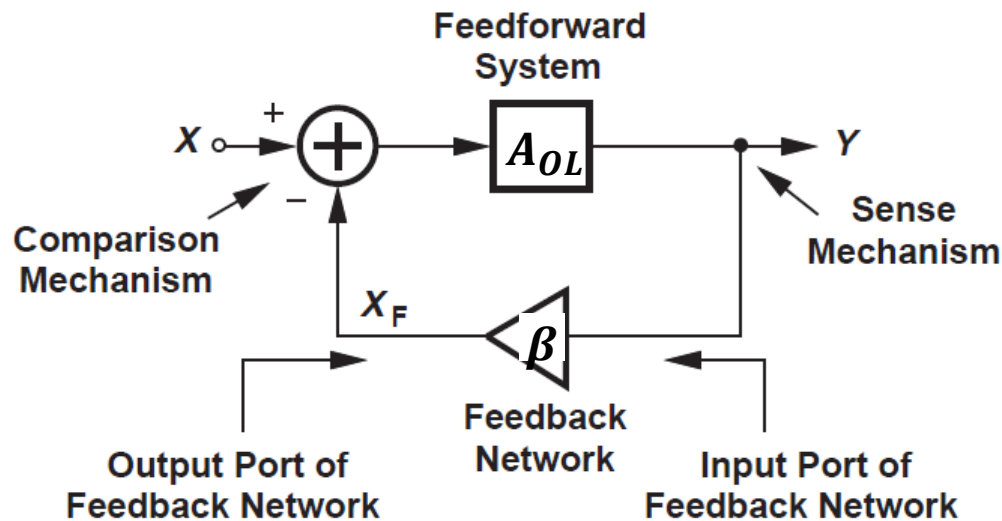
$$E = \frac{X}{1 + \beta A_{OL}} \rightarrow 0$$



Loop Gain

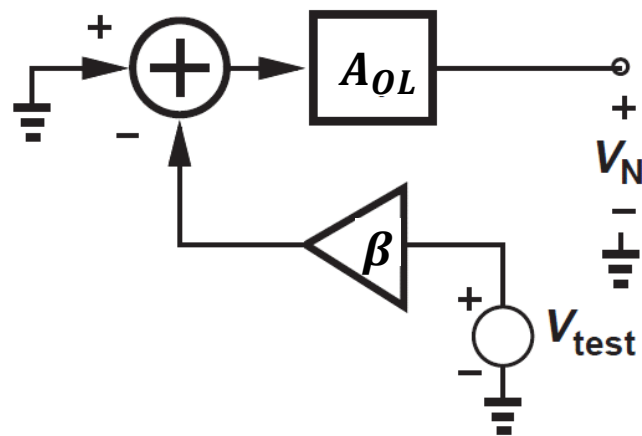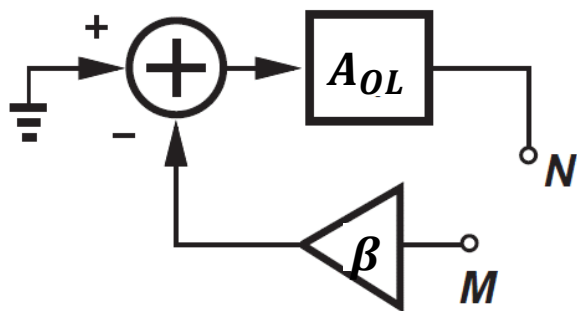- ❑ Break the loop \rightarrow Apply a test source \rightarrow Calculate the gain around the loop
- ❑ Loop gain $= \beta \cdot A_{OL}$
- ❑ But the loading changes when we break the loop!
 - We may add a dummy load
 - STB simulation takes care of this 😊



Why Negative Feedback?



- ❑ We use a very high gain amplifier (A_{OL}), but end up with a much smaller gain $\frac{A_{OL}}{1+\beta \cdot A_{OL}} \approx \frac{1}{\beta}$
- ❑ We can design high gain amplifiers, but we really do not need all that gain
- ❑ High gain is the balance that we use to buy other useful properties
- ❑ Negative feedback properties
 - Gain Desensitization → Accurate, stable, and linear gain
 - Bandwidth Extension
 - Modification of I/O Impedances

Gain Desensitization

- ❑ In IC design, we cannot control absolute values due to PVT, load, and input signal variations
- ❑ But we can precisely control ratios of MATCHED components

$$A_{CL} = \frac{Y}{X} = \frac{A_{OL}}{1 + \beta \cdot A_{OL}} = \frac{A_{OL}}{1 + \frac{R_2}{(R_1 + R_2)} \cdot A_{OL}} \approx \frac{R_1 + R_2}{R_2} = 1 + \frac{R_1}{R_2}$$

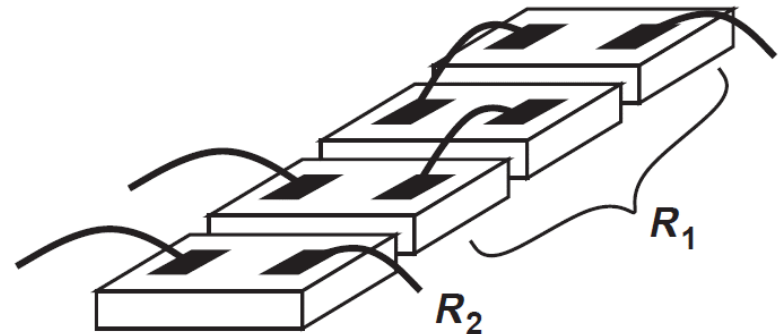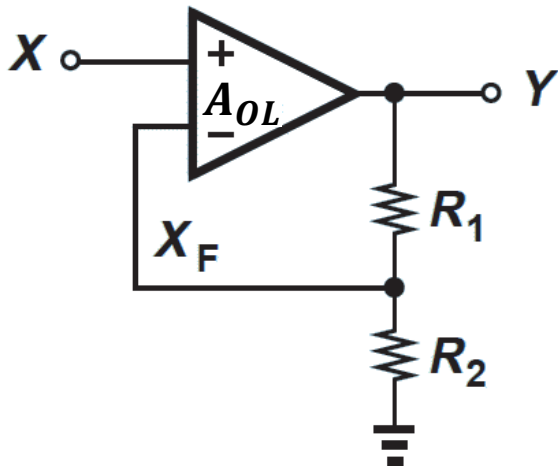- ❑ $R_1 = 3R$ and $R_2 = R \Rightarrow A_{CL} = 4 \Rightarrow$ Accurate, stable, and linear



Bandwidth Extension

$$A_{CL}(s) = \frac{A_{OL}(s)}{1 + \beta \cdot A_{OL}(s)}$$

$$A_{OL}(s) = \frac{A_o}{1 + \frac{s}{\omega_{p,OL}}}$$

$$A_{CL}(s) = \frac{\frac{A_o}{(1 + \beta A_o)}}{1 + \frac{s}{(1 + \beta A_o)\omega_{p,OL}}}$$


$$\omega_{p,CL} = (1 + \beta A_o)\omega_{p,OL}$$

- ❑ CL DC gain reduced by $(1 + \beta A_o)$
- ❑ CL bandwidth extended by $(1 + \beta A_o)$
- ❑ GBW (and UGF) remains constant

Bandwidth Extension



$$A_{CL}(s) = \frac{\frac{A_o}{(1 + \beta A_o)}}{1 + \frac{s}{(1 + \beta A_o)\omega_{p,OL}}}$$

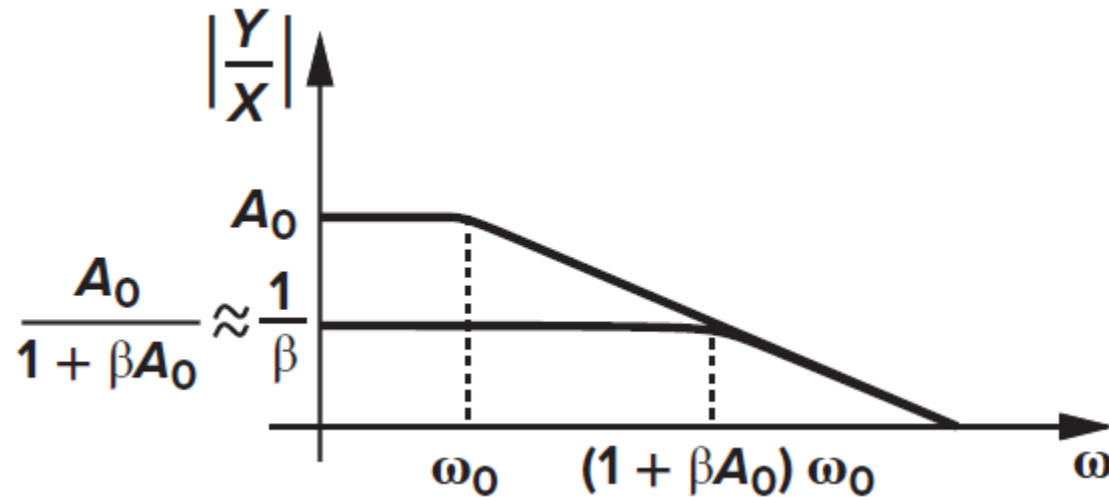- ❑ CL DC gain reduced by $(1 + \beta A_o)$
- ❑ CL bandwidth extended by $(1 + \beta A_o)$
- ❑ GBW (and UGF) remains constant



Bandwidth Extension

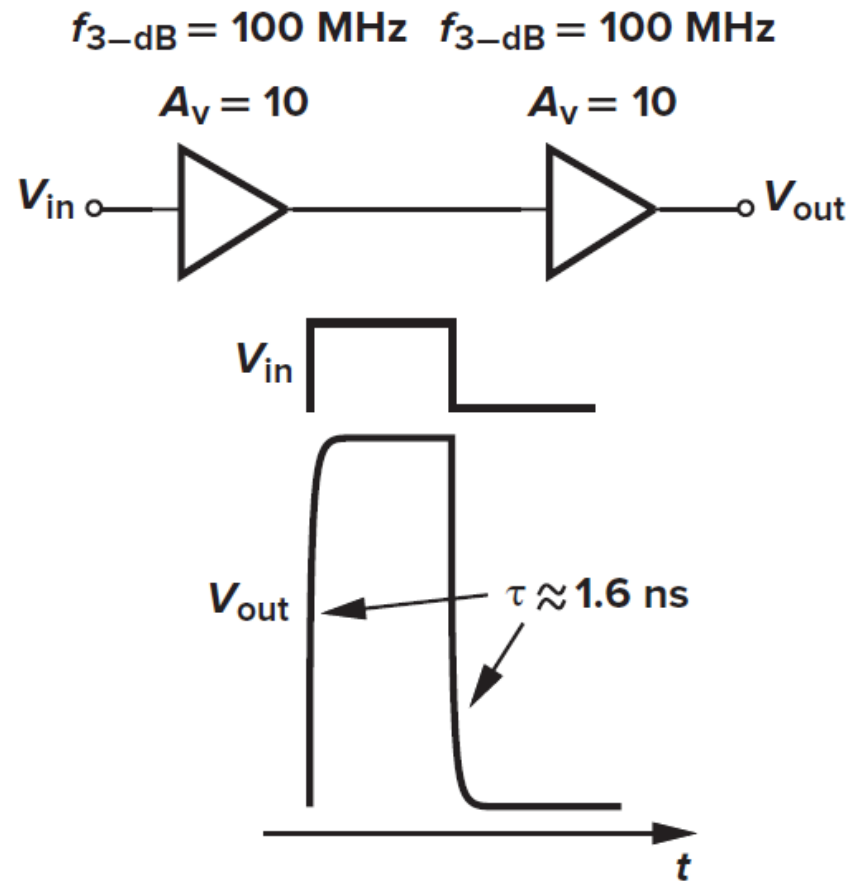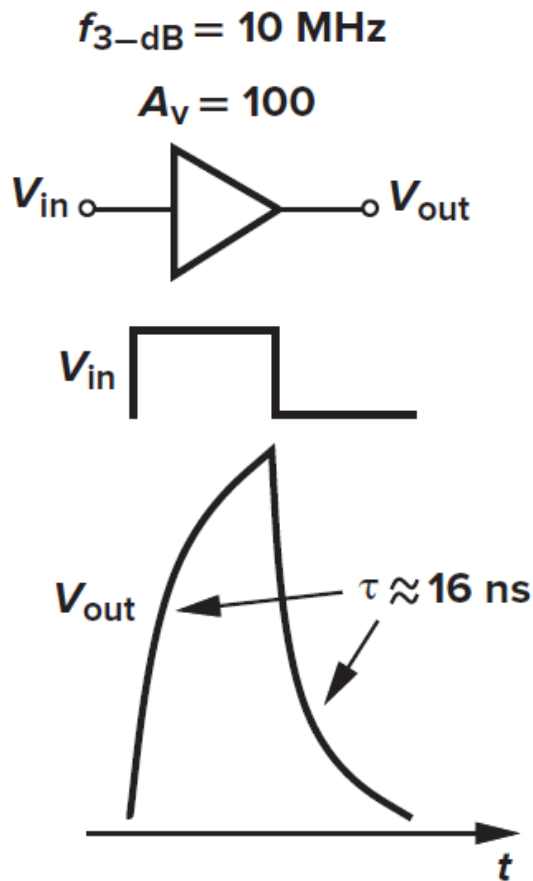- ❑ Cascade of feedback amplifiers provides the same gain and a much faster response → But power consumption is doubled





Modification of I/O Impedances

- Example: voltage sensing – voltage mixing feedback

$$I_{in}R_{in} = V_{in} - V_F$$

$$= V_{in} - (I_{in}R_{in})A_0\beta$$
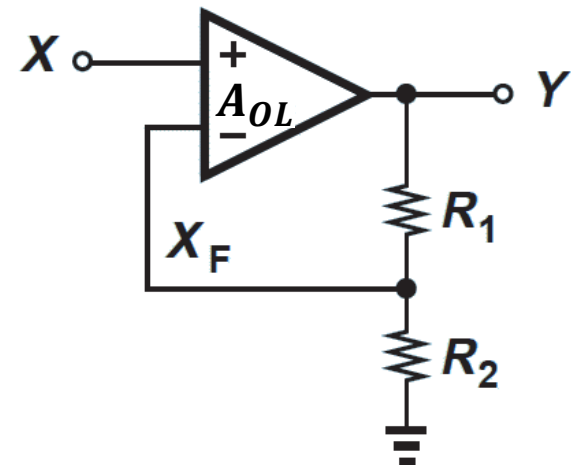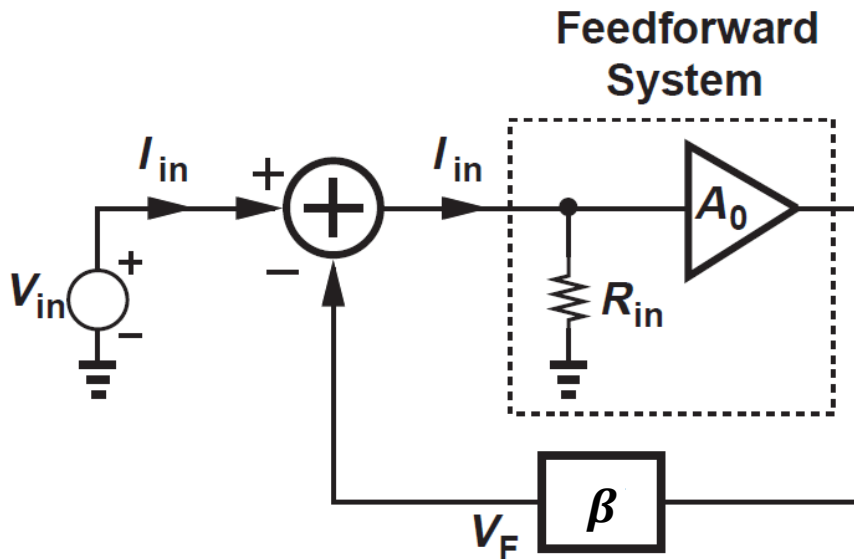
$$\frac{V_{in}}{I_{in}} = R_{in}(1 + \beta A_0)$$





Modification of I/O Impedances

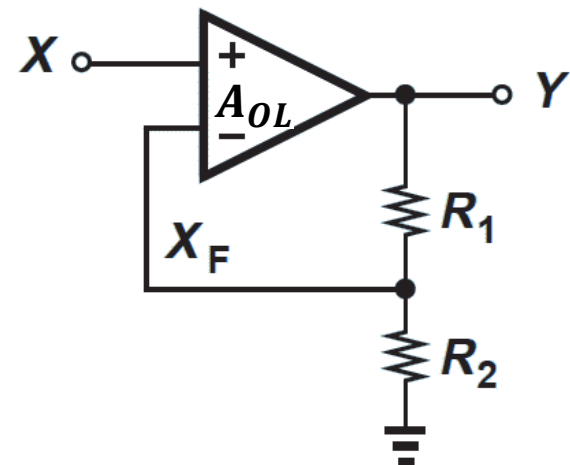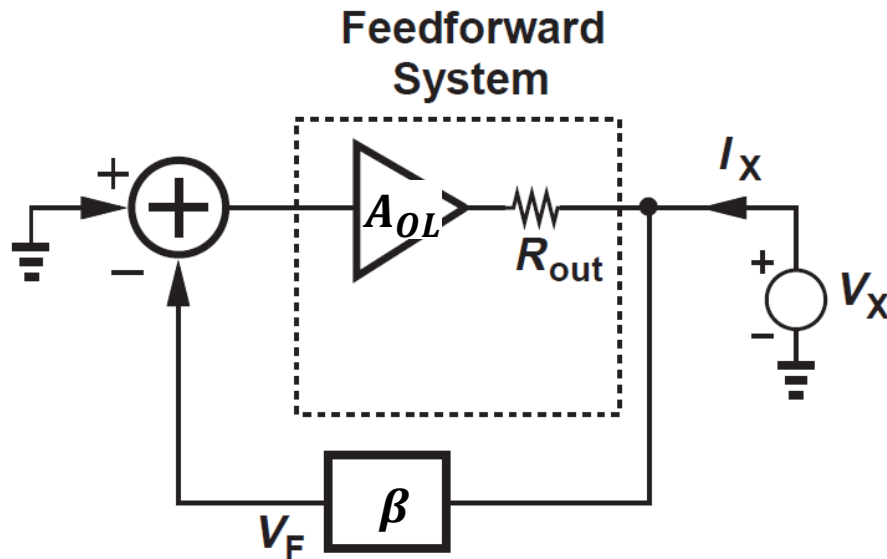- Example: voltage sensing – voltage mixing feedback


$$I_X = \frac{V_X - (-\beta A_0 V_X)}{R_{out}}$$

$$\frac{V_X}{I_X} = \frac{R_{out}}{1 + \beta A_0}$$




Modification of I/O Impedances

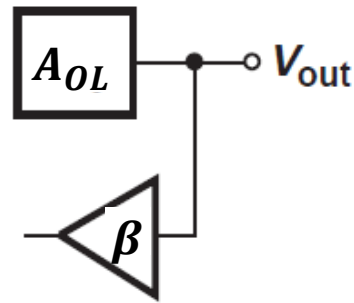
- ❑ Shunt sensing/mixing \rightarrow R decreases
- ❑ Series sensing/mixing \rightarrow R increases



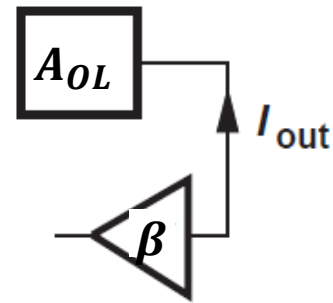
Output impedance falls by $1 + \text{loop gain}$.



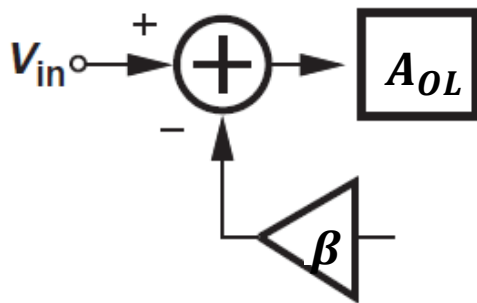Output impedance rises by $1 + \text{loop gain}$.



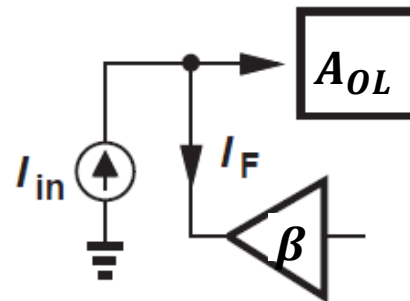
Input impedance rises by $1 + \text{loop gain}$.



Input impedance falls by $1 + \text{loop gain}$.

Stability of Feedback System

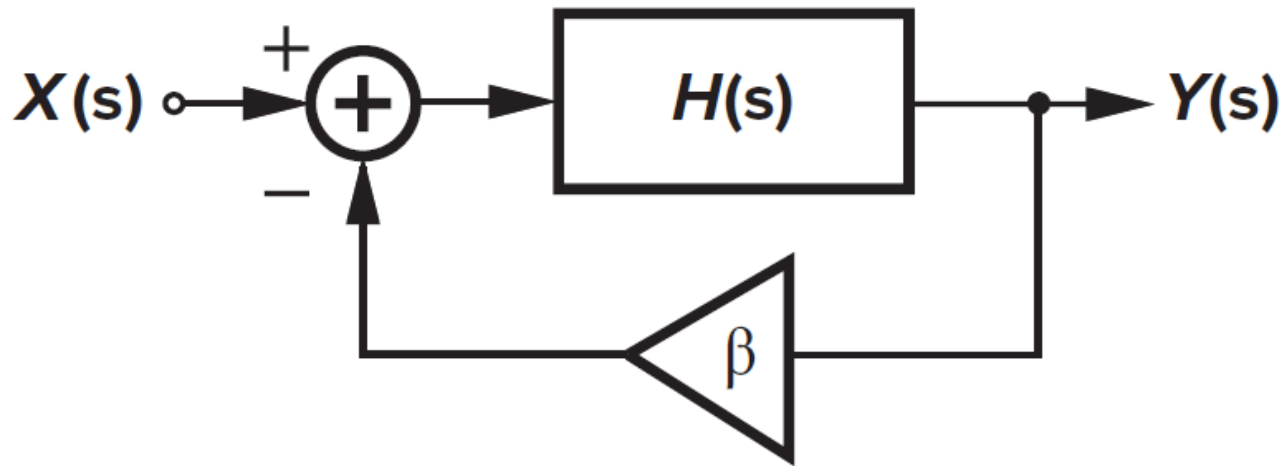
$$H_{CL}(s) = \frac{Y(s)}{X(s)} = \frac{H(s)}{1 + \beta H(s)}$$



Barkhausen's Oscillation Criteria



$$H_{CL}(s) = \frac{Y(s)}{X(s)} = \frac{H(s)}{1 + \beta H(s)}$$

$$|\beta H(s)| = 1$$
$$\angle \beta H(s) = -180$$



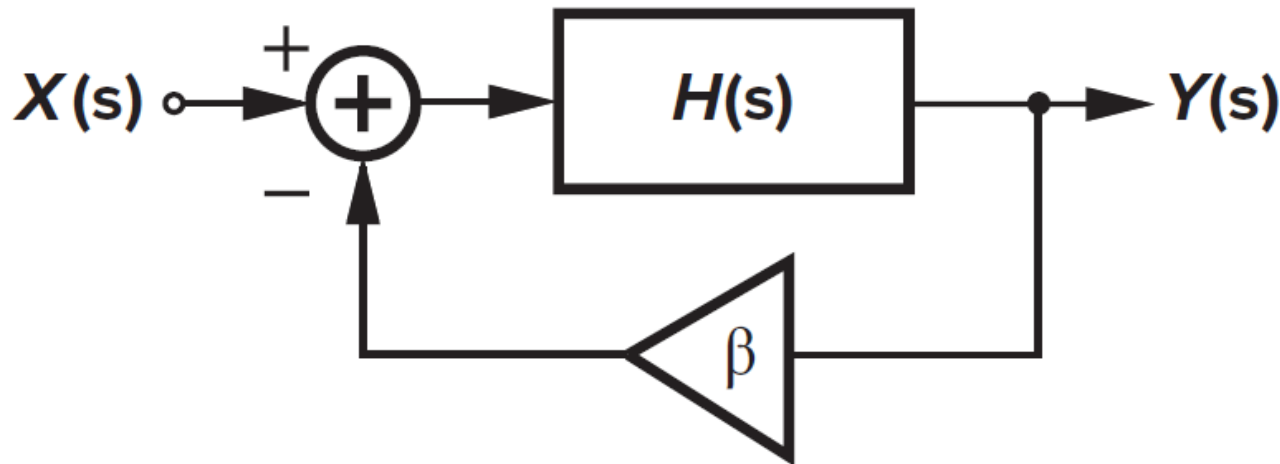


Stable vs Unstable System: Bode Plot

- ❑ Gain crossover frequency (GX): @ $|\beta H(s)| = 1$
- ❑ Phase crossover frequency (PX): @ $\angle \beta H(s) = -180^\circ$
- ❑ For a stable system: $GX < PX$

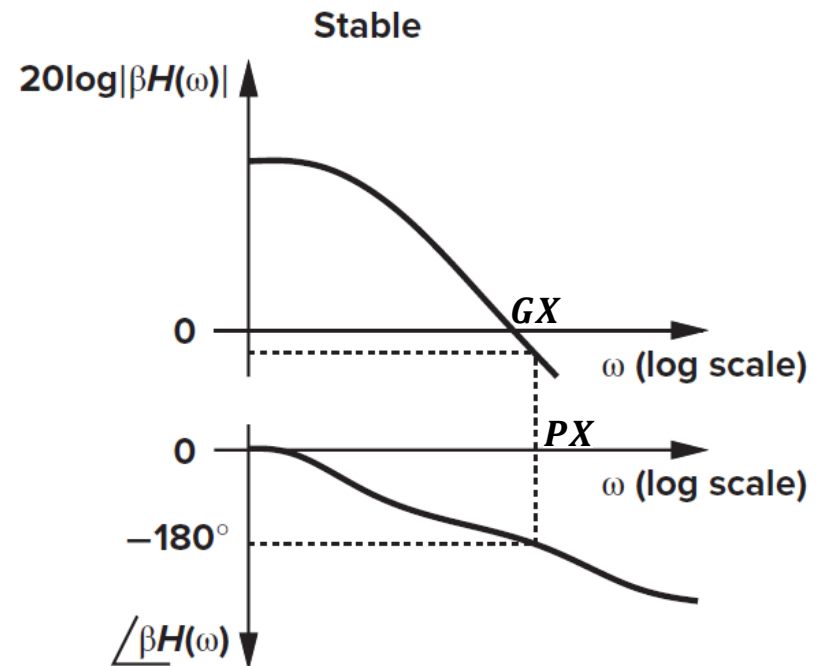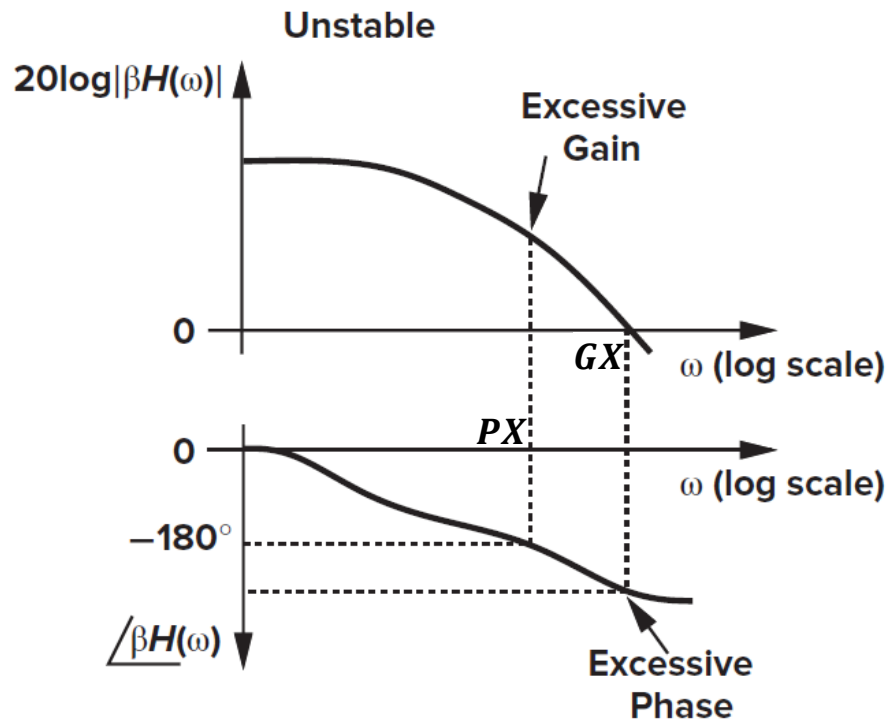


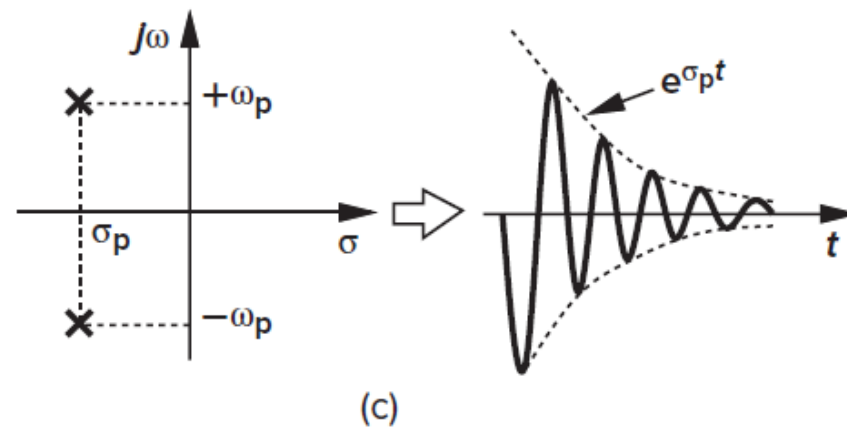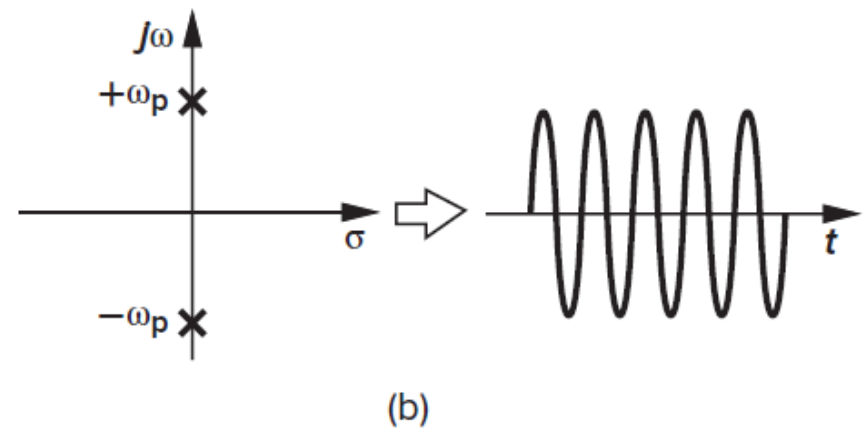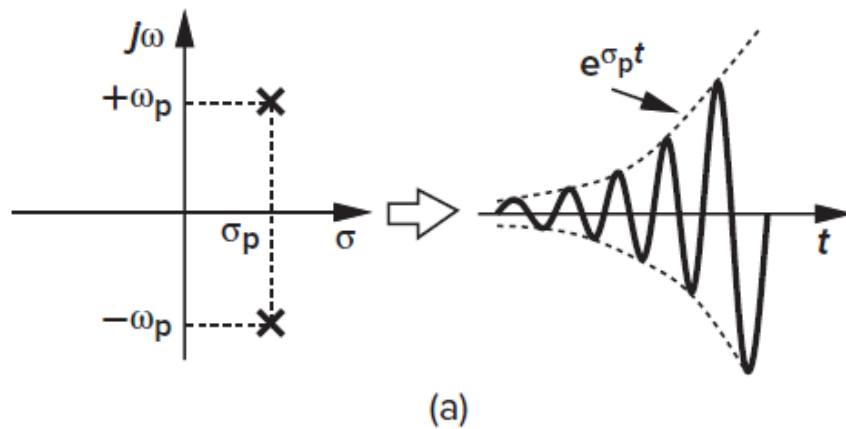Stable vs Unstable System: Pole-Zero Plot




Effect of Feedback Factor (β)

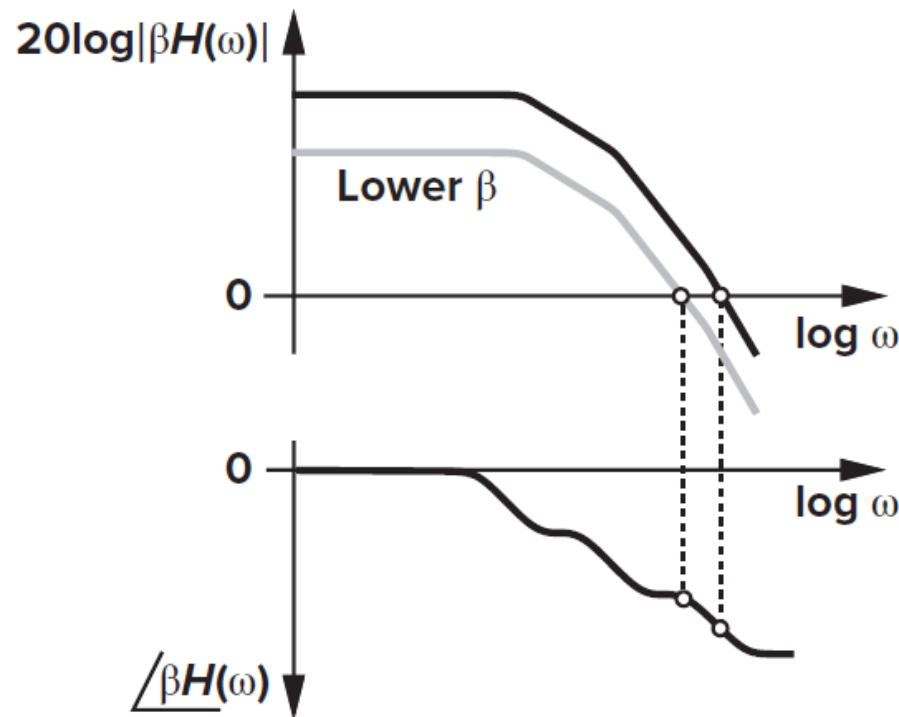- ❑ We assume β is independent of frequency: $\angle\beta H$ independent of β
- ❑ If we apply no feedback ($\beta = 0$), the circuit will never oscillate
- ❑ Worst-case stability corresponds to $\beta = 1 \rightarrow \beta H = H \rightarrow$ OL gain
 - Worst case for unity-gain feedback \rightarrow buffer \rightarrow smallest CL gain




Single-Pole System: Bode Plot
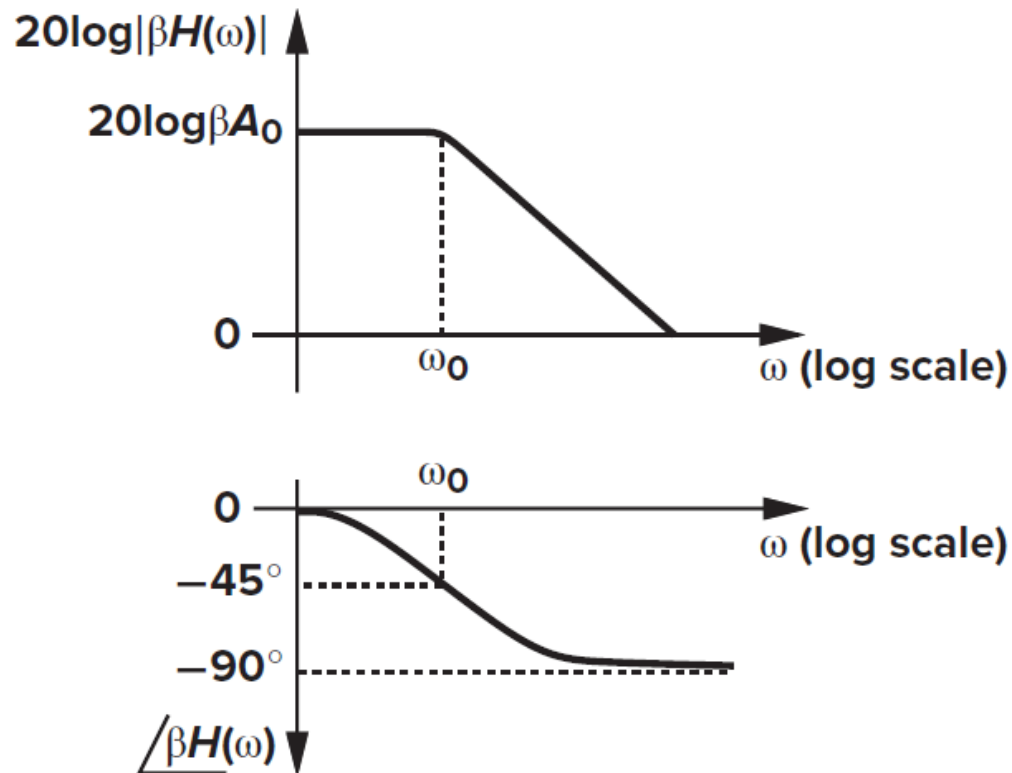
$$\frac{Y}{X}(s) = \frac{\frac{A_0}{1 + \beta A_0}}{1 + \frac{s}{\omega_0(1 + \beta A_0)}}$$




Single-Pole System: Root Locus

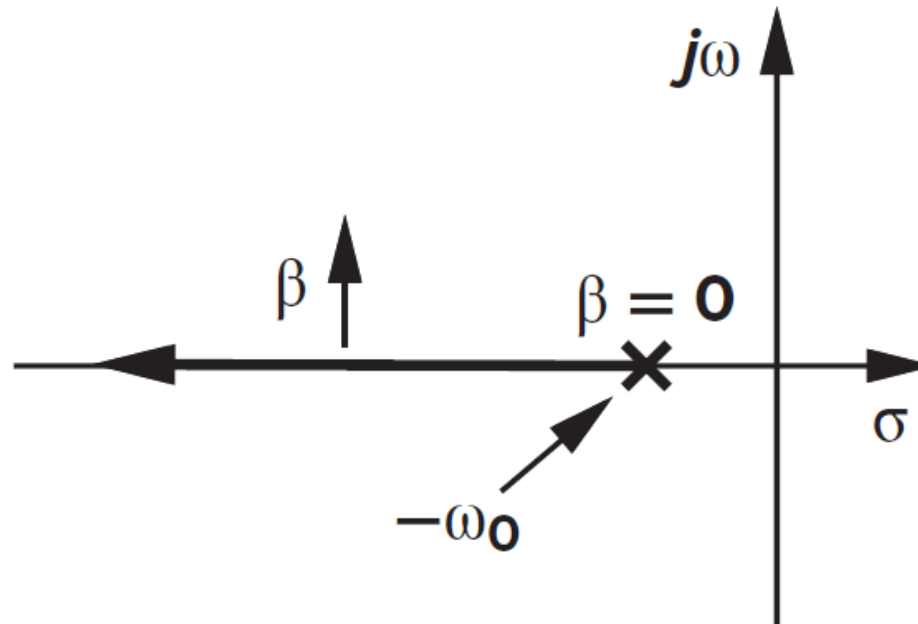- ❑ The locus exists on real axis to the left of an odd number of poles and zeros.
- ❑ The locus starts at the open-loop poles and end at the open-loop zeros or at infinity.




Two-Pole System: Bode Plot


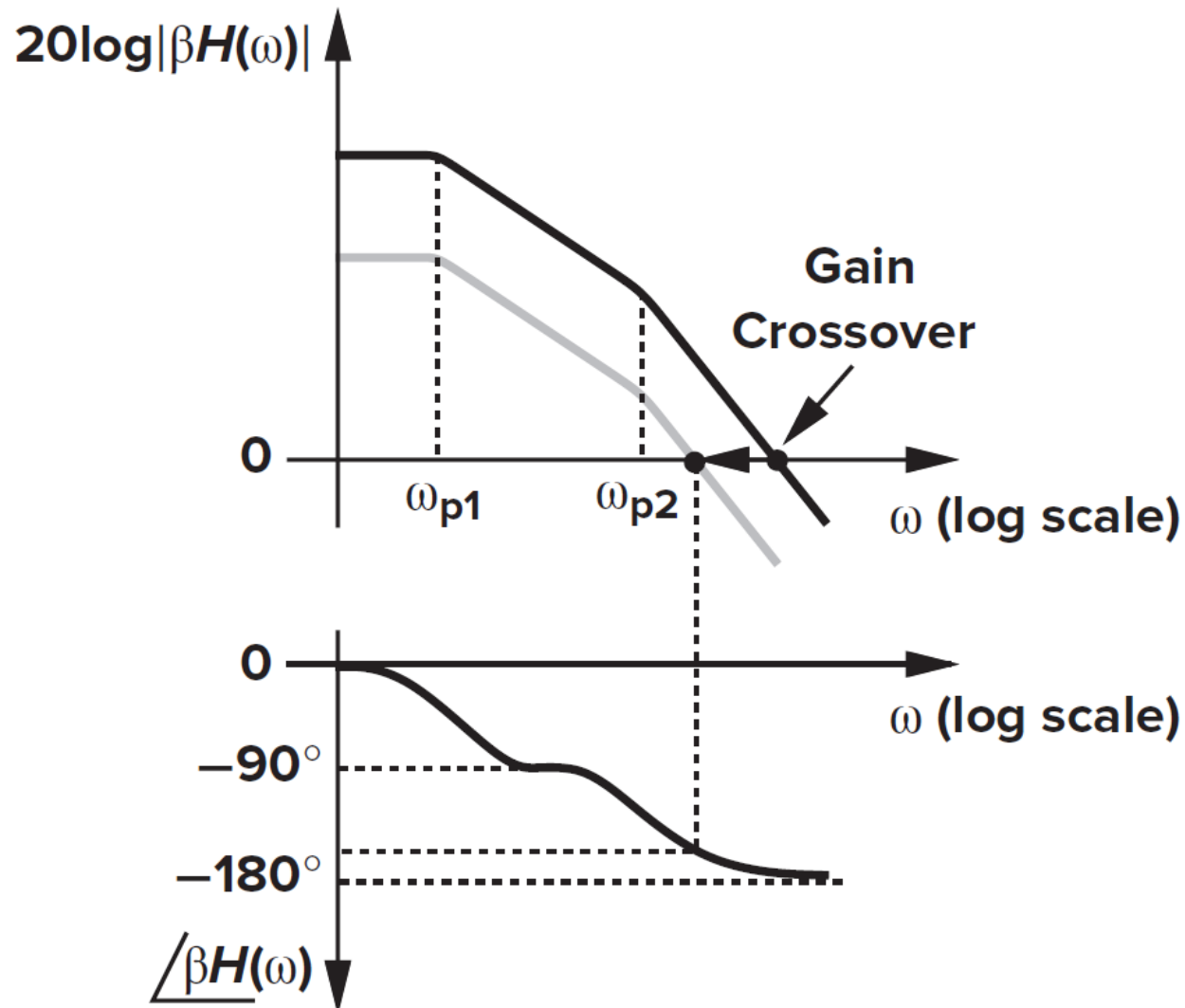


Two-Pole System: Root Locus

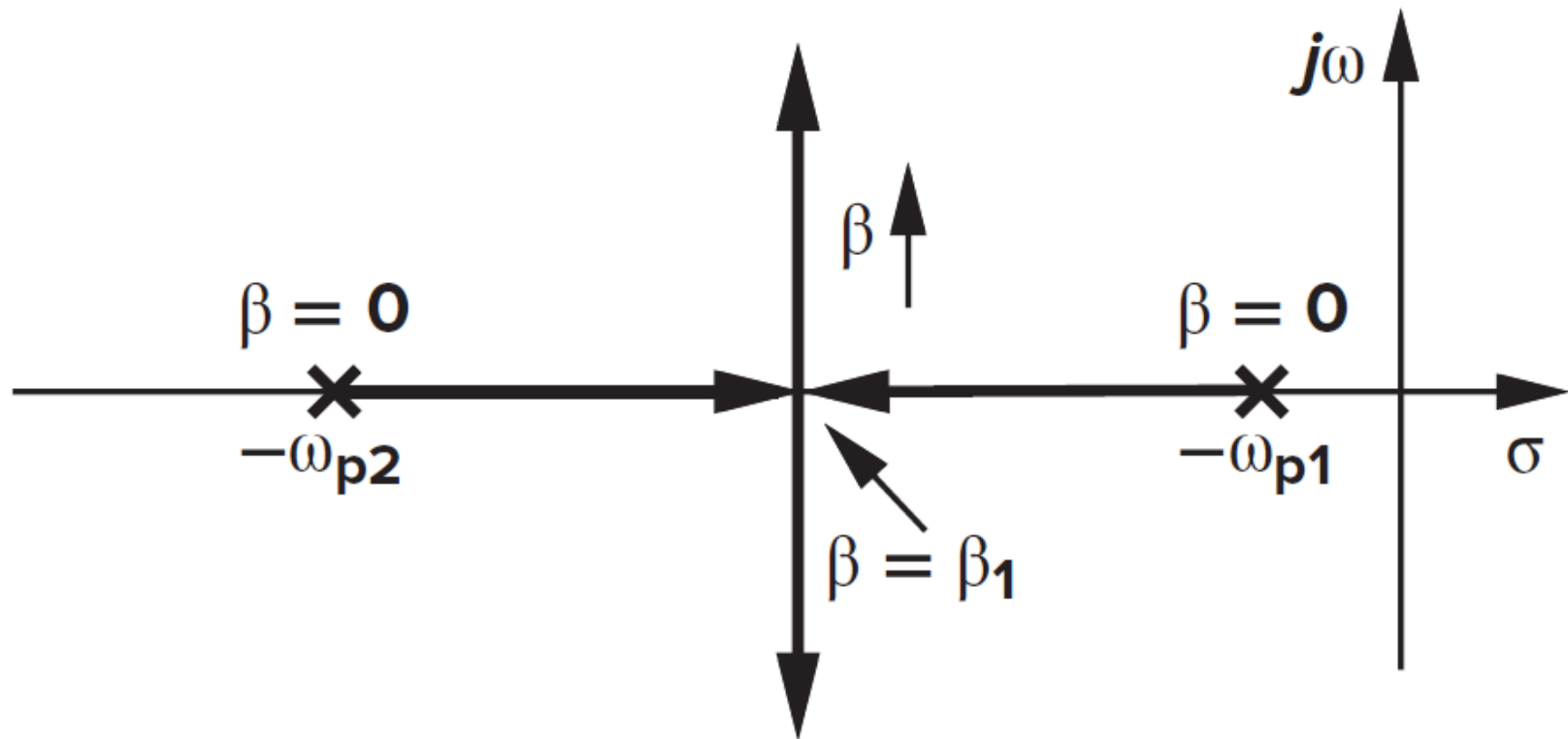- ❑ The locus exists on real axis to the left of an odd number of poles and zeros.
- ❑ The locus starts at the open-loop poles and end at the open-loop zeros or at infinity.





Three-Pole System

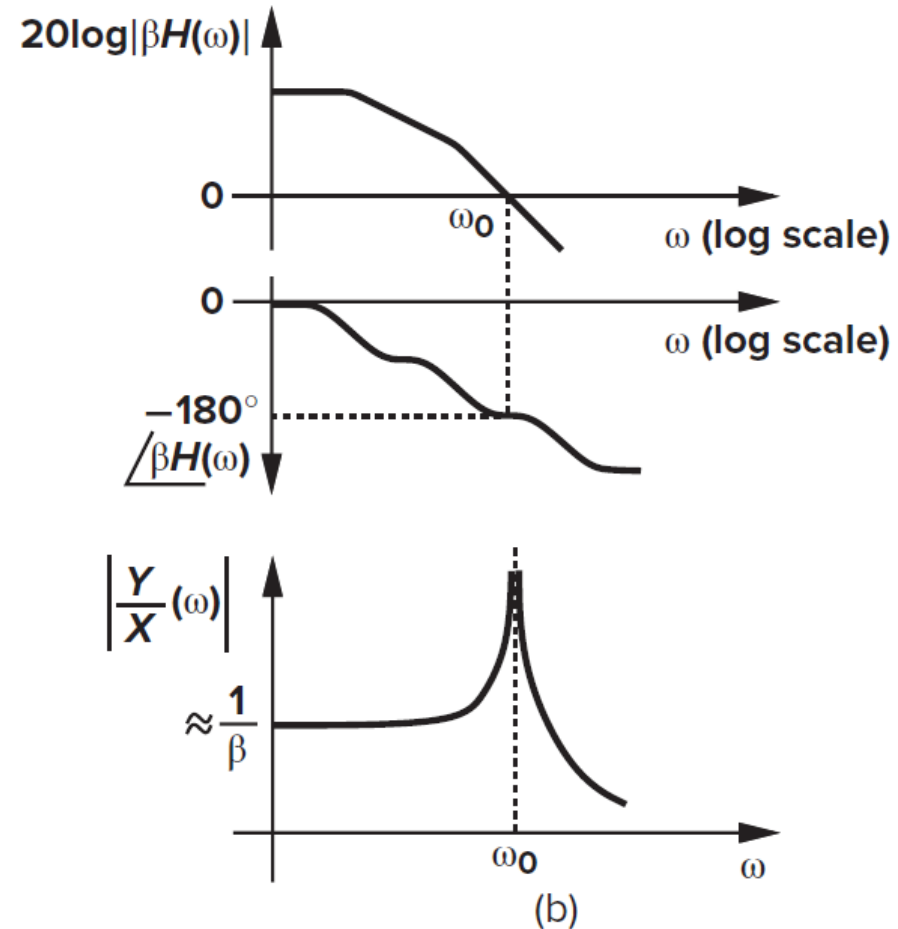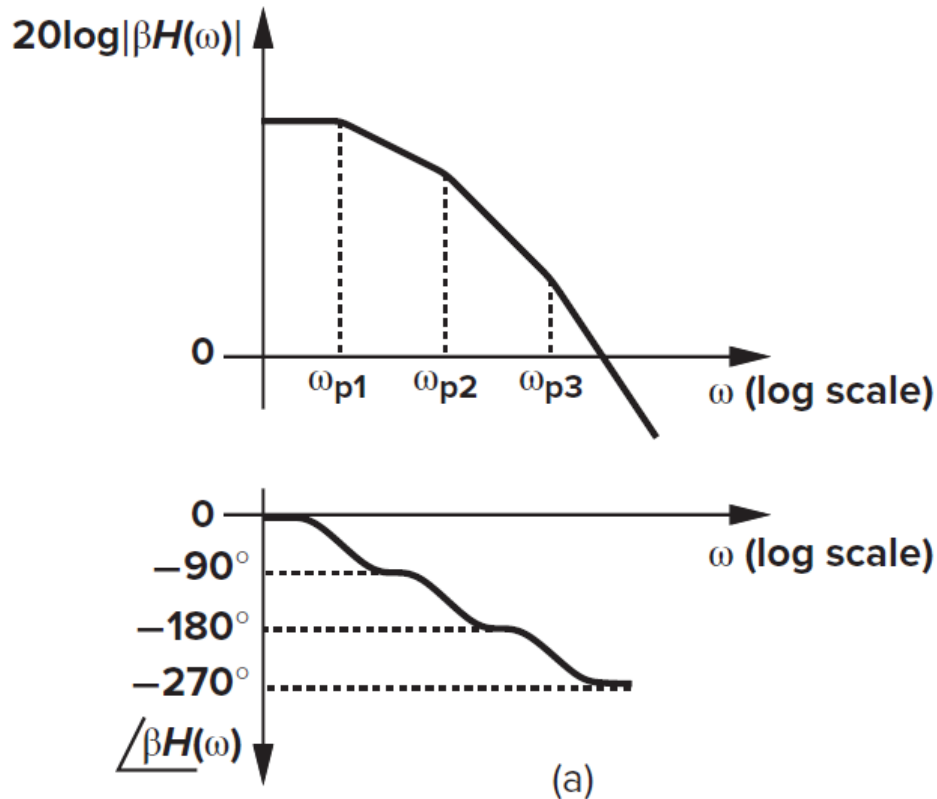

Phase Margin (PM)



□ $PM > 0 \rightarrow$ stable, but...

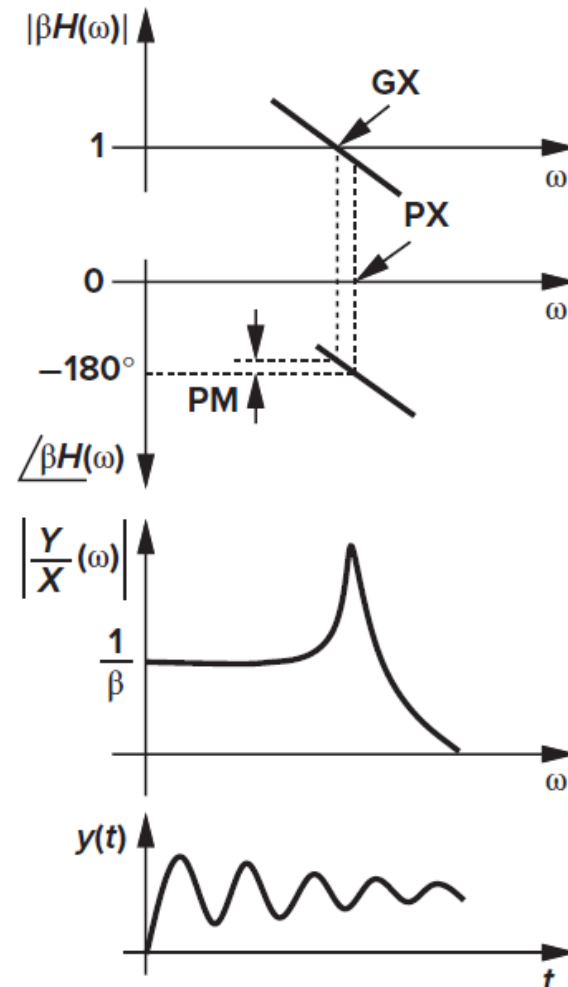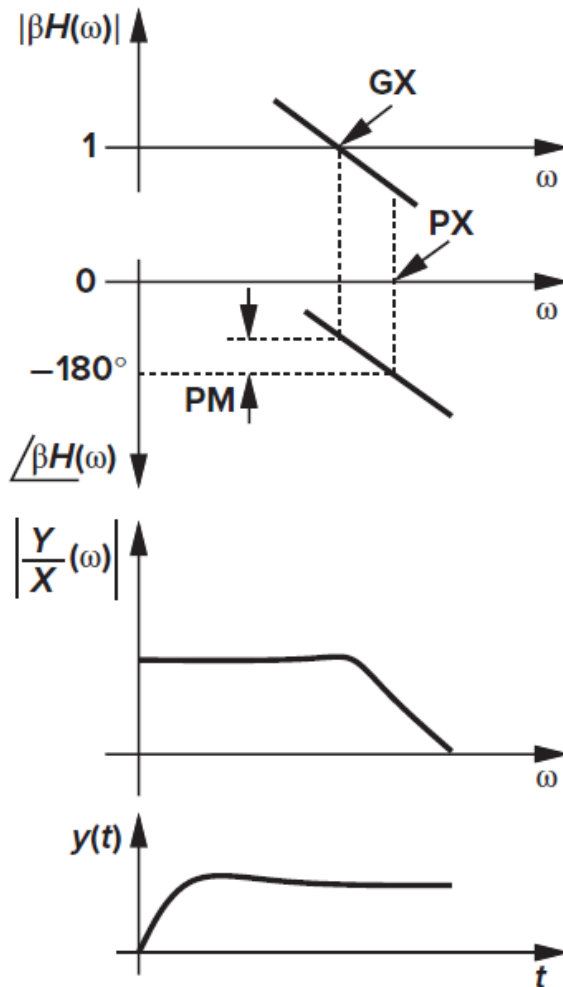- Low PM \rightarrow frequency domain peaking \rightarrow time domain ringing






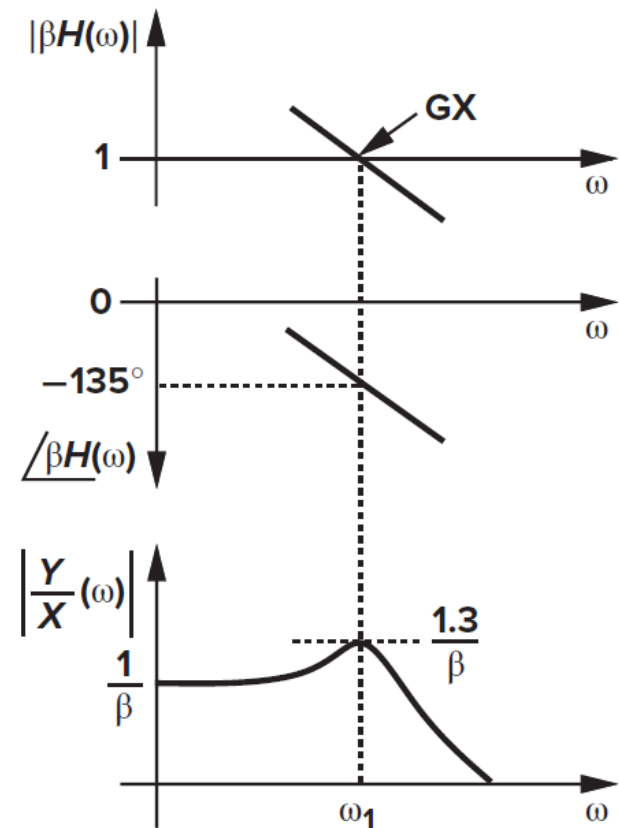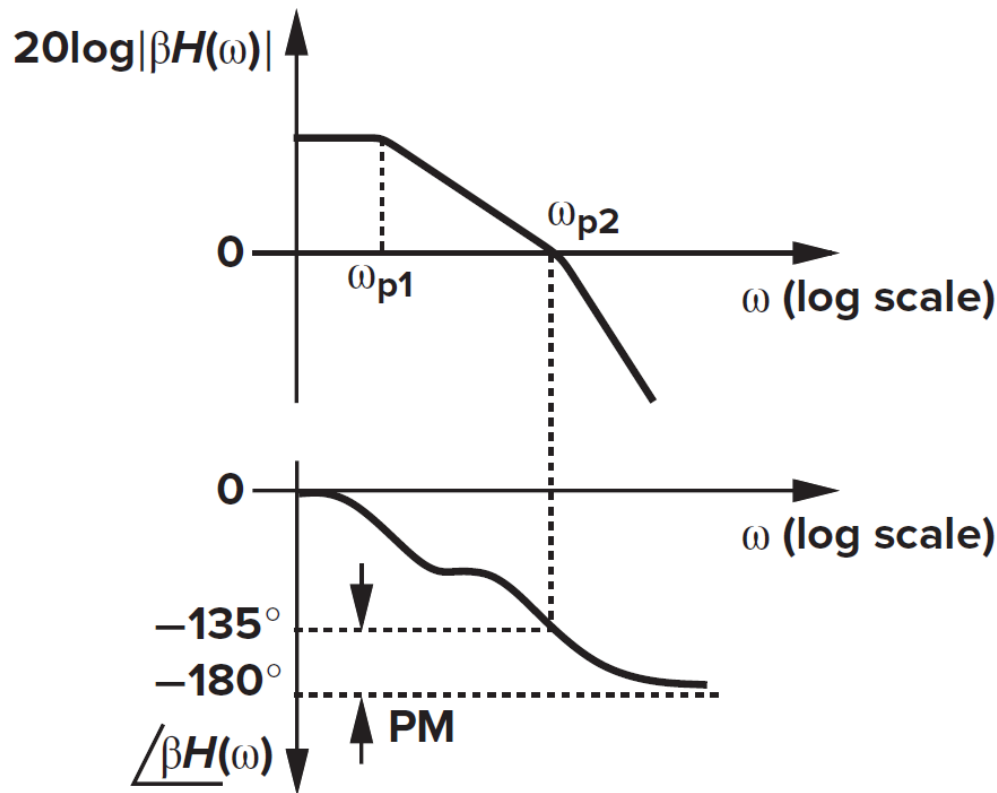

Phase Margin: Ultimate GBW

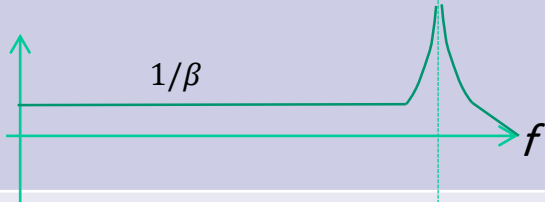- ❑ If $\omega_{p2} = \omega_u$: PM = $45^\circ \rightarrow$ typically inadequate (peaking/ringing)
- ❑ The ultimate ω_u cannot exceed $\omega_{p2} \rightarrow \omega_{p1} < \omega_u < \omega_{p2}$
 - For $\omega < \omega_u$ the Bode plot is similar to a 1st order system






Optimum Phase Margin

PM	Peaking	Closed Loop Response
0	∞	
5	$\frac{11.5}{\beta}$	
45	$\frac{1.3}{\beta}$	
60	$\frac{1}{\beta}$	
90	$\frac{0.707}{\beta}$	

Optimum Phase Margin

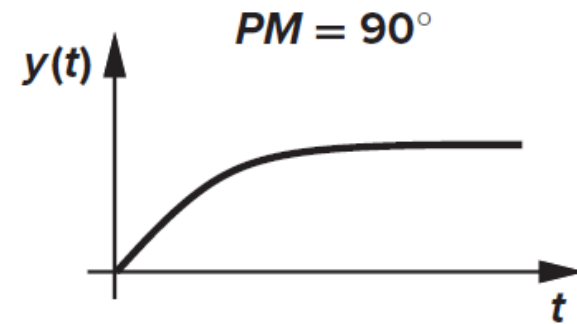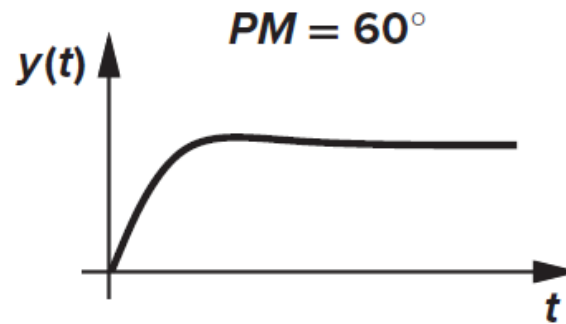
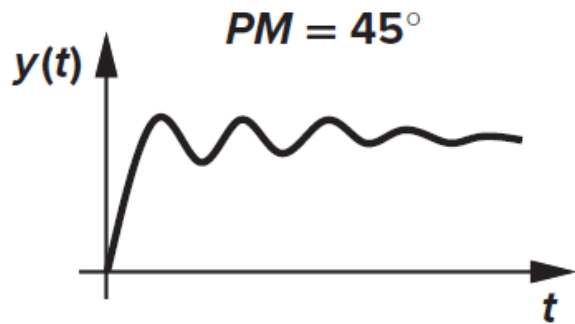
- ❑ PM = 60° is optimum
- ❑ But we must take some extra margin to account for variations



ω_{p2}/ω_u	PM
1	45°
2	60°
3	72°

Frequency Compensation

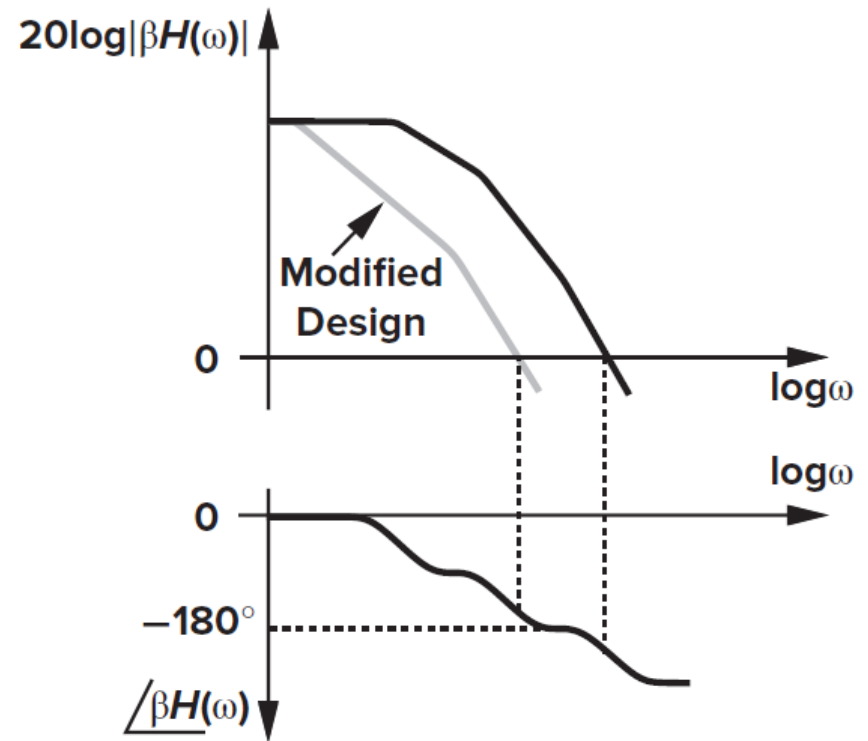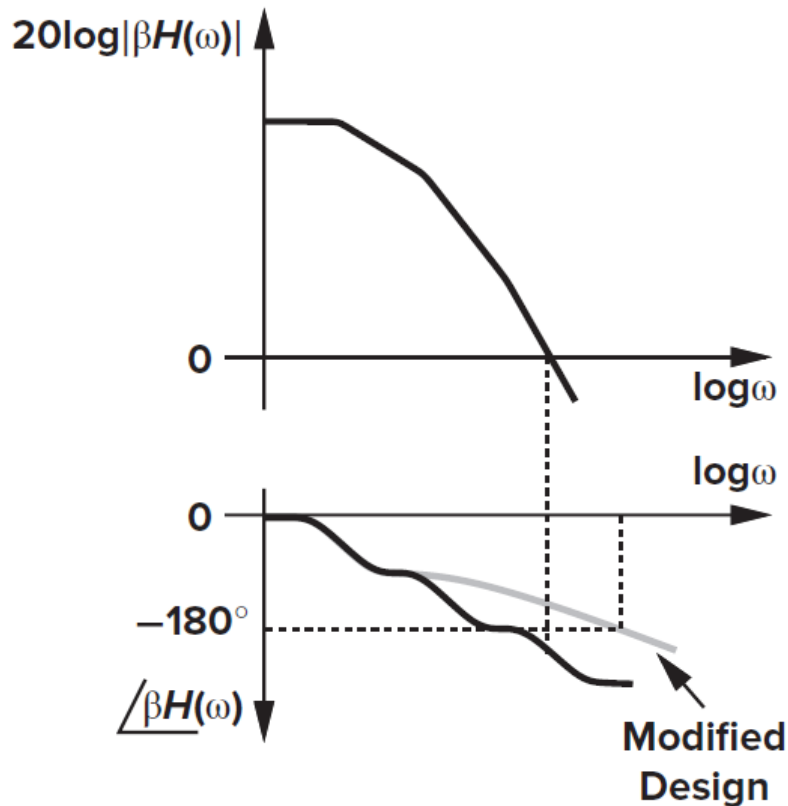- ❑ We need G_X much smaller than P_X
- ❑ Push P_X outwards: minimize poles \rightarrow minimize nodes/stages
- ❑ Push G_X inwards: lower GBW



Thank you!