

وَمَا أُوتِيتُمْ مِنَ الْعِلْمِ إِلَّا قَلِيلًا


Analog IC Design

Lecture 02 Review on Circuits Basics


Dr. Hesham A. Omran

Integrated Circuits Lab (ICL)
Electronics and Communications Eng. Dept.
Faculty of Engineering
Ain Shams University


Ohm's Law

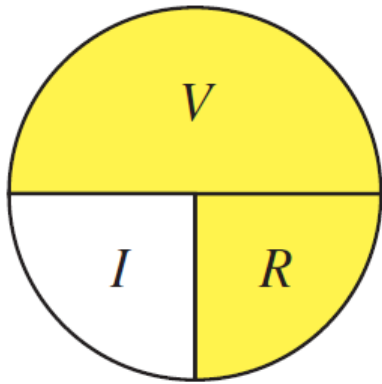

$$I = \frac{V}{R}$$

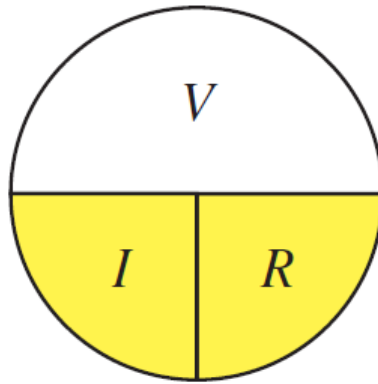

$$V = IR$$

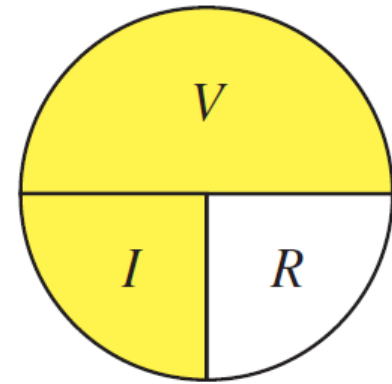


$$R = \frac{V}{I}$$

Kirchhoff Current Law (KCL)

- ❑ The sum of all currents flowing into a node is zero

$$\Sigma I = 0$$
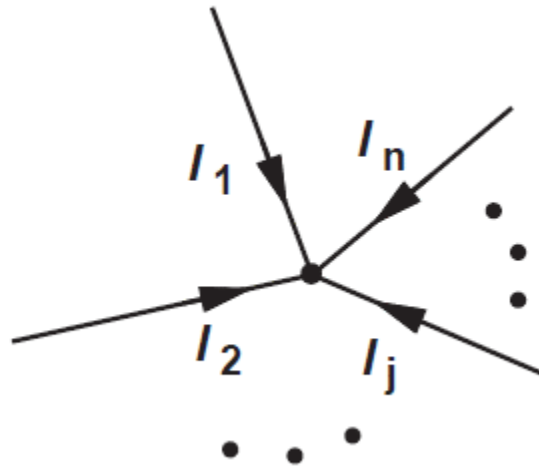
$$I_1 + I_2 + \cdots + I_j + \cdots + I_n = 0$$




Kirchhoff Voltage Law (KVL)

- The sum of all voltage drops around any closed loop is zero

$$\Sigma V = 0$$

$$V_1 + V_2 + V_3 + V_4 = 0$$

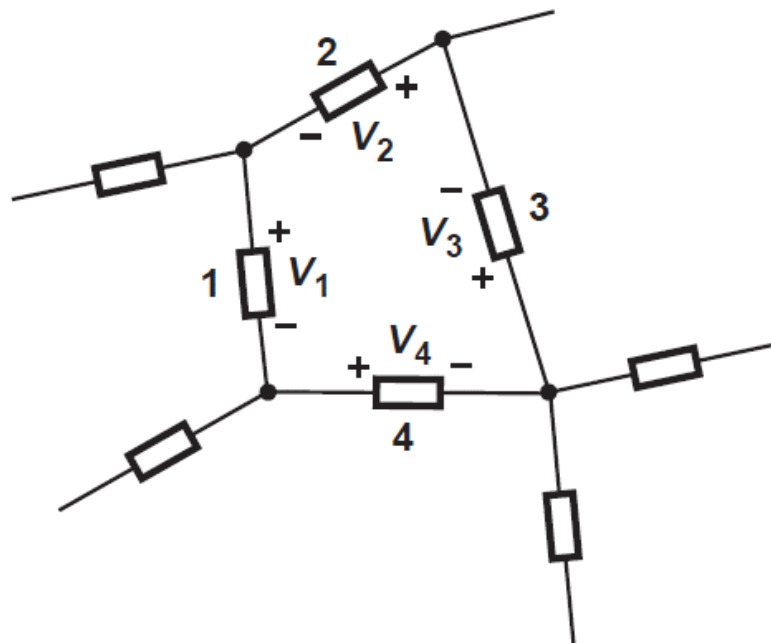


Kirchhoff Voltage Law (KVL)

- The sum of all voltage drops around any closed loop is zero

$$\Sigma V = 0$$

$$-V_1 + V_2 + V_3 + V_4 = 0$$

$$V_1 = V_2 + V_3 + V_4$$

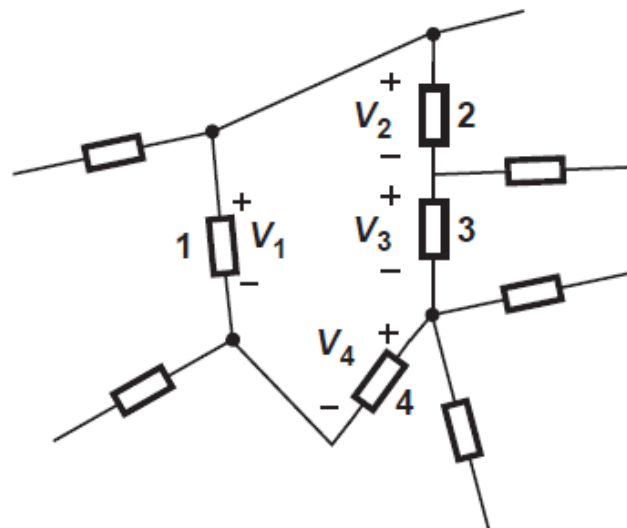


Resistor Combinations

- ❑ Resistors in series: Largest resistance dominates



$$R_{eq} = R_1 + R_2 + R_3$$

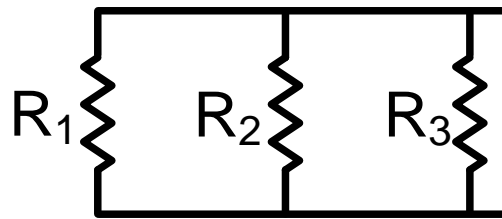
- ❑ Resistors in parallel: Smallest resistance dominates




$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Voltage and Current Dividers
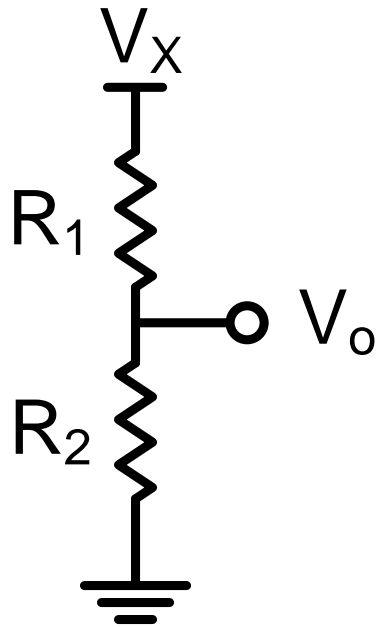
$$V_o = V_X \cdot \frac{R_2}{R_1 + R_2}$$




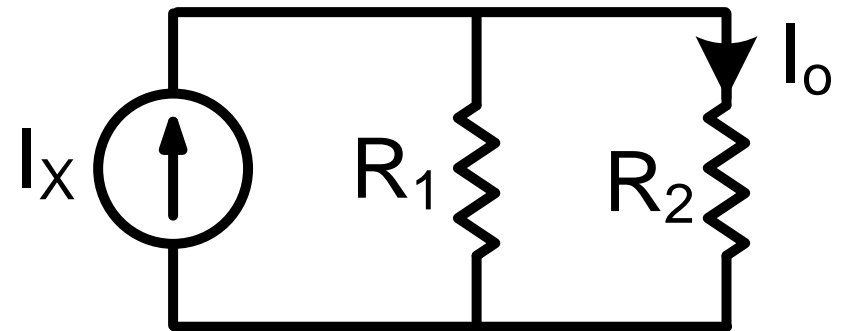
$$I_o = I_X \cdot \frac{R_1}{R_1 + R_2}$$



Thevenin Equivalent

$$V_{Thev} = V_{o.c.}$$

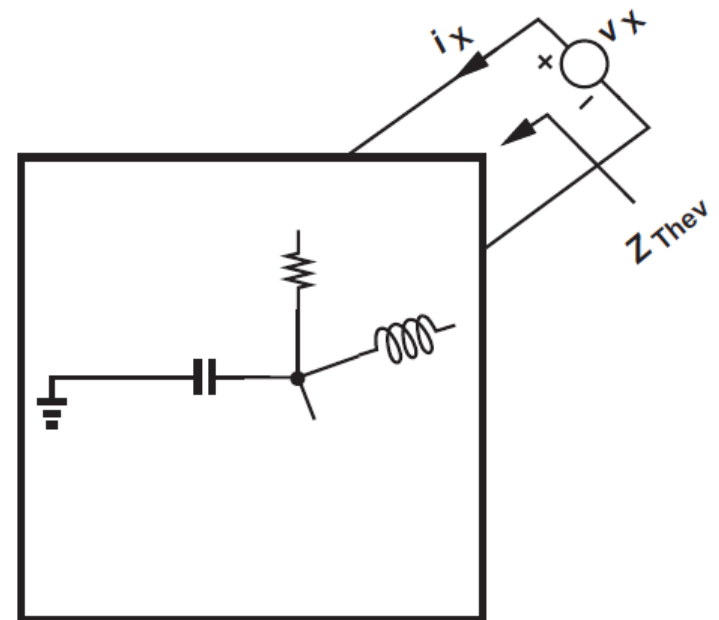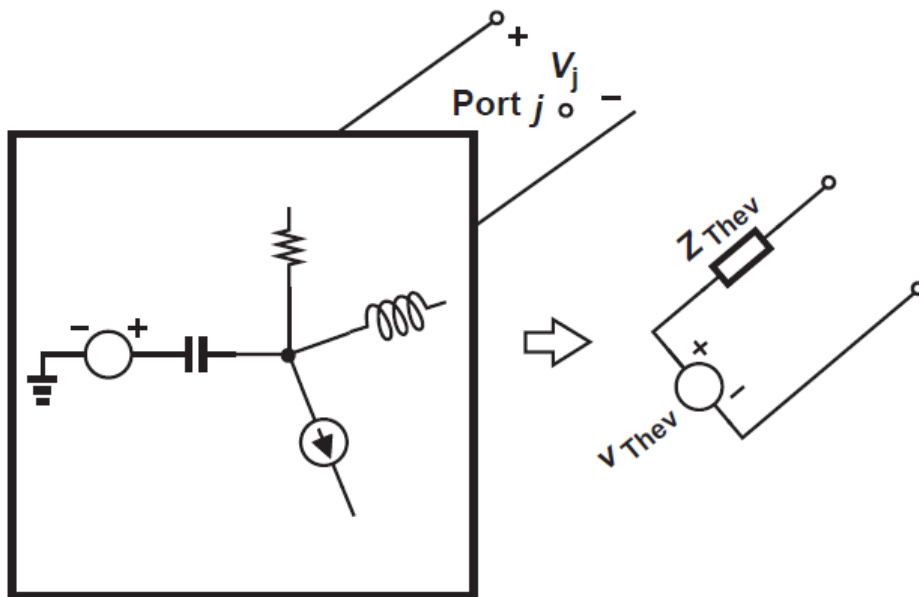


Norton Equivalent

$$I_{Nor} = I_{s.c.}$$

$$Z_{Nor} = Z_{Thev}$$
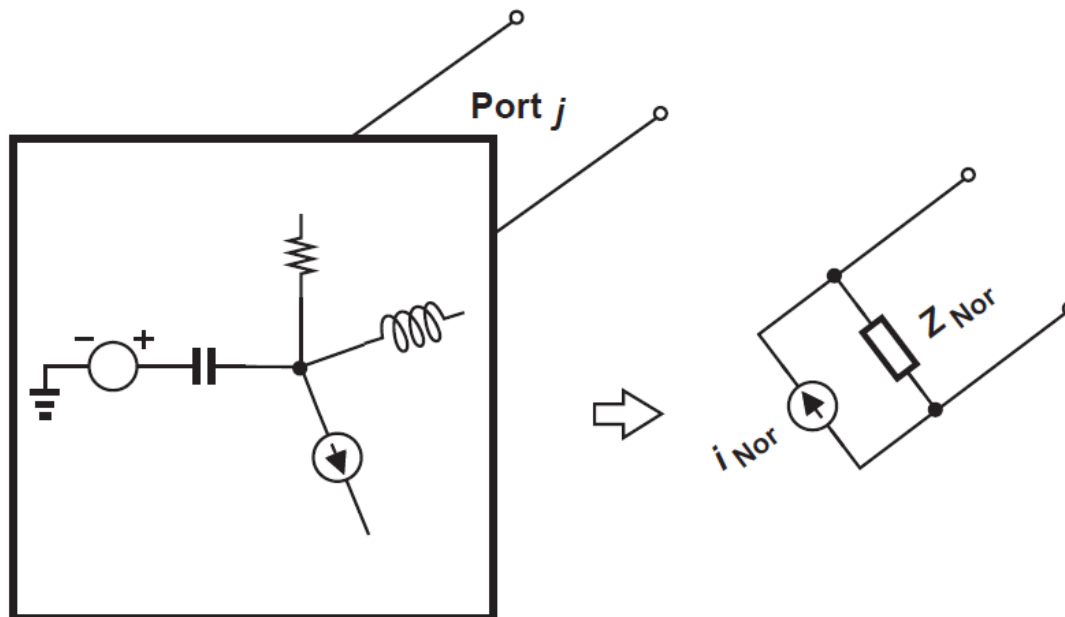
$$V_{Thev} = V_{o.c.} = I_{Nor} \times Z_{Nor}$$




Superposition Theorem


- ❑ Deactivate all independent sources except one
 - Independent voltage source \rightarrow s.c.
 - Independent current source \rightarrow o.c.
 - Do NOT deactivate dependent sources
- ❑ Solve the circuit
- ❑ Repeat the previous two steps for every source
- ❑ Algebraically add all the results

We use this frequently to separate AC and DC solutions


Superposition Theorem

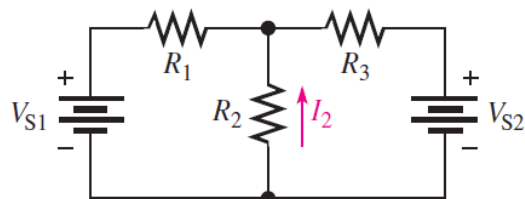

(a) Problem: Find I_2 .

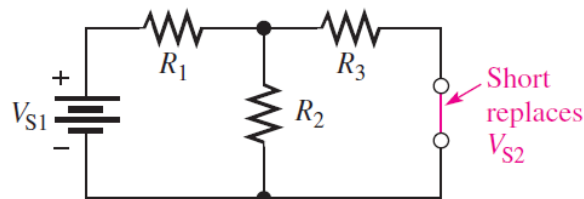

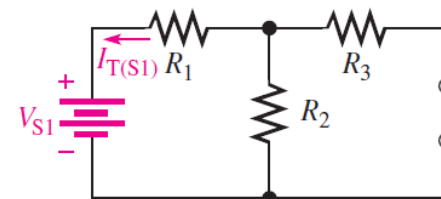
(b) Replace V_{S2} with zero resistance (short).



(c) Find R_T and I_T looking from V_{S1} :


$$R_{T(S1)} = R_1 + R_2 \parallel R_3$$

$$I_{T(S1)} = V_{S1}/R_{T(S1)}$$

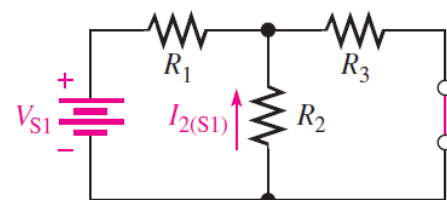


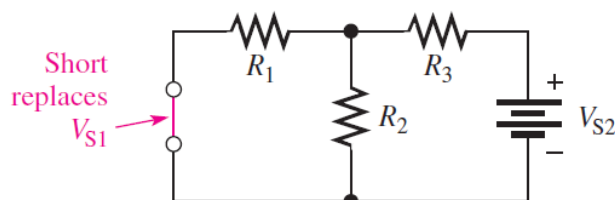(d) Find I_2 due to V_{S1} :

$$I_{2(S1)} = \left(\frac{R_3}{R_2 + R_3} \right) I_{T(S1)}$$



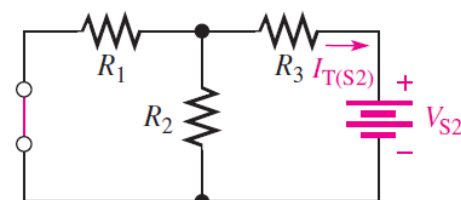
(e) Replace V_{S1} with zero resistance (short).



(f) Find R_T and I_T looking from V_{S2} :


$$R_{T(S2)} = R_3 + R_1 \parallel R_2$$

$$I_{T(S2)} = V_{S2}/R_{T(S2)}$$

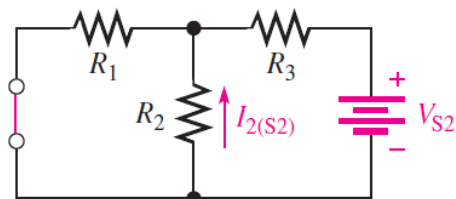

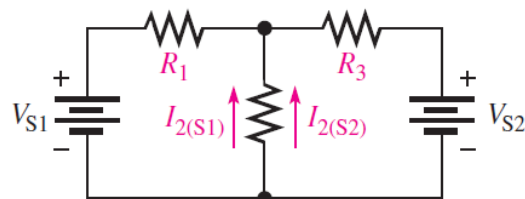(g) Find I_2 due to V_{S2} :

$$I_{2(S2)} = \left(\frac{R_1}{R_1 + R_2} \right) I_{T(S2)}$$



(h) Restore the original sources. Algebraically add $I_{2(S1)}$ and $I_{2(S2)}$ to get the actual I_2 (they are in same direction):

$$I_2 = I_{2(S1)} + I_{2(S2)}$$

Capacitance

$$Q = CV$$

$$i = \frac{dQ}{dt} = C \frac{dV}{dt}$$

$$V = V_o \cos \omega t = V_o \cdot \operatorname{Re}\{e^{j\omega t}\} \Rightarrow V_o e^{j\omega t}$$

$$i = C \frac{dV}{dt} = j\omega C (V_o e^{j\omega t}) = j\omega C \cdot V$$


$$Z = \frac{V}{i} = \frac{1}{j\omega C} = \frac{1}{sC} \Rightarrow X_C = \frac{1}{\omega C}$$

$$\omega \uparrow\uparrow \Rightarrow X_C \rightarrow 0 \Rightarrow s.c.$$

$$\omega \downarrow\downarrow \Rightarrow X_C \rightarrow \infty \Rightarrow o.c.$$


Capacitance Combinations

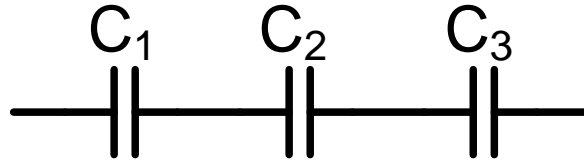- ❑ Capacitors in series: Smallest capacitor dominates



$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

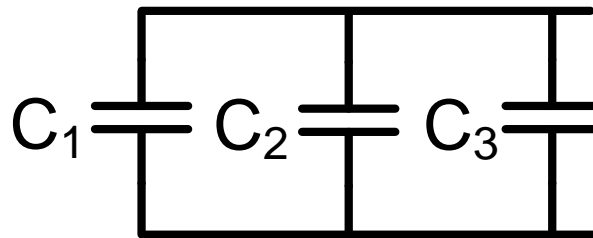
- ❑ Capacitors in parallel: Largest capacitor dominates




$$C_{eq} = C_1 + C_2 + C_3$$

Frequency Response


LPF

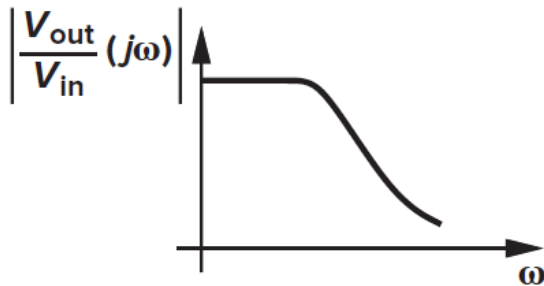

BPF

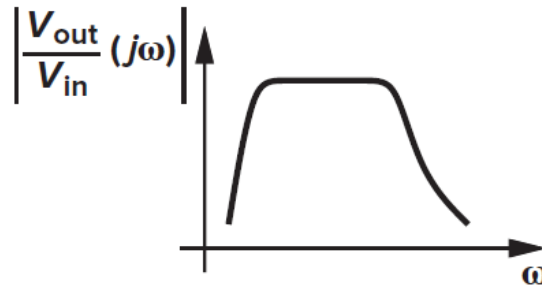

HPF

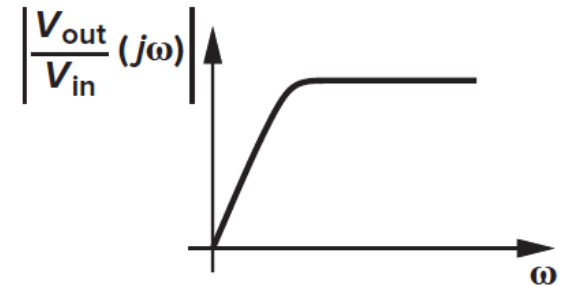

Poles and Zeros


- ❑ Transfer function

$$H(s) = \frac{N(s)}{D(s)}$$

- ❑ Zeros: roots of numerator $\Rightarrow N(s)$
- ❑ Poles: roots of denominator $\Rightarrow D(s)$
- ❑ Frequency response: $s \Rightarrow j\omega$

$$H(j\omega) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = |H(j\omega)|e^{j\phi}$$


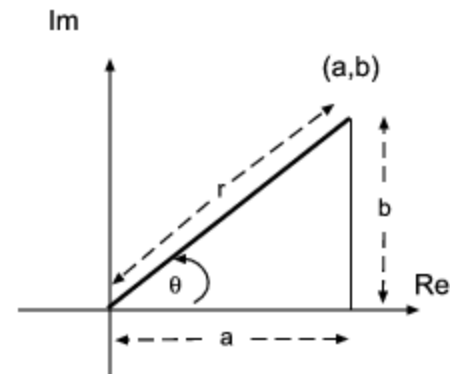
- ❑ Magnitude($a + jb$) = $\sqrt{a^2 + b^2}$
- ❑ Phase($a + jb$) = $\tan^{-1} \frac{b}{a}$



1st Order LPF

$$H(s) = \frac{v_{out}}{v_{in}} = \frac{1/sC}{R + 1/sC} = \frac{1}{1 + sRC} = \frac{1}{1 + s\tau}$$
$$H(j\omega) = \frac{v_{out}}{v_{in}} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + \frac{j\omega}{\omega_c}}$$

- ❑ $\tau = RC$: time constant
- ❑ $\omega_c = \frac{1}{\tau} = \frac{1}{RC}$: cutoff/corner frequency
- ❑ Poles: $s_p = -\frac{1}{\tau} = -\omega_c$
- ❑ Zeros: ?
- ❑ $|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$
- ❑ $P(H(j\omega)) = -\tan^{-1} \frac{\omega}{\omega_c}$

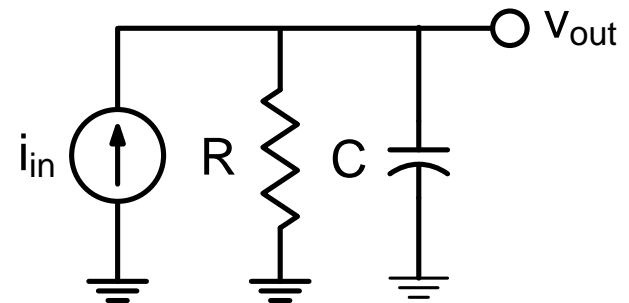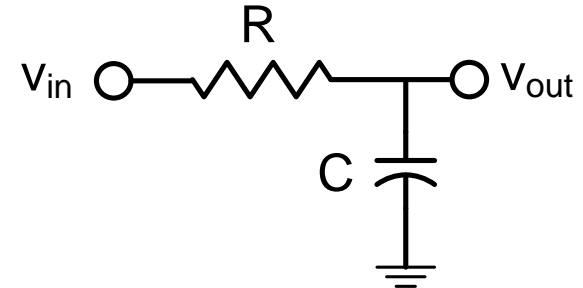


Bode Plot Rules

	Pole	Zero
Magnitude	-20 dB/decade Actual Mag @ pole: -3 dB	+20 dB/decade Actual Mag @ zero: +3 dB
Phase	-90° Actual Phase @ pole: -45°	LHP zero: +90° Actual Phase @ zero: +45° RHP zero: -90° Actual Phase @ zero: -45°


1st Order LPF

$20 \log |H(j\omega)|$ (dB)

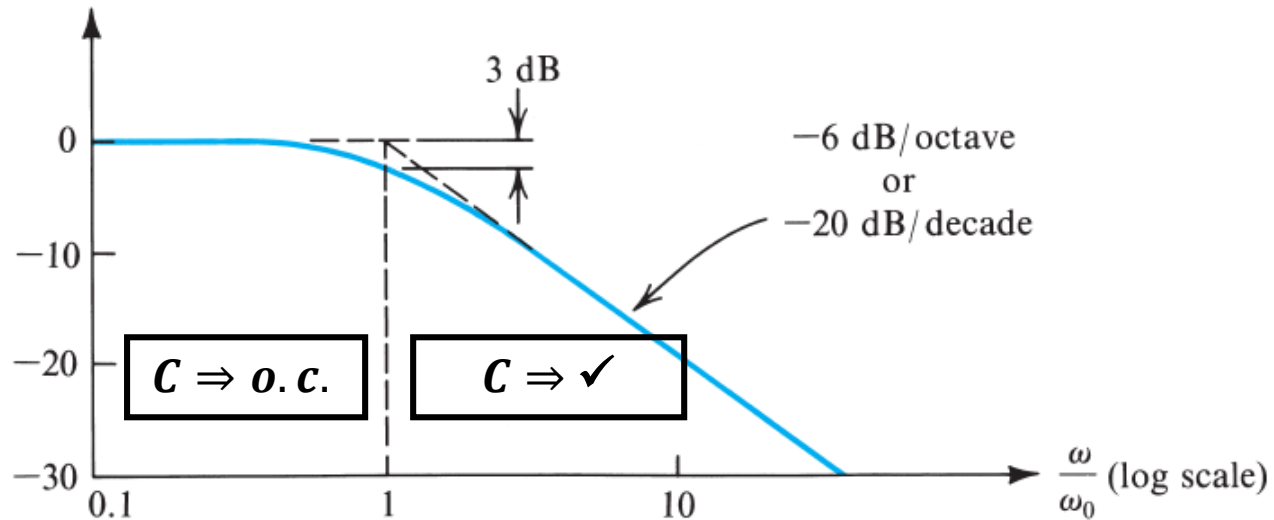

(a)

$\angle H(j\omega)$

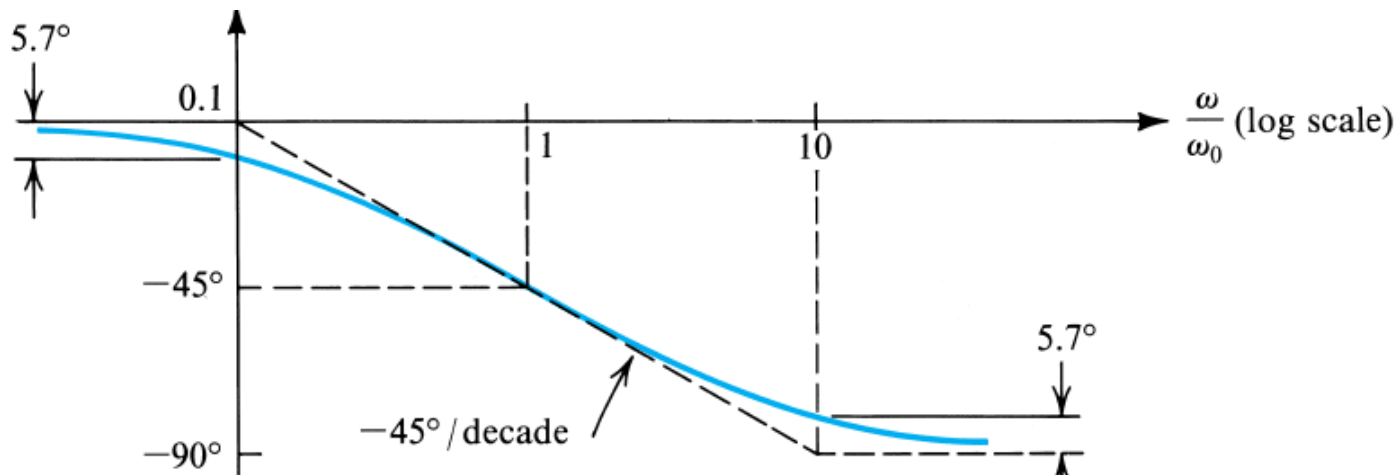

(b)

1st Order HPF

$$H(s) = \frac{v_{out}}{v_{in}} = \frac{R}{R + 1/sC} = \frac{sRC}{1 + sRC} = \frac{s\tau}{1 + s\tau}$$


$$H(j\omega) = \frac{v_{out}}{v_{in}} = \frac{R}{R + 1/j\omega C} = \frac{j\omega RC}{1 + j\omega RC} = \frac{\frac{j\omega}{\omega_c}}{1 + \frac{j\omega}{\omega_c}}$$

❑ Poles: $s_p = -\frac{1}{\tau} = -\omega_c$

❑ Zeros: $s_z = 0$

❑ $|H(j\omega)| = \frac{\frac{\omega}{\omega_c}}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$

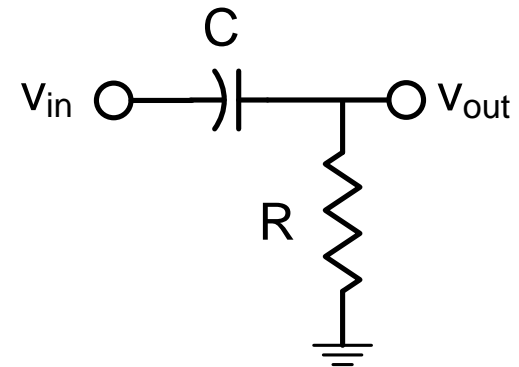❑ $P(H(j\omega)) = 90^\circ - \tan^{-1} \frac{\omega}{\omega_c}$




Bode Plot Rules


	Pole	Zero
Magnitude	-20 dB/decade Actual Mag @ pole: -3 dB	+20 dB/decade Actual Mag @ zero: +3 dB
Phase	-90° Actual Phase @ pole: -45°	LHP zero: +90° Actual Phase @ zero: +45° RHP zero: -90° Actual Phase @ zero: -45°

1st Order HPF

$20 \log|H(j\omega)|$ (dB)

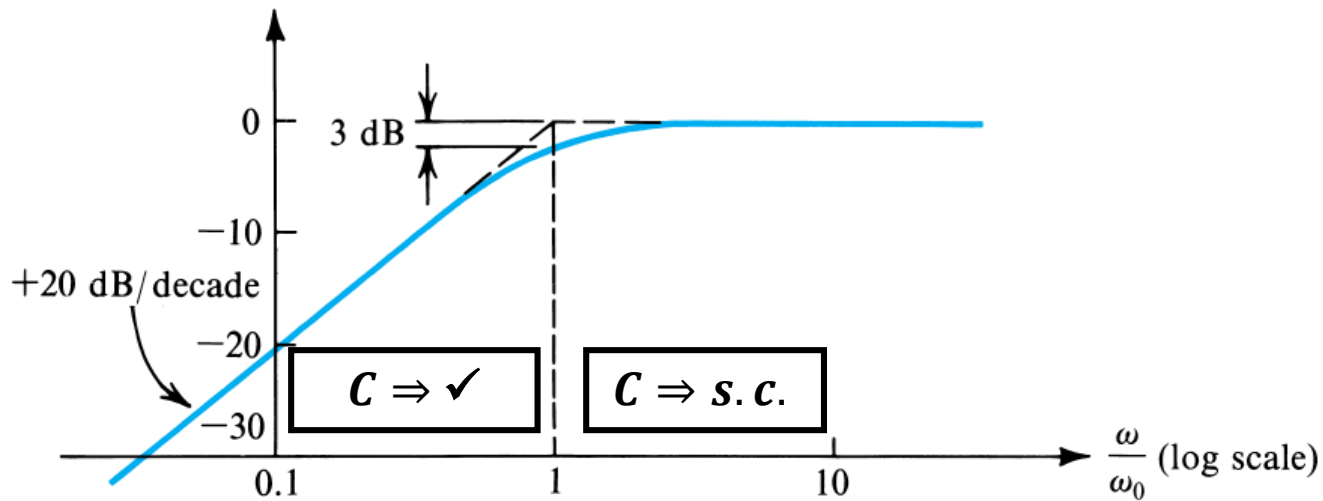

(a)

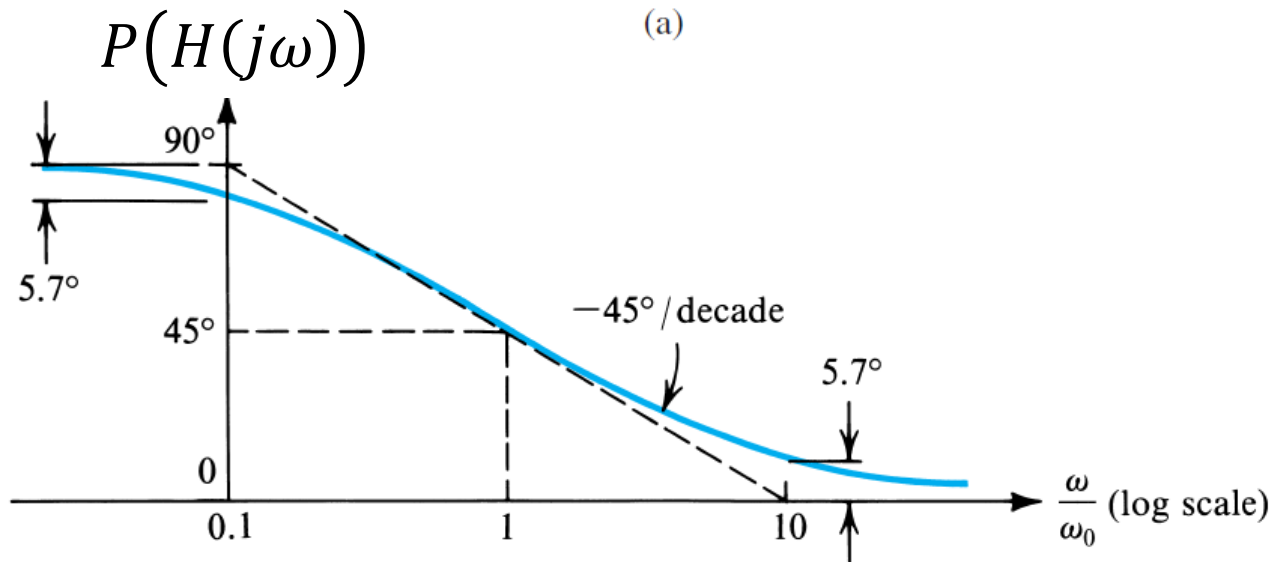

(b)

Thank you!