

وَمَا أُوتِيتُمْ مِنَ الْعِلْمِ إِلَّا قَلِيلًا

Analog IC Design

Lecture 06 Basic Amplifier Stages



Dr. Hesham A. Omran

Integrated Circuits Lab (ICL)
Electronics and Communications Eng. Dept.
Faculty of Engineering
Ain Shams University


MOSFET in Saturation

- ❑ The channel is pinched off if the difference between the gate and drain voltages is not sufficient to create an inversion layer
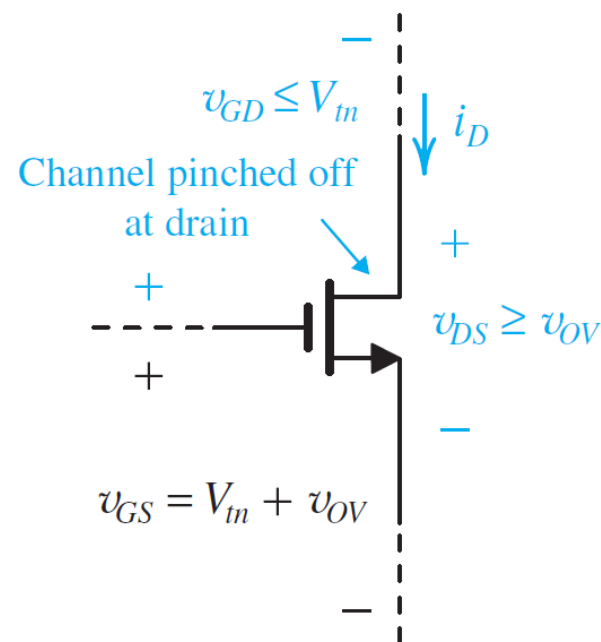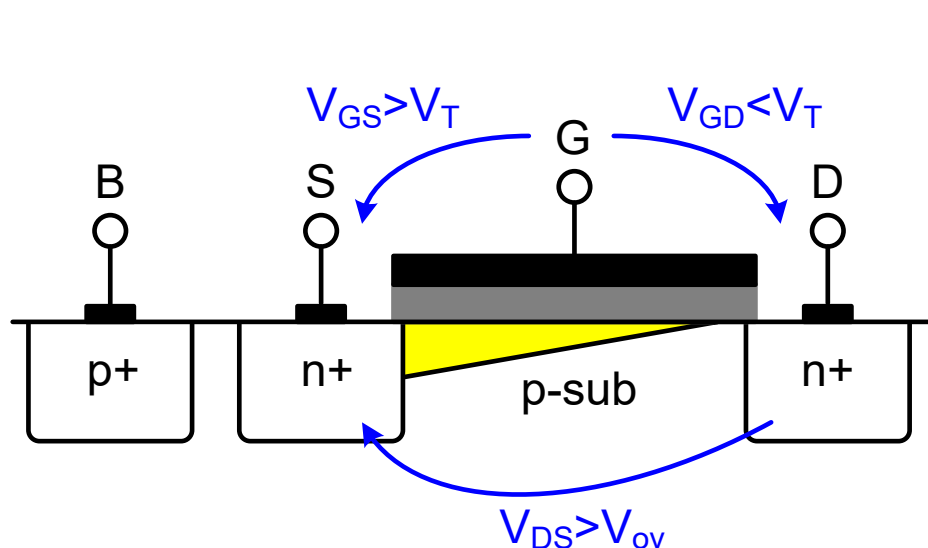
$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \cdot V_{ov}^2 (1 + \lambda V_{DS})$$



Regions of Operation Summary

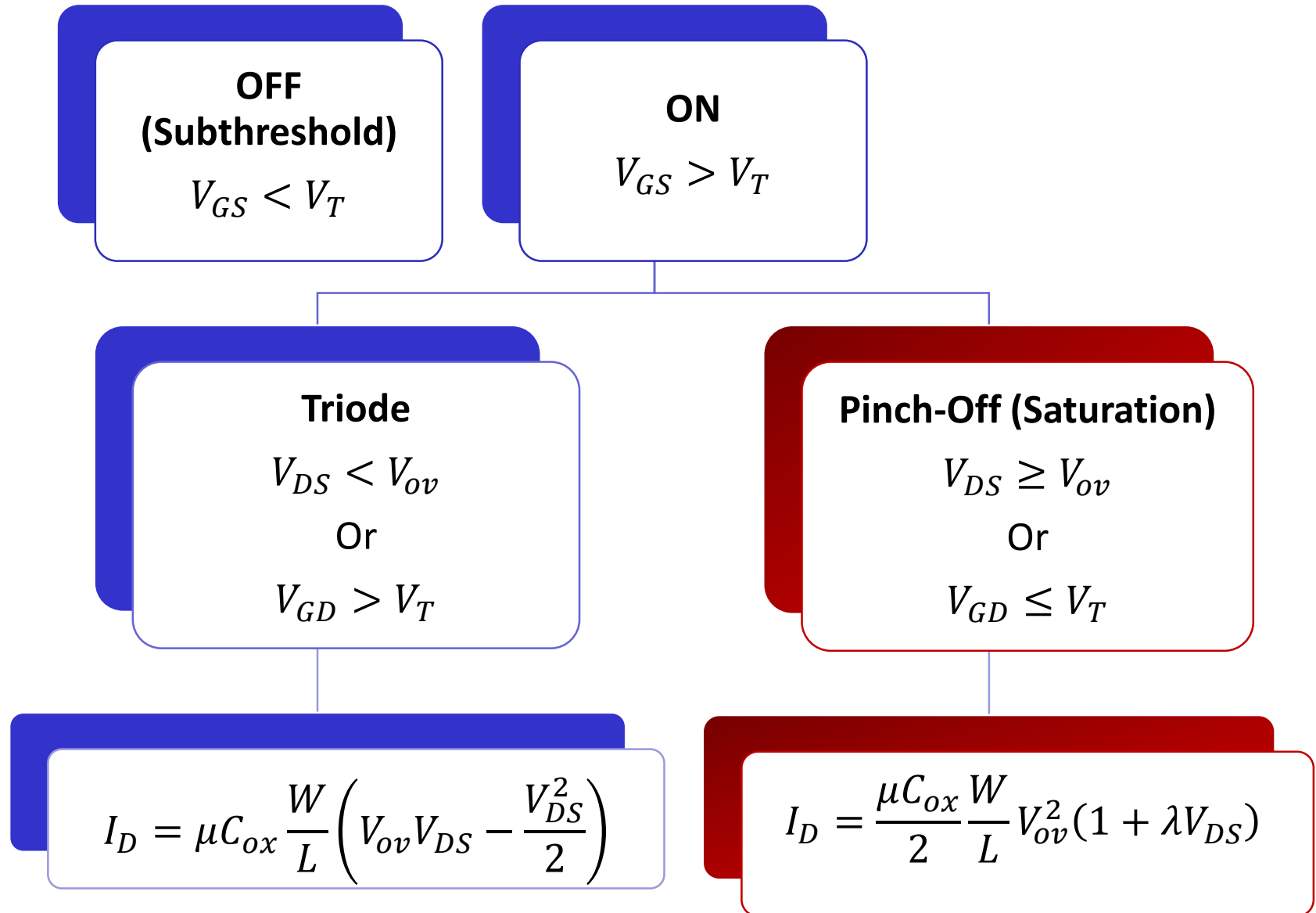

Long-Channel Square-Law Assumptions


- ❑ Square-Law: $I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} V_{ov}^2 (1 + \lambda V_{DS})$
- ❑ Valid “relatively” if
 - Relatively long channel length
 - Moderate overdrive voltage (e.g., $V_{ov} \approx 100 - 300mV$)
 - For small V_{ov} : weak inversion and subthreshold operation
 - ID-VGS relation becomes exponential
 - For large V_{ov} : velocity saturation happens before pinch-off
 - ID-VGS relation becomes linear
- ❑ If the above assumptions are not valid
 - Use gm/ID design methodology
- ❑ Actually, better to use gm/ID even if the above assumptions are valid!

Low-Frequency Small-Signal Model

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu C_{ox} \frac{W}{L} V_{ov} = \sqrt{\mu C_{ox} \frac{W}{L} \cdot 2I_D} = \frac{2I_D}{V_{ov}}$$

$$g_{mb} = \eta g_m, \quad \eta \approx 0.1 - 0.25$$
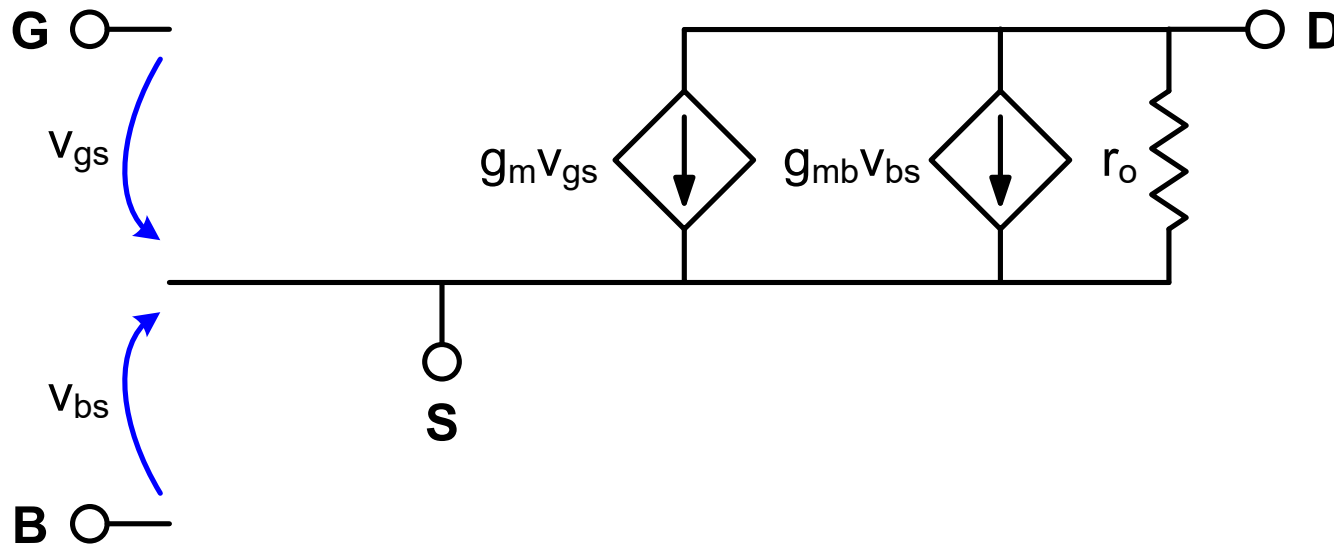
$$r_o = \frac{1}{\frac{\partial I_D}{\partial V_{DS}}} = \frac{1}{\lambda I_D}, \quad \lambda \propto \frac{1}{L}$$



Large and Small Signal Analysis


	Large Signal Analysis	Small Signal Analysis
Model	Large signal model	Small signal model
Linearity	Non-linear	Linear
Simulation	DC and transient analysis	AC analysis
Purpose	Calculate bias point, signal swing, distortion, etc.	Calculate A_v , R_{in} , R_{out} , BW , etc.
VDC	✓	s.c.
IDC	✓	o.c.
Capacitor	o.c. (in DC)	?
Inductor	s.c. (in DC)	?

Today


- ❑ Why Amplifiers?
- ❑ R_{in}/out Shortcuts
- ❑ GmRout Method
- ❑ Basic Amplifier Topologies
 - Common Source
 - Common Gate
 - Common Drain

Why Amplifiers?

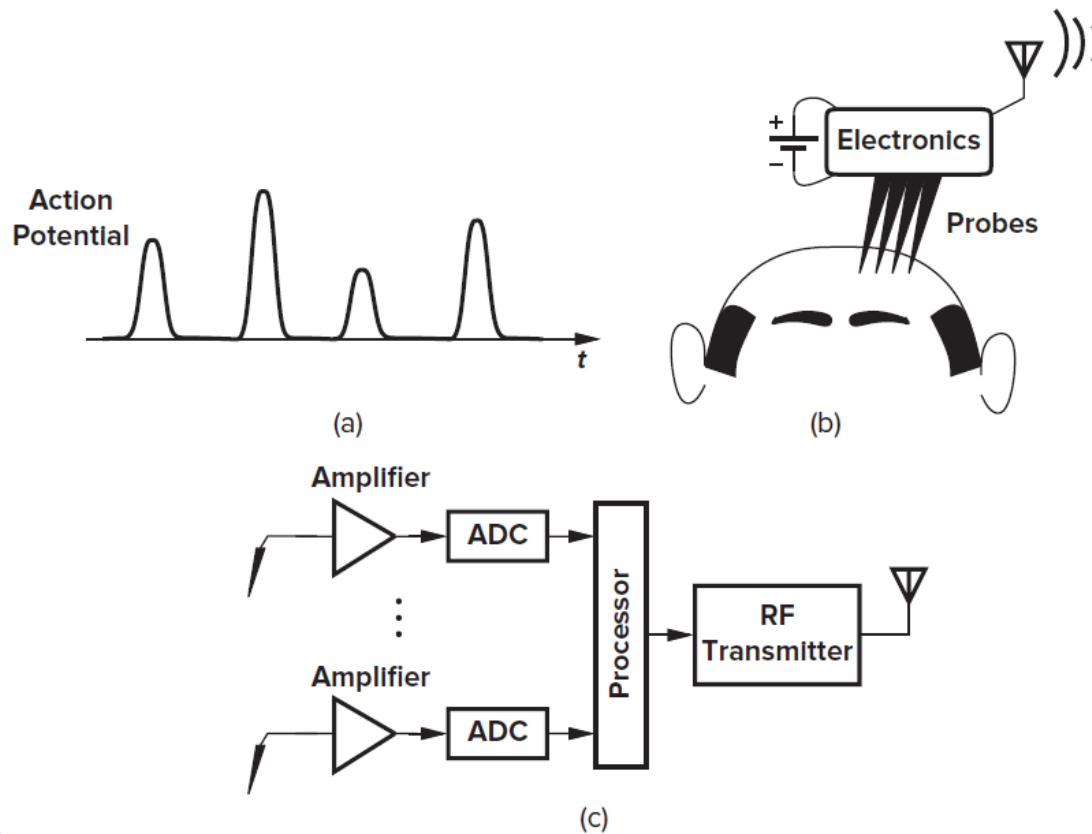- ❑ All the physical signals in the world around us are analog
 - Voice, light, temperature, pressure, etc.
- ❑ We (will) always need an “analog” interface circuit to connect between our physical world and our digital electronics




Analog Design Octagon

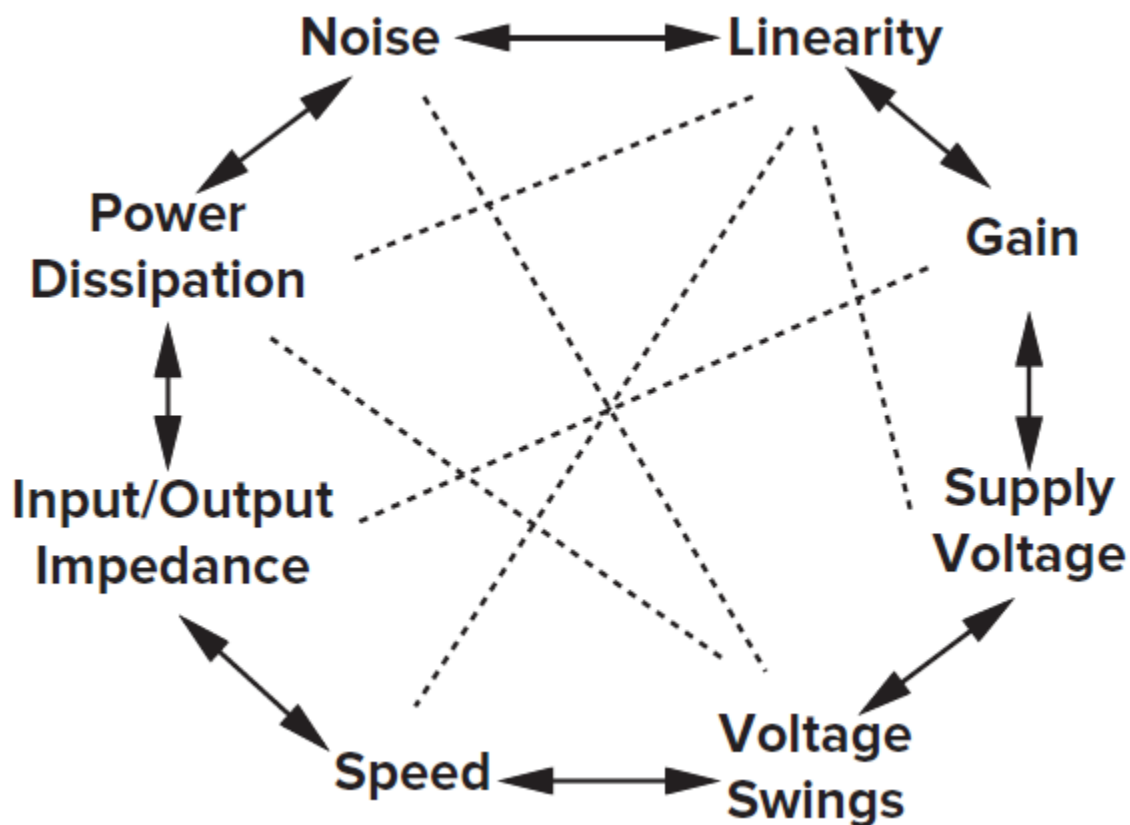

Direct Analysis on Schematics

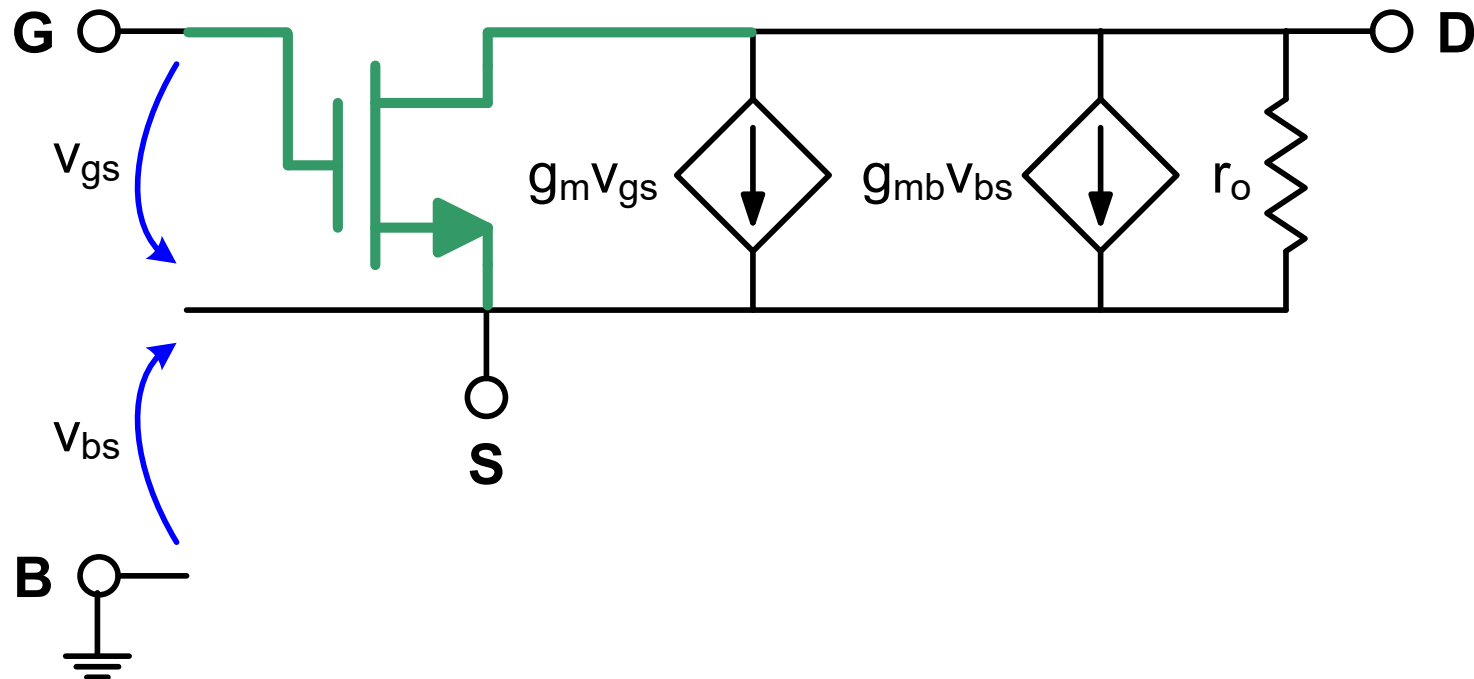- ❑ No need to draw the small signal model every time
- ❑ Just remember we have two VCCSs and r_o between D and S




Intrinsic Gain

$$v_{out} = -(g_m v_{in}) r_o$$
$$|A_v| = \left| \frac{v_{out}}{v_{in}} \right| = g_m r_o$$


- $g_m r_o$ is the max gain that can be obtained from a single transistor
- Common approximations that we usually use
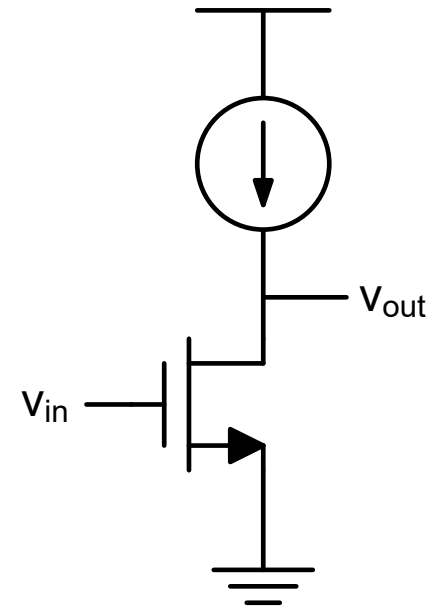
$$g_m r_o \gg 1$$
$$r_o \gg \frac{1}{g_m}$$
$$r_o + \frac{1}{g_m} \approx r_o$$
$$r_o // \frac{1}{g_m} \approx \frac{1}{g_m}$$



Rin/out Shortcuts

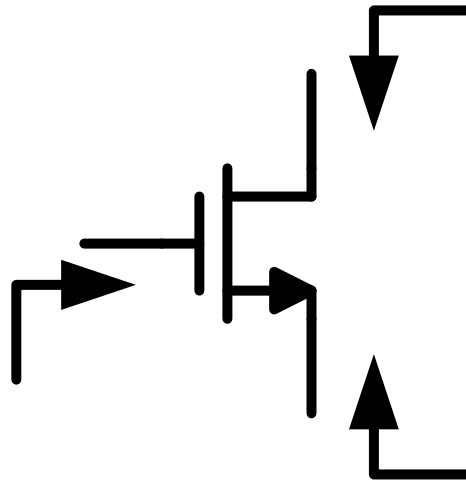- Find equivalent impedance looking from Gate, Source, and Drain




Looking From Drain

- Apply KCL at v_y (note that $v_{gs} = -v_y$)

$$\frac{v_y}{R_S} + \frac{v_y - v_x}{r_o} + (g_m + g_{mb})v_y = 0$$

- But $v_y = i_x R_S$ and $g_m r_o \gg 1$
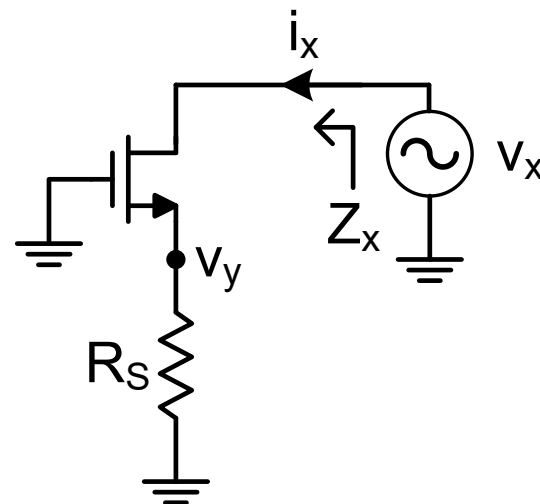
$$R_x = \frac{v_x}{i_x} \approx r_o [1 + (g_m + g_{mb})R_S]$$



Looking From Drain

- Apply KCL at v_y (note that $v_{gs} = -v_y$)

$$\frac{v_y}{R_S} + \frac{v_y - v_x}{r_o} + (g_m + g_{mb})v_y = 0$$

- But $v_y = i_x R_S$ and $g_m r_o \gg 1$



$$R_x = \frac{v_x}{i_x} \approx r_o [1 + (g_m + g_{mb})R_S]$$

- Special case: $R_S = 0$ (G and S ac s.c.)


$$R_x \approx r_o$$

(Active load)

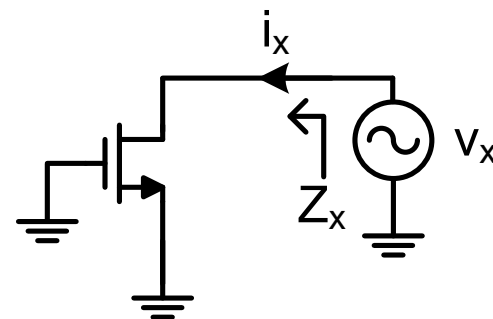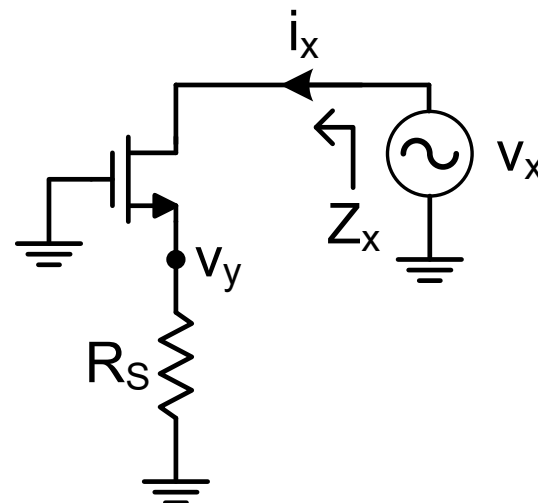- **Drain is a high-impedance node (H.I.N.)**




Active Load (Source OFF)

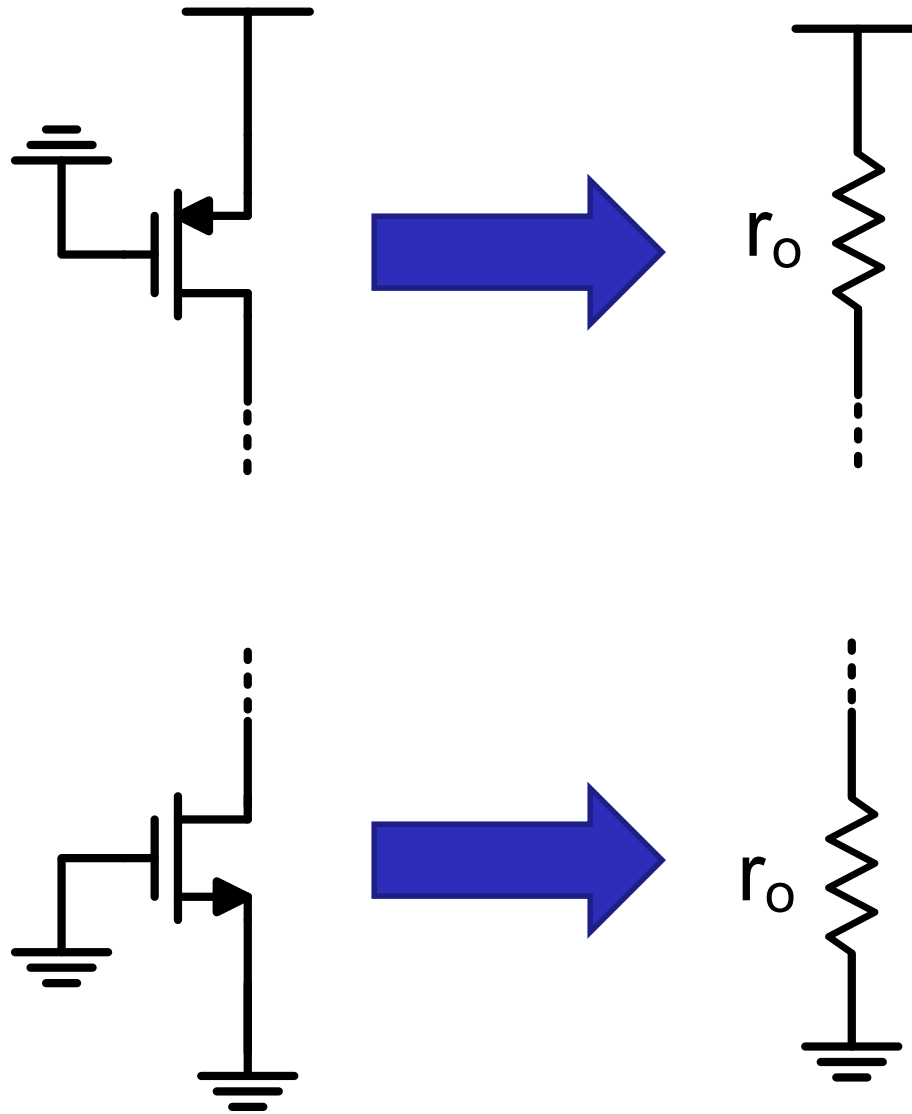

Bonus Question

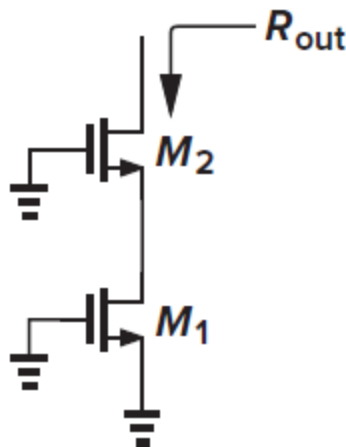- ❑ Assume M_1 and M_2 have the same g_m and r_o , and neglect body effect
- ❑ Find R_{out}




Looking From Source

- Apply KCL at v_y (note that $v_{gs} = -v_x$)

$$\frac{v_y}{R_D} + \frac{v_y - v_x}{r_o} - (g_m + g_{mb})v_x = 0$$

- But $v_y = i_x R_D$ and $g_m r_o \gg 1$
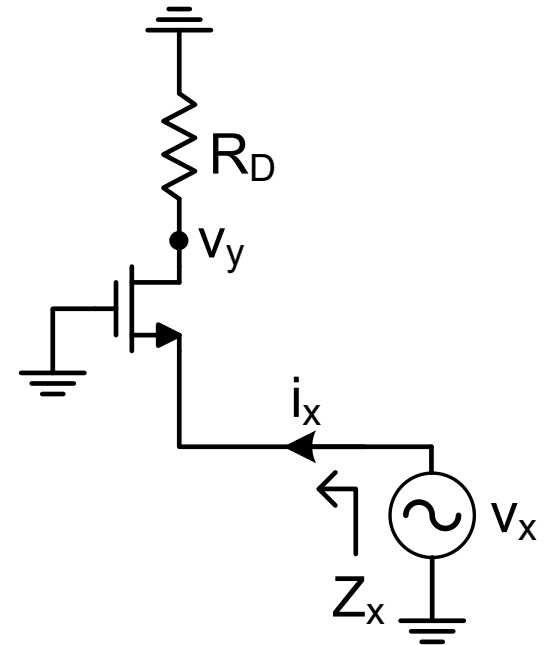
$$R_x = \frac{v_x}{i_x} \approx \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$$



Looking From Source

- Apply KCL at v_y (note that $v_{gs} = -v_x$)

$$\frac{v_y}{R_D} + \frac{v_y - v_x}{r_o} - (g_m + g_{mb})v_x = 0$$

- But $v_y = i_x R_D$ and $g_m r_o \gg 1$



$$R_x = \frac{v_x}{i_x} \approx \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$$

- Special case: $R_D = 0$ (G & D ac s.c.)

$$R_x \approx \frac{1}{g_m + g_{mb}}$$



(Diode connected)

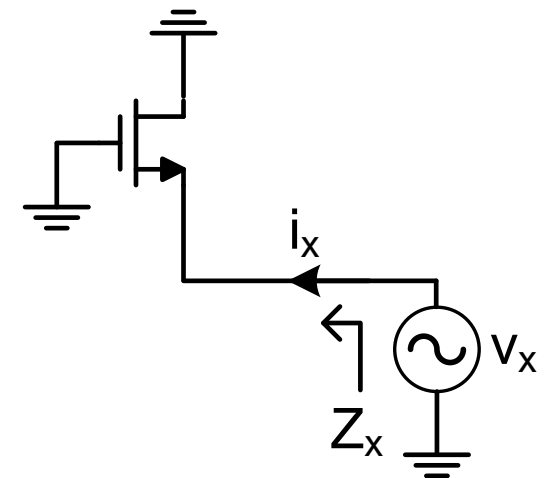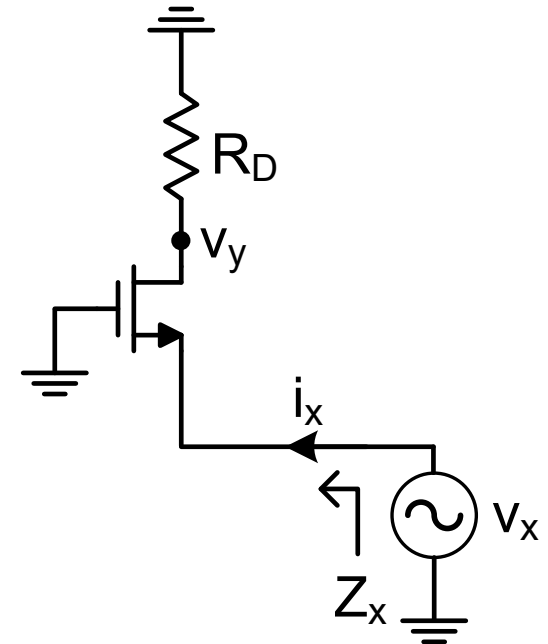- Source is a low impedance node (L.I.N.)




Diode Connected (Source Absorption)

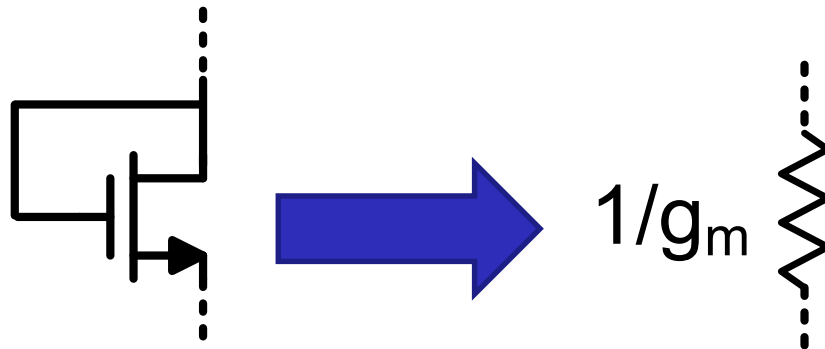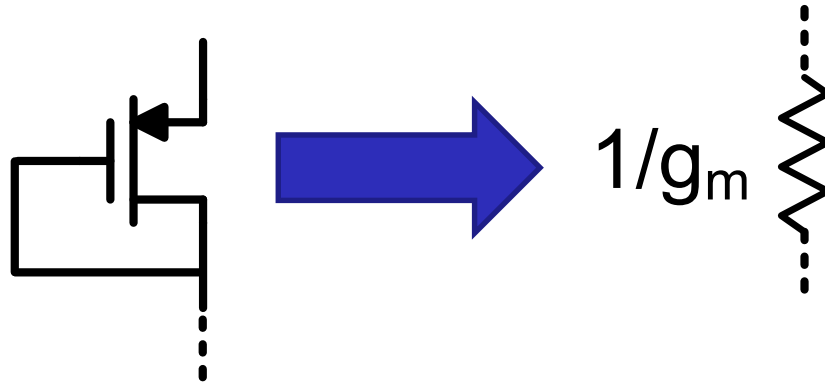- ❑ Always in saturation
- ❑ Bulk effect: $g_m \rightarrow g_m + g_{mb}$




Bonus Question

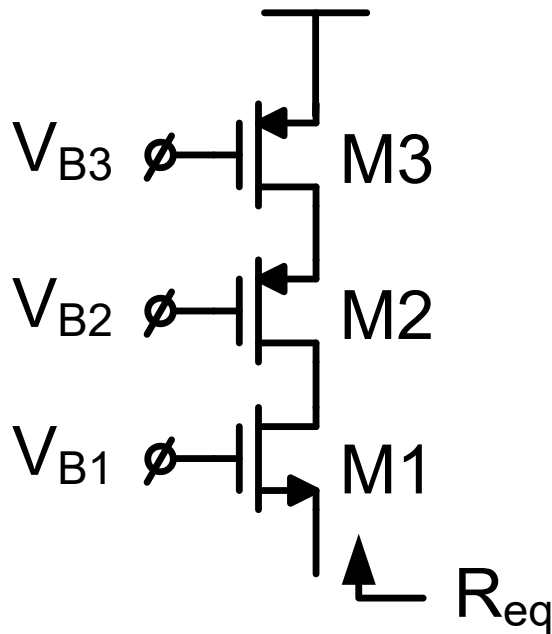- ❑ Assume M1, M2, and M3 have the same g_m and r_o . Ignore body effect.
- ❑ Find R_{eq}



Rin/out Shortcuts Summary

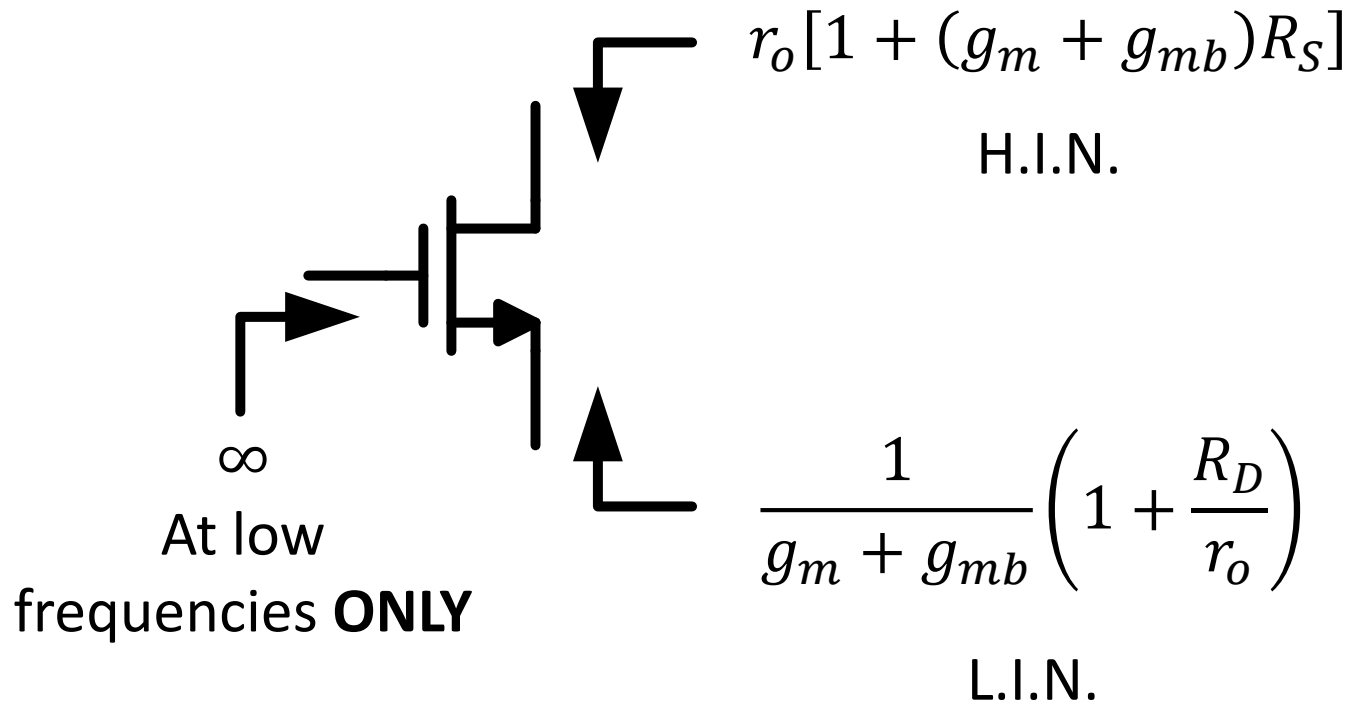

Amplifier Model

- O.C. voltage gain


$$v_{out,oc} = A_v v_{in}$$

$$A_v = \frac{v_{out,oc}}{v_{in}}$$

- Rin/out

$$R_{in} = \frac{v_{in}}{i_{in}}$$
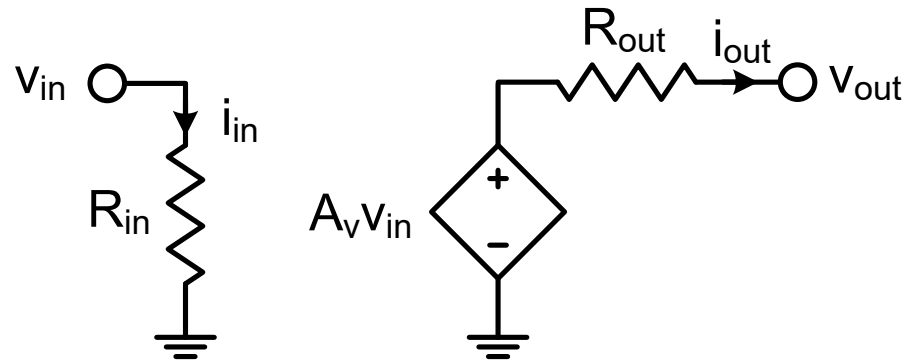
$$R_{out} = \frac{v_x}{i_x} @ v_{in} = 0$$



Amplifier Model

□ Transconductance

$$i_{out,sc} = G_m v_{in}$$

$$G_m = \frac{i_{out,sc}}{v_{in}}$$



□ Thevenin \Leftrightarrow Norton

$$A_v v_{in} = (G_m v_{in}) R_{out}$$

$$A_v = \frac{v_{out,oc}}{v_{in}} = G_m R_{out}$$

□ S.C. Current Gain
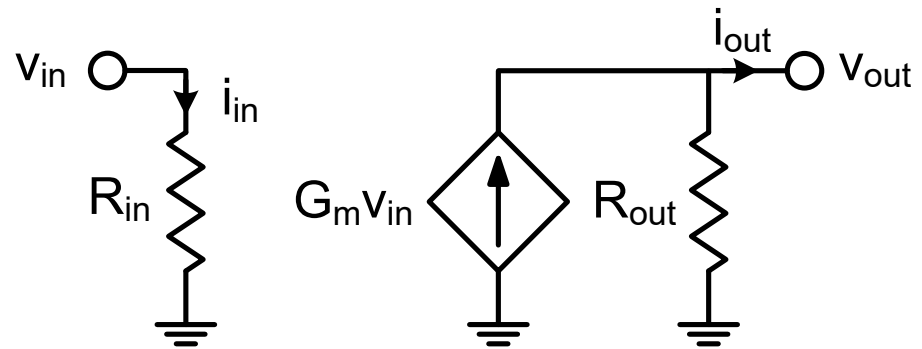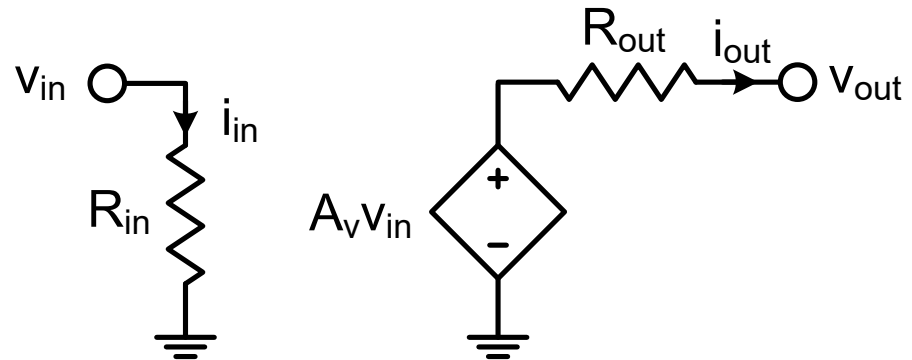
$$A_i = \frac{i_{out,sc}}{i_{in}} = G_m R_{in}$$



Why GmRout?

$$R_{out} = \frac{v_x}{i_x} @ v_{in} = 0$$



$$G_m = \frac{i_{out,sc}}{v_{in}}$$

$$A_v = G_m R_{out}$$


$$A_i = G_m R_{in}$$

□ Divide and conquer

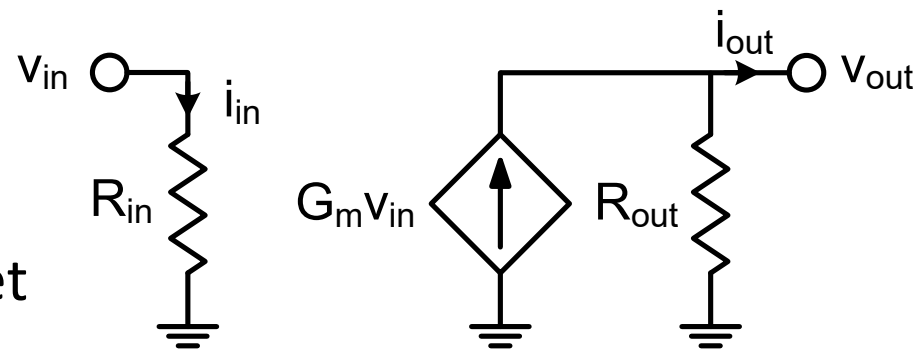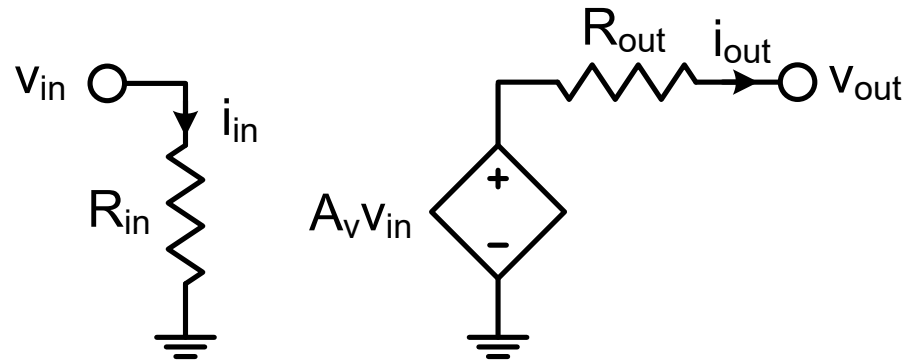
- Rout simplified: $v_{in}=0$
- Gm simplified: $v_{out}=0$
- We already need $R_{in/out}$
- We can quickly and easily get $R_{in/out}$ from the shortcuts




Basic Amplifier Topologies

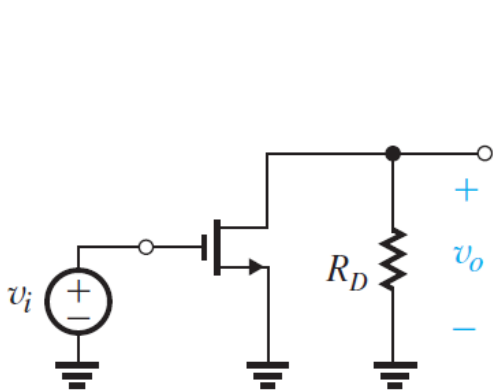

(a) Common Source (CS)

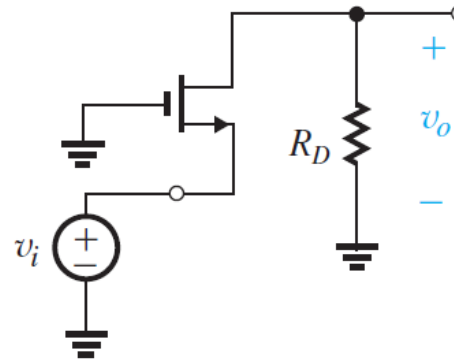

(b) Common Gate (CG)

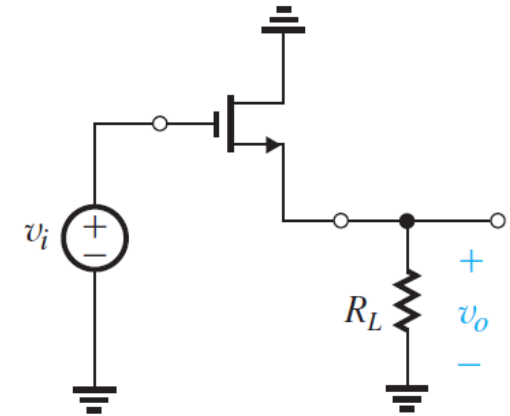

(c) Common Drain (CD)
or Source Follower

Topology	Input	Output
Common-Source	Gate	Drain
Common-Gate	Source	Drain
Common-Drain (Source-Follower)	Gate	Source

Common Source (CS)

□ KCL at v_x


$$i_{out,sc} + g_m(v_{in} - v_x) + g_{mb}(-v_x) - \frac{v_x}{r_o} = 0$$

□ But $v_x = -i_{out,sc}R_S$ and $g_m r_o \gg 1$

$$G_m = \frac{i_{out,sc}}{v_{in}} \approx \frac{-g_m}{1 + (g_m + g_{mb})R_S}$$

$$R_{out} \approx R_D // r_o [1 + (g_m + g_{mb})R_S]$$

$$A_v = G_m R_{out}$$

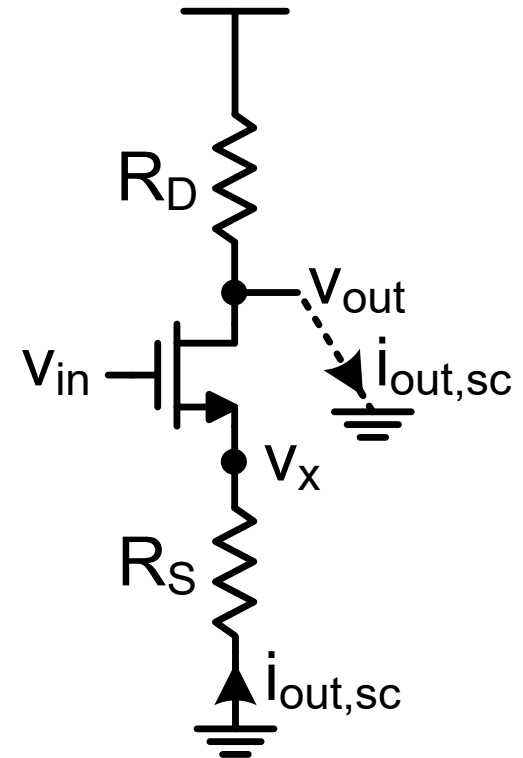

Common Source (CS)

- KCL at v_x

$$i_{out,sc} + g_m(v_{in} - v_x) + g_{mb}(-v_x) - \frac{v_x}{r_o} = 0$$


- But $v_x = -i_{out,sc}R_S$ and $g_m r_o \gg 1$

$$G_m = \frac{i_{out,sc}}{v_{in}} \approx \frac{-g_m}{1 + (g_m + g_{mb})R_S}$$

$$R_{out} \approx R_D // r_o [1 + (g_m + g_{mb})R_S]$$

$$A_v = G_m R_{out}$$

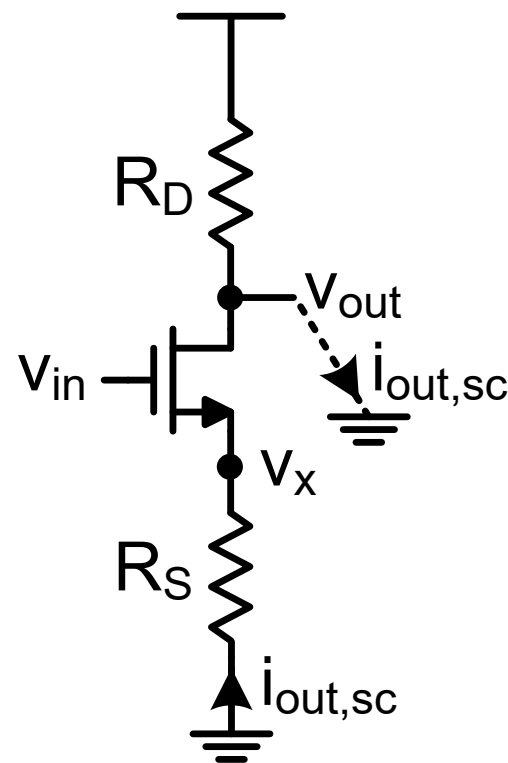- If R_D is ac o.c.: $A_v = -g_m r_o$
- If $R_D \ll R_{LFD}$: $A_v \approx \frac{-g_m R_D}{1 + (g_m + g_{mb})R_S}$
- If $R_S = 0$: $A_v = -g_m (R_D // r_o)$



Common Source (CS)

$$G_m = \frac{i_{out,sc}}{v_{in}} \approx \frac{-g_m}{1 + (g_m + g_{mb})R_S}$$

$$R_{out} \approx R_D // r_o [1 + (g_m + g_{mb})R_S]$$


$$A_v = G_m R_{out}$$

- If S and B are connected (for PMOS):

$$A_v \approx \frac{-R_D // R_{LFD}}{\frac{1}{g_m} + R_S} = - \frac{\text{Drain Res.}}{\frac{1}{g_m} + \text{Source Res}}$$

- If $R_S \gg \frac{1}{g_m}$ & $R_D \ll R_{LFD}$: $A_v \approx \frac{-R_D}{R_S} \rightarrow \text{Linear}$

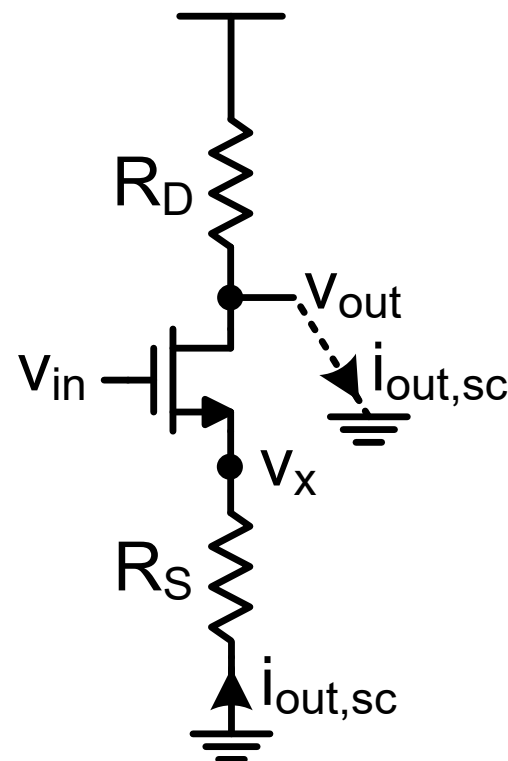- R_S reduces $G_m \rightarrow$ **Source degeneration**
 - But improves linearity



Common Gate (CG)

- KCL at v_{out}


$$i_{out,sc} + (g_m + g_{mb})(-v_{in}) - \frac{v_{in}}{r_o} = 0$$

- But $g_m r_o \gg 1$

$$G_m = \frac{i_{out,sc}}{v_{in}} \approx g_m + g_{mb}$$

$$R_{out} \approx R_D // r_o \text{ (why?)}$$

$$A_v = G_m R_{out}$$

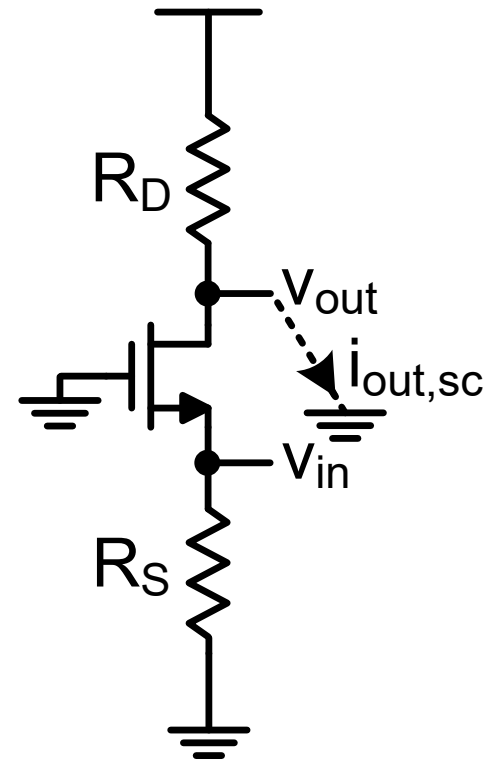

Common Gate (CG)

- KCL at v_{out}

$$i_{out,sc} + (g_m + g_{mb})(-v_{in}) - \frac{v_{in}}{r_o} = 0$$

- But $g_m r_o \gg 1$


$$\mathbf{G_m = \frac{i_{out,sc}}{v_{in}} \approx g_m + g_{mb}}$$

$$R_{out} \approx R_D // r_o \text{ (why?)}$$

$$A_v = G_m R_{out}$$

- If R_D is ac o.c.: $A_v = (g_m + g_{mb})r_o$
- If $R_D \ll r_o$: $A_v \approx (g_m + g_{mb})R_D$

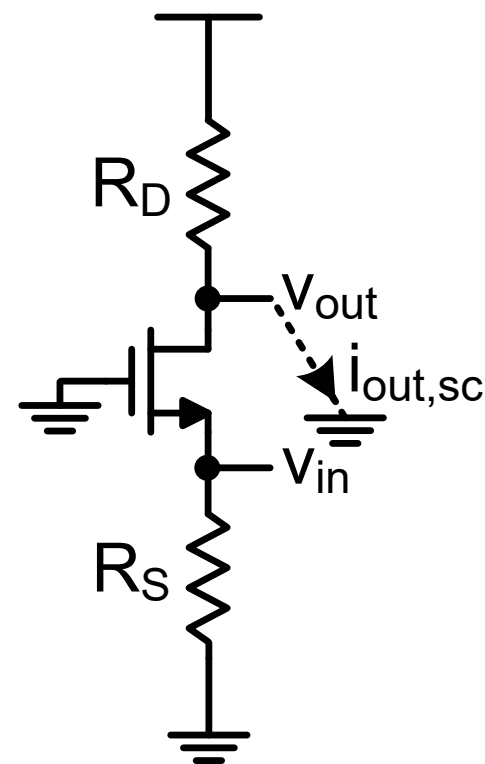- For PMOS connect S and B: $(g_m + g_{mb}) \rightarrow g_m$
- Note that $A_i = G_m R_{in} \approx \mathbf{1}$ (**Current Buffer**)



Common Drain (CD) – Source Follower

□ KCL at v_x


$$i_{out,sc} - g_m v_{in} - \frac{v_x}{r_o} = 0$$

□ But $v_x = -i_{out,sc} R_D$ and $g_m r_o \gg 1$

$$G_m = \frac{i_{out,sc}}{v_{in}} \approx \frac{g_m}{1 + R_D/r_o}$$

$$R_{out} \approx R_S // \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$$

$$A_v = G_m R_{out}$$

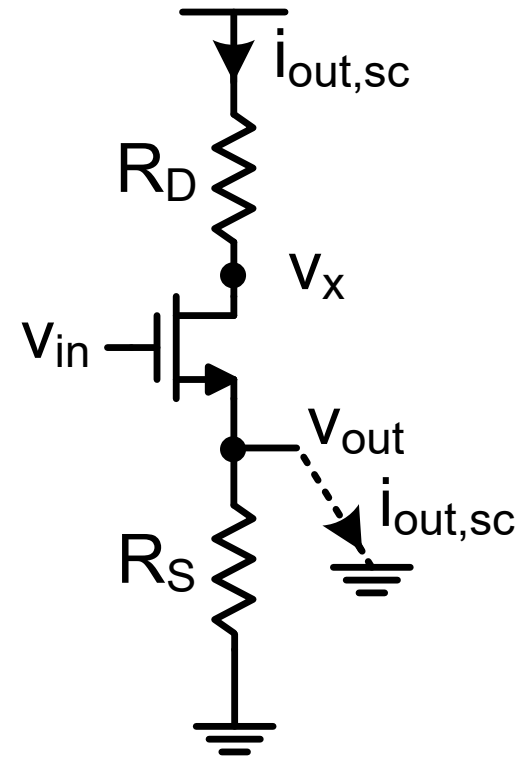

Common Drain (CD) – Source Follower

□ KCL at v_x

$$i_{out,sc} - g_m v_{in} - \frac{v_x}{r_o} = 0$$

□ But $v_x = -i_{out,sc} R_D$ and $g_m r_o \gg 1$

$$G_m = \frac{i_{out,sc}}{v_{in}} \approx \frac{g_m}{1 + R_D/r_o}$$


$$R_{out} \approx R_S // \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$$

$$A_v = G_m R_{out}$$

□ If $R_S \gg R_{LFS}$: $A_v \approx \frac{g_m}{g_m + g_{mb}}$



□ If S and B are connected (for PMOS):

$$A_v \approx 1$$

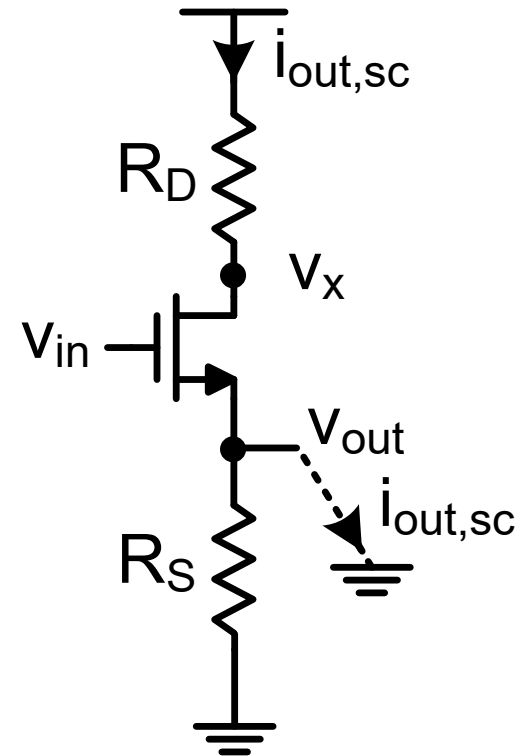

Why Source Follower?

1. Buffer
2. Level-shifter

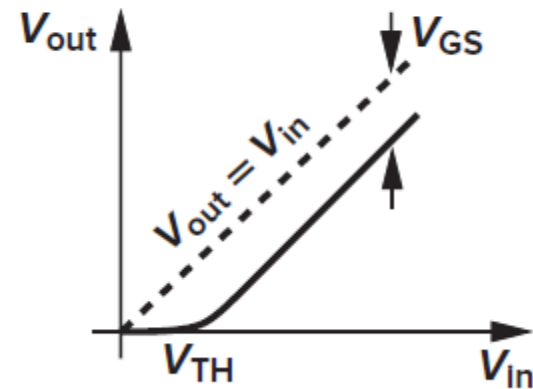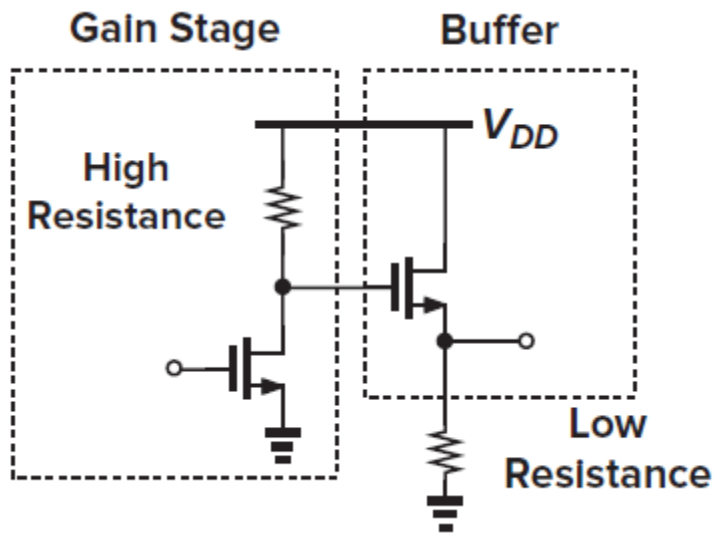


Summary of Basic Topologies

	CS	CG	CD (SF)
	Voltage & current amplifier	Current buffer	Voltage buffer
Rin	∞	$R_S // \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$	∞
Rout	$R_D // r_o [1 + (g_m + g_{mb})R_S]$	$R_D // r_o$	$R_S // \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$
Gm	$\frac{-g_m}{1 + (g_m + g_{mb})R_S}$	$g_m + g_{mb}$	$\frac{g_m}{1 + R_D/r_o}$


Q: CS With Diode-Connected Load

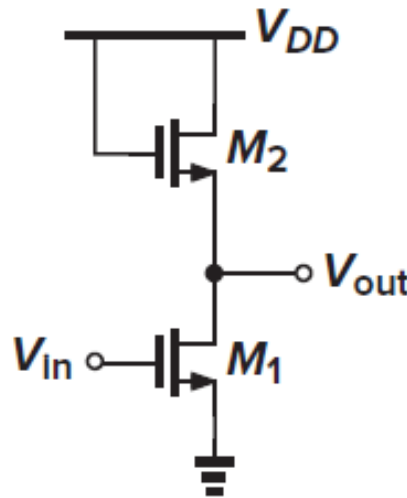- ❑ Find the gain using GmRout (ignore body effect)
 - Express the gain in terms of $(W/L)_1$ and $(W/L)_2$
- ❑ This is a “linear” CS amplifier




Q: Complementary CS (Inverter Amp)

- Find the gain using GmRout

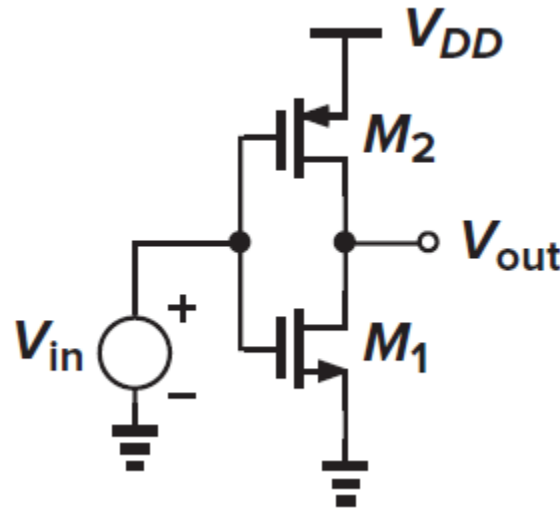


Output Signal Swing

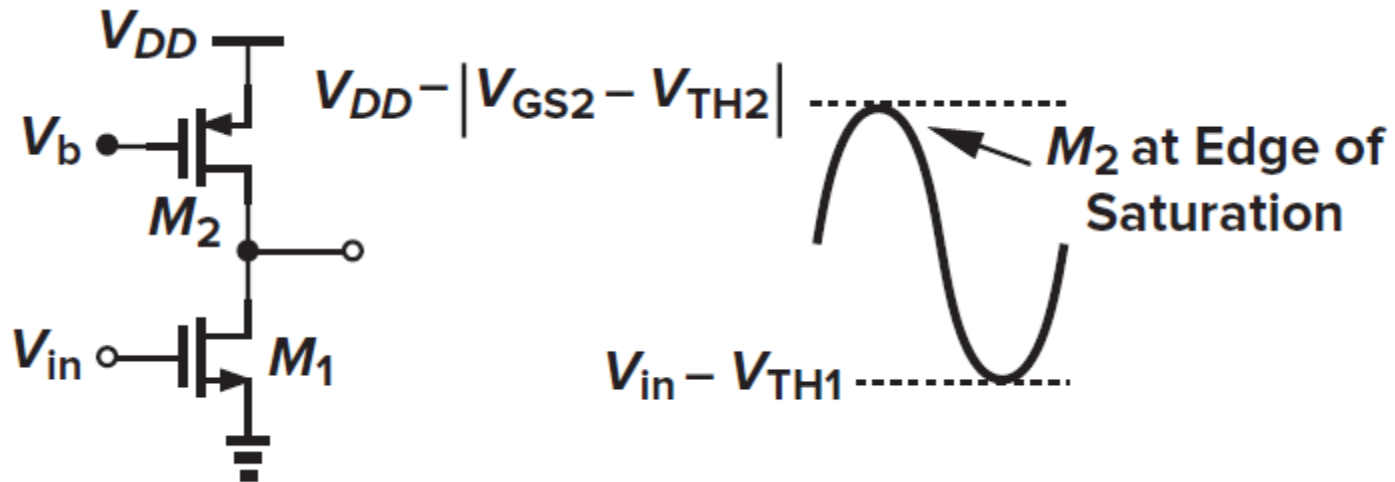


Thank you!

Voltage Amplifier Model

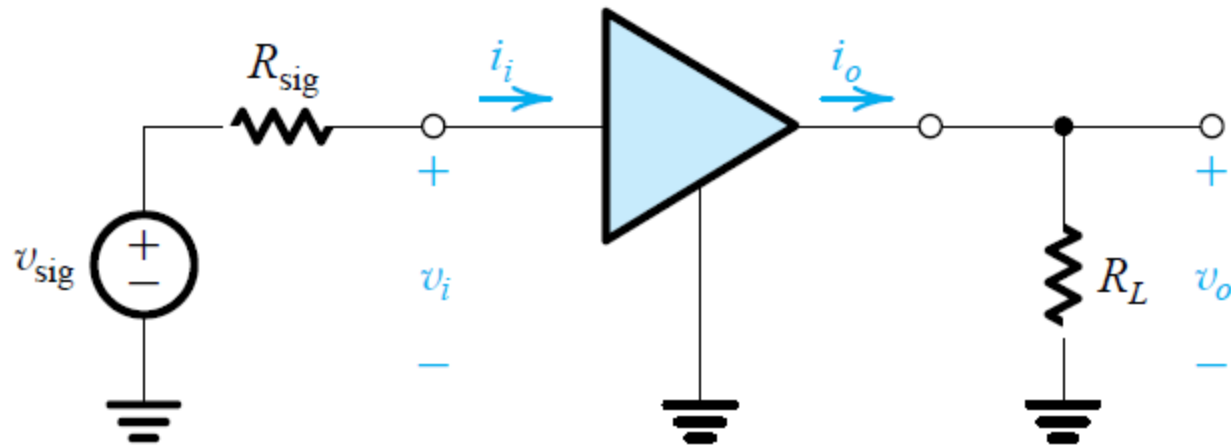

(a)

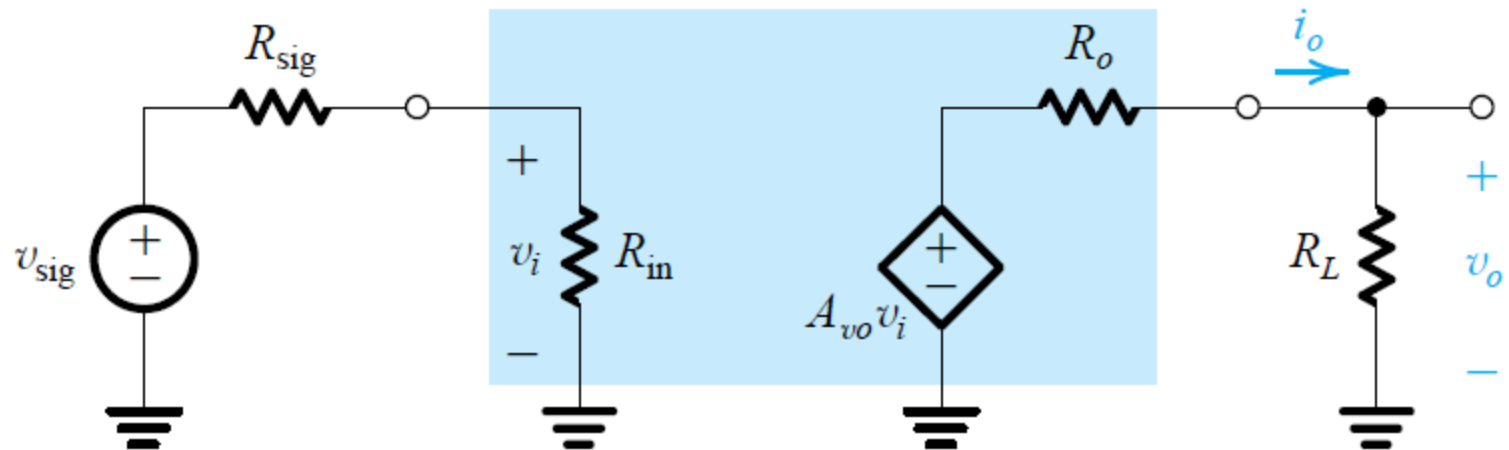


(b)

What If the Amplifier Is Loaded?


□ Voltage gain
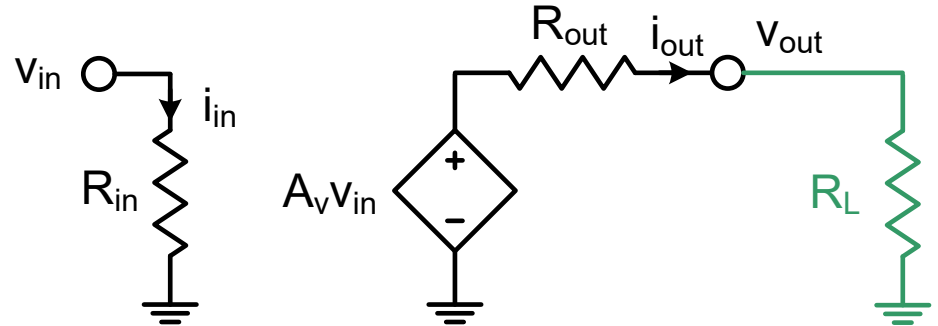
$$\begin{aligned} A'_v &= A_v \frac{R_L}{R_{out} + R_L} \\ &= G_m R_{out} \frac{R_L}{R_{out} + R_L} \\ &= G_m (R_{out} // R_L) \end{aligned}$$





□ Current gain

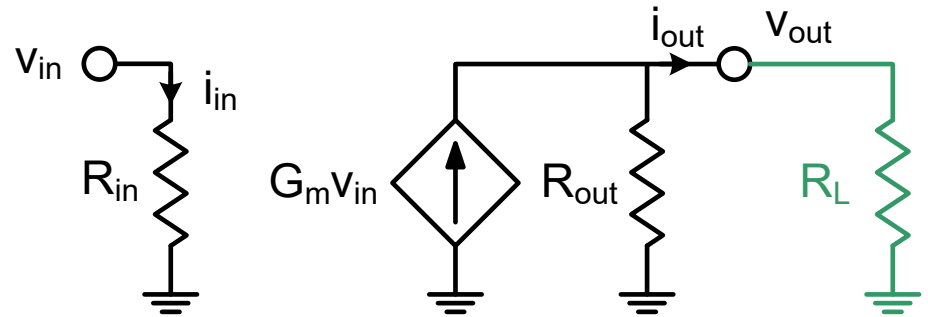
$$A'_i = A_i \frac{R_{out}}{R_{out} + R_L}$$




Input and Output Impedances

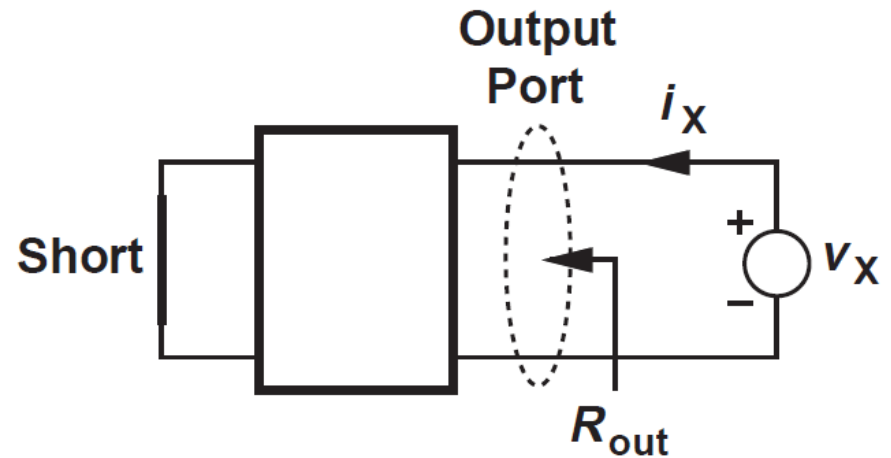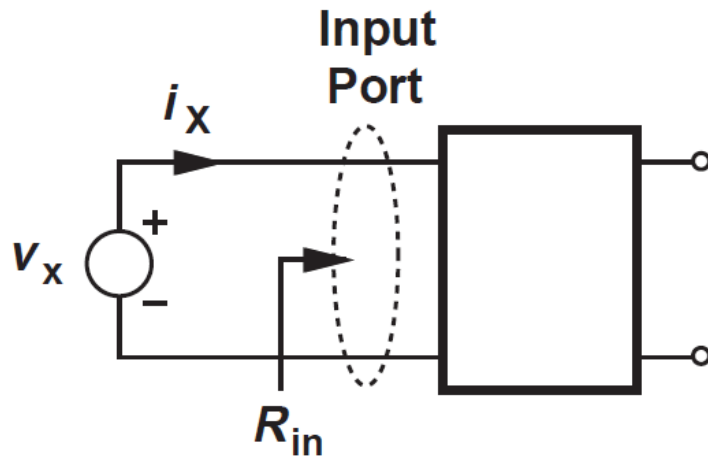


MOSFET Amplifier

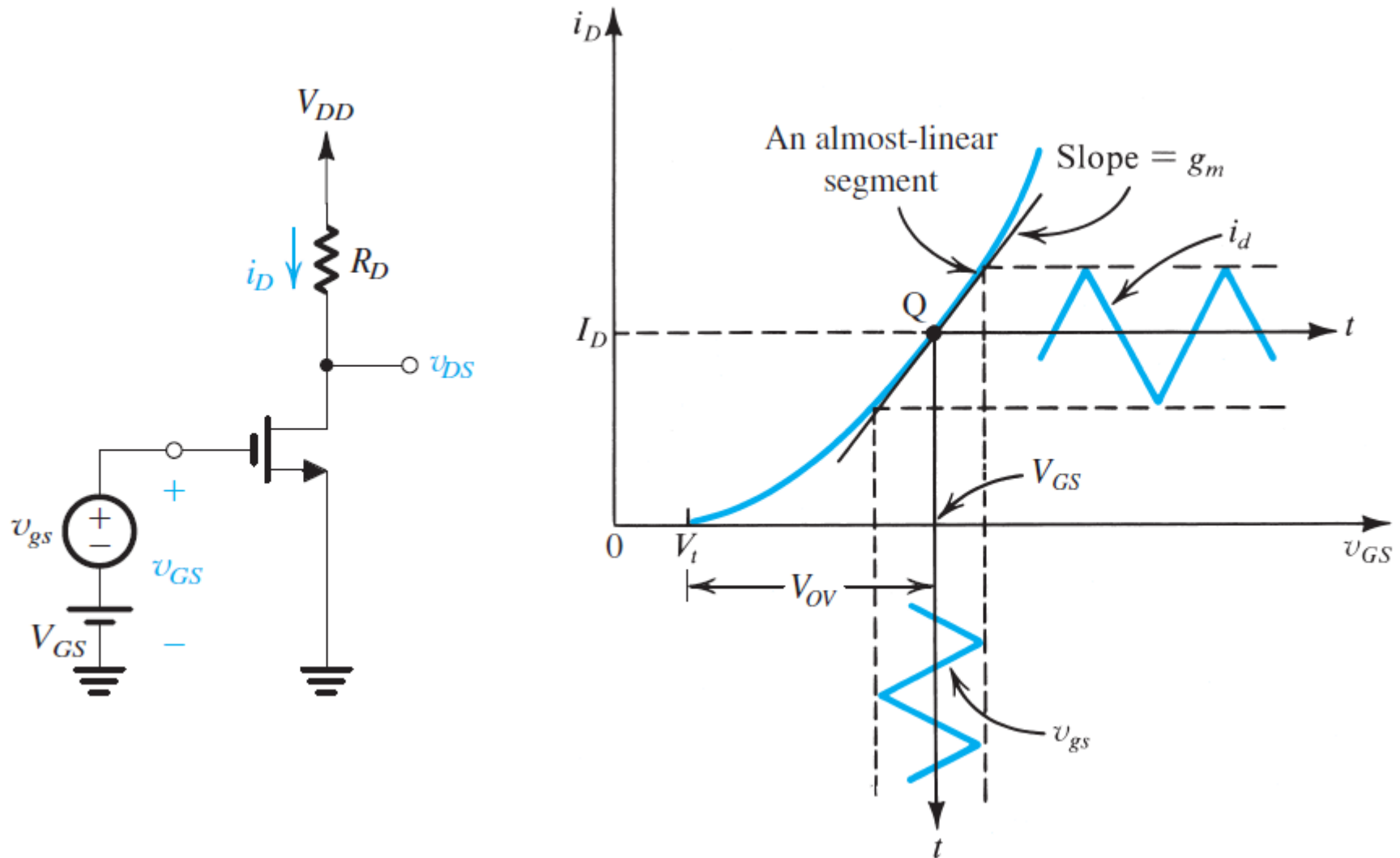

MOSFET Amplifier

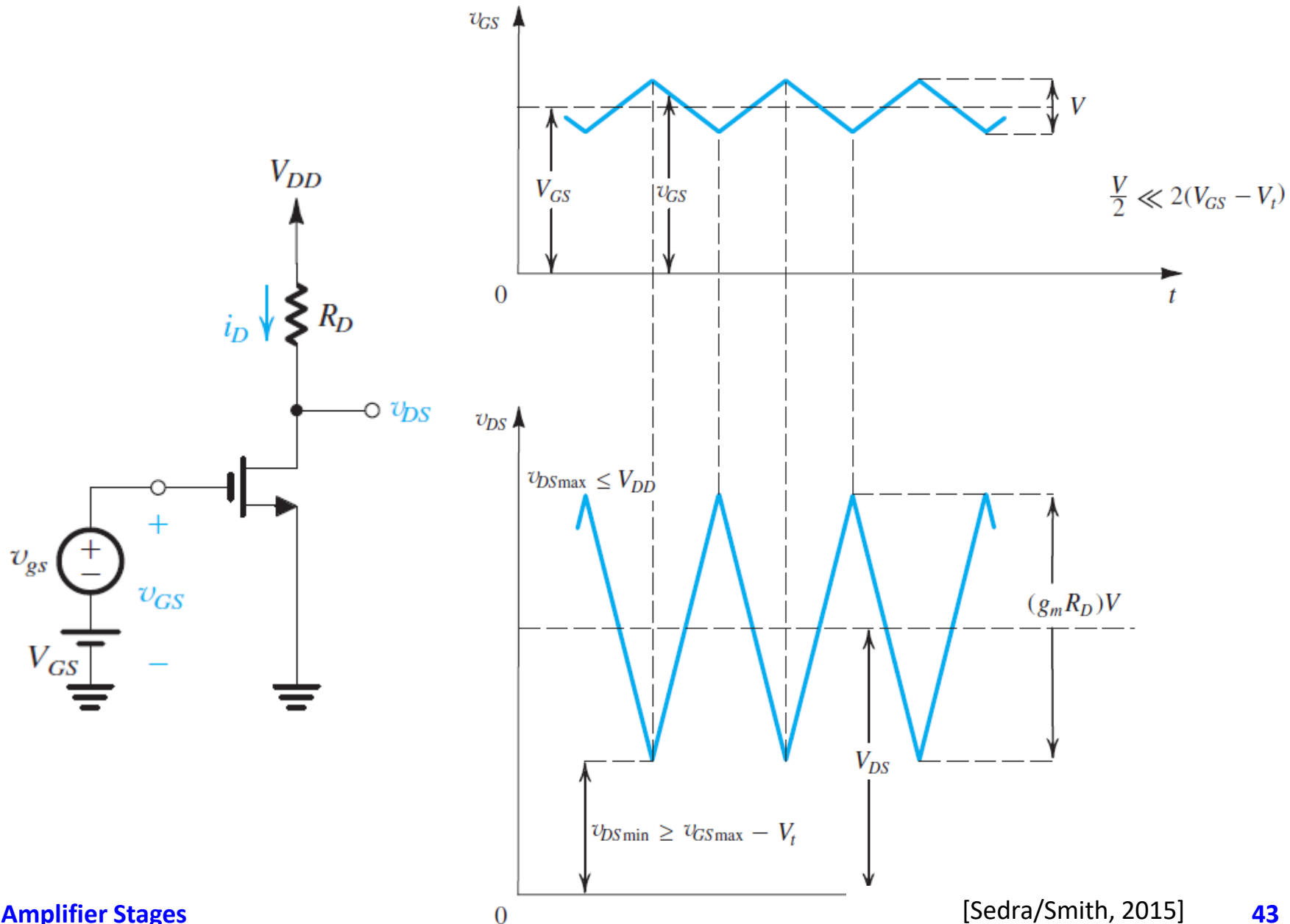

MOSFET Amplifier

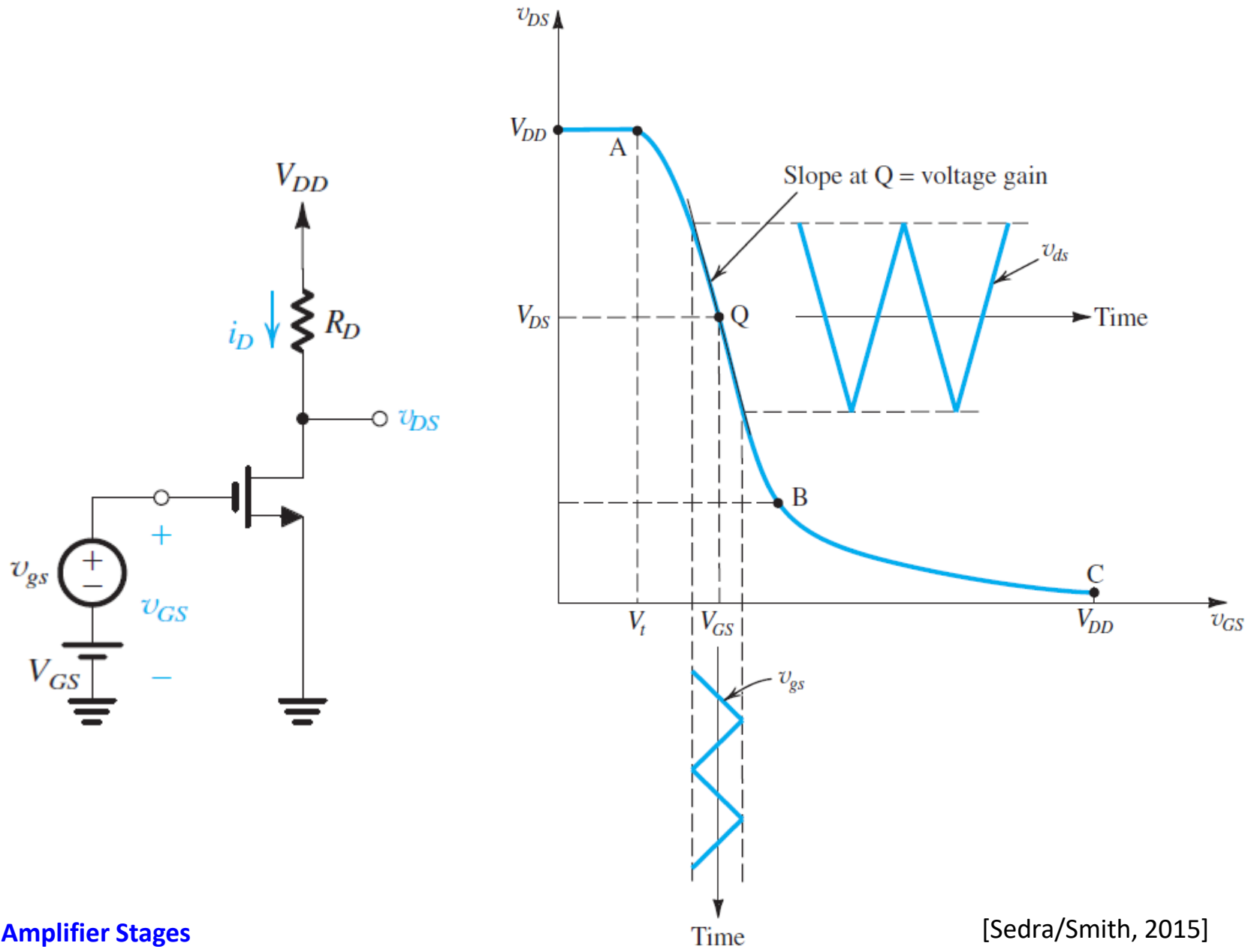

CS Large Signal Behavior

- ❑ Large signal gain is non-linear: $A_v = f(v_{in})$
- ❑ Small signal gain is also non-linear: $g_m = f(v_{in})$
- ❑ For linear gain, A_v should NOT be $f(v_{in})$
- ❑ A_v and g_m are max at edge of triode
 - But they are highly non-linear
 - And the available signal swing vanishes

