

وَمَا أُوتِيتُمْ مِنَ الْعِلْمِ إِلَّا قَلِيلًا

## Analog IC Design

### Lecture 10 Current Mirrors



**Dr. Hesham A. Omran**

Integrated Circuits Lab (ICL)  
Electronics and Communications Eng. Dept.  
Faculty of Engineering  
Ain Shams University
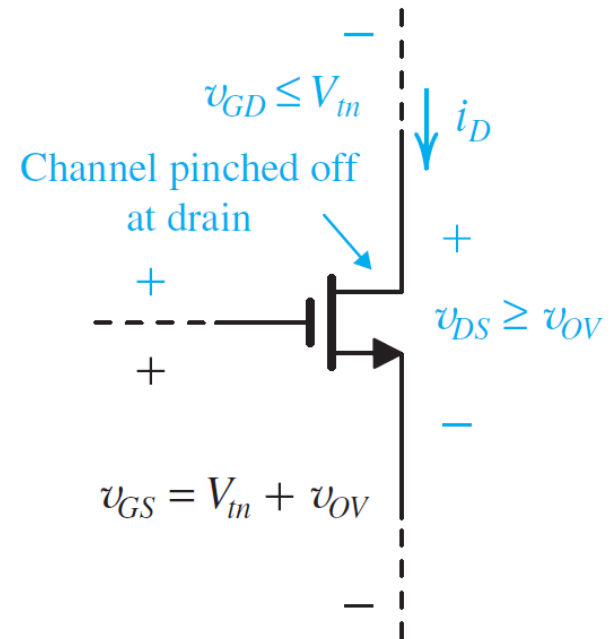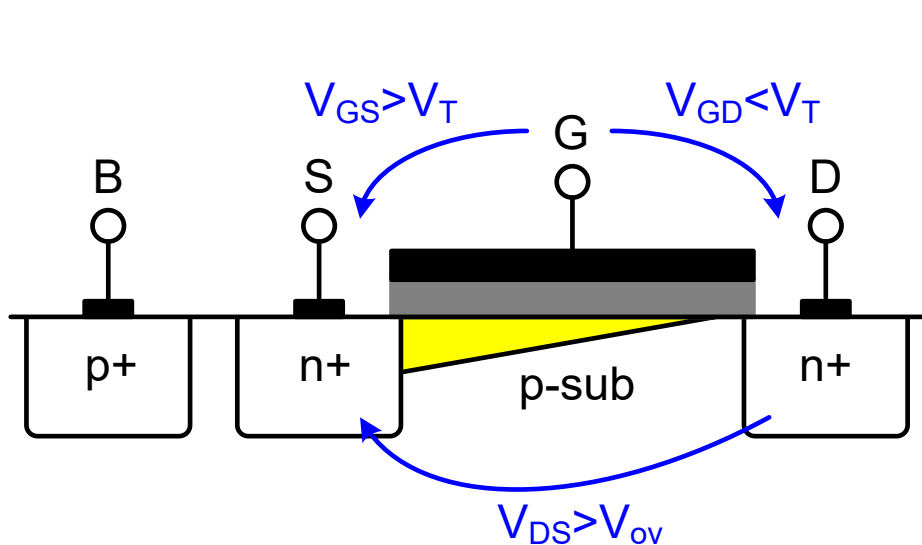
# MOSFET in Saturation

- ❑ The channel is pinched off if the difference between the gate and drain voltages is not sufficient to create an inversion layer

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \cdot V_{ov}^2 (1 + \lambda V_{DS})$$



# Regions of Operation Summary

**OFF**  
**(Subthreshold)**

$$V_{GS} < V_T$$

**ON**

$$V_{GS} > V_T$$

**Triode**

$$V_{DS} < V_{ov}$$

Or

$$V_{GD} > V_T$$

**Pinch-Off**  
**(Saturation)**

$$V_{DS} \geq V_{ov}$$

Or

$$V_{GD} \leq V_T$$

$$I_D = \mu C_{ox} \frac{W}{L} \left( V_{ov} V_{DS} - \frac{V_{DS}^2}{2} \right)$$


$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} V_{ov}^2 (1 + \lambda V_{DS})$$

# Low-Frequency Small-Signal Model


$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu C_{ox} \frac{W}{L} V_{ov} = \sqrt{\mu C_{ox} \frac{W}{L} \cdot 2I_D} = \frac{2I_D}{V_{ov}}$$

$$g_{mb} = \eta g_m, \quad \eta \approx 0.1 - 0.25$$

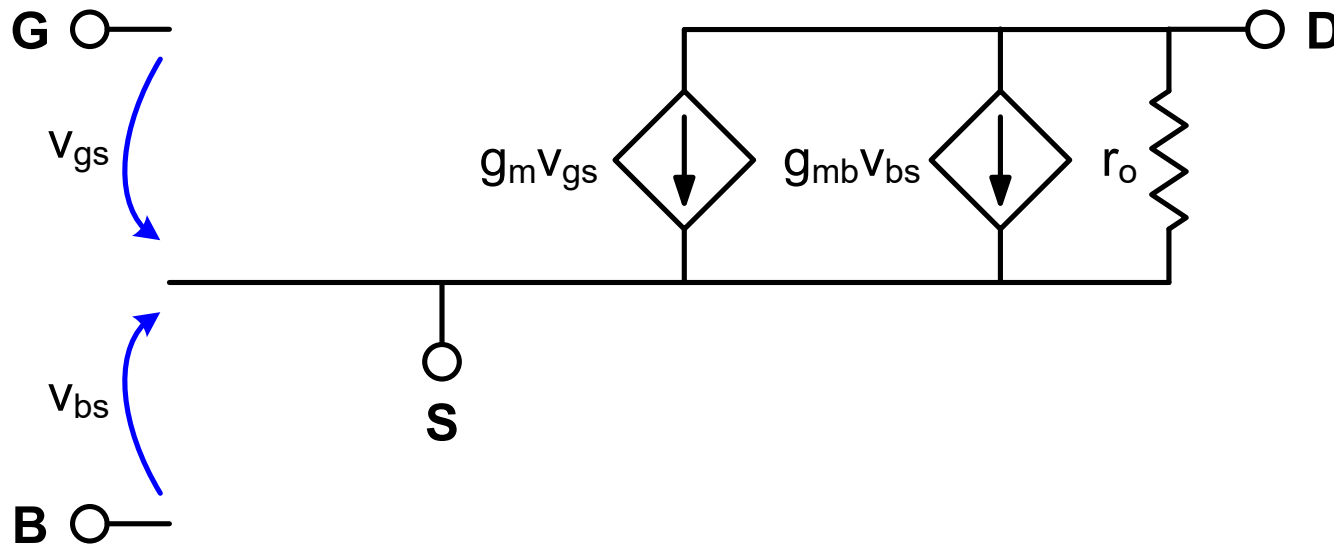
$$r_o = \frac{1}{\frac{\partial I_D}{\partial V_{DS}}} = \frac{1}{\lambda I_D}, \quad \lambda \propto \frac{1}{L}$$



# Rin/out Shortcuts Summary


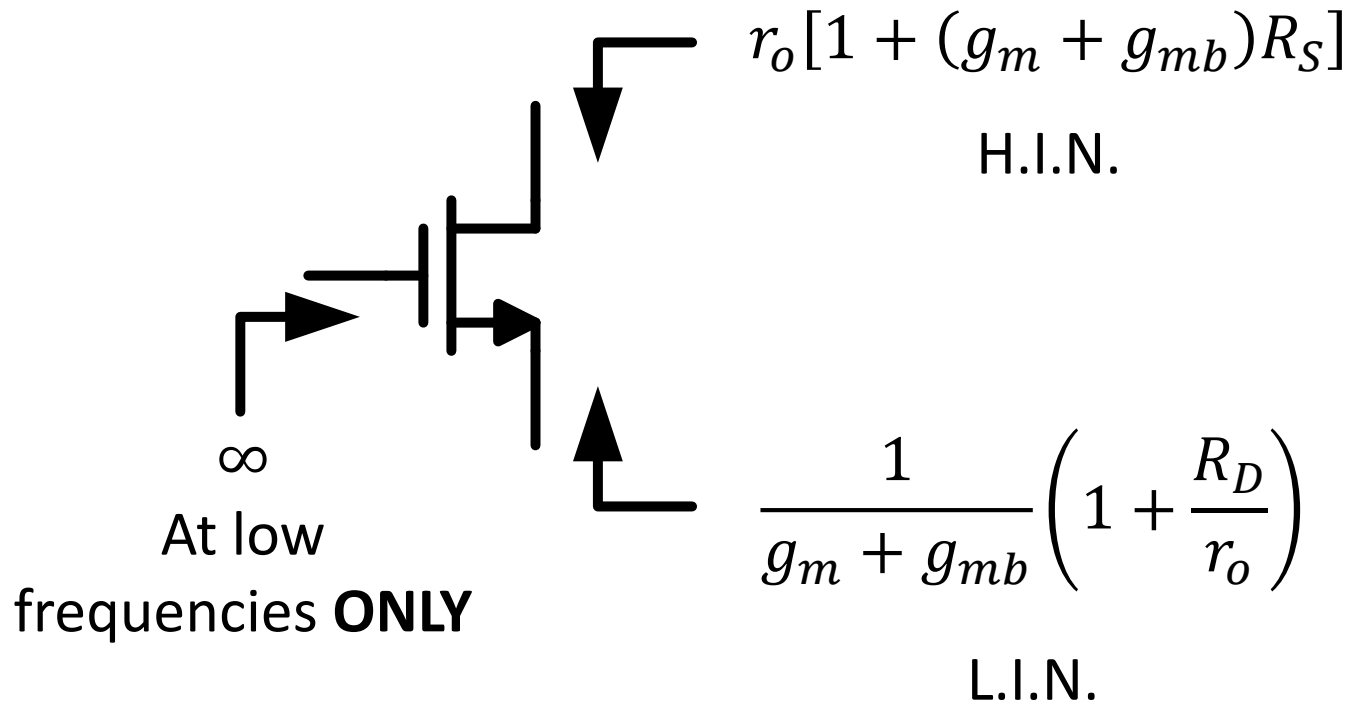


# Active Load (Source OFF)

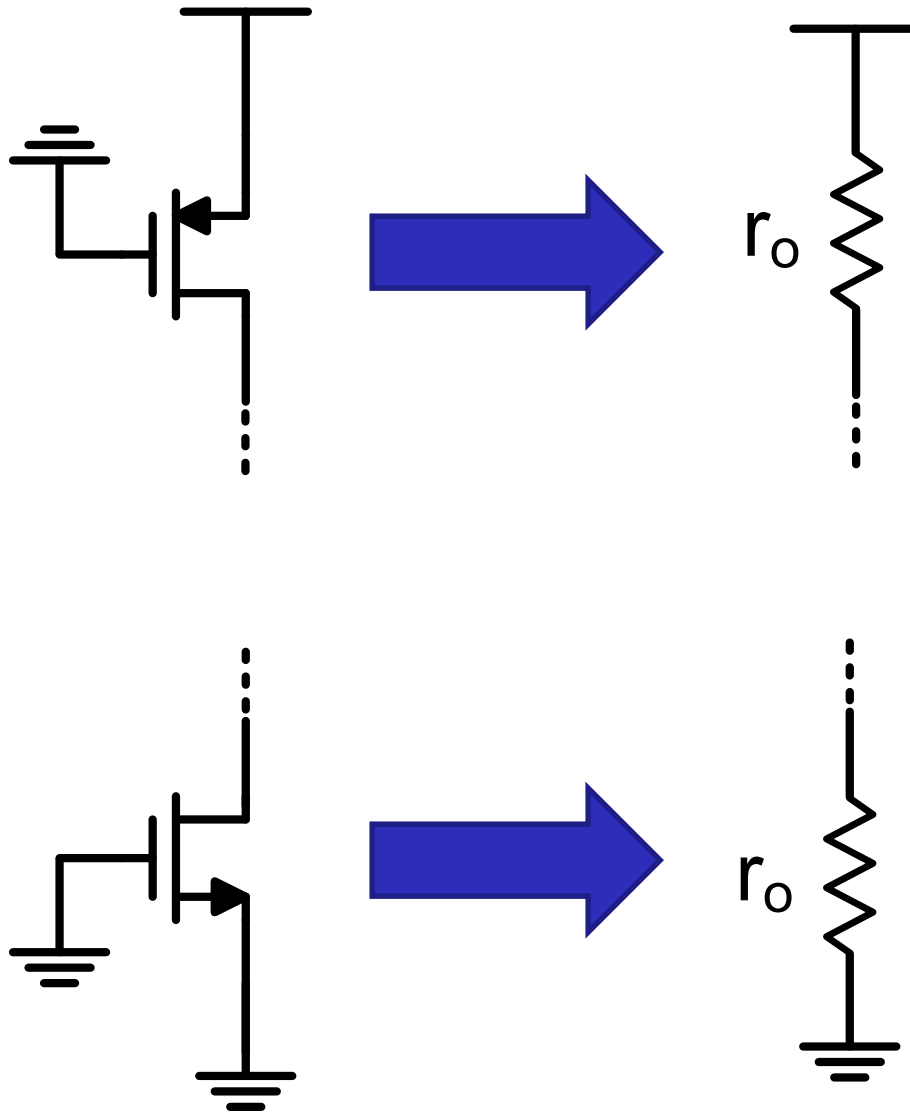
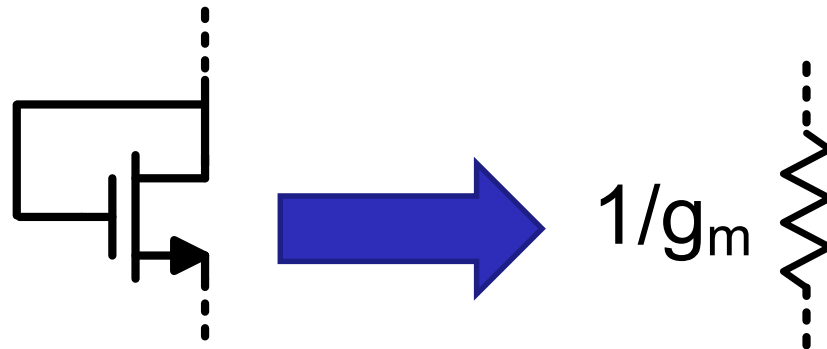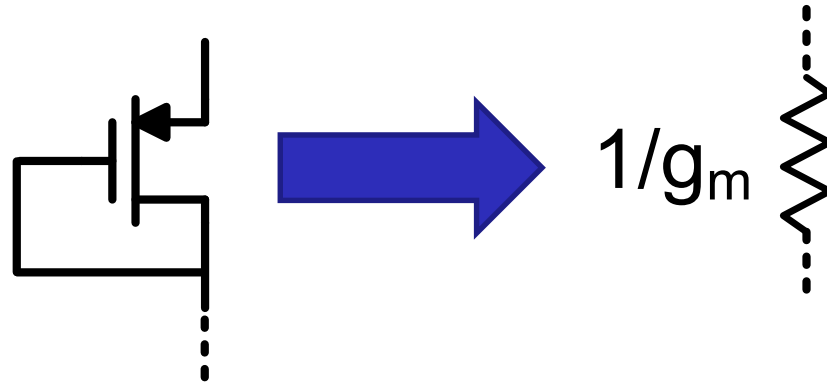
# Diode Connected (Source Absorption)

- ❑ Always in saturation
- ❑ Bulk effect:  $g_m \rightarrow g_m + g_{mb}$



# Why GmRout?

$$R_{out} = \frac{v_x}{i_x} @ v_{in} = 0$$



$$G_m = \frac{i_{out,sc}}{v_{in}}$$

$$A_v = G_m R_{out}$$

$$A_i = G_m R_{in}$$


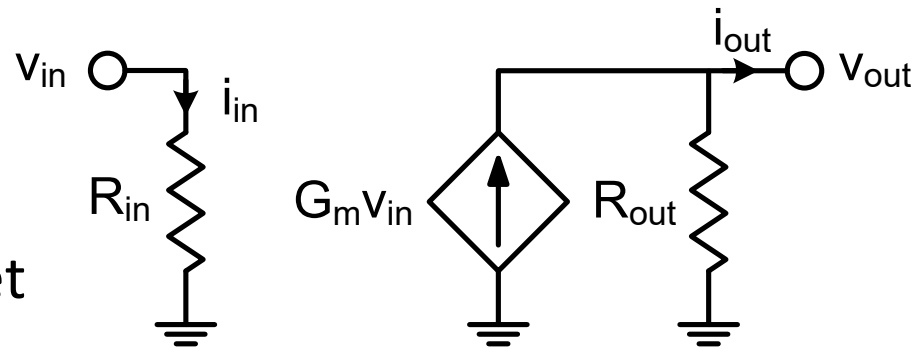
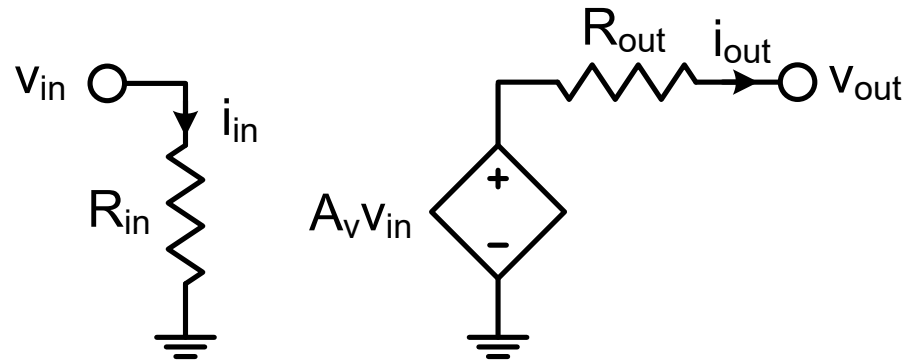
## □ Divide and conquer

- Rout simplified:  $v_{in}=0$
- Gm simplified:  $v_{out}=0$
- We already need  $R_{in/out}$
- We can quickly and easily get  $R_{in/out}$  from the shortcuts








# Summary of Basic Topologies

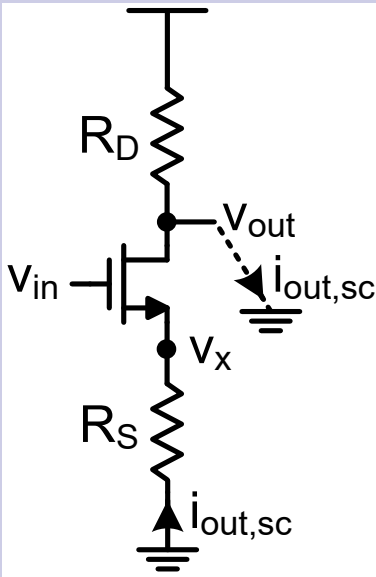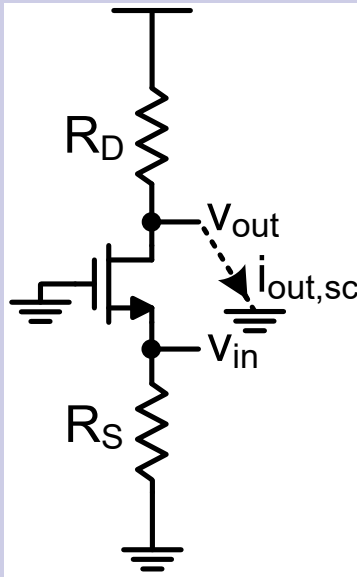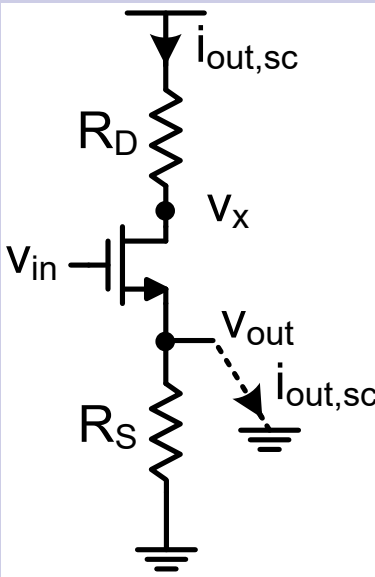	CS	CG	CD (SF)
			
	Voltage & current amplifier	Current buffer	Voltage buffer
<b>Rin</b>	$\infty$	$R_S // \frac{1}{g_m + g_{mb}} \left( 1 + \frac{R_D}{r_o} \right)$	$\infty$
<b>Rout</b>	$R_D // r_o [1 + (g_m + g_{mb})R_S]$	$R_D // r_o$	$R_S // \frac{1}{g_m + g_{mb}} \left( 1 + \frac{R_D}{r_o} \right)$
<b>Gm</b>	$\frac{-g_m}{1 + (g_m + g_{mb})R_S}$	$g_m + g_{mb}$	$\frac{g_m}{1 + R_D/r_o}$

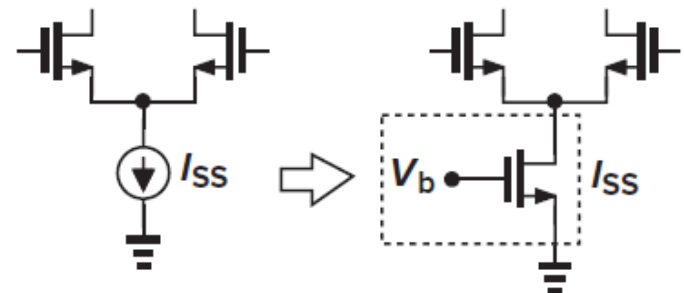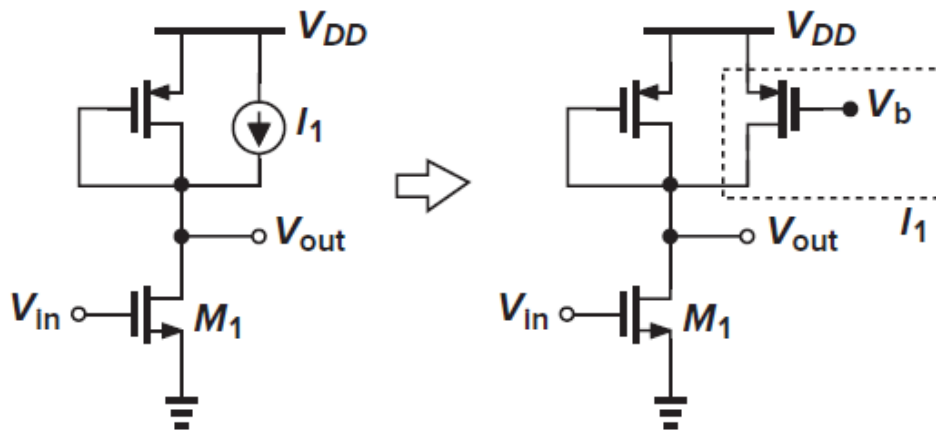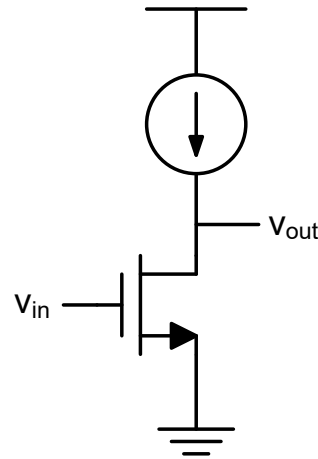
# Why Current Source?

- ❑ Current sources act as a large resistor without consuming excessive voltage headroom (and without consuming excessive chip area)



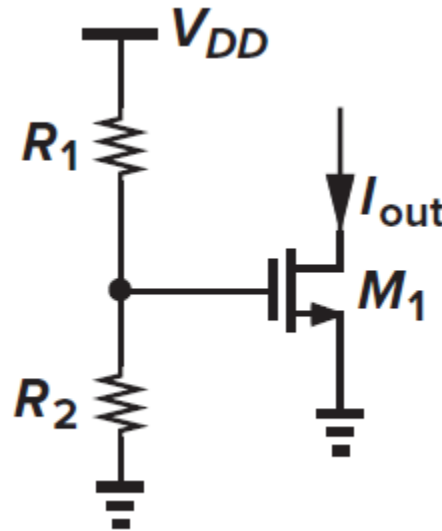
# BAD Current Source

- ❑ Sensitive to PVT (process, voltage, and temperature) variations






$$I_{out} \approx \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)^2$$

# How to Generate Robust Currents?

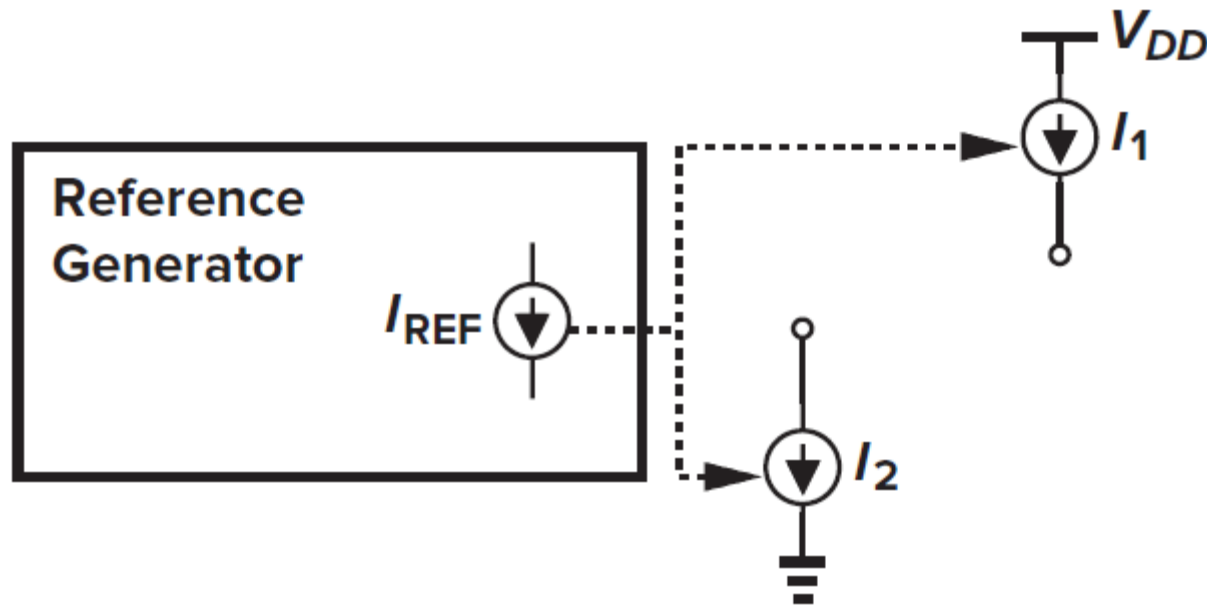


# How to Copy (Mirror) Currents?

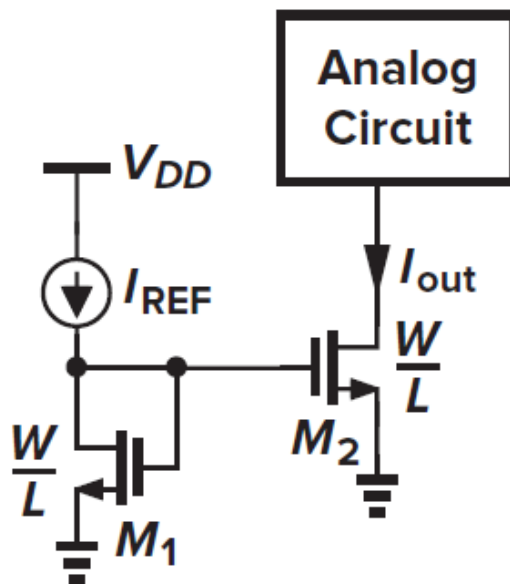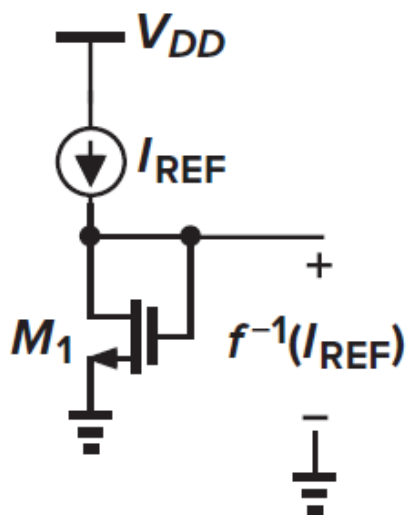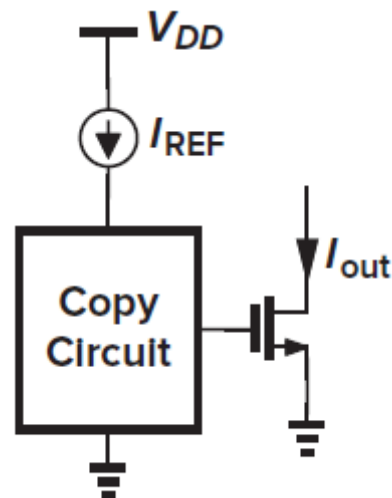


$$I_{out} = \frac{(W/L)_2}{(W/L)_1} I_{REF}$$

# Is This a Current Mirror?

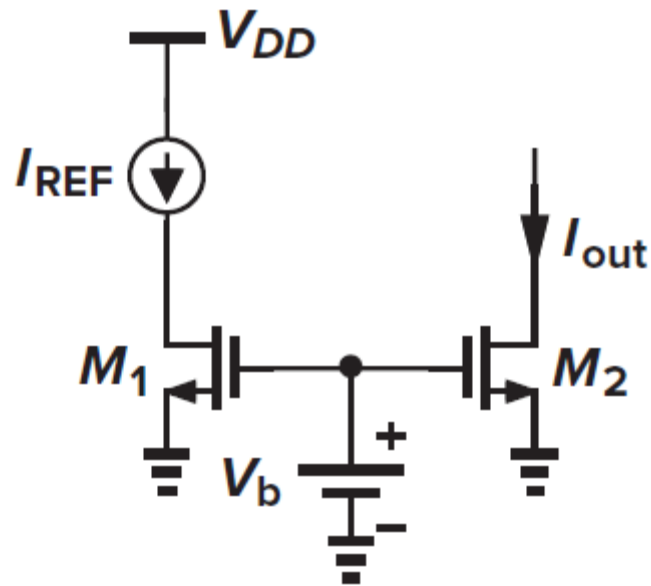


# Sink and Source Currents

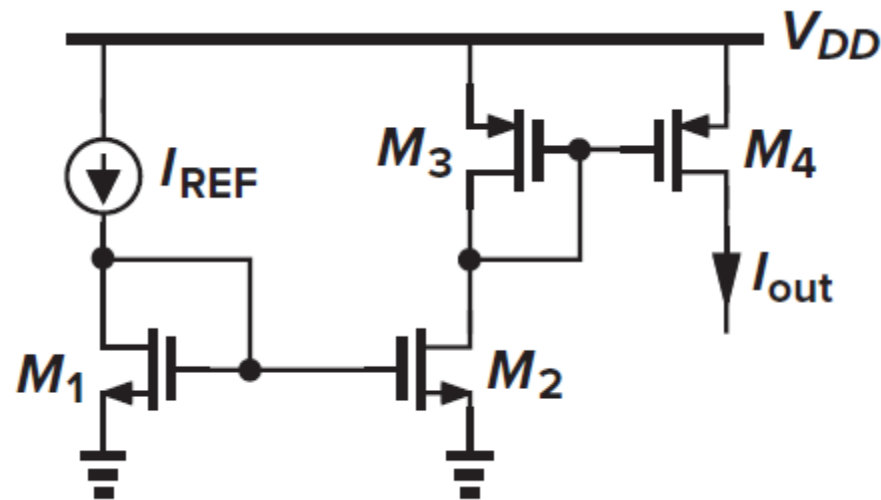


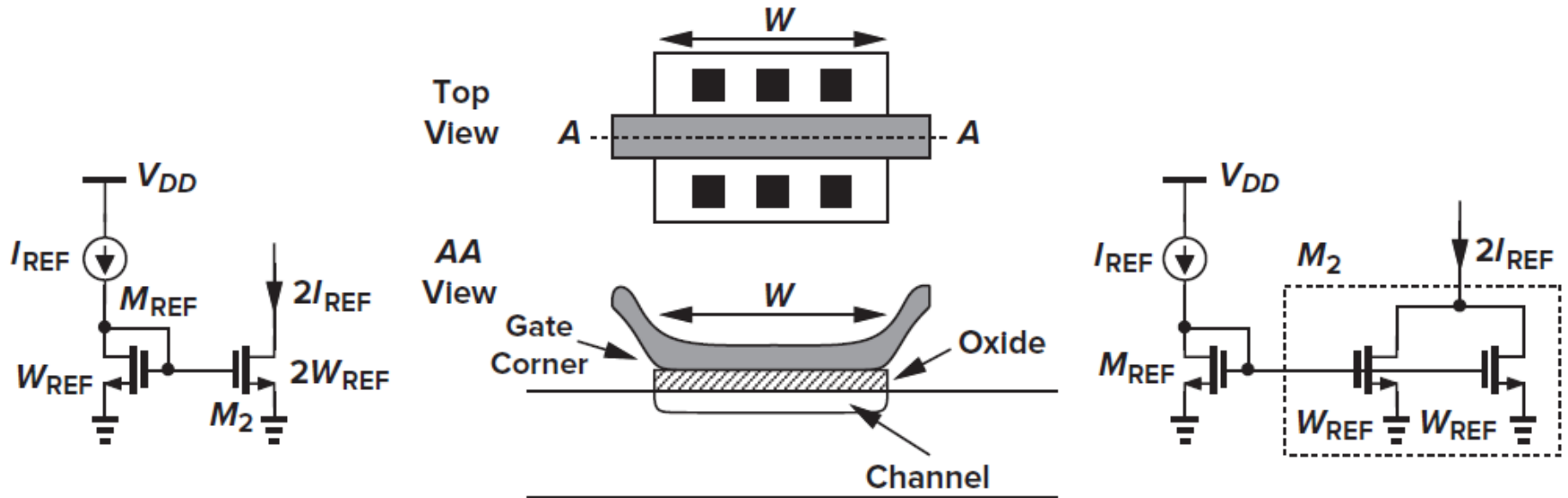
# Accurate Mirroring

- ❑ ALWAYS use matched unit transistors (same L, W, orientation, etc.)





# Scale Current Up and Down

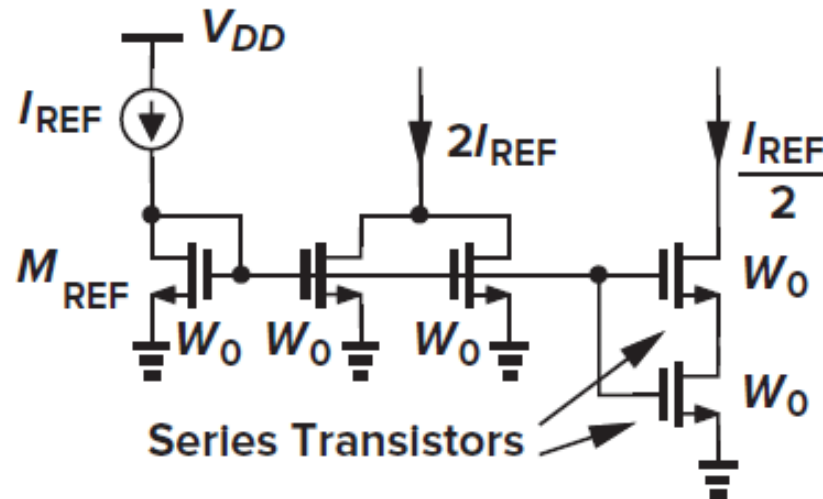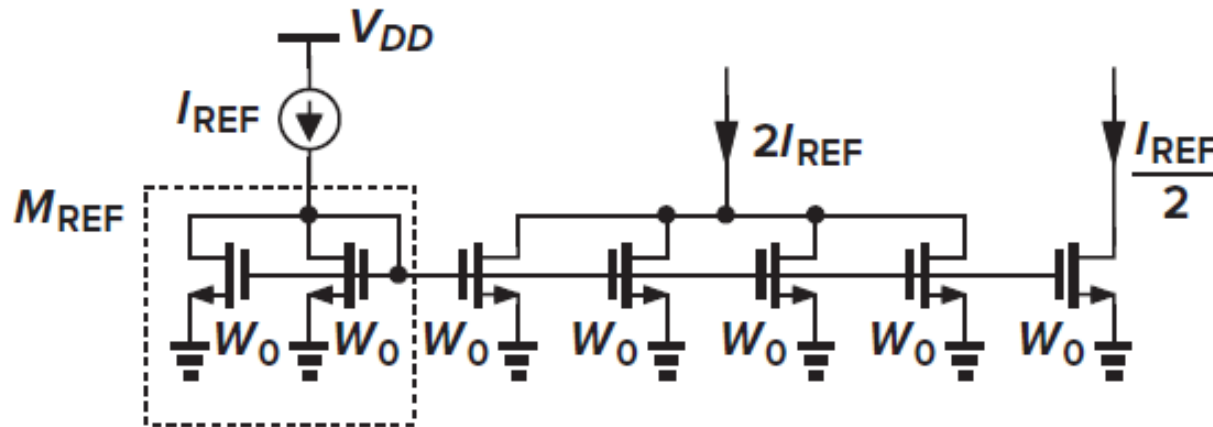


# $V_{DS}$ Dependence

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS1})$$

$$I_{D2} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS2})$$


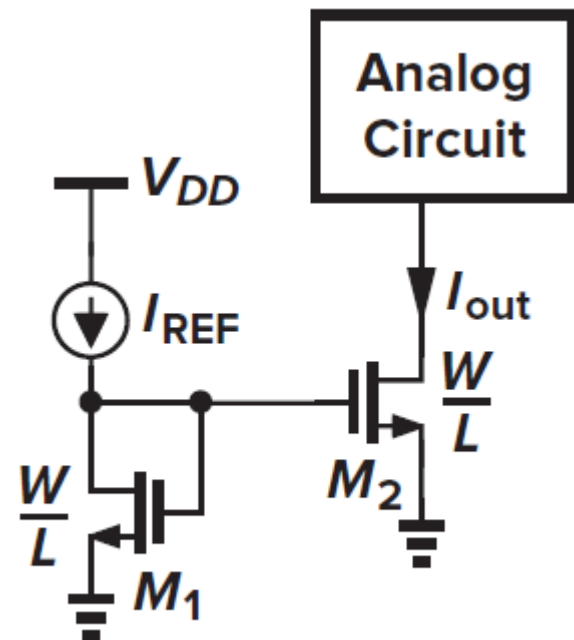
$$\frac{I_{D2}}{I_{D1}} = \frac{(W/L)_2}{(W/L)_1} \cdot \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}}$$



❑ First solution: Force  $V_{DS2}$  to be equal to  $V_{DS1}$

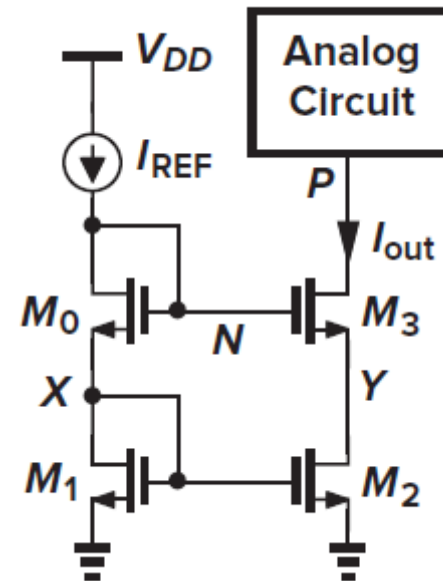
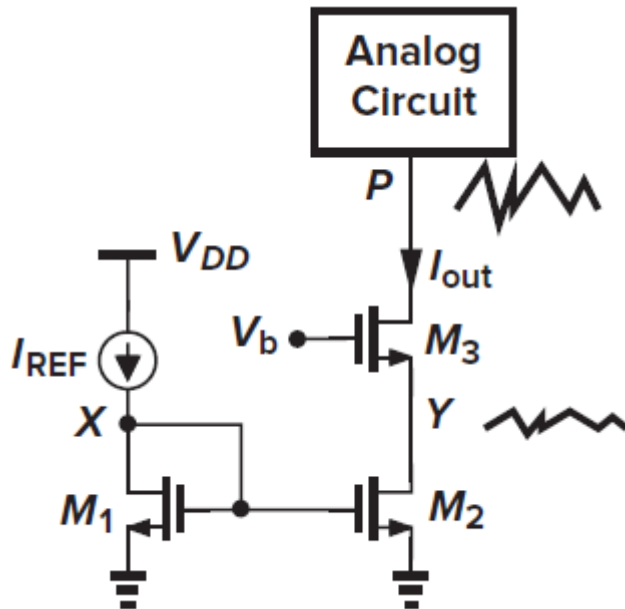
# Cascode Current Mirror

- $V_{DS2} = V_{DS1} = V_{GS1} = V_{TH1} + V_{ov1}$
- The cascode also boosts  $R_{out} = \frac{\Delta V_{out}}{\Delta I_{out}} \rightarrow$  Less current variation


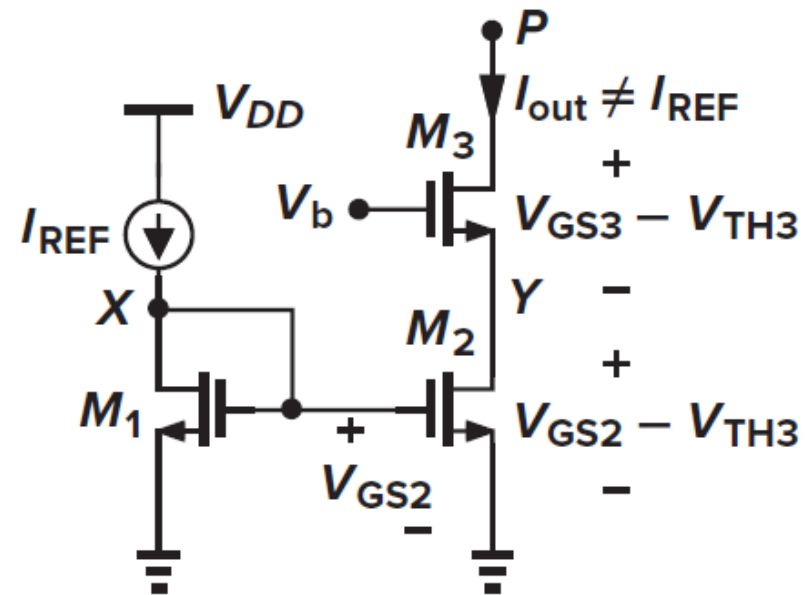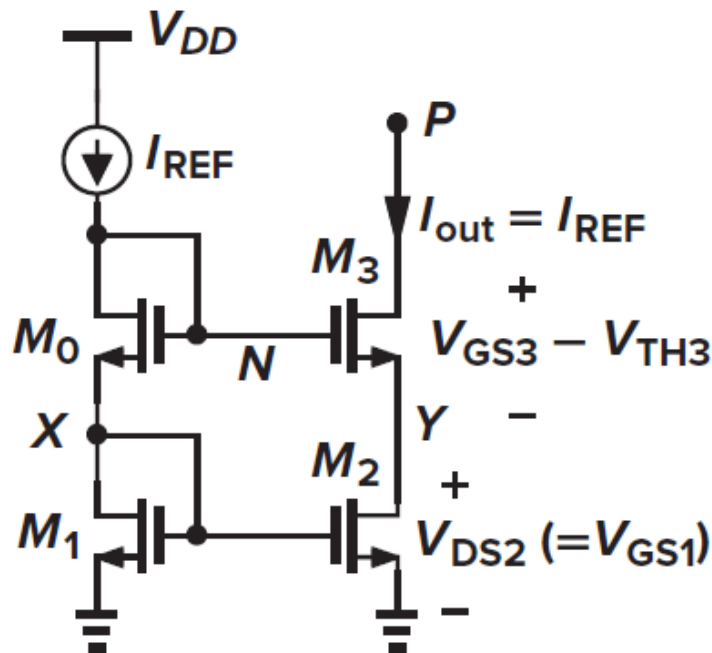
# Cascode CM Wastes Headroom

- ❑ Cascode wastes headroom, but we need to keep  $V_{DS}$  equal
- ❑ First solution wastes headroom: Do not force  $V_{DS2}$  to be equal to  $V_{DS1}$
- ❑ Second solution: force  $V_{DS1}$  to be equal to  $V_{DS2}$  😊




# Low Voltage Cascode CM

- ❑ A.k.a. wide swing current mirror, low compliance current mirror


$$V_{TH0} + V_{ov0} + V_{ov1} < V_b < V_{TH0} + V_{TH1} + V_{ov1}$$

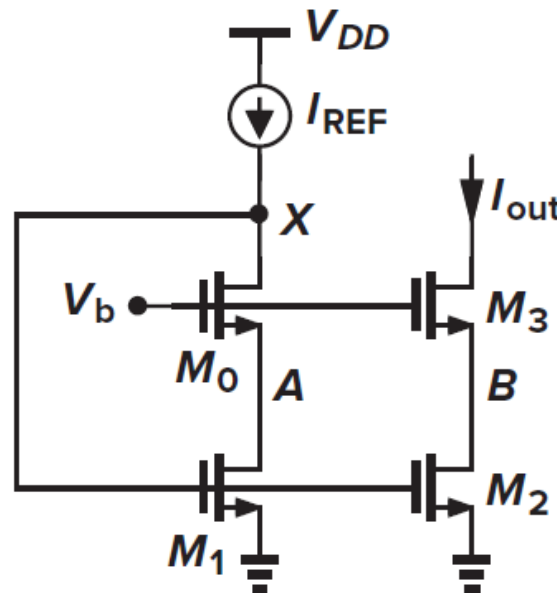- ❑ What is the magic battery that will generate  $V_b$ ?



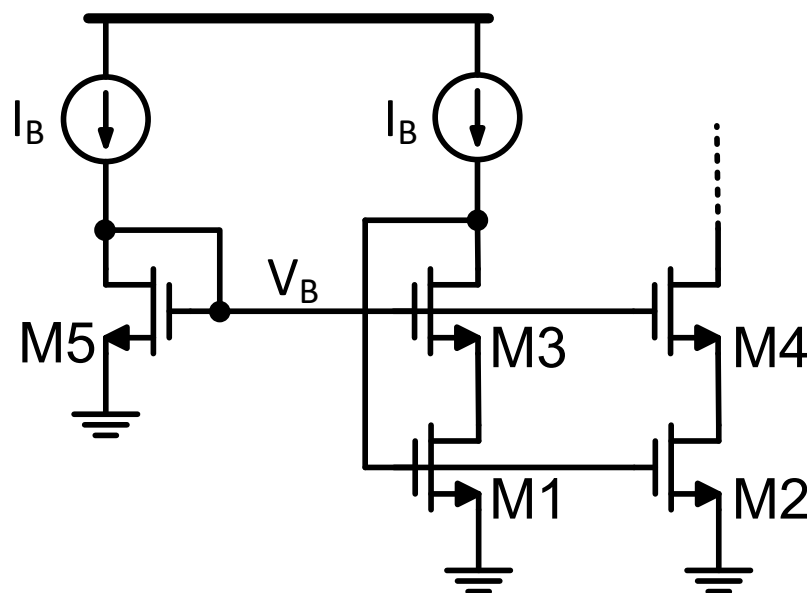
# How to Generate $V_B$ ?

- ❑ Assume M1-M4 have the same W/L
- ❑ Length of M5 should be a little  $> 4L$ 
  - Bias M1 and M2 a little more into saturation
  - Account for body effect of M3 and M4
- ❑ M5 may be implemented as unit transistors in series


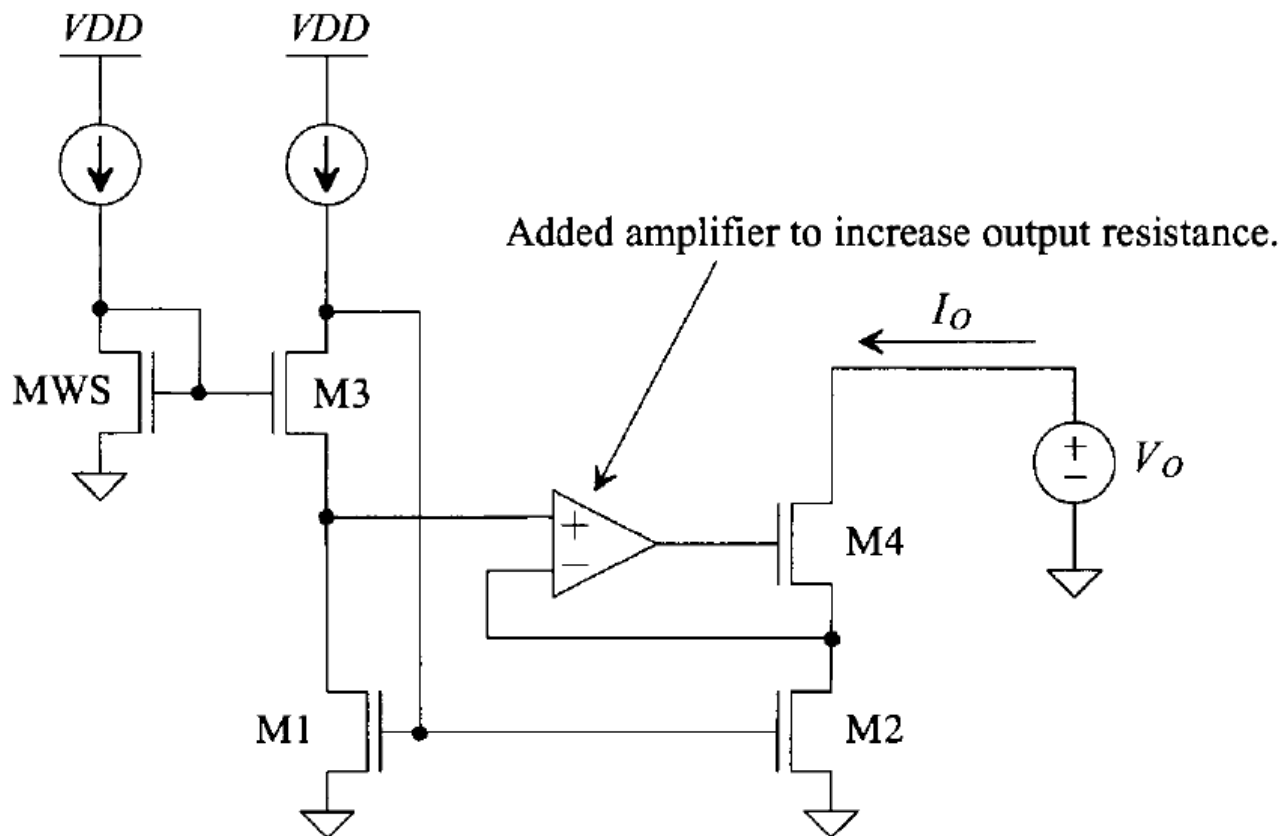
# Regulated (Super) Cascode CM

- Feedback keeps  $V_{DS1} \approx V_{DS2}$  and boosts  $R_{out}$   
 $R_{out} \approx r_{o,super}(1 + g_{m,super}R_S) = r_{o4}(Ag_{m4}r_{o2}) \sim A(g_m r_o^2)$



---

**Thank you!**