

## Analog IC Design

### Lab 02

### Common Source Amplifier

#### 1. Amplifier Design

- We would like to design a resistive loaded CS amplifier. First, we will create a design chart to help in the design process.
- Create a testbench for an NMOS transistor similar to the NMOS characterization testbench that you used in Lab 01. Use  $W = 10\mu m$  and  $L = 2\mu m$ .
- Sweep  $V_{GS}$  from 0 to 0.7V with 10mV step. Set  $V_{DS} = \frac{1}{3}V_{DD}$ .
- Report the following parameters vs  $V_{GS}$ :
  - $v_{dss}$  and  $v_{th\_d}$  overlaid on the same plot ( $v_{dss}$  is the drain-source saturation voltage, i.e.,  $V_{DS} > v_{dss}$  for saturation. It is equivalent to  $V_{ov}$  for a square-law device. It is also known as  $v_{dsat}$ .  $v_{th\_d}$  is equal to  $V_{ov} = V_{GS} - V_{TH}$ )
  - ID
- What is the relation between  $v_{dss}$  and  $v_{th\_d}$ ? Why?
- Find the point at which  $v_{dss} = 100mV$ . Report  $V_{GS}$ ,  $v_{th\_d}$ , and ID at this point. We will use these parameters for our amplifier.
- Choose RD (the resistive load) such that the voltage drop across it is roughly  $\frac{2}{3}V_{DD}$ .

#### 2. OP Analysis

- Create a testbench for the resistive loaded CD amplifier using the  $V_{GS}$  and the RD that you got from the previous part.
- Simulate the DC OP. Report the following parameters in a table:
  - vgs
  - vth
  - $v_{th\_d}$
  - $v_{dss}$
  - vds
  - region (region is one of the small signal parameters of the transistor model)
  - gm
  - gds
- What is the relation ( $<$ ,  $\ll$ ,  $=$ ,  $>$ ,  $\gg$ ) between  $v_{th\_d}$  and  $(v_{gs} - v_{th})$ ? Why?
- What is the relation ( $<$ ,  $\ll$ ,  $=$ ,  $>$ ,  $\gg$ ) between  $v_{th\_d}$  and  $v_{dss}$ ? Why?
- What is the relation ( $<$ ,  $\ll$ ,  $=$ ,  $>$ ,  $\gg$ ) between vds and  $v_{dss}$ ? What is the operating region? Why?
- What is the relation ( $<$ ,  $\ll$ ,  $=$ ,  $>$ ,  $\gg$ ) between gm and gds?
- What is the intrinsic gain?
- Calculate the amplifier gain analytically. What is the relation ( $<$ ,  $\ll$ ,  $=$ ,  $>$ ,  $\gg$ ) between the amplifier gain and the intrinsic gain?
- Report a snapshot of the amplifier with DC voltages annotated.

#### 3. Gain Non-Linearity

- Perform a DC sweep for the input voltage from 0 to  $V_{DD}$  with 2mV step.
- Report  $V_{OUT}$  vs  $V_{IN}$ . Is the relation linear? Why?

- c) Calculate the derivative of  $V_{OUT}$  using the calculator. The derivative is itself the small signal gain. Is the gain linear (independent of the input)? Why?
- d) Apply a transient stimulus (sine wave of 1kHz frequency and 10mV amplitude superimposed on the DC input voltage). Run transient simulation for 2ms. Plot  $g_m$  vs time using this command “.plot tran S(M1-> $g_m$ )”. Does  $g_m$  vary with the input signal? What does that mean?
- e) Is this amplifier linear? Comment.

#### 4. Maximum gain

- a) We want to find  $R_D$  that will give max gain. Run a nested DC sweep (not a parametric sweep) with  $V_{IN}$  as the primary variable and  $R_D$  as the secondary variable.
- b) Report the derivative of  $V_{OUT}$  (i.e., the gain) vs  $V_{IN}$  with  $R_D$  as a parameter. You should adjust the sweep range of  $R_D$  such that the max gain (the peak) increases with  $R_D$  then decreases again.
- c) Use .EXTRACT command to plot the max gain vs  $R_D$ .
- d) What is the value of  $R_D$  that gives the highest gain? What is the highest gain?
- e) Find an analytical expression for the highest gain while ignoring  $r_o$ . Compare with the simulated max gain. Is scaling down the supply voltage good for gain? Comment.